



Boolean Algebra Relations			
A•A = A	A+A = A	A+A = A	
$A \cdot \overline{A} = 0$	A+Ā = 1	A+Ā = 1	
A•1 = A	A+1 = 1		
A•0 = 0	0 A+0 = A		
A•B = B•A	A•B = B•A A+B = B+A		
A•(B•C) = (A•B)•	$(A \bullet B) \bullet C \qquad A + (B + C) = (A + B) + C$		
$A \bullet (B+C) = A \bullet B + A \bullet C$			
$\overline{A \cdot B} = \overline{A} + \overline{B}$			
$\overline{A} \cdot \overline{B} = \overline{A + B}$ $\int De Morgan's laws$			
EECS40, Fall 2003	Lecture 29, Slide 3	Prof. King	





Logical Sufficiency of NOR Gates			
Show how to re using only NOR	alize the AND, OR, and NC gates	DT functions	
 Since the basic logic functions (AND, OR, and NOT) can be realized by using only NOR gates, NOR gates are sufficient to realize any combinational logic function. 			

Synthesis of Logic Circuits Suppose we are given a truth table for a logic function. Is there a method to implement the logic function using basic logic gates? **Answer:** There are lots of ways, but one simple way is the "sum of products" implementation method: 1) Write the sum of products expression based on the truth table for the logic function 2) Implement this expression using standard logic gates. We may not get the most efficient implementation this way, but we can simplify the circuit afterwards... Prof. King

EECS40. Fall 2003

Lecture 29, Slide 7

Logic Synthesis Example: Adder Input Output S₁ using sum-of-products: С Β S₁ Α S₀ 1) Find where S_1 is **1** 0 0 0 0 0 1 1 2) Write down each product of 0 0 0 inputs which create a 1 1 1 0 0 0 **ABC** ABC 1 1 1 0 0 ABC ABC 1 0 0 0 1 3) Sum all of the products 1 1 1 0 0 $\overline{A}BC + A\overline{B}C + A\overline{B}\overline{C} + A\overline{B}C$ 1 1 1 0 0 4) Draw the logic circuit 1 1 1 1 1 EECS40, Fall 2003 Lecture 29, Slide 8 Prof. King







