

Lecture #37

ANNOUNCEMENTS

- Prof. King's Office Hour on Wed 11/26 changed to 3-4PM
 - In order to receive extra credit for your Tutebot project, you must endow it with added functionality.
 - Examples: reaction to light, heat, sound; edge avoidance; capability to "learn" where objects are (memory)
- Simply adding LEDs is not sufficient to earn extra credit!

OUTLINE

- » Interconnect parameters
- » Interconnect modeling

Reading (Rabaey *et al.*)

Chapter 4: pp. 104-127


Chapter 5: pp. 172-173

Interconnects


- An ***interconnect*** is a thin-film wire that electrically connects 2 or more components in an integrated circuit.
- Interconnects can introduce parasitic (unwanted) components of capacitance, resistance, and inductance. These "***parasitics***" detrimentally affect
 - performance (e.g. propagation delay)
 - power consumption
 - reliability
- As transistors are scaled down in size and the number of metal wiring layers increases, the impact of interconnect parasitics increases.
 - Need to model interconnects, to evaluate their impact

Interconnect Resistance & Capacitance

 Metal lines run over thick oxide covering the substrate
 → contribute **RESISTANCE & CAPACITANCE** to the output node of the driving logic gate



Wire Resistance

 

$$R_{wire} = \frac{\rho L}{H W} = R_s \frac{L}{W}$$

Material	$\rho (\Omega\cdot m)$
Silver (Ag)	1.6×10^{-8}
Copper (Cu)	1.7×10^{-8}
Gold (Au)	2.2×10^{-8}
Aluminum (Al)	2.7×10^{-8}
Tungsten (W)	5.5×10^{-8}

Material	Sheet Res. (Ω/\square)
n, p well diffusion	1000 to 1500
n+, p+ diffusion	50 to 150
n+, p+ diffusion with silicide	3 to 5
polysilicon	150 to 200
polysilicon with silicide	4 to 5
Aluminum	0.05 to 0.1

Interconnect Resistance Example

Typical values of R_n and R_p are **~10 kΩ**, for $W/L = 1$

... but R_n , R_p are much lower for large transistors
(used to drive long interconnects with reasonable t_p)

Compare with the resistance of a 0.5μm-thick Al wire:


$$R_{\square} = \rho / H = (2.7 \mu\Omega\text{-cm}) / (0.5 \mu\text{m}) = 5.4 \times 10^{-2} \Omega / \square$$

Example: $L = 1000 \mu\text{m}$, $W = 1 \mu\text{m}$

$$\begin{aligned} \rightarrow R_{\text{wire}} &= R_{\square} (L / W) \\ &= (5.4 \times 10^{-2} \Omega / \square)(1000/1) = \mathbf{54 \Omega} \end{aligned}$$

Wire Capacitance: The Parallel Plate Model

single wire over
a substrate:

 

$$C_{pp} = \frac{\epsilon_{di}}{t_{di}} WL$$

Relative Permittivities

Material	ϵ_r
Free space	1
Aerogels	~1.5
Polyimides (organic)	3-4
Silicon dioxide	3.9
Glass-epoxy (PC board)	5
Silicon Nitride (Si_3N_4)	7.5
Alumina (package)	9.5
Silicon	11.7


Parallel-Plate Capacitance Example

- Oxide layer is typically ~500 nm thick
- Interconnect wire width is typically ~0.5 μm wide (1st level)
 \Rightarrow capacitance per unit length = 345 fF/cm = 34.5 aF/ μm


Example: $L = 30 \mu\text{m}$

$\rightarrow C_{pp} \cong 1 \text{ fF}$ (compare with $C_n \sim 2 \text{ fF}$)

Fringing-Field Capacitance

 

 For $W/t_{di} < 1.5$, C_{fringe} is dominant




Wire capacitance per unit length:

$$C_{wire} \cong C_{pp} + C_{fringe} = \frac{w\epsilon_{di}}{t_{di}} + \frac{2\pi\epsilon_{di}}{\log(t_{di}/H)} \quad w = W - \frac{H}{2}$$

Modeling an Interconnect

Problem: Wire resistance and capacitance to underlying substrate is spread along the length of the wire

“Distributed RC line”

 


We will start with a simple model...

Lumped RC Model


Model the wire as single capacitor and single resistor:

 - C_{wire} is placed at the end of the interconnect
→ adds to the gate capacitance of the load
- R_{wire} is placed at the logic-gate output node
→ adds to the MOSFET equivalent resistance




Cascaded CMOS Inverters w/ Interconnect

Equivalent resistance R_{dr}

 

 Using “lumped RC” model for interconnect:



$$\begin{aligned}\tau_D &= R_{dr} C_{intrinsic} + (R_{dr} + R_{wire})(C_{wire} + C_{fanout}) \\ &= R_{dr} C_{intrinsic} + (R_{dr} + R_{wire})C_{fanout} + (R_{dr} + R_{wire})C_{wire}\end{aligned}$$

Effect of Interconnect Scaling

$$R_{wire} C_{wire} = \left[\rho \frac{L}{WH} \right] \left[\frac{\epsilon_{di}}{t_{di}} (WL) + \frac{2\pi\epsilon_{di}L}{\log(t_{di}/H)} \right] \propto \rho\epsilon_{di}L^2$$

- Interconnect delay scales as square of L
 \Rightarrow minimize interconnect length!
- If W is large, then it does not appear in $R_{wire} C_{wire}$
 - Capacitance due to fringing fields becomes more significant as W is reduced; C_{wire} doesn't actually scale with W for small W