

EECS 40, Fall 2007
Prof. Chang-Hasnain

Homework #3


Due at 5:00 pm in 240 Cory on THURSDAY, 9/27/07

Total Points: 100

- Put (1) your name and (2) discussion section number on your homework.
 - You need to put down all the derivation steps to obtain full credits of the problems. Numerical answers alone will at best receive low percentage partial credits.
 - No late submission will be accepted expect those with prior approval from Prof. Chang-Hasnain.
 - Problems of this HW are from Hambley 4th Edition
1. (Inductance and Capacitance) Read the «practical application » on p. 143-144. Answer the question on p. 144 : « Identify the features in Figure PA3.2 that are analogous to each of the circuit elements in Figure PA3.1 ». (8 points)
 2. (Inductance and Capacitance) (16 points)

$$x(t) = \begin{cases} 0 & \text{on } (-\infty, 1], \\ 4^*t-4 & \text{on } (1,2), \\ -4^*t+12 & \text{on } [2,3) \\ 0 & \text{on } [3, \infty) \end{cases}$$
 - a. The voltage $v(t)$ and current $i(t)$ across a .5F capacitor adhere to passive convention. Also, $V(0) = 0V$, and $i(0) = 0A$. Determine $i(t)$, power, and stored energy when $v(t)=x(t)$ as given above, and sketch. (8 points)
 - b. Find an expression for $v(t)$ when $i(t)=x(t)$, and sketch. (4 points)
 - c. Suppose instead that we are measuring current and voltage across a 4H inductor. Find an expression for $i(t)$ when $v(t)=x(t)$, and sketch. (4 points)
 3. P3.33 (Physical Characteristics of Capacitors) (5 points)
 4. P3.65 (Inductances in Series and Parallel) (10 points)
 5. P4.6 (First-Order RC Circuits) (10 points)
 6. P4.17 (First-Order RC Circuits). (16 points)
 - f) Also find an expression for the energy stored in capacitor 2, as a function of time. (3 points)
 - g) Find an expression for the power dissipated as a function of time by the resistor. (3 points)

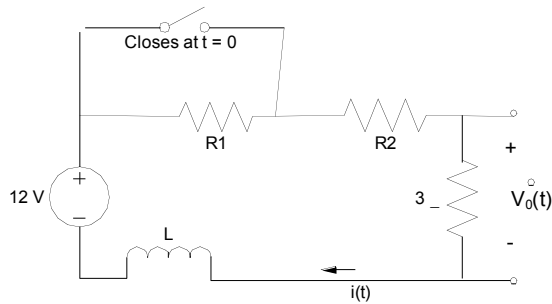7. (First order RL circuits). The circuit is at steady state at $t < 0$. The output V_0 of the circuit is given by $V_0(t) = 6 - 3e^{-35t}$ V when $t > 0$. (15 points)
- Write the initial voltage (at $t=0^-$) as a function of R_1 and R_2 . (3 points)
 - Write the steady state voltage (at $t=\infty$) in terms of R_1 and R_2 . (3 points)
 - Write the time constant for $t > 0$. (3 points)
 - Determine the values L , R_1 , and R_2 . (6 points)



8. P4.27 (DC Steady State) (5 points)
9. (RL and RC Circuits with General Sources). Consider a voltage source V_s across an inductor L and a resistor R . Write the differential equation for $i(t)$, and find the complete solution if $V_s = 15\cos(150t)$. (15 points)