

EECS 40, Fall 2007
Prof. Chang-Hasnain

Homework #4

Due at 5 pm in 240 Cory on Thursday, 10/04/07

Total Points: 100

- **Put (1) your name and (2) discussion section number on your homework.**
- **You need to put down all the derivation steps to obtain full credits of the problems. Numerical answers alone will at best receive low percentage partial credits.**
- **No late submission will be accepted expect those with prior approval from Prof. Chang-Hasnain.**
- **Problems of this HW are from Hambley 4th Edition**

P4.57 (Second-Order Circuits) (5 points)

The sketch should look like the $\zeta = 0.1$ curve in Fig 4.29. Severely underdamped ($\zeta \ll 1$) second-order circuits display a lot of overshoot and ringing.

P4.61 (Second-Order Circuits) (20 points)

This circuit is considered on pages 185-186.

a) Writing eq. 4.101 using KCL and comparing with 4.106 gives $\zeta = 1/(2RC) = 2 \cdot 10^7$, $\omega_0 = 1/(LC)^{.5} = 10^7$, and $\zeta = \zeta/\omega_0 = 2$. (3 pts)

Therefore our circuit is overdamped. (2 pts)

b) Using equation 4.100 (before differentiating) and evaluating at $t=0+$, we get

$$C v'(0+) + 1/R v(0+) + 1/L \int_0^t v(t) dt + i_L(0+) = i_n(0+)$$

Plugging in $v(0+) = 0$ and $i_L(0+) = 0$ and $v(t) = 0$ for $t < 0$, and $i_n(0+) = 1A$, we get $V'(0+) =$

$$1/C = 10^9.$$

c) Under steady-state conditions, the inductor acts as a short circuit. So $i_L(\infty)=0$, so the particular solution $v_p(t) = 0$. (5 pts)

d) The complementary solution (that which solves the homogenous equation) is of the form $K_1 \exp(s_1 t) + K_2 \exp(s_2 t)$. The particular solution was 0 by part (c). So the complete solution is $v(t) = K_1 \exp(s_1 t) + K_2 \exp(s_2 t)$. Plugging this into the differential equation in 4.106 gives us the $s_1 = -\alpha + \sqrt{\alpha^2 + \omega_0^2}$ and $s_2 = -\alpha - \sqrt{\alpha^2 + \omega_0^2}$. Evaluating these gives $-2.679 \cdot 10^6$ and $-37.32 \cdot 10^6$. Next, use the initial conditions

$$v(0+) = 0 \text{ and } v'(0+) = 10^9:$$

$$v(0+) = 0 = K_1 + K_2$$

$$v'(0+) = 10^9 = s_1 K_1 + s_2 K_2.$$

Solving, one finds $K_1 = 28.87$ and $K_2 = -28.87$. Therefore the solution is

$$v(t) = 28.87 \exp(s_1 t) - 28.87 \exp(s_2 t).$$

P5.10 (Sinusoidal Currents and Voltages) You may also sketch the Lissajous figures by hand. (10 points, 2.5 for each plot)

You can do this in MATLAB as follows:

```
Theta_vect = [ 90 45 0 0]*pi/180;
```

```
for i = 1:4
```

```
Wx = 2*pi;
```

```
Wy = Wy_vect(i)
```


```
Theta = Theta_vect(i);
```

```
t = 0:0.01:20;
```

```
x = cos(Wx*t);
```

```
y = cos(Wy*t + Theta);
```

```
Subplot(2,2,i)
plot(x,y)
end
```

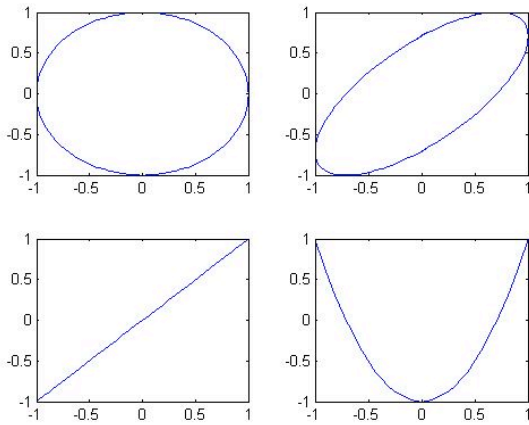

P5.16 (RMS-value) (5 points)

$$V_{\text{rms}} = \sqrt{\left(\frac{1}{T} \int_0^T v^2(t) dt \right)} = \sqrt{\left(\int_0^1 [3 \exp(-t)]^2 dt \right)} = \sqrt{\left(\int_0^1 [9 \exp(-2t)] dt \right)} = \sqrt{\left(\frac{9}{2} [\exp(-2t)]_{t=0}^{t=1} \right)} = \sqrt{\left(4.5*(1-\exp(-2)) \right)} = 1.973 \text{ V}$$

Elementary operations (Complex Arithmetic) (12 points, 2 each)

Perform the following operations:

- $(5 + j3) + (3 - j7) = (5+3) + j(3-7) = 8 - j4$
- $(2 + j5) - (9 + j4) = (2-9) + j(5-4) = -7 + j$
- $(7 + j8)(4 - j2) = 4*7 + j(8*4 - 2*7) - j^2 2*8 = 28 + 16 + j(18) = 44 + j18$

$$d) \frac{(1+j3)}{(4+j9)} = (4-j9)(1+j3)/(16+81) = (4 + 27 + 3j)/(97) = (31 + 3j)/97 = 0.3196 + j 0.0309$$

$$e) \text{ Convert } (1+j3) \text{ into polar form. } = (1+9)^{.5} * e^{(j \arctan(3/1))} = 10^{.5} * \exp(j \arctan(3)) = 3.16 \exp(j 1.25 * 180/\pi) = 3.16 \exp(j 72^\circ)$$

$$f) \text{ Convert } 2e^{j35^\circ} \text{ into rectangular form } = 2\cos(35^\circ) + j \sin(35^\circ) = 1.64 + j 1.15$$

P5.25 (Phasors) (10 points)

$$V_1(t) = 100 \cos(\omega t + 45^\circ)$$

$$V_2(t) = 150 \sin(\omega t + 60^\circ)$$


Rewriting as phasors, we get:

$$V_1 = 100 \angle 45^\circ = 70.71 + j 70.71$$

$$V_2 = 150 \angle -30^\circ = 129.9 - j 75$$

$$V_s = V_1 + V_2 = 200.6 - j 4.29 = 200.6 \angle -1.23^\circ$$
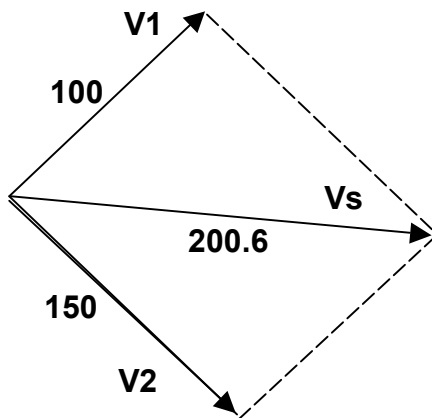
$$V_s(t) = 200.6 \cos(\omega t - 1.23^\circ)$$



V2 lags V1 by 75°. Vs lags V1 by 46.23°. Vs leads V2 by 28.77°.


P5.24 (Phasors) (8 points)

The magnitude of the phasors are $8\sqrt{2}$ and $3\sqrt{2}$. If the phase angle is the same then you get the maximal value by just adding the phasor magnitudes to get $11\sqrt{2}$. The minimal value is achieved when they are 180° out of phase, so that you just subtract them to get $5\sqrt{2}$.

Wheatstone Bridge (Complex Impedances) (? points)

The circuit on the right hand side shows a generalized version of the Wheatstone Bridge. Z_1, Z_2, Z_3, Z_4 are complex impedances.

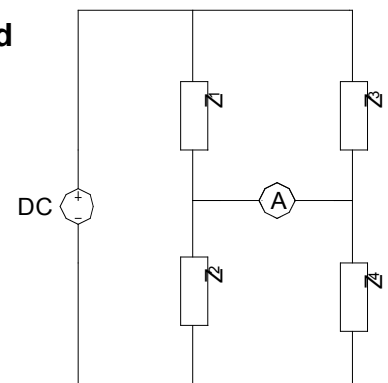Derive the condition for the current through the amperemeter to be zero. (3 points)



$$Z_1/(Z_1 + Z_2) = Z_3/(Z_3+Z_4) \quad \square \quad Z_4/Z_3 = Z_2/Z_1$$

Let $f = 60\text{Hz}$, Z_1 consists of a 60Ω resistor and a 0.2H inductance, Z_2 is a 100Ω resistor. Z_3 consists of a 200Ω resistor and a $10 \mu\text{F}$ capacitor. Calculate the complex impedances of Z_1, Z_2, Z_3 . (9 points)

$$Z_1 = R + j\omega L = 60 + j(2\pi \cdot 60) \cdot 0.2 = 60 + j 75.4 = (60^2 + 75^2)^{.5} \square \arctan(75/60) = 96.4 \square 51.5^\circ$$

$$Z_2 = 100$$

$$Z_3 = 200 - j/(\omega C) = 200 - j/(2\pi \cdot 60 \cdot 10 \cdot 10^{-6}) = 200 - j 53 \sim 200 = 206.9 \square -14.8^\circ$$

(3 points each)

Calculate Z_4 such that there is no current flowing through the amperemeter.

With which circuit elements can you construct Z_4 ? (6 points)

$$Z_4 = Z_3 * Z_2 / Z_1 = (206.9 \angle -14.8^\circ) * 100 / (96.4 \angle 51.5^\circ) = 214.6 \angle -66.3^\circ = 86.3 - j196.5$$

We can construct Z_4 out of a 86.3Ω resistor and a capacitor satisfying $1/(\omega C) = j196.5$, so $C = 1/(\omega * 196.5) = 1/(2\pi * 60 * 196.5) = 13.5 \mu\text{F}$.

(2 point writing right equations, 2 point identifying correct element based on sign, 2 point computations)

P5.38 (Complex Impedances) (10 points)

a) From the plot, we see that $T = 4\text{ms}$, so $f = 1/T = 250\text{ Hz}$ and $\omega = 2\pi f = 500\pi$ (1 point). Current lags (1 point) voltage by $1\text{ms} = T/4 = 90^\circ$, so we have an inductance (1 point for correct, based on previous part). $\omega L = V_m/I_m = 5\pi$, so $L = 3.18\text{ mH}$ (2 points).

b) We see that $T = 8\text{ms}$, so $\omega = 2\pi f = 250\pi$ (1 point). Current leads (1 point) voltage by 2ms , or 90° , so we have a capacitance (1 point). $1/\omega C = V_m/I_m = (10\text{V})/(4\text{mA}) = 2.5 * 10^3 = 2500$, so $C = .5093 \mu\text{F}$ (2 points).