
EE40
Lecture 21
Prof. Chang-Hasnain

10/22/07
Reading: Chap. 14

Recap: Transfer Function

- Transfer function= $H(f) = V_{out}/V_{in}$
- It is a complex number and typically a function of frequency.

$$\mathbf{H}(f) = \frac{\mathbf{V}_{out}}{\mathbf{V}_{in}} = \frac{V_{out}}{V_{in}} \angle (\theta_{out} - \theta_{in})$$

$$\mathbf{H}(f) = |\mathbf{H}(f)| \angle \theta(f)$$

$|\mathbf{H}(f)|$ is the magnitude

$\theta(f)$ is the phase

Both are functions of frequency f .

Cascaded Transfer Function - 1

$$\mathbf{H}(f) = \mathbf{H}_1(f) \cdot \mathbf{H}_2(f)$$

$$|\mathbf{H}(f)| = |\mathbf{H}_1(f)| \cdot |\mathbf{H}_2(f)|$$

$$\theta(f) = \theta_1(f) + \theta_2(f)$$

$$y = 20 \log |\mathbf{H}(f)| = 20 \log |\mathbf{H}_1(f)| + 20 \log |\mathbf{H}_2(f)| = y_1 + y_2$$

- Bode magnitude plot will be the sum of the two magnitude plots in dB
- Phase will be sum

Cascade Transfer Function - 2

$$\mathbf{H}(f) = \frac{\mathbf{H}_1(f)}{\mathbf{H}_2(f)}$$

$$\theta(f) = \theta_1(f) - \theta_2(f)$$

$$Y = 20 \log |\mathbf{H}(f)| = 20 \log |\mathbf{H}_1(f)| - 20 \log |\mathbf{H}_2(f)|$$

- Bode magnitude plot will be the difference of the two magnitude plots in dB
- Phase will be difference

Example 1

$$H(\omega) = H_1(\omega) \cdot H_2(\omega)$$


$$H_1(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_1}} \quad \text{Low pass}$$

$$H_2(\omega) = \frac{1}{1 - j\frac{\omega}{\omega_2}} \quad \text{High pass}$$

$$\text{if } \omega_1 > \omega_2, \quad BW = \frac{\omega_2 - \omega_1}{2\pi}$$

The cascaded filter is band pass

if $\omega_1 < \omega_2$, nothing passes

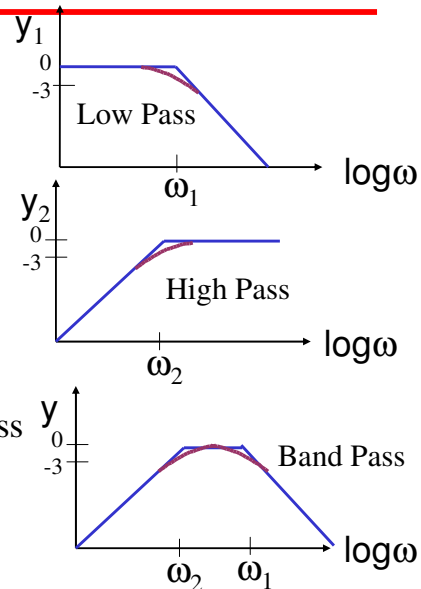

Example 2

$$H(\omega) = H_1(\omega) \cdot H_2(\omega)$$


$$H_1(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_1}} \quad \text{Low pass}$$

$$H_2(\omega) = \frac{1}{1 + j\frac{\omega}{\omega_2}} \quad \text{Low pass}$$

The cascaded filter is low pass.

if $\omega_1 = \omega_2$, y is 6dB down

Corresponding to $Q = \frac{1}{2}$, $\zeta = 1$

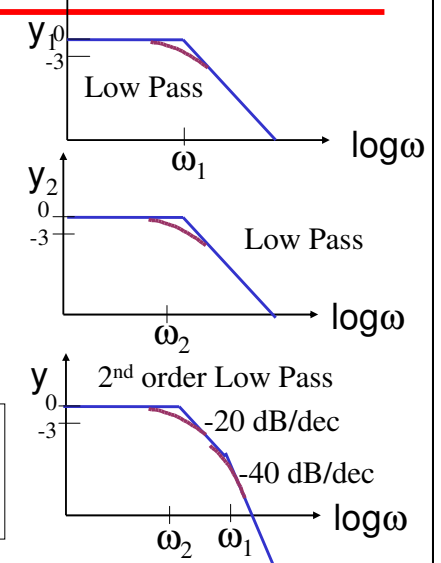

Chapter 14


- OUTLINE
 - Op-Amp from 2-Port Blocks
 - Op-Amp Model and its Idealization
 - Negative Feedback for Stability
 - Components around Op-Amp define the Circuit Function
- Reading
 - Chap 14

The Operational Amplifier

- The **operational amplifier** (“*op amp*”) is a basic building block used in analog circuits.
 - Its behavior is modeled using a dependent source.
 - When combined with resistors, capacitors, and inductors, it can perform various useful functions:
 - **amplification/scaling** of an input signal
 - **sign changing** (inversion) of an input signal
 - **addition** of multiple input signals
 - **subtraction** of one input signal from another
 - **integration** (over time) of an input signal
 - **differentiation** (with respect to time) of an input signal
 - **analog filtering**
 - **nonlinear functions** like exponential, log, sqrt, etc
 - Isolate input from output; allow cascading

Op Amp Terminals

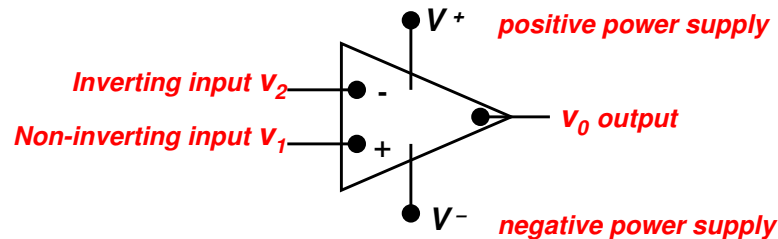- 3 signal terminals: 2 inputs and 1 output
- IC op amps have 2 additional terminals for DC power supplies
- Common-mode signal = $(v_1 + v_2)/2$
- Differential signal = $v_1 - v_2$



Model for Internal Operation

- A is differential gain or open loop gain
- Ideal op amp

$$A \rightarrow \infty$$

$$R_i \rightarrow \infty$$

$$R_o = 0$$


- Common mode gain = 0

$$v_{cm} = \frac{(v_1 + v_2)}{2}, v_d = v_1 - v_2$$

$$v_o = A_{cm}v_{cm} + A_d v_d$$

$$\text{Since } v_o = A(v_1 - v_2), A_{cm} = 0$$


- Circuit Model

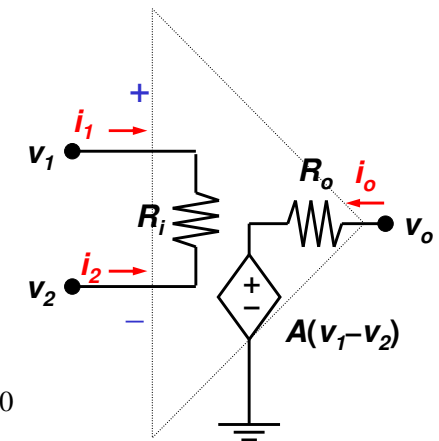

Model and Feedback

- Negative feedback
 - connecting the output port to the negative input (port 2)
- Positive feedback
 - connecting the output port to the positive input (port 1)
- Input impedance: R looking into the input terminals
- Output impedance: Impedance in series with the output terminals

- Circuit Model

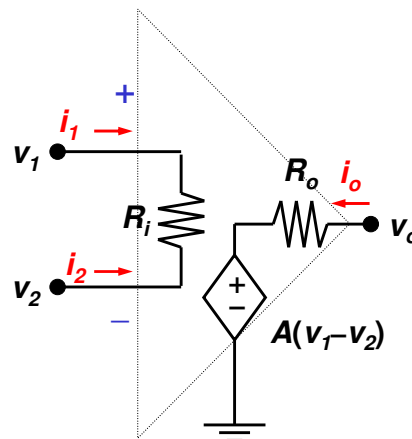


Summing-Point Constraint

- Check if under negative feedback
 - Small v_i result in large v_o
 - Output v_o is connected to the inverting input to reduce v_i
 - Resulting in $v_i = 0$
- Summing-point constraint
 - $v_1 = v_2$
 - $i_1 = i_2 = 0$
- Virtual short circuit
 - Not only voltage drop is 0 (which is short circuit), input current is 0
 - This is different from short circuit, hence called “virtual” short circuit.

Non-Inverting Amplifier

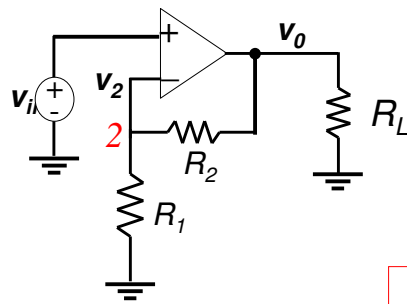- Ideal voltage amplifier $Closed\ loop\ gain = A_v = \frac{v_o}{v_{in}}$



$$v_1 = v_2 = v_{in}, i_1 = i_2 = 0$$

Use KCL At Node 2.

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$

$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1}$$


$$Input\ impedance = \frac{v_{in}}{i} \rightarrow \infty$$

Ideal voltage source – independent of load resistor

Since V_o is independent of R_L , Output impedance is 0.

Inverting Amplifier

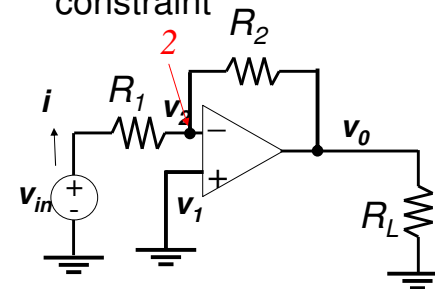- Negative feedback \rightarrow checked $Closed\ loop\ gain = A_v = \frac{v_o}{v_{in}}$
- Use summing-point constraint $v_1 = v_2 = 0, i_1 = i_2 = 0$
Use KCL At Node 2.



$$i = \frac{(v_{in} - v_2)}{R_1} = \frac{(v_{out} - v_2)}{R_2}$$

$$v_o = -\frac{R_2 v_o}{R_1}$$

$$Input\ impedance = \frac{v_{in}}{i} = R_1$$


Ideal voltage source – independent of load resistor

Since V_o is independent of R_L , Output impedance is 0.

EE40 Lecture 22 Prof. Chang-Hasnain

10/24/07
Reading: Chap. 14

Voltage Follower

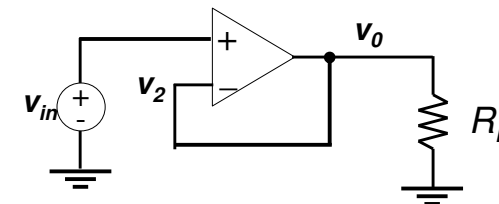


$$R_2 = 0$$

$$R_1 \rightarrow \infty$$

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$

$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1} = 1 + \frac{R_2}{R_1} = 1$$

Example 1

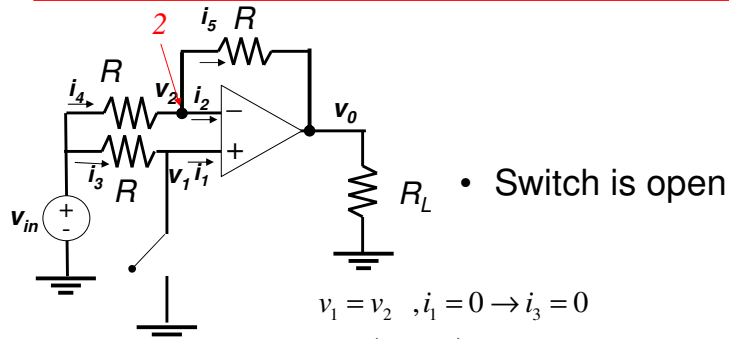

• Switch is open


$$v_1 = v_2, i_1 = 0 \rightarrow i_3 = 0$$

$$i_3 = \frac{(v_{in} - v_1)}{R} \rightarrow v_1 = v_2 = v_{in} \rightarrow i_4 = 0 \rightarrow i_5 = 0$$

$$i_5 = \frac{(v_0 - v_2)}{R} \rightarrow v_0 = v_2 = v_{in}$$

$$A = \frac{v_o}{v_{in}} = 1, R_{in} \rightarrow \infty$$

Example 1

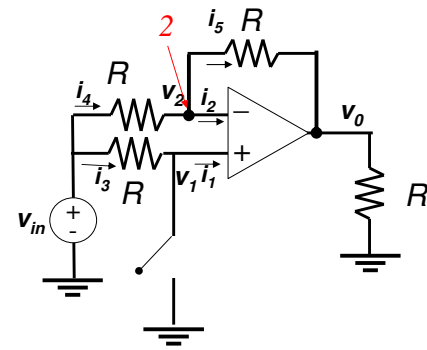

• Switch is closed

$$v_1 = v_2 = 0, i_1 = 0 \rightarrow i_3 = 0$$

$$i_4 = \frac{(v_{in} - v_2)}{R} = i_5 = -\frac{(v_0 - v_2)}{R}$$


$$v_0 = -v_{in}$$

$$A = \frac{v_o}{v_{in}} = -1, R_{in} = R/2$$

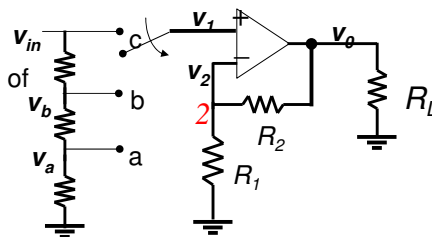Example 2

• Design an analog front end circuit to an instrument system

- Requires to work with 3 full-scale of input signals (by manual switch):
0 ~ ±1, 0 ~ ±10, 0 ~ ±100 V
- For each input range, the output needs to be 0 ~ ±10 V
- The input resistance is 1MΩ



$$v_o = (1 + \frac{R_2}{R_1})v_1$$

$$v_1 = v_{in} \text{ Switch at } c$$

$$v_1 = \frac{R_a + R_b}{R_a + R_b + R_c} v_{in} \text{ Switch at } b$$

$$v_1 = \frac{R_a}{R_a + R_b + R_c} v_{in} \text{ Switch at } a$$

Example 2 (cont'd)

$$R_{in} = R_a + R_b + R_c = 1M\Omega$$

$$\text{Max } A_v = 10 = (1 + \frac{R_2}{R_1}) \text{ Switch at } c$$


$$A_v = 1 = \frac{R_a + R_b}{R_a + R_b + R_c} (1 + \frac{R_2}{R_1}) \text{ Switch at } b \therefore \frac{R_a + R_b}{R_a + R_b + R_c} = 0.1$$

$$A_v = 0.1 = \frac{R_a}{R_a + R_b + R_c} (1 + \frac{R_2}{R_1}) \text{ Switch at } a \therefore \frac{R_a}{R_a + R_b + R_c} = 0.01$$


$$\therefore R_a = 10k\Omega, R_b = 90k\Omega, R_c = 900k\Omega$$

$$R_2 = 9R_1$$

Summing Amplifier

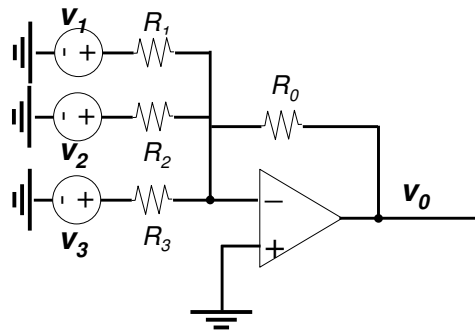


Difference Amplifier

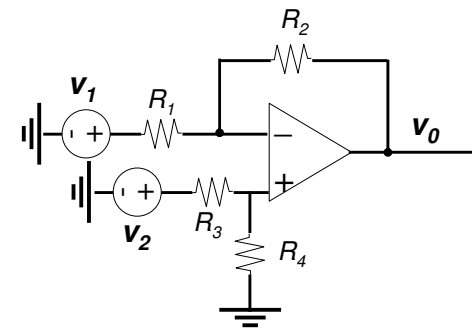


Integrator


- Want $v_o = K \int v_{in} dt$

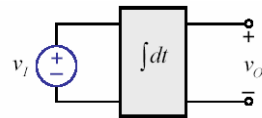

- What is the difference between:

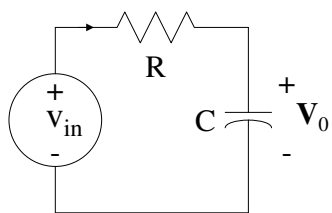



$$v_o \approx \frac{1}{RC} \int v_i dt$$

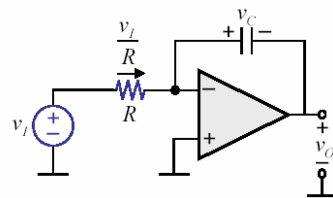

$$v_o = -\frac{1}{C} \int \frac{v_i}{R} dt$$

Differentiator


- Want

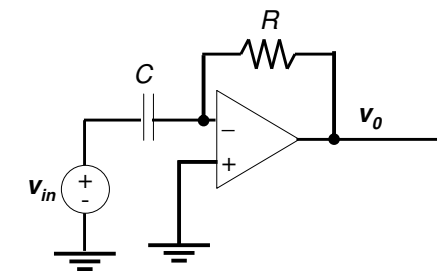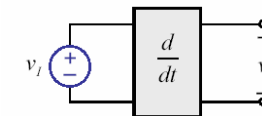

EE40 Lecture 23 Prof. Chang-Hasnain

10/26/07
Reading: Chap. 14


Bridge Amplifier

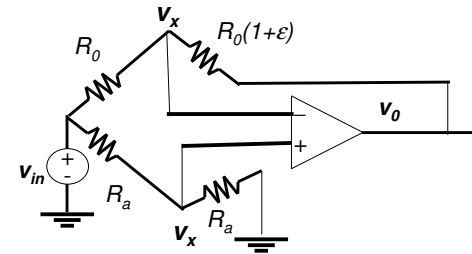

Application: Digital-to-Analog Conversion

A DAC can be used to convert the digital representation of an audio signal into an analog voltage that is then used to drive speakers -- so that you can hear it!

"Weighted-adder D/A converter"

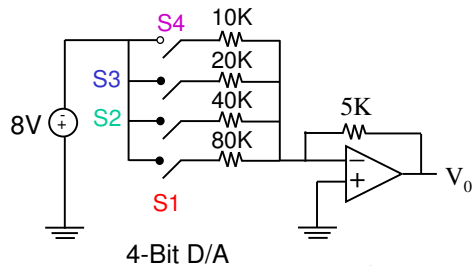


(Transistors are used as electronic switches)

- S1 closed if LSB = 1
- S2 " if next bit = 1
- S3 " if " " = 1
- S4 " if MSB = 1

Binary number	Analog output (volts)
0000	0
0001	.5
0010	1
0011	1.5
0100	2
0101	2.5
0110	3
0111	3.5
1000	4
1001	4.5
1010	5
1011	5.5
1100	6
1101	6.5
1110	7
1111	7.5

MSB LSB


Characteristic of 4-Bit DAC

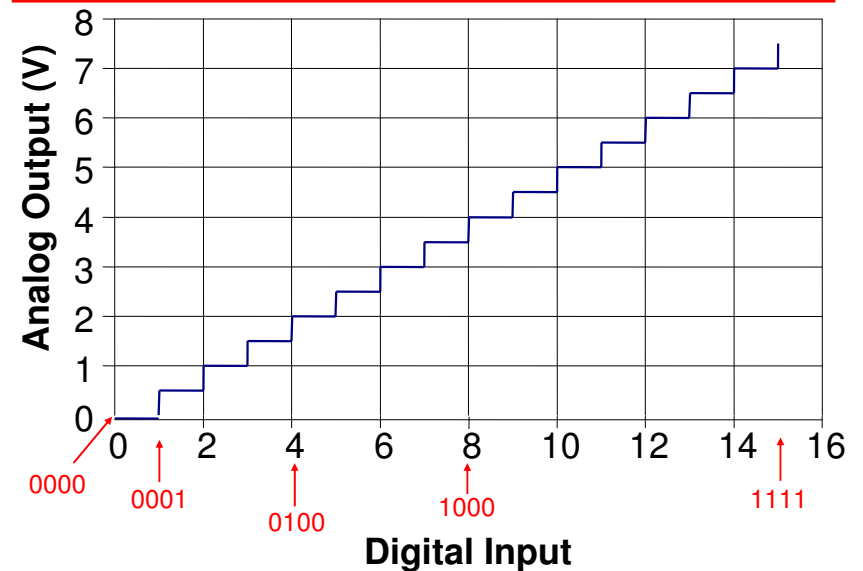

Active Filter

- Contain few components
- Transfer function that is insensitive to component tolerance
- Easily adjusted
- Require a small spread of components values
- Allow a wide range of useful transfer functions

Active Filter Example

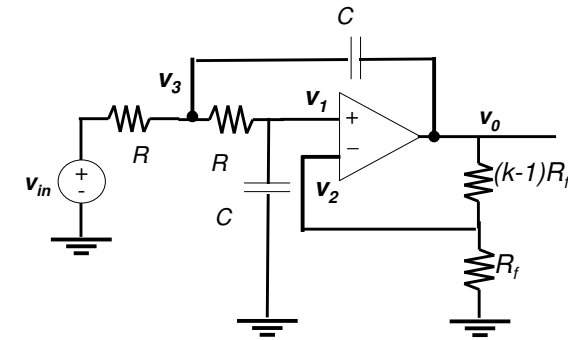

Active Filter Solution

$$v_1 = v_2 = \frac{v_o}{k}$$

$$\text{Use KCL At Node A} \Rightarrow \frac{(v_3 - v_1)}{R} = j\omega C v_1$$

$$\text{Use KCL At Node B} \Rightarrow \frac{(v_{in} - v_3)}{R} = j\omega C (v_3 - v_o) + \frac{(v_3 - v_1)}{R}$$

$$\frac{v_o}{v_{in}} = \frac{k}{1 - \omega^2 R^2 C^2 + j\omega RC(3-k)}$$

$$\text{Let } \omega_B = 1/RC$$

$$|H(\omega)| = \left| \frac{v_o}{v_{in}} \right| = \frac{k}{\sqrt{\left(1 - \frac{\omega^2}{\omega_B^2}\right)^2 + \frac{\omega^2}{\omega_B^2} (3-k)^2}}$$


$$\omega = 0, |H(\omega)| = k \text{ DC gain}$$

$$\omega = \omega_B, |H(\omega)| = \frac{k}{3-k}$$

$$\omega \gg \omega_B, |H(\omega)| = \frac{k}{\left(\frac{\omega^2}{\omega_B^2}\right)} \sim \omega^{-2}$$

$20 \log |H(\omega)|$ decays at a rate of 40dB/decade

Cascaded Active Filter Example

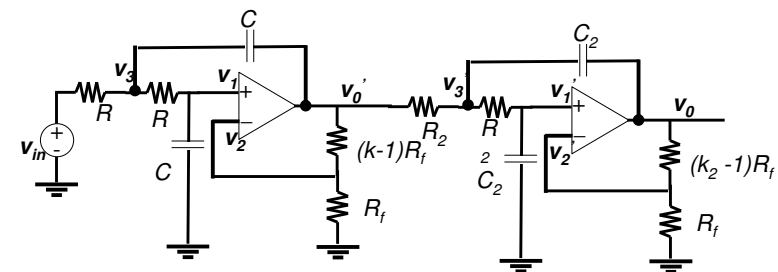

Cascaded Active Filter Solution

$$\frac{v_o}{v_{in}} = \frac{k_2}{1 - \omega^2 R_2^2 C_2^2 + j\omega R_2 C_2 (3 - k_2)} \frac{k}{1 - \omega^2 R^2 C^2 + j\omega RC(3 - k)}$$

Let $\omega_B = 1/RC$, $\omega_{B2} = 1/R_2 C_2$

$$|H(\omega)| = \left| \frac{v_o}{v_{in}} \right| = \frac{k_2}{\sqrt{\left(1 - \frac{\omega^2}{\omega_{B2}^2}\right)^2 + \frac{\omega^2}{\omega_{B2}^2} (3 - k_2)^2}} \frac{k}{\sqrt{\left(1 - \frac{\omega^2}{\omega_B^2}\right)^2 + \frac{\omega^2}{\omega_B^2} (3 - k)^2}}$$

$\omega = 0, |H(\omega)| = k_2 k$ DC gain

$$\omega = \omega_B, |H(\omega)| = \frac{k_2}{3 - k_2} \frac{k}{3 - k}$$

$$\omega \gg \omega_B, |H(\omega)| = \frac{k_2 k}{\left(\frac{\omega^4}{\omega_{B2}^2 \omega_B^2}\right)} \sim \omega^{-4}$$

$20 \log |H(\omega)|$ decays at a rate of 80dB/decade