

---

**EE40**  
**Lecture 33**  
**Prof. Chang-Hasnain**

11/28/07  
Clamp Circuit

## Clamp circuit

---


- It is a diode wave-shaping circuit
- It is used to add a DC component to an AC input wave forms so that
  - Either positive or negative peaks are clamped to not exceed a certain value.
- Consideration: capacitor is large so that
  - Under AC steady-state, capacitor voltage stays constant
- Do not worry about the first few cycles when you solve the clamp circuit – except for the level shifter (lecture notes 11/28-2).

## Steps to solve clamp circuit:

---


- Get the DC steady state value for  $V_0$  for  $V_{in}=0$ 
  - Under time variation, i.e. with  $V_{in}=V_a \sin(\omega t)$ , the min or max value of  $V_0$  should be this value.
- Decide whether it is clamped at max or min side.
  - The clamping happens when the diodes are ON, i.e. when there is current flow. This is to say when diode is forward-biased or Zener is reverse-biased at  $V_{BR}$ .

## Example: Figure 10.33 (p 495)

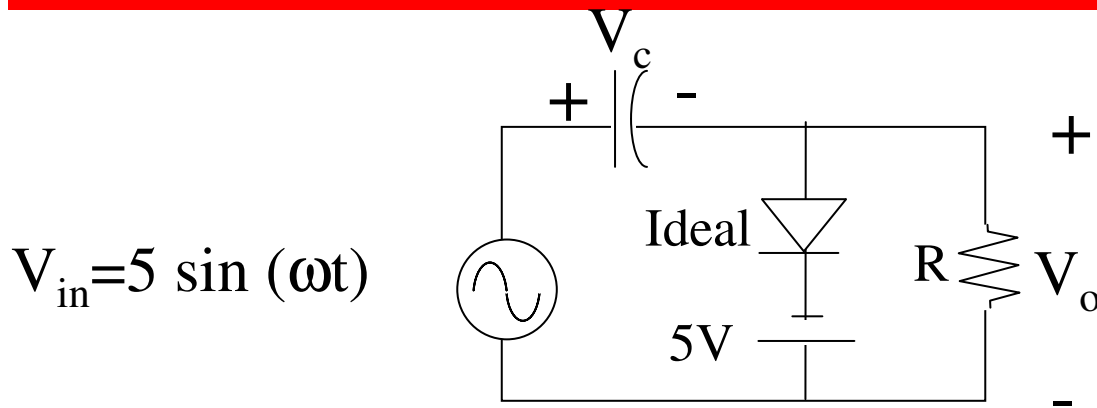

1. Get the DC steady state value for  $V_o$  for  $V_{in}=0$ 
  1. This is when the capacitor is open circuit.
  2. In this case, the diode is ON and since it is an ideal diode, there is no voltage across it.
  3.  $V_o = -5V$
  4.  $V_o = V_{in} - V_c$ ; since  $V_{in}=0$ ,  $V_c=5V$
2.  $V_o = V_D - 5$ ; since  $V_D$  cannot be larger than 0,  $V_o$  cannot be larger than -5. This is the same as saying  $V_o \leq -5$
3. So in this case,  $V_o = 5 \sin(\omega t) - 5$

## Example: Figure 10.34 (p 495)

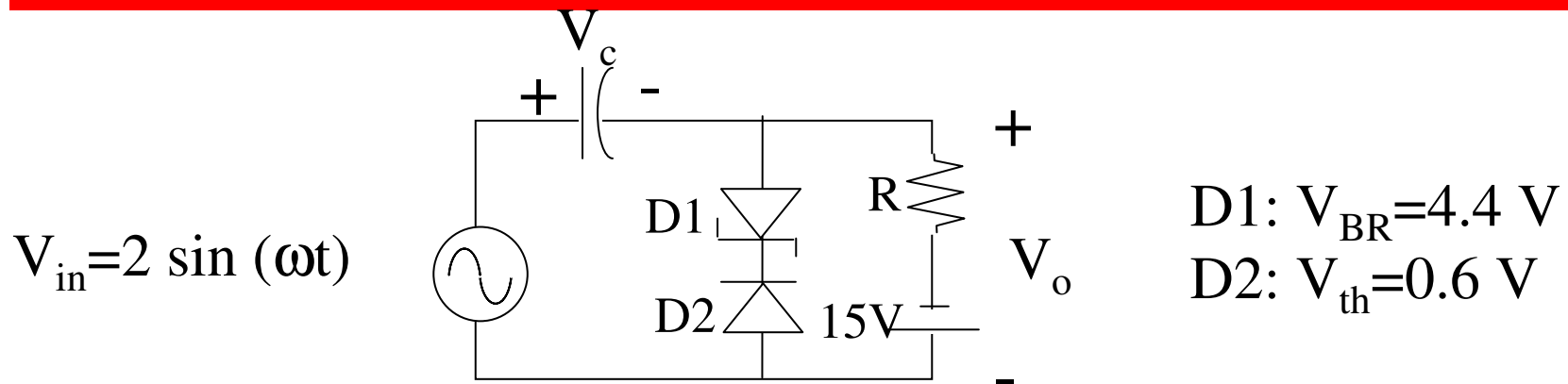

1. Get the DC steady state value for  $V_o$  for  $V_{in}=0$ 
  1. This is when the capacitor is open circuit.
  2. In this case, the diode D2 (and D1) has to be ON and a 15V is applied in forward bias condition and larger than  $4.4+0.6=5\text{V}$ .
  3.  $V_o = -(0.6+4.4) = -5\text{V}$
2.  $V_o = -(V_{D2} - V_{D1})$ ; since  $V_{D2}$  cannot be larger than 0.6,  $V_{D1}$  cannot be smaller than 4.4,  $V_{D2} - V_{D1}$  cannot be larger than 5. Hence,  $V_o$  cannot be smaller than -5.  $V_o \geq -5$
3. So in this case,  $V_o = 2 \sin(\omega t) - 3$