

Administrivia

- People on the waitlist?
- Midterm stuff
 - Look under Exams link on the EECS 40 homepage
- HW #2 deadline is extended till Friday, July 11th, 12:10 pm.
- HW #3 is up. Due next Wednesday July 16th (before midterm).

Last Time...

- Operational Amplifiers
- Do you have questions on op-amps?


This Time...

- Source transformations
- Maximum power transfer theorem
- Review of circuit analysis

Source transformations

- Another circuit reduction technique - makes life easier if applied quickly and correctly.
- Like the name implies - we can transform a voltage source in series with a resistance to a current source in parallel with a resistance (and vice-versa)


Source transformations - Theory

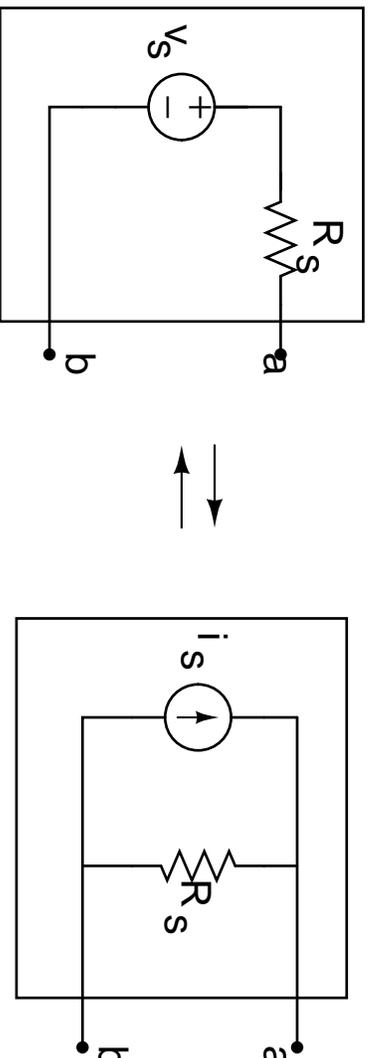

- We need to find a relationship between i_s and v_s so the two configurations above are equal.
- By “equal” I mean - a load resistor R_L connected across ab experiences the same current flow in both configurations (and hence the same voltage drop in both configurations).

Source transformations - example 1

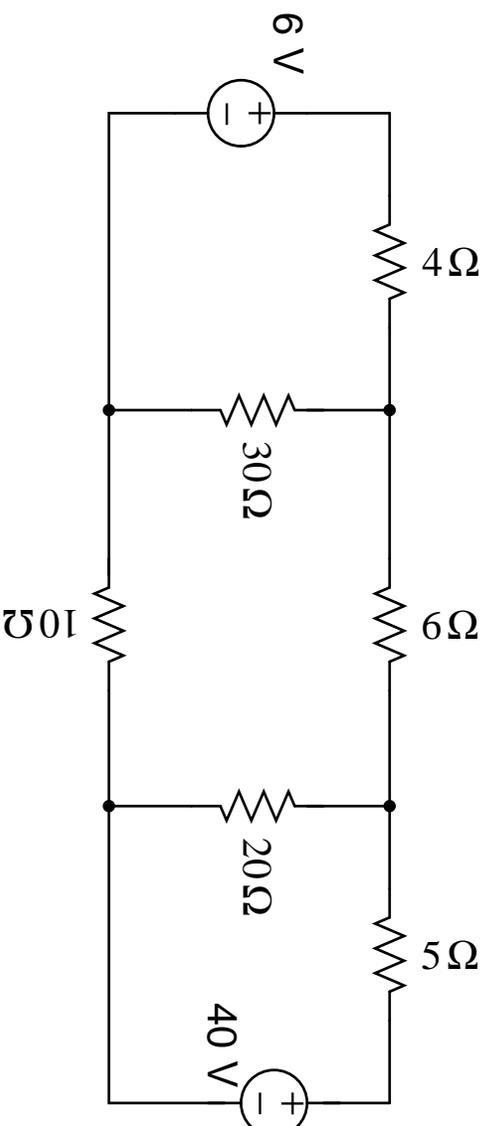
- (Ex. 4.8) Find the power associated with the 6 V source in figure below.



- Let us think about this problem first...


Source transformations - tips

- Concept of a Norton equivalent:

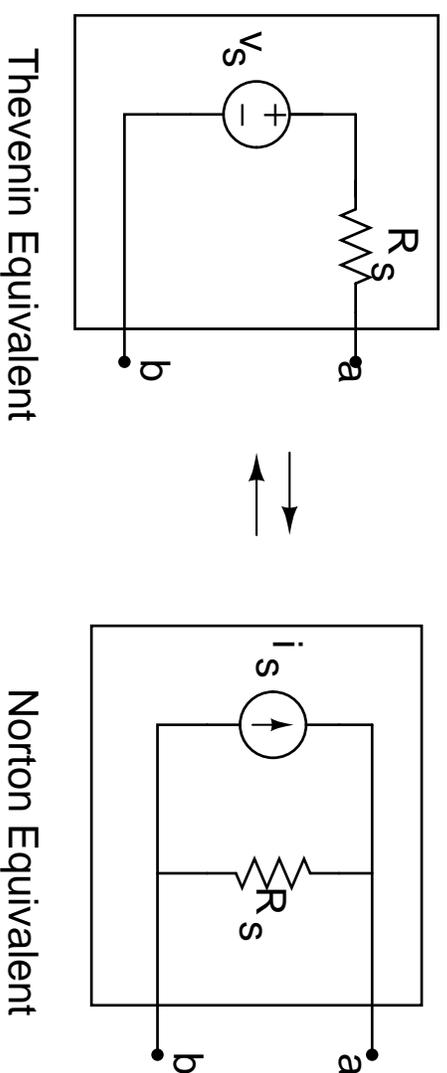


Source transformations - tips

- Other equivalent circuits:

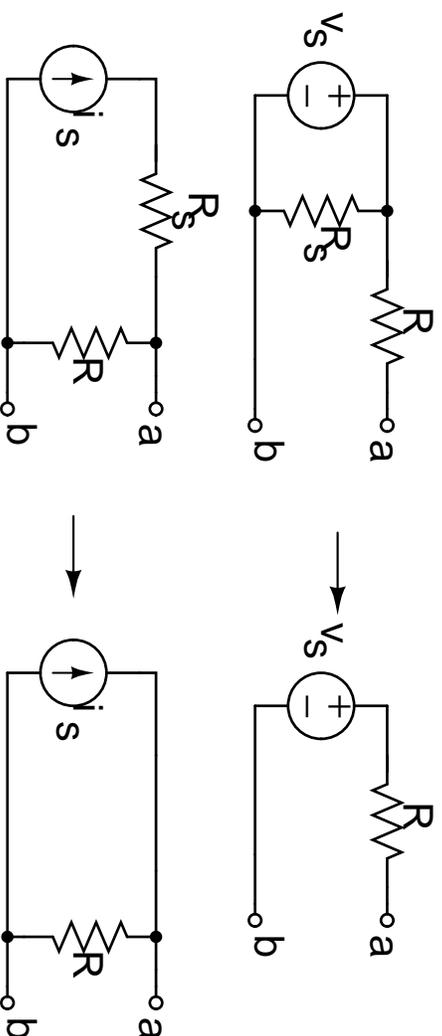

Maximum power transfer theorem

- Concept:

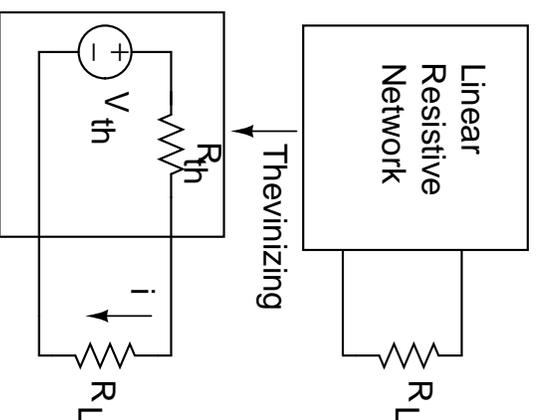

- Question: What value of R_L maximizes the power delivered to R_L ?
- Application: “Matching” of components in audio system. For example, if the output impedance of an amplifier is 8Ω , it should be used with an 8Ω loudspeaker to achieve maximum power output.

Maximum power transfer theorem

- Result: Maximum power is dissipated in R_L when $R_L = R_{th}$
 - Proof: First, the expression for power dissipated in R_L :

$$P(R_L) = i^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L$$

- Differentiate P with respect to R_L , set it equal to zero (V_{th} and R_{th} are given, R_L is the variable).

Review of circuit analysis

- Circuit Analysis Technique: NODAL ANALYSIS. Steps:
 - Select a reference node
 - Label the unknown node voltages
 - Write KCL at each unknown node
 - Use device I/V characteristics to rewrite unknown currents in terms of unknown node voltages
 - If you have dependent sources, you need constraint equations.
 - Sometimes a supernode might be useful.
- Circuit Simplification Technique(s):
 - Combining resistors in parallel and series.
 - Voltage and current divider

Review of circuit analysis

- Circuit Simplification Technique(s):
 - Thevenin's theorem
 - Source transformations
 - Norton's theorem
- Applications:
 - RC circuits
 - Op amps
 - Maximum power transfer theorem

Summary

- Official circuit analysis part of the course is over!
- Wrapped up with source transformations and maximum power transfer theorem.

In Conclusion...

- Next time:
 - Guest lecturer: Prof. Tsu-Jae King.
 - Homepage: <http://www.eecs.berkeley.edu/~tking>
 - Please skim through chapter 5 in reader.
 - After guest lecture, I will review HW #2.
- REMEMBER CHECK FOR CALBOT KIT - I will talk about Calbot on Monday.
- Questions?