

# EE 40

## Final Exam Review Set #1


### Solutions

For the design problems, many solutions are possible!

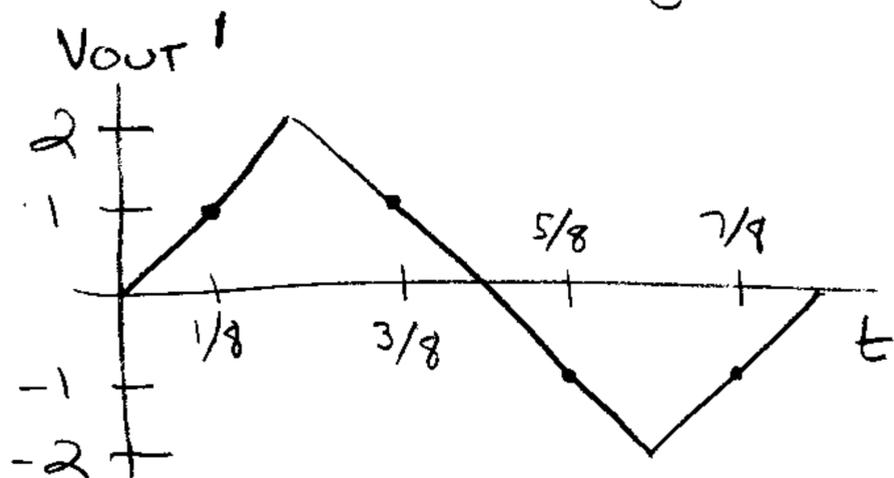
Problem 1: Work backwards.

$V_{out}$  looks like the "tips" of a triangle wave. Clippers cut off the tips of wave forms.

So if I could get a triangle wave input  $V_{out}'$



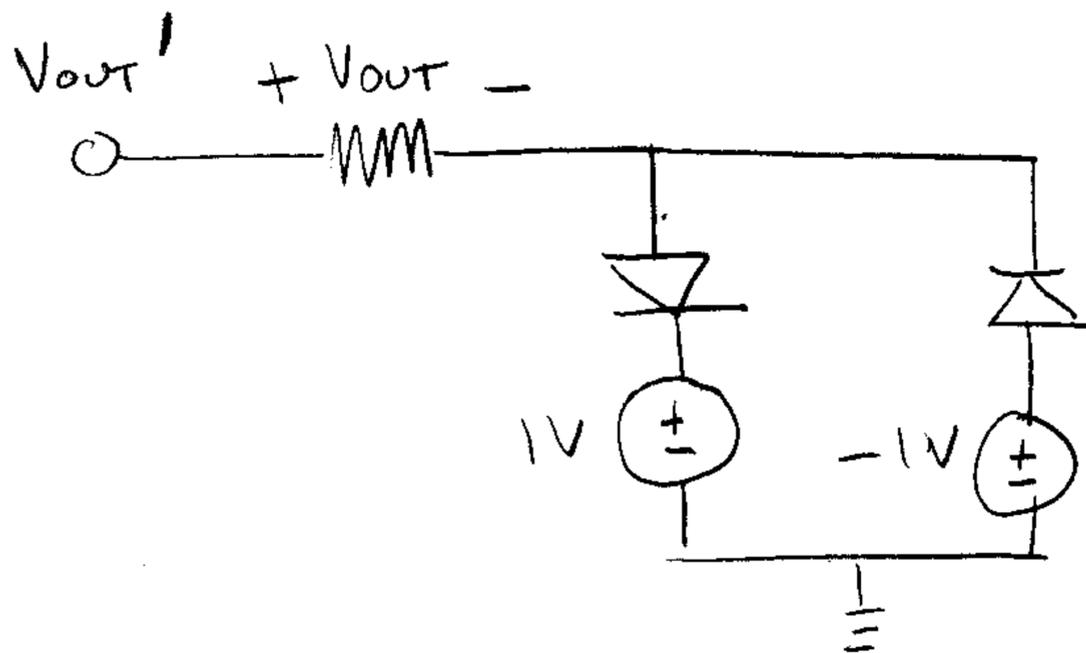
then putting this through a clipper would work.




assuming ideal diode model - adjust voltage sources for  $V_F \neq 0$ .

2


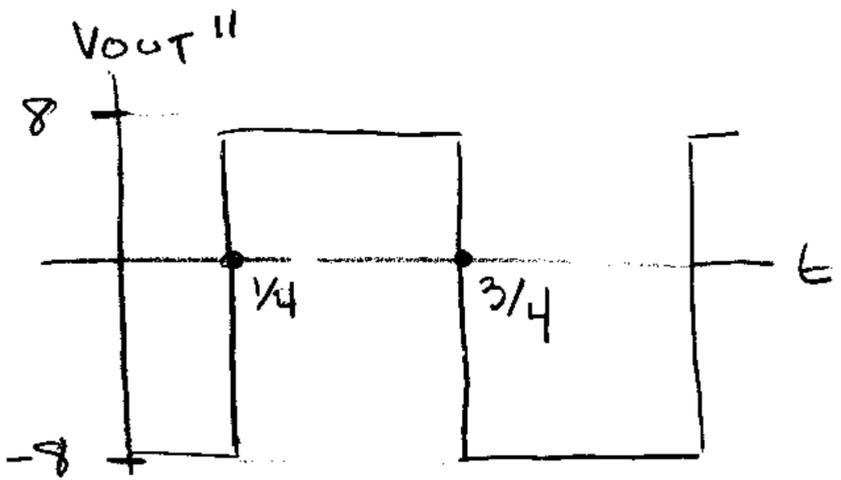
How to get  $V_{out}^1$ ? Integrate square wave.  
Suppose I use an integrator with  $RC=1$ .  
Then to get  $V_{out}^1$ , send through  $V_{out}^2$ :



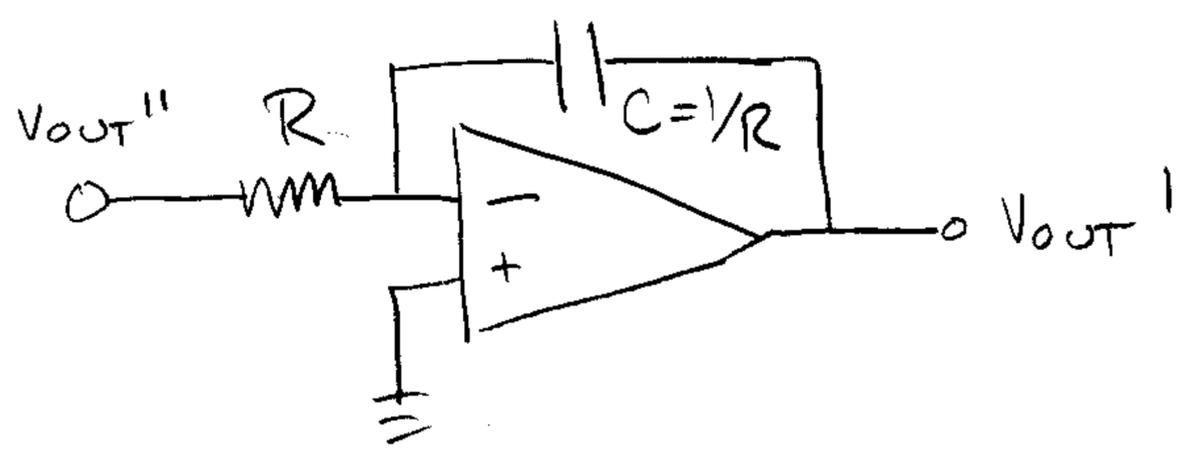
$V_{out}^1$  increases at a rate of  $8V/s$  for  $1/4s$ , decreases at  $8V/s$  for  $1/2s$ , increases for  $1/2s$ , etc. Integrator adds - sign!



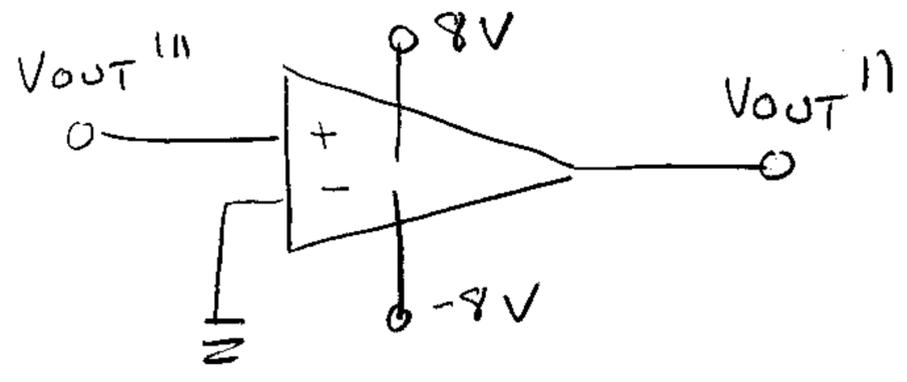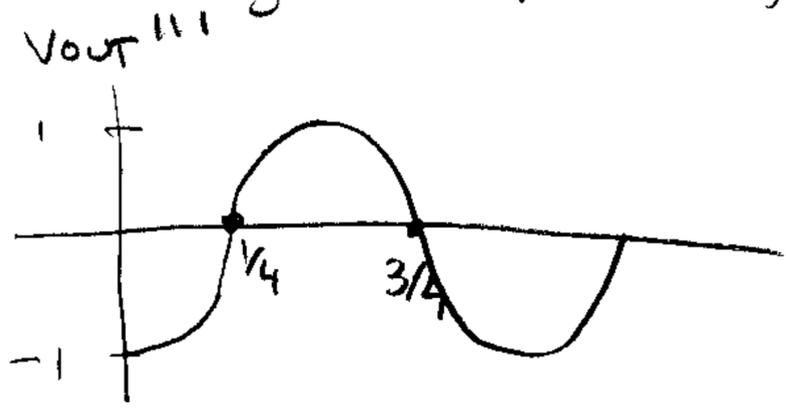How to get  $V_{out}^2$ ? If we put  $-\cos(2\pi t)$  through comparator, that would work.




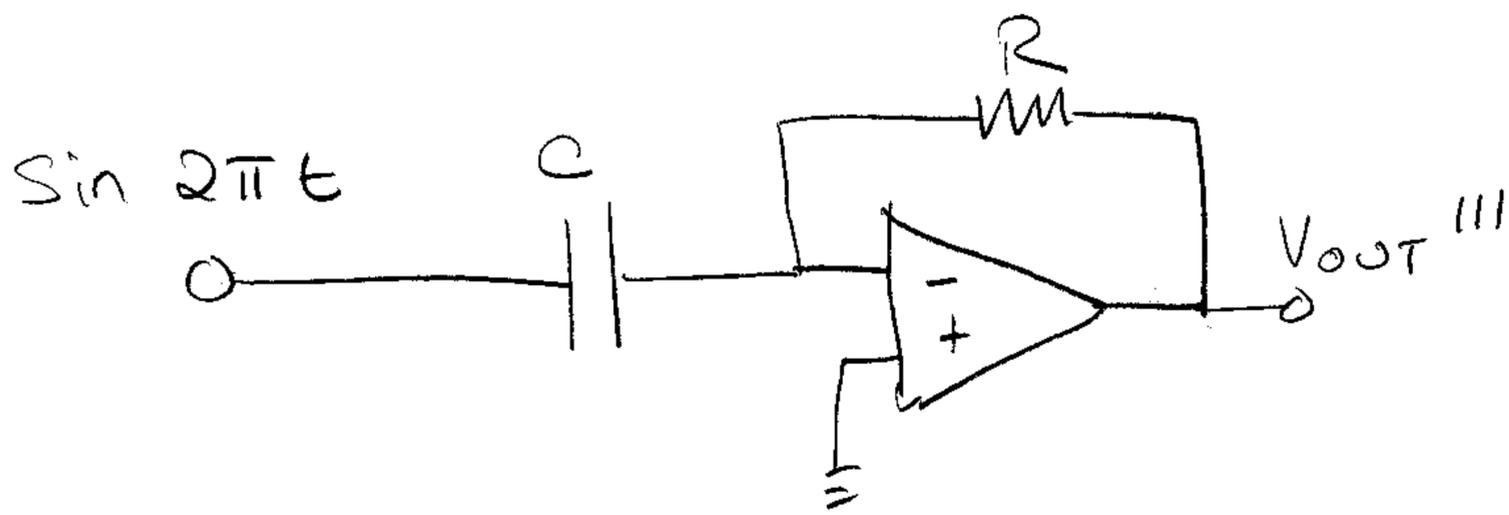To get  $V_{out}^3 = -\cos 2\pi t$ , use the differentiator (which adds - sign). The  $2\pi$  scaling factor that comes out can either be cancelled by setting  $RC = 1/2\pi$  or ignored since it is lost after the comparator.



Put all the circuits together for final design.


Problem 2<sup>o</sup>

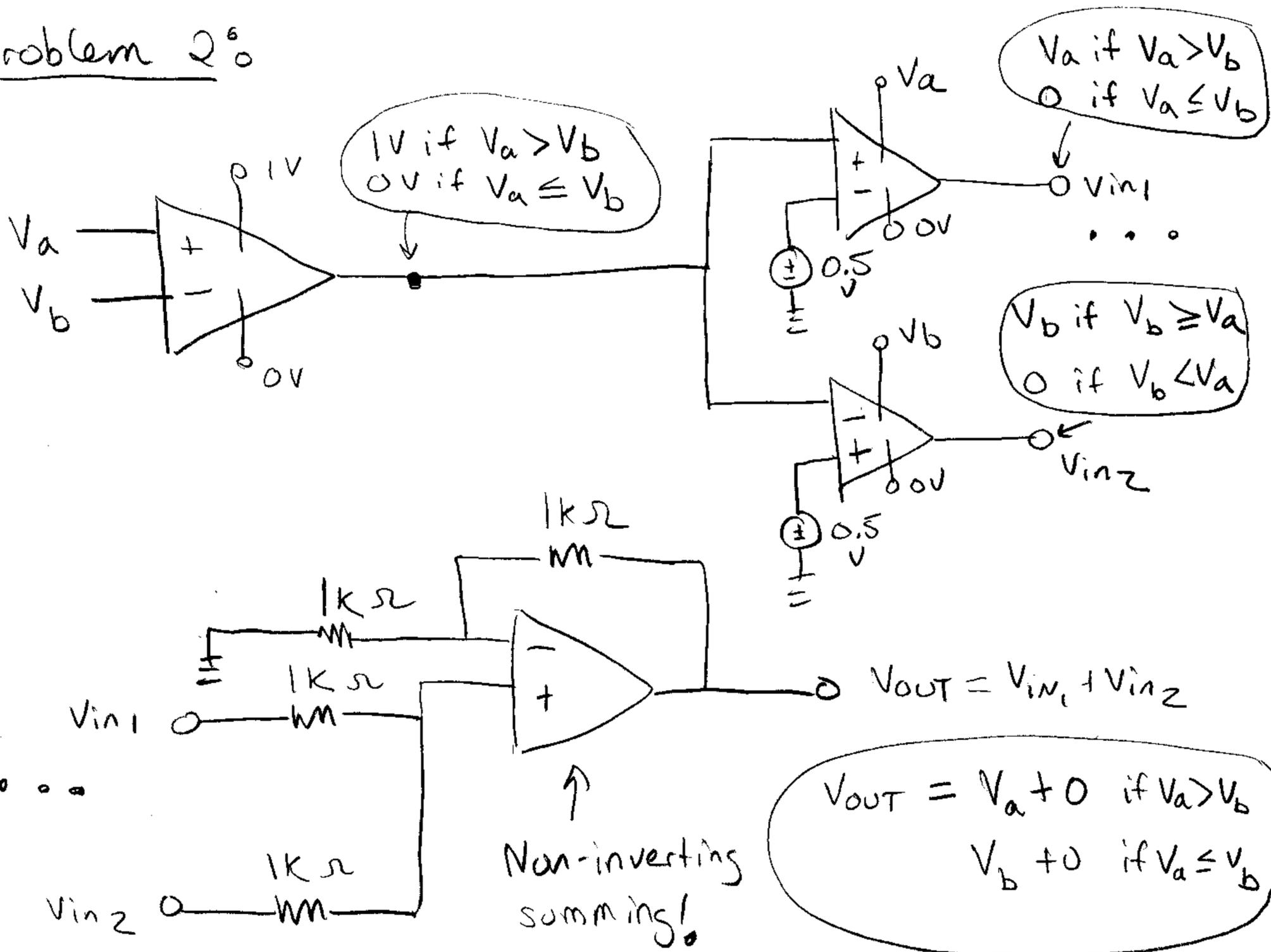



$$V_{out} = \max \{ V_a, V_b \}$$

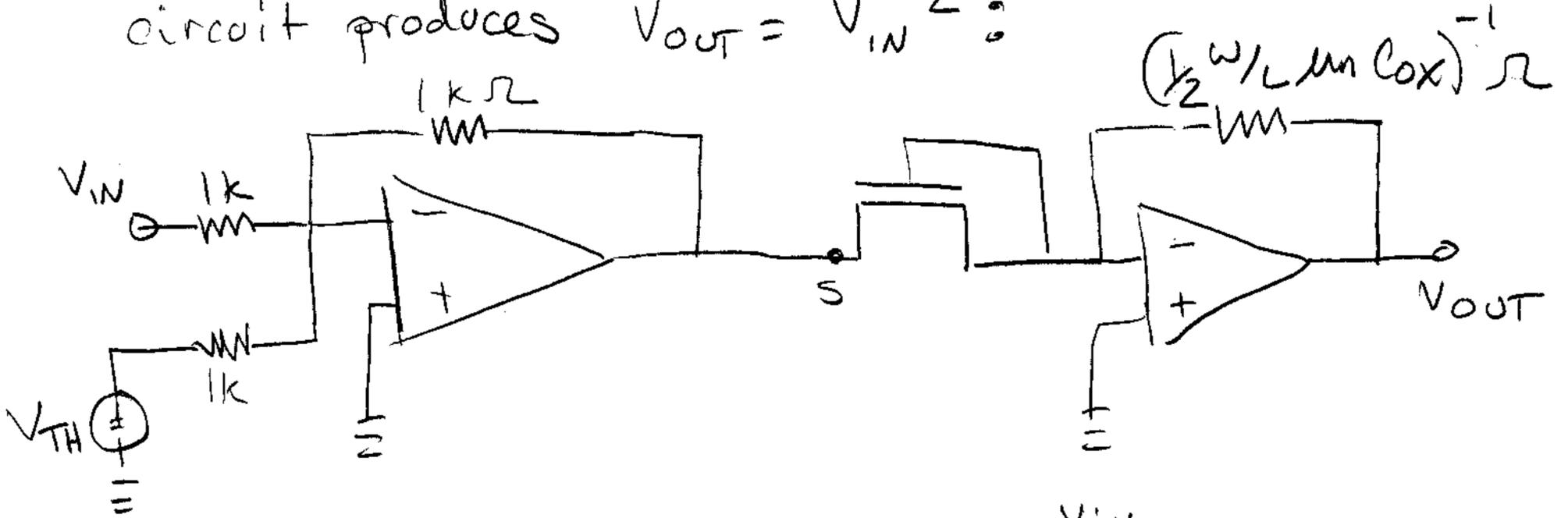Problem 3° (one of many solutions!)


In Homework 7, we found that the following circuit produces  $V_{OUT} = V_{IN}^2$ :



Let's now abbreviate the above by  $V_{IN} \rightarrow [X^2] \rightarrow V_{OUT}$

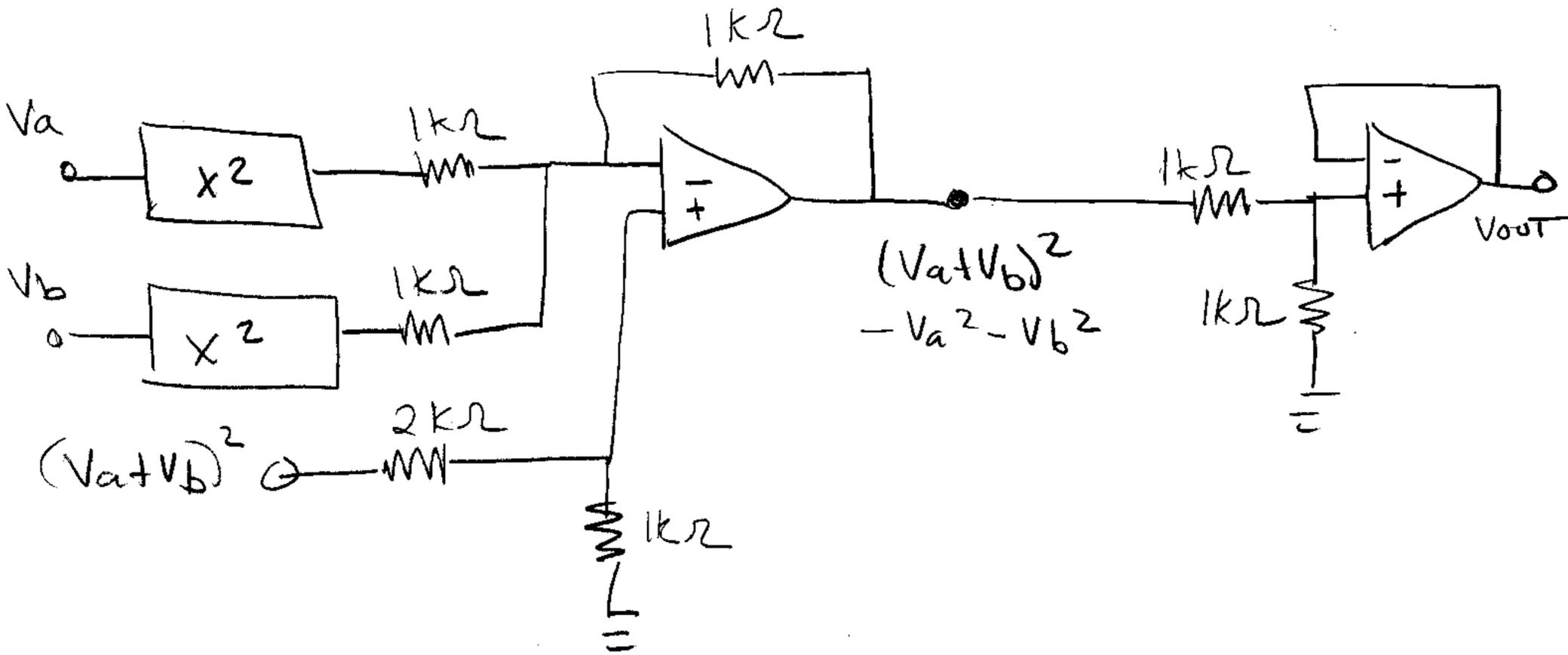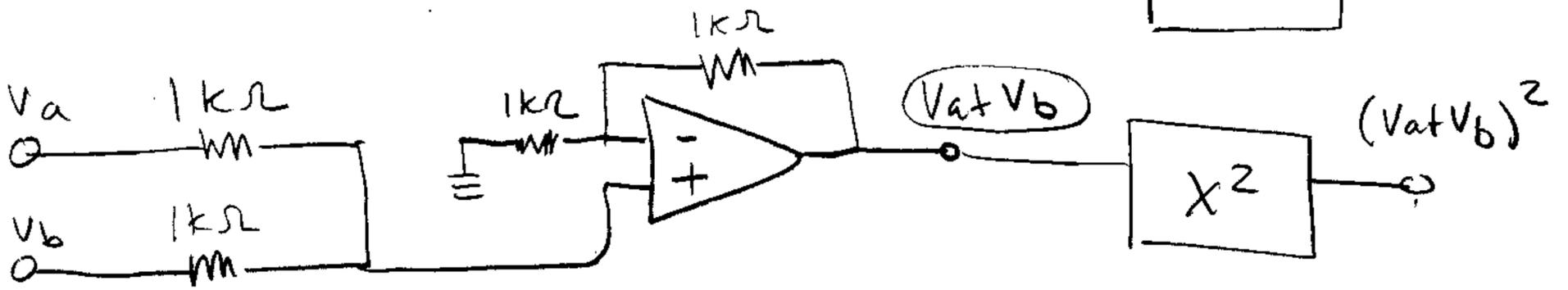

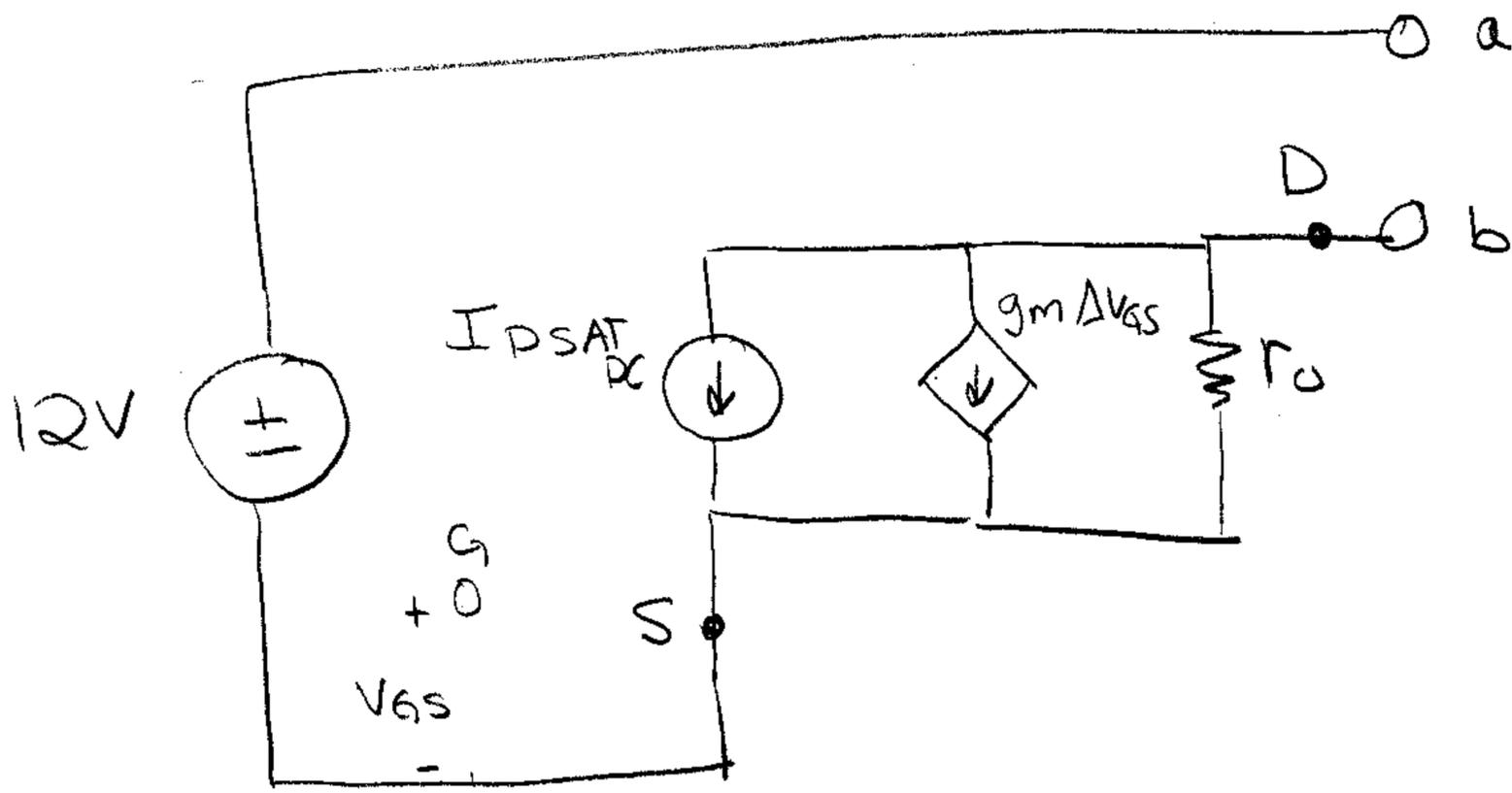
Problem 4: Replace transistor w/ small-signal model:




$$I_{DSAT\_DC} = \frac{1}{2} (1 \text{ mA/V}^2) (3 \text{ V} - 1 \text{ V})^2 = 2 \text{ mA}$$

$$g_m = \frac{W}{L} \mu_n C_{ox} (V_{GS\_DC} - V_{TH}) = 1 \text{ mA/V} \cdot \frac{1}{2} (3 \text{ V} - 1 \text{ V}) = 2 \text{ mA/V}$$

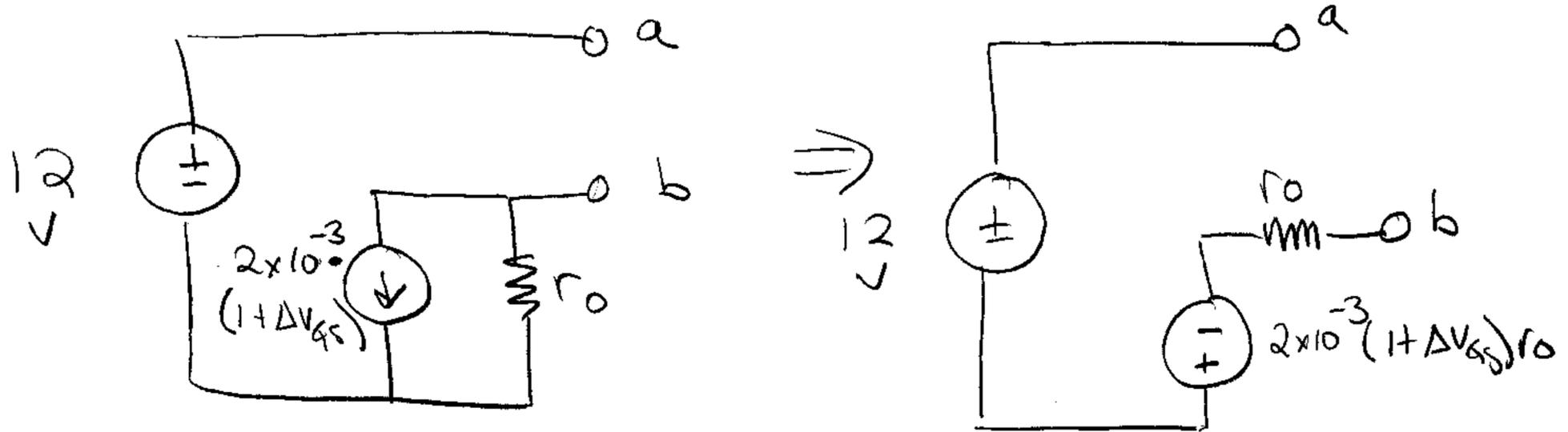
Leaving  $\Delta V_{GS}$  in equations so


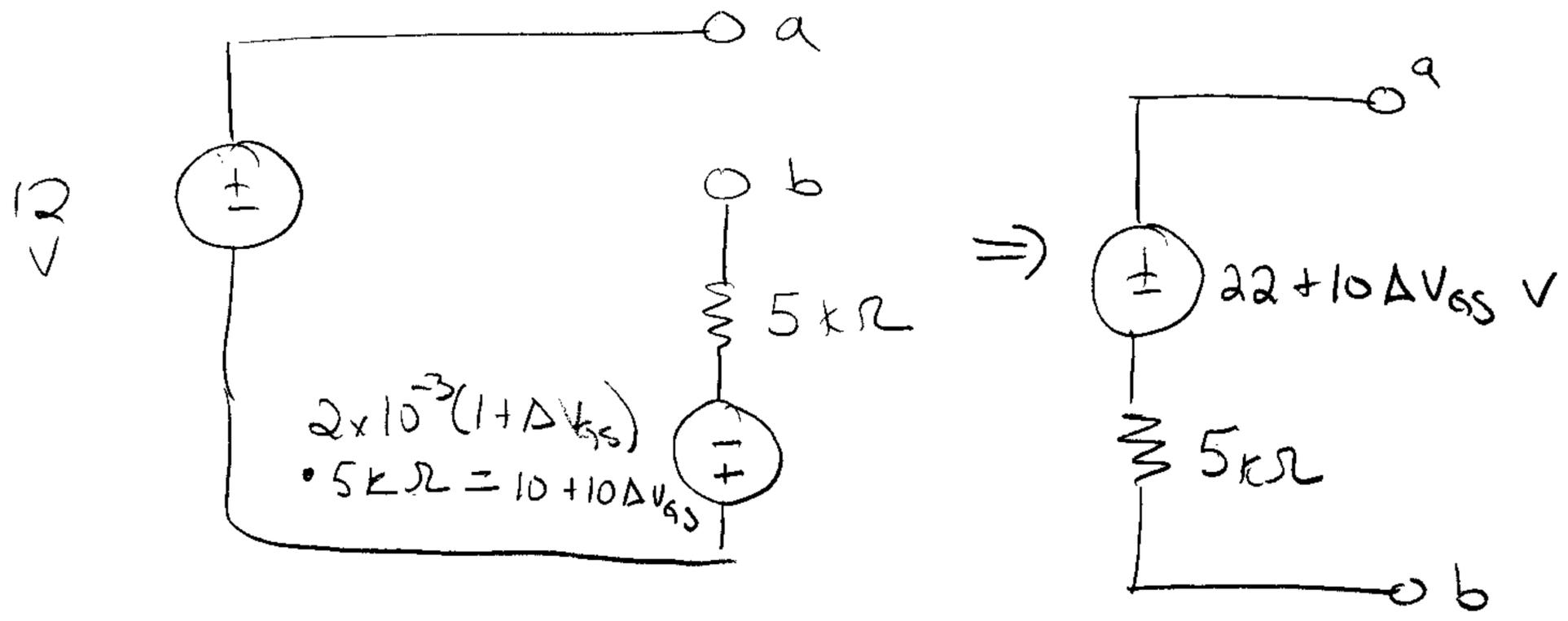
$$r_o = \frac{1}{\lambda I_{DSAT\_DC}} = \frac{1}{0.01 \cdot 2 \text{ mA}} = 5 \text{ k}\Omega$$





Problem 5° In class, we found that for

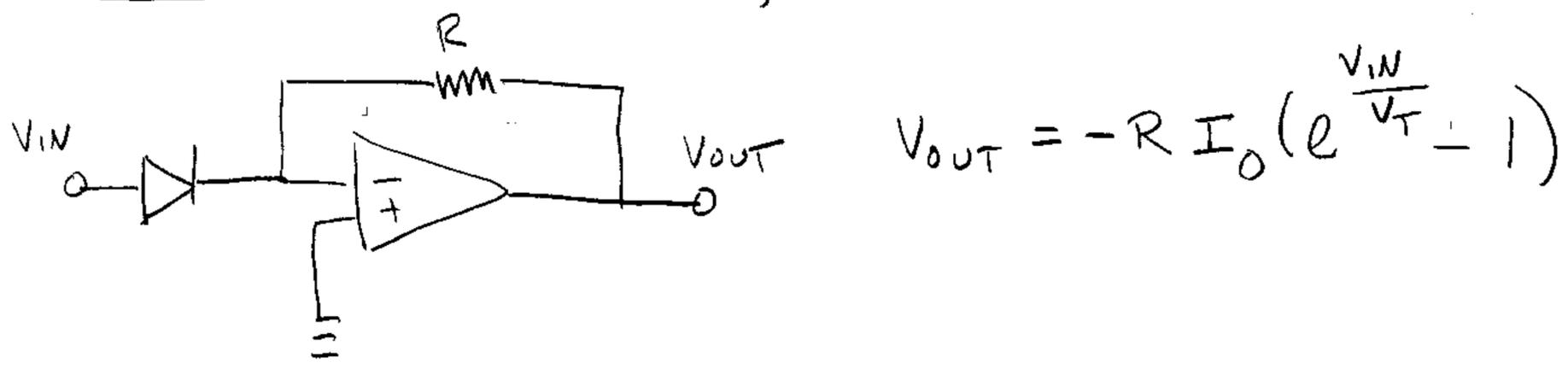

So we can pre-multiply  $V_{IN}$  by  $V_T$ , then scale by  $-1/R I_0$ , and then add 1 V.

At room temperature,  $V_T = 0.026 \text{ V}$ .

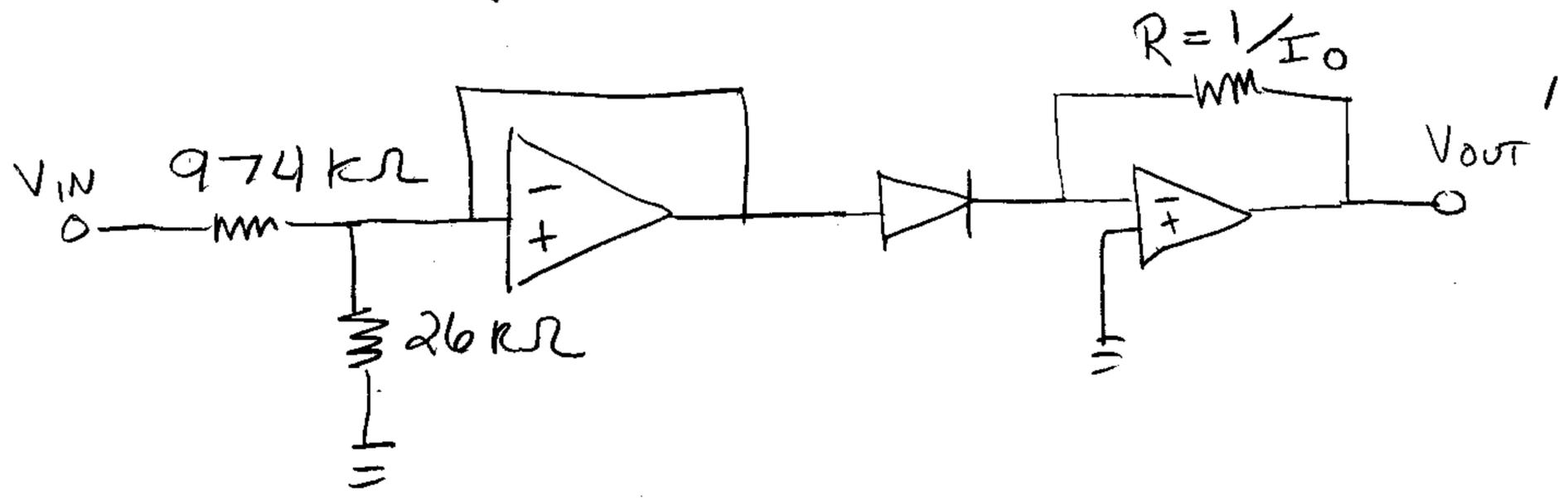

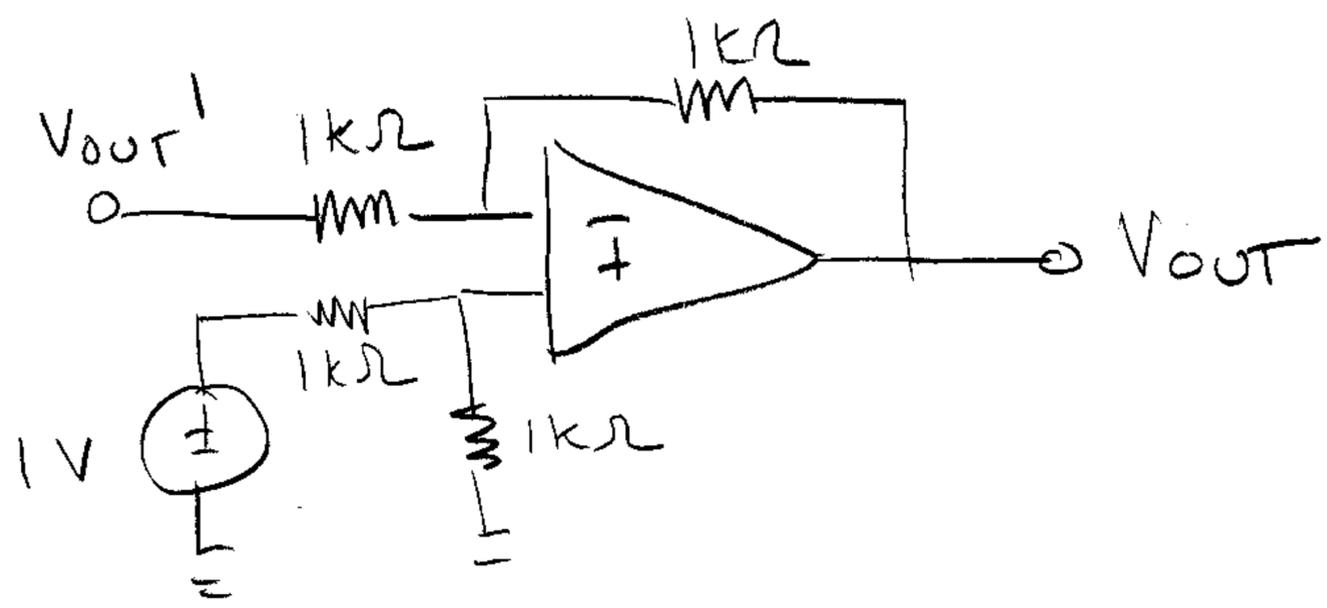


Problem 6:

- $I_0$  can be extremely small ( $10^{-15} A$ ). To make  $R = V/I_0$ , need "exa-ohm" resistance - not possible. Other gain elements with  $10^{15}$  gain also impractical.
  - $V_T$  changes with temperature, proportionally. Changes in temperature that normally occur in circuits would throw off results.
- Other issues may also exist!

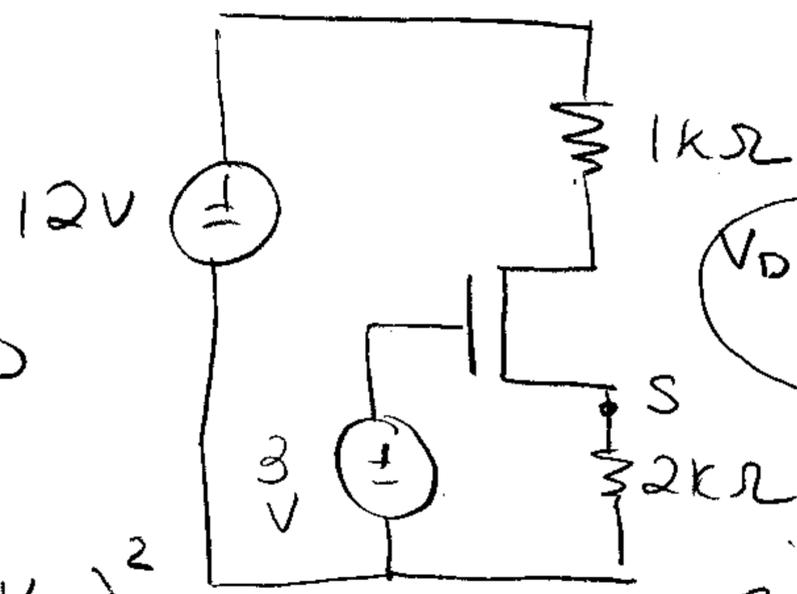Problem 7:

$V_{GS} = 3V - 2kI_D$   
 $12V = 1kI_D + V_{DS} + 2kI_D$   
 Hope for saturation!



$V_{DS} = 12V - 3kI_D$   
 $= 11.66V$

$I_D = \frac{1}{2} \mu_n C_{ox} (V_{GS} - V_{TH})^2$   
 $= 100 \mu A / V^2 (3V - 2kI_D - 1V)^2$


Solve  $\Rightarrow I_D = \{4.4 \mu A, 114 \mu A\}$

impossible, results in  $V_{DS} < 0$

Problem 8: If  $\mu N$  increases due to heat, then  $I_D$  will increase. Then the voltage over the  $2k\Omega$  resistor will increase, lowering  $V_{GS}$ . This counteracts the increase in  $I_D$  and results in a current supply which varies less due to temp changes.

Problem 9:

$t=0: V_{OUT} = 1V$

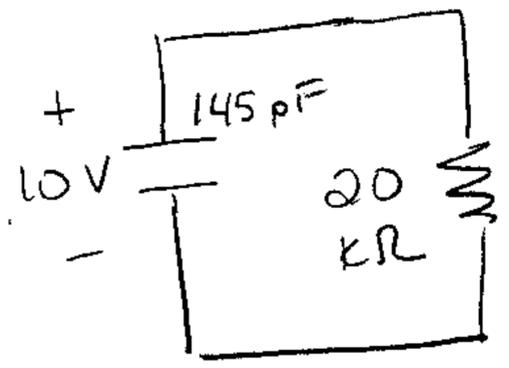


Stays until  $V_{C2} = 5V$ .

It takes  $0.69\tau$  to discharge halfway.

$A + 0.69\tau = 0.69(145pF)(20k\Omega) = 2\mu s$

switch flips.

$t = 2\mu s \quad V_{OUT} = -1V$

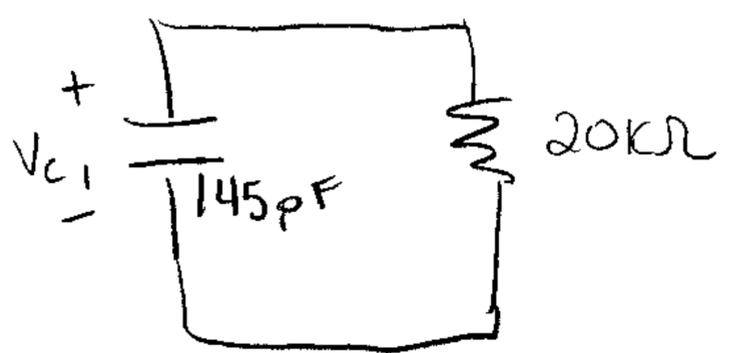

$C_1$  has been charging for  $2\mu s$  in circuit with  $10V$  &  $10k\Omega$ .

$V_{C1}(2\mu s) = 10V(1 - e^{-\frac{2\mu s}{10k \cdot 145pF}}) = 7.5V$

How long to discharge to  $5V$ ?

$5V = 7.5e^{-\frac{\Delta t}{20k \cdot 145pF}}$

$\Delta t = 1.176\mu s$

switch flips at  $t = 3.176\mu s$

$t = 3.176\mu s \quad V_{OUT} = 1V$

$C_2$  has been charging, starting at  $5V$ , for  $1.176\mu s$ .

$V_{C2}(t = 1.176\mu s) = 10(1 - e^{-\frac{-(t-2\mu s)}{10k \cdot 145pF}}) + 5e^{-\frac{-(t-2\mu s)}{10k \cdot 145pF}} = 7.77V$

How long to discharge to  $5V$ ?

$\Delta t = (t - 3.176\mu s) = 1.28\mu s$

switch flips at  $4.45\mu s \quad V_{OUT} = -1V$

Ok we get the idea. How about a general formula?

(9)

Suppose we know  $\Delta t_k$ , the time between the last two switches. Let's find  $\Delta t_{k+1}$ , the time to the next switch.

The capacitor of interest charged for  $\Delta t_k$  in the charging circuit. It charged to:

$$V_{c0} = 10 \left( 1 - e^{-\frac{\Delta t_k}{\tau_c}} \right) + 5 e^{-\frac{\Delta t_k}{\tau_c}}$$

where  $\tau_c = 10000 \Omega \cdot 145 \text{ pF} = 1.45 \mu\text{s}$

Rewrite more simply as

$$V_{c0} = 10 - 5 e^{-\frac{\Delta t_k}{1.45 \mu\text{s}}}$$

How long to discharge capacitor down to 5V?  $\Delta t_{k+1}$ .



$$5 \text{ V} = V_{c0} e^{-\frac{\Delta t_{k+1}}{\tau_d}} \quad \text{where } \tau_d = 20 \text{ k}\Omega \cdot 145 \text{ pF} = 2.9 \mu\text{s}$$

Solve:

$$\Delta t_{k+1} = -2.9 \mu\text{s} \cdot \ln \left( \frac{5 \text{ V}}{V_{c0}} \right)$$


$$= -2.9 \mu\text{s} \cdot \ln \frac{5 \text{ V}}{10 - 5 e^{-\frac{\Delta t_k}{1.45 \mu\text{s}}}}$$

This is our update formula.

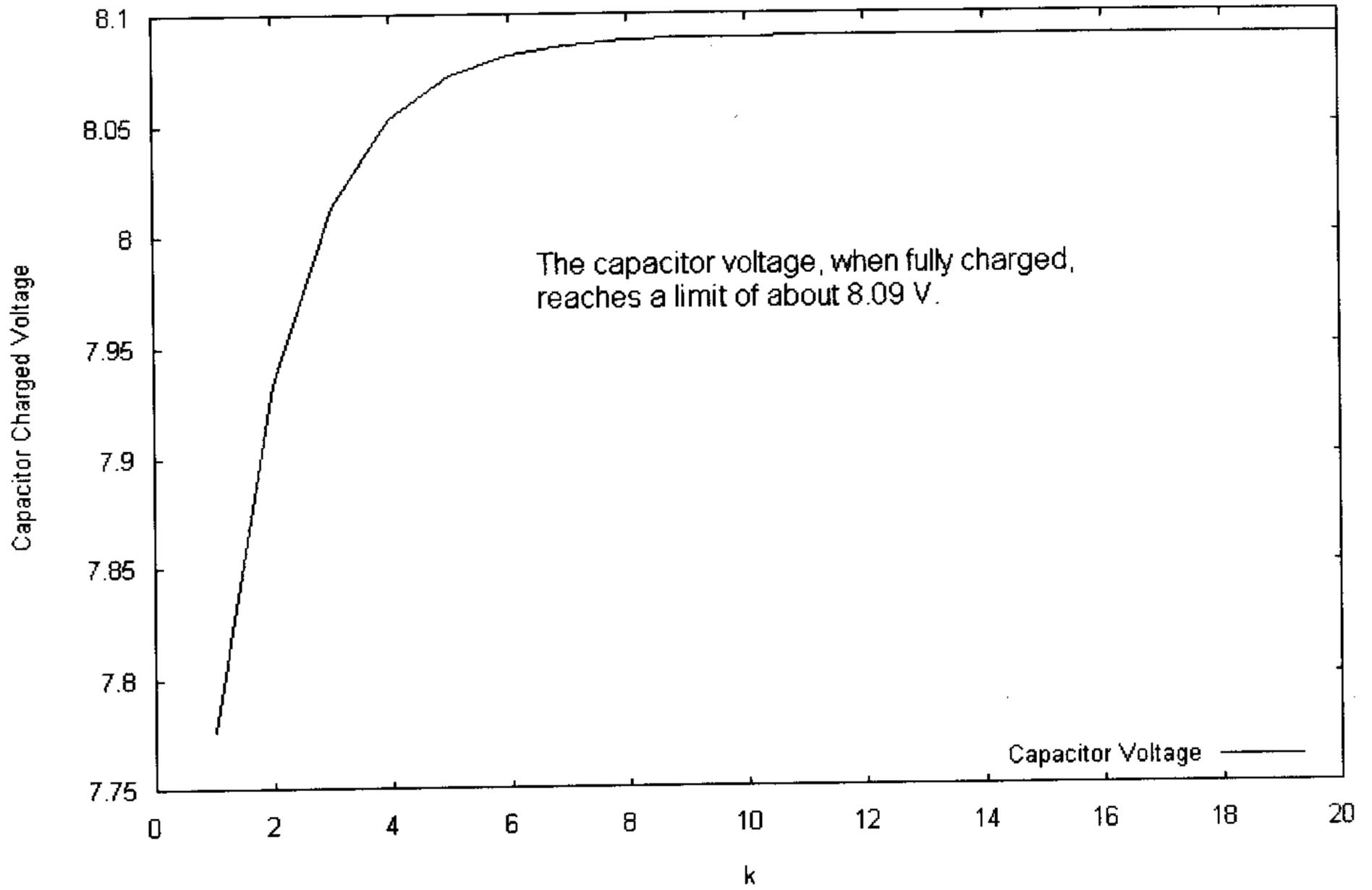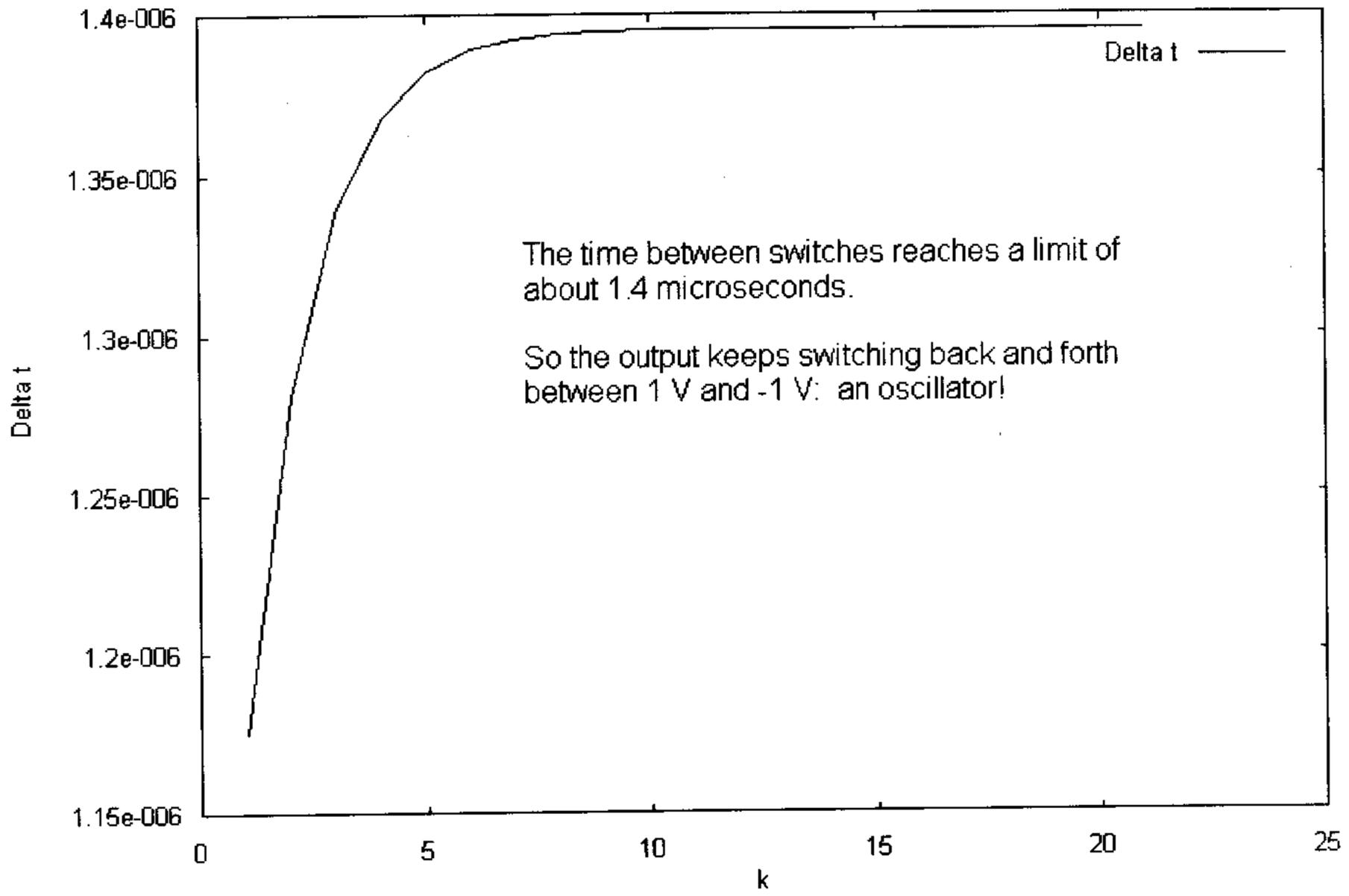

# Problem 10%

11

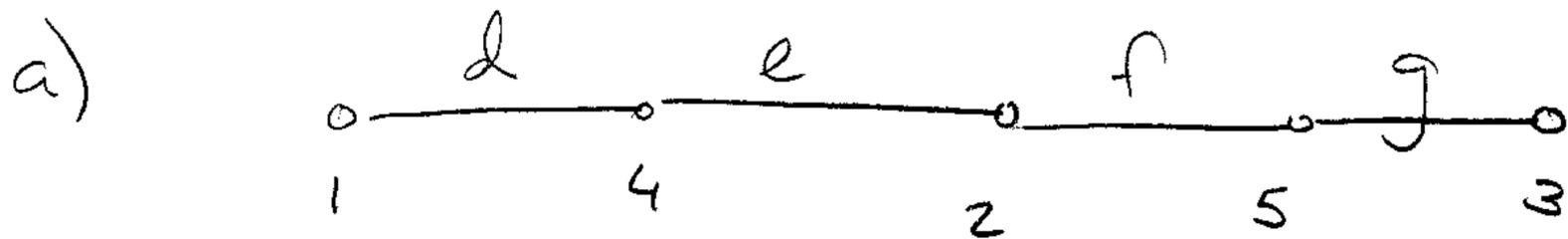

Fund. cut sets:

Cutting d separates 1 from  $\{4, 2, 5, 3\}$ ,

To fully separate: cut  $\{d, b, a\}$ .

Cutting e separates  $\{1, 4\}$  from  $\{2, 5, 3\}$ .

To fully separate: cut  $\{e, a, b, h\}$ .

Cutting f separates  $\{1, 4, 2\}$  from  $\{5, 3\}$ .

To fully separate: cut  $\{f, h, c, a\}$ .

Cutting g separates  $\{1, 4, 2, 5\}$  from  $\{3\}$ .

To fully separate: cut  $\{a, c, g\}$ .

b) Your answers will vary depending on the reference node: replace the appropriate node voltage with zero.

Set  $\{d, b, a\}$ : Current through d unknown (voltage source) but it tells us  $V_1 - V_4 = 10$ .

Set  $\{e, a, b, h\}$ :  $2A + \frac{V_1 - V_2}{2} + \frac{V_4 - V_2}{2} + \frac{V_4 - V_5}{10} = 0$   
"a"      "b"      "e"      "h"

Set  $\{f, h, c, a\} :$   $\frac{V_2 - V_5}{20} + \frac{V_4 - V_5}{10} + \frac{V_2 - V_3}{4} + 2A = 0$   
 "f" "h" "c" "a"

Set  $\{a, c, g\} :$   $2A + \frac{V_2 - V_3}{4} + \frac{V_5 - V_3}{5} = 0$   
 "a" "c" "g"