 


### Homework Assignment #13

Not to be handed in. Be sure to complete to prepare for the final.  
Solutions will be posted week of May 10.

#### **Problem 1: Interconnect Delay**


Consider the cascaded CMOS inverters below:



We are interested in the propagation delay of Inverter A (between  $V_{in}$  and  $V_{out}$ ). The equivalent on-resistance  $R_{dr}$  of the NMOSFET or PMOSFET in Inverter A is  $10\text{ k}\Omega$ . The intrinsic capacitance  $C_{intrinsic}$  (due to the drain pn-junction capacitances and gate-overlap capacitances for Inverter A) is  $3\text{ fF}$ ; the fanout capacitance  $C_{fanout}$  (input capacitance of Inverter B, *i.e.* the MOSFET gate capacitances for Inverter B) is  $3\text{ fF}$ .

Suppose the oxide ( $\text{SiO}_2$ , with dielectric permittivity  $\epsilon_{\text{SiO}_2} = 3.45 \times 10^{-13}\text{ F/cm}$ ) between the aluminum (resistivity =  $2.7\text{ }\mu\Omega\text{-cm}$ ) metal layer and the silicon substrate is  $1\text{ }\mu\text{m}$  thick (*i.e.*  $t_{di} = 1\text{ }\mu\text{m}$ ). If the aluminum interconnect thickness  $H$  is  $0.5\text{ }\mu\text{m}$  and its width  $W$  is  $1\text{ }\mu\text{m}$ , how long must it be in order for the interconnect delay ( $(0.69R_{dr} + 0.38R_{wire})C_{wire}$ ) to account for half of the propagation delay for Inverter A? (Use the equation on Slide 8 of Lecture 26 for the interconnect capacitance, and the last equation on Slide 13 of Lecture 26 for the propagation delay.)

#### **Problem 2: Coupling Capacitance**

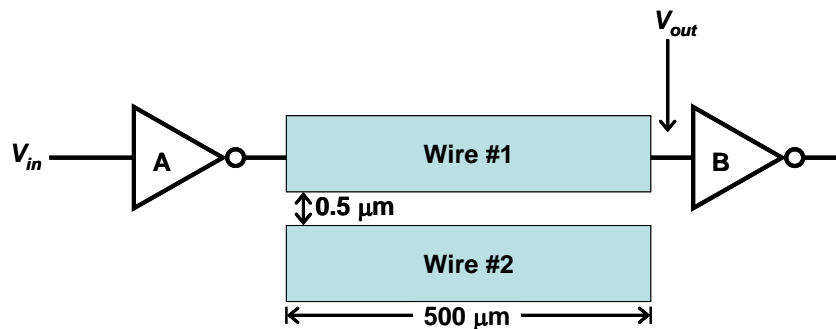

The figure above shows Inverter A driving Inverter B. Wire #1, connecting the output of Inverter A to the input of Inverter B, is close to Wire #2. Let's examine how the capacitive coupling between Wire #1 and Wire #2 can affect the propagation delay for Inverter A. Assume that the CMOS technology and inverter design are the same as in Problem 1. Each of the aluminum wires is  $0.5\text{ }\mu\text{m}$  thick and  $2\text{ }\mu\text{m}$  wide, and they are spaced  $0.5\text{ }\mu\text{m}$  apart. **For this problem, you can assume the fringing-field capacitance of the wires is negligible.**

- Calculate the resistance of Wire# 1 and verify that it is small compared to  $R_{dr}$  of Inverter A.
- A Stanford engineering student treats Wire# 2 as a floating line. What RC time constant does s/he get? (Use the equation in Slide 20 of Lecture 26.)
- You decide to make a more conservative estimate of the delay by treating Wire #2 as a grounded line. What RC time constant do you get? (Use the equation in Slide 19 of Lecture 26.)

### **Problem 3: Ring Oscillator Analysis**

- a) You have an 11 stage ring oscillator. Each inverter in the ring has the following parameters:  $R_n = 4 \text{ k}\Omega$ ,  $R_p = 5 \text{ k}\Omega$ ,  $C_n = 6 \text{ fF}$ ,  $C_p = 12 \text{ fF}$ ,  $V_{DD} = 2.5 \text{ V}$ ,  $V_{iL} = 0.9 \text{ V}$ ,  $V_{iH} = 1.6 \text{ V}$ . Determine the frequency and period of this ring oscillator. Only consider the gate capacitances listed here, neglect other capacitances.
- b) One of the inverters in the ring oscillator of part (a) is replaced with an inverter that is 10 times larger, i.e. it has 10 times the gate capacitance and 1/10 driving resistance. Find the frequency and period of this modified ring oscillator.