


Lecture #12

Announcement

- Midterm 1 on Tues. 3/2/04, 9:30-11
- A-M last initials in 10 Evans
- N-Z initials in Sibley auditorium
- Closed book, no electronic devices
- One sheet 8.5x11 inch of your notes
- Covers material through op-amps, i.e. hw #1-4


OUTLINE

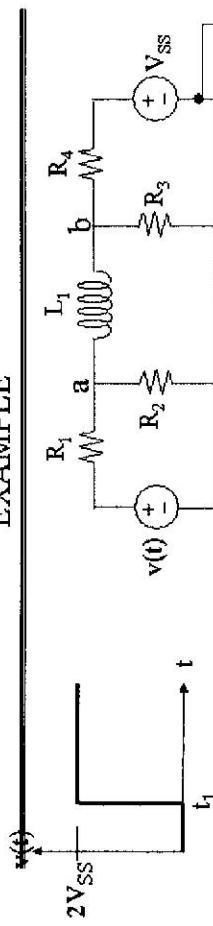- RC, RL review
- Propagation delay
- Energy consumption of simple RC circuit
- Circuit transient response examples
- Midterm questions?



Solution: $V_a, V_b = ?$

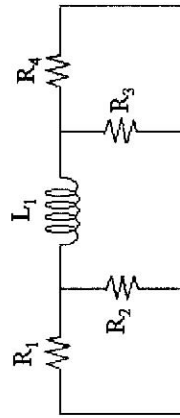To find R_{eff} , short voltage sources and find R at terminals of L:




So $\tau = L/R =$

TRANSIENTS IN SINGLE-INDUCTOR OR SINGLE-CAPACITOR CIRCUITS - THE EASY WAY


- 1) Find Resistance seen from terminals of L or C (short voltage sources, open current sources).
- 2) The circuit time constant is L/R or RC (for every node, every current, every voltage).
- 3) Use initial conditions and inductor/capacitor rules to find initial values of all transient variables. (Capacitor voltage and inductor current must be continuous.)
- 4) Find $t = \infty$ value of all variables by setting all time derivatives to zero.
- 5) Sketch the time-behavior of all transient variables, based on initial and final values and known time constant.
- 6) Write the equation for each transient variable by inspection.

EXAMPLE con't

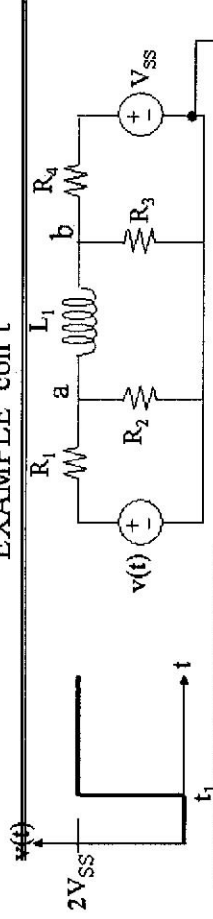


Find initial inductor current

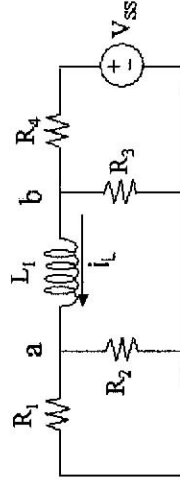For $t < t_1, v(t) = 0, di/dt = 0$ so inductor voltage is zero (like a wire):




EXAMPLE con't

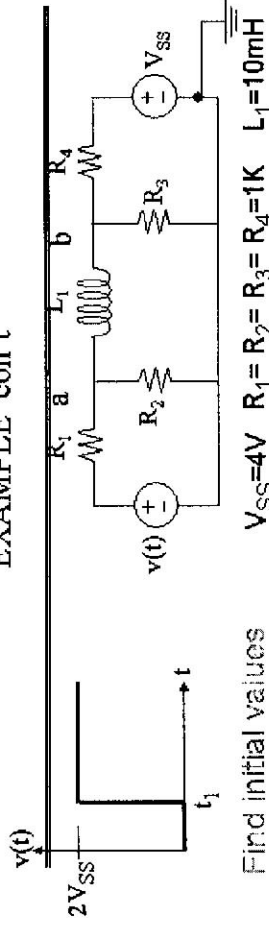

Find initial values

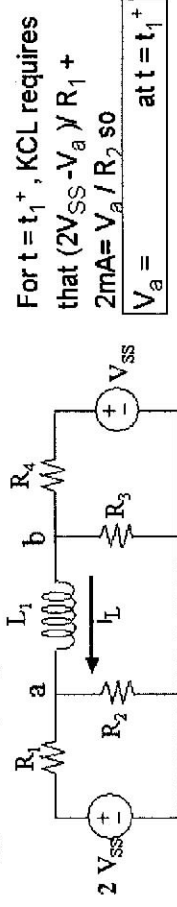
For $t = t_1^+$, $v(t) = 2V_{SS}$, $i_L = V_{SS} / 4 \times 1 / R_1 \parallel R_2 = 2mA$



For $t = t_1^+$, KCL requires that $(2V_{SS} - V_a) / R_1 + 2mA = V_a / R_2$ so $V_a = \dots$ at $t = t_1^+$


Similarly, KCL requires that $(V_{SS} - V_b) / R_4 = V_b / R_3 + 2mA$ so $V_b = \dots$ at $t = t_1^+$

EXAMPLE con't

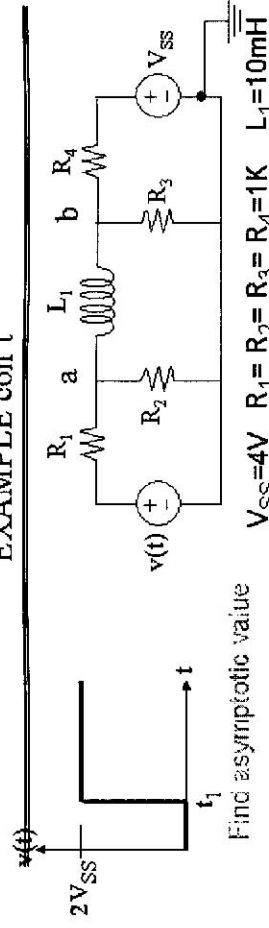

Find asymptotic value

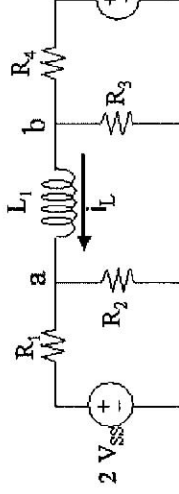As $t \rightarrow \infty$, $v(t) = 2V_{SS}$, $di_L/dt = 0$ so $V_a = V_b = L_1$ acts like simple wire again.



Thus For $t \gg t_1$ $V_a = V_b = \dots$

EXAMPLE continued

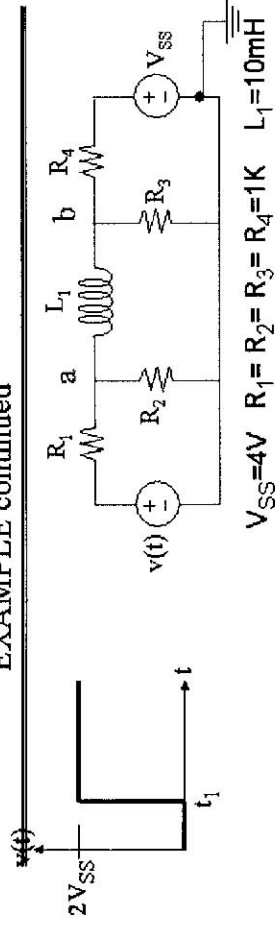




Table of initial and final values

Variable	v_a	v_b	i_L
$t = t_1^+$	5V	1V	2mA
$t = \infty$	3V	3V	-2mA
τ	10 μ s	10 μ s	10 μ s

We plot these three variables on the following page:

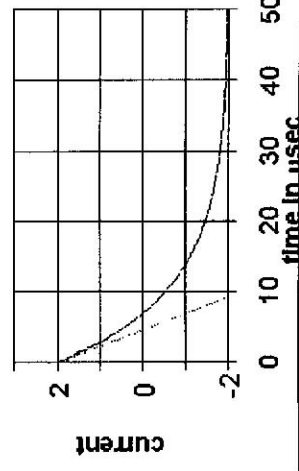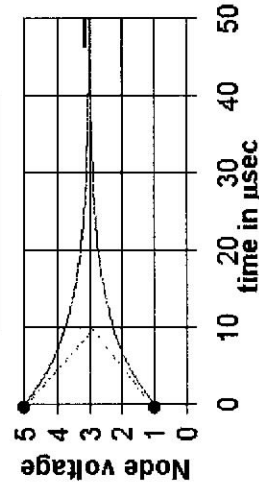EXAMPLE, continued

The voltage at node a and b are constructed by plotting initial and final value, and using the initial slope, shown as dotted line.



Voltage Ranges for Digital Signals

- A digital signal varies with time, typically between between ground (0 Volts) and the power supply voltage (V_{supply}).
- A digital voltage signal has two defined states "high" (corresponding to logical state 1) or "low" (corresponding to logical state 0)
- Each of the two states corresponds to a range of voltages, for example:


logical 1 state: voltage $> V_{supply}/2$

logical 0 state: voltage $< V_{supply}/2$

Propagation Delay t_p

- The propagation delay t_p of a logic gate defines how quickly the output voltage responds to a change in input voltage. It is measured between the 50% transition points of the input and output voltage waveforms.

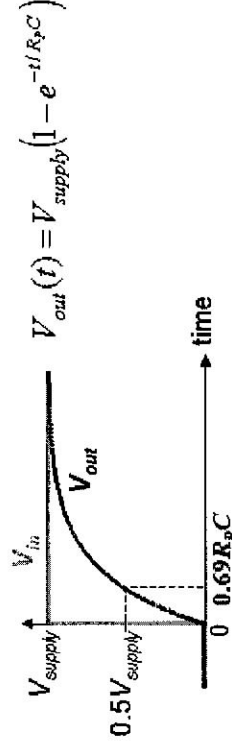Example: Output voltage changing from "low" to "high"




Formula for Propagation Delay t_p

- A logic gate can display different response times for rising or falling input waveforms, so two definitions of propagation delay are necessary.

$$t_p = \frac{t_{pLH} + t_{pHL}}{2}$$

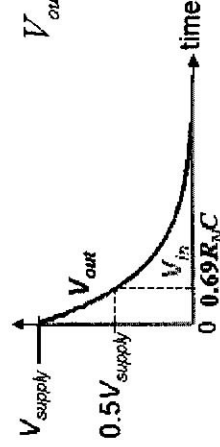Example: Output voltage changing from "high" to "low"




$$V_{out}(t) = V_{high}e^{-t/R_pC}$$

Energy Consumption of Simple RC Circuit


- In charging a capacitor, the energy which is delivered to the capacitor is $\frac{1}{2}CV_{supply}^2$
- The energy delivered by the source is

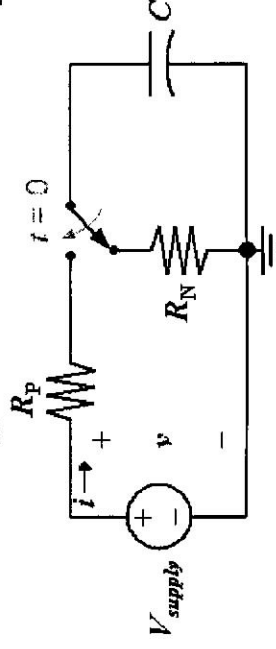How much energy is delivered to the resistor R_p ?



- In discharging a capacitor, the energy which is delivered to the resistor R_N is $\frac{1}{2} C V_{supply}^2$

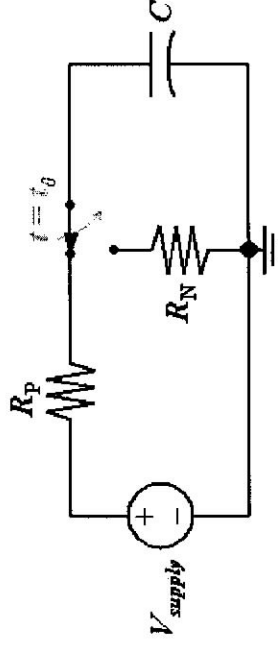- Thus, in one complete cycle (charging and discharging), the total energy delivered by the voltage source is $C V_{supply}^2$



DRAM Example (cont'd)

- The charges stored on C_{cell} and $C_{bit-line}$ prior to reading are $Q_{cell,initial} = C_{cell} V_{cell,initial} = (10^{-13} \text{ F})(2\text{V}) = 2 \times 10^{-13} \text{ C}$ and $Q_{bit-line,initial} = C_{bit-line} V_{bit-line,initial} = (10^{-12} \text{ F})(1\text{V}) = 1 \times 10^{-12} \text{ C}$

$$Q_{total,initial} = Q_{cell,initial} + Q_{bit-line,initial} = 1.2 \times 10^{-12} \text{ C}$$

- The final voltages on each capacitor are equal.

$$\Rightarrow Q_{total,final} = C_{cell} V_{final} + C_{bit-line} V_{final}$$


- Total charge is conserved:

$$Q_{total,final} = (C_{cell} + C_{bit-line}) V_{final} = Q_{total,initial}$$

$$V_{final} = \frac{Q_{total,initial}}{C_{cell} + C_{bit-line}} = \frac{1.2 \times 10^{-12} \text{ C}}{1.1 \times 10^{-12} \text{ F}} \approx 1.09 \text{ Volts}$$

DRAM (Dynamic Memory Device) Example

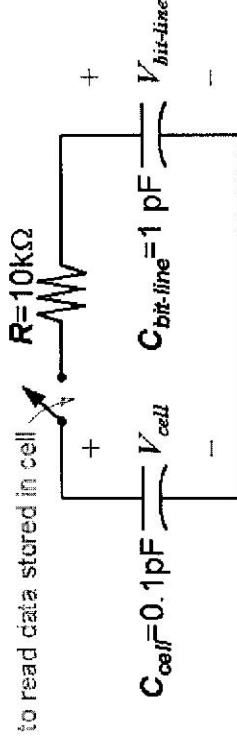
- The operation of a DRAM cell (which stores one bit of information) can be modeled as an RC circuit:



- Suppose the bit line is pre-charged to 1 V before the cell is read, and that the cell is programmed to 2 V. What is the final value of the bit-line voltage, after the switch is closed?

DRAM Example (cont'd)

- Sketch the bit-line voltage waveform

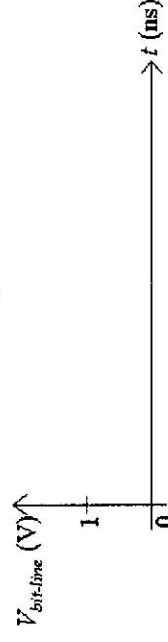


- Is energy conserved? Explain.

Plan for coming weeks


- We will be studying semiconductor devices and technology for the next several weeks
 - How does a transistor work?
(need to learn about semiconductors and diode devices first)
 - How are transistors used as amplifiers?
 - modeled as dependent current source
 - How are transistors used to implement digital logic gates?
 - modeled as resistive switch
(circuit performance is limited by RC delay)

RC Circuit Transient Analysis Example

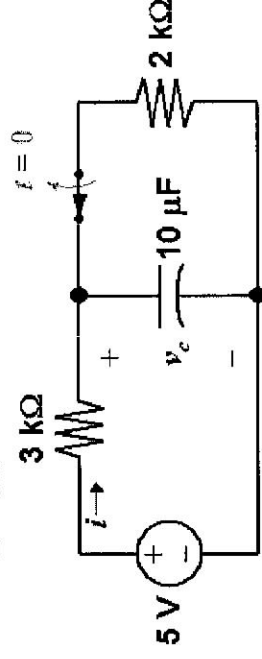The switch is closed for $t < 0$, and then opened at $t = 0$.
Find the voltage $v_c(t)$ for $t \geq 0$.



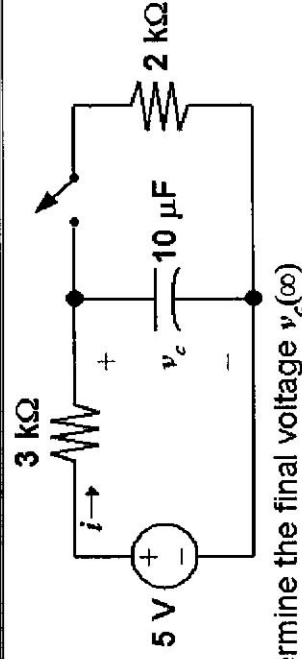1. Determine the initial voltage $v_c(0)$



2. Determine the final voltage $v_c(\infty)$

3. Calculate the time constant τ

$$v_c(t) = v_c(\infty) + [v_c(0) - v_c(\infty)]e^{-t/\tau}$$