

Lecture #16


OUTLINE

- MOSFET I_D vs. V_{GS} characteristic
- Circuit models for the MOSFET
 - resistive switch model
 - small-signal model
- Rabaey *et al.*: Chapter 3.3.2

MOSFET V_T Measurement

- V_T can be determined by plotting I_D vs. V_{GS} using a low value of V_{DS} :
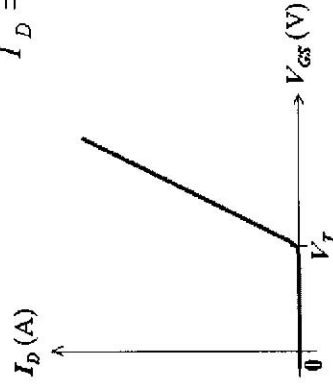
$$I_D = k'_n \frac{W}{L} \left[V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS}$$




MOSFET I_D vs. V_{GS} Characteristic

- Typically, V_{DS} is fixed when I_D is plotted as a function of V_{GS}


Long-channel MOSFET

$$V_{DS} = 2.5 \text{ V} > V_{DSAT}$$

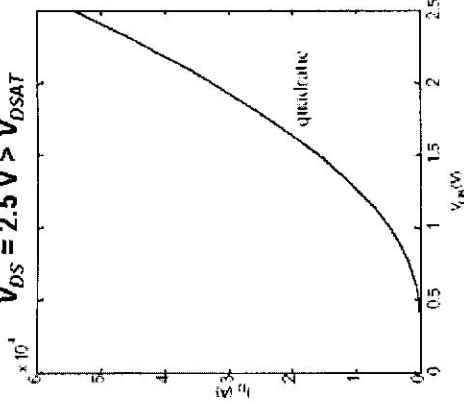

Short-channel MOSFET

$$V_{DS} = 2.5 \text{ V} > V_{DSAT}$$

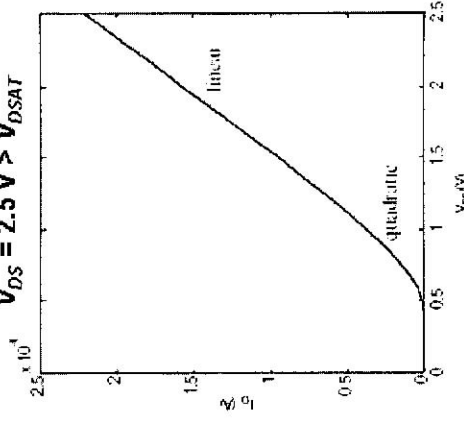


Subthreshold Conduction (Leakage Current)

- The transition from the ON state to the OFF state is gradual. This can be seen more clearly when I_D is plotted on a logarithmic scale:

- In the subthreshold ($V_{GS} < V_T$) region,


$$I_D \propto \exp\left(\frac{qV_{GS}}{nkT}\right)$$

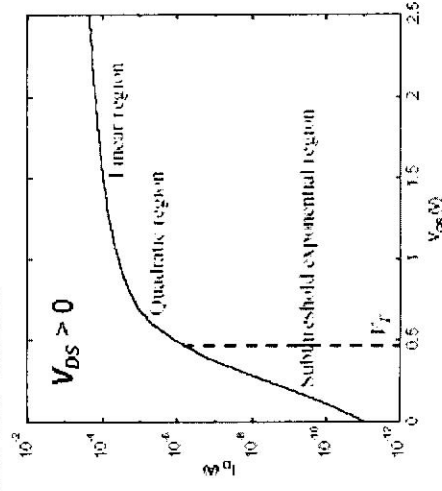This is essentially the channel-source pn junction current. (Some electrons diffuse from the source into the channel, if this pn junction is forward biased.)



Qualitative Explanation for Subthreshold Leakage

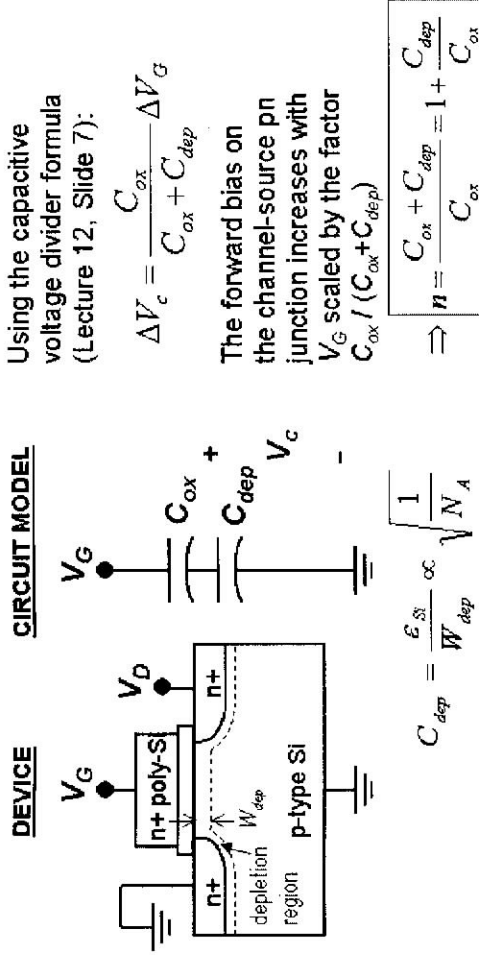- The channel V_c (at the Si surface) is capacitively coupled to the gate voltage V_G :



EECS40, Spring 2004


Lecture 16, Slide 5

Prof. Sanders

V_T Design Trade-Off

(Important consideration for digital-circuit applications)

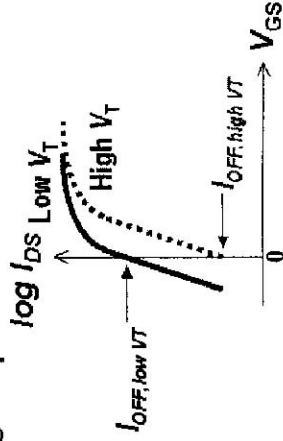- Low V_T is desirable for high ON current
 $I_{DSAT} \propto (V_{DD} - V_T)^\eta$ $1 < \eta < 2$
 where V_{DD} is the power-supply voltage
 ... but high V_T is needed for low OFF current




EECS40, Spring 2004

Lecture 16, Slide 7

Prof. Sanders

Slope Factor (or Subthreshold Swing) S

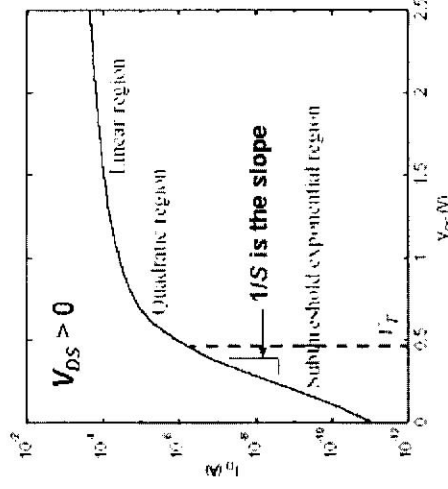- S is defined to be the inverse slope of the log (I_D) vs. V_{GS} characteristic in the subthreshold region:



$$S \equiv \eta \left(\frac{kT}{q} \right) \ln(10)$$

Units: Volts per decade

Note that $S \geq 60$ mV/dec at room temperature:

$$\left(\frac{kT}{q} \right) \ln(10) = 60 \text{ mV}$$

EECS40, Spring 2004



Lecture 16, Slide 6

Prof. Sanders

The MOSFET as a Resistive Switch

- For digital circuit applications, the MOSFET is either OFF ($V_{GS} < V_T$) or ON ($V_{GS} = V_{DD}$). Thus, we only need to consider two I_D vs. V_{DS} curves:

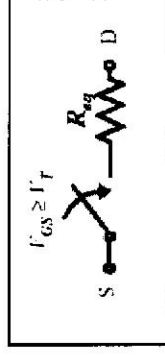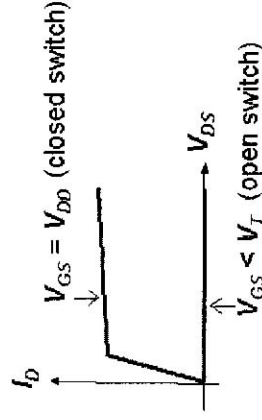- the curve for $V_{GS} < V_T$
- the curve for $V_{GS} = V_{DD}$




EECS40, Spring 2004

Lecture 16, Slide 8

Prof. Sanders

Equivalent Resistance R_{eq}

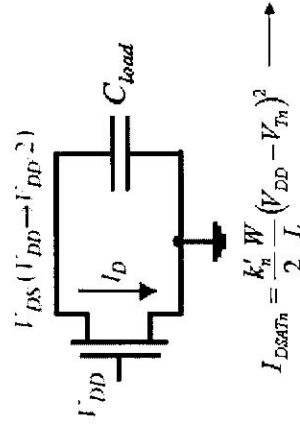- In a digital circuit, an n-channel MOSFET in the ON state is typically used to discharge a capacitor connected to its drain terminal:
 - gate voltage $V_G = V_{DD}$
 - source voltage $V_S = 0$ V
 - drain voltage V_D initially at V_{DD} , discharging toward 0 V



$$I_{DSATn} = \frac{k'_n W}{2 L} (V_{DD} - V_{Th})^2 \longrightarrow$$

The value of R_{eq} should be set to the value which gives the correct propagation delay (time required for output to fall to $\frac{1}{2}V_{DD}$):

$$R_{eq} \approx \frac{3}{4} \frac{V_{DD}}{I_{DSATn}} \left(1 - \frac{5}{6} \lambda_n V_{DD} \right)$$

Typical MOSFET Parameter Values

- For a given MOSFET fabrication process technology, the following parameters are known:
 - V_T (~ 0.5 V)
 - C_{ox} and k' (< 0.001 A/V^2)
 - V_{DSAT} (≤ 1 V)
 - λ (≤ 0.1 V^{-1})

Example R_{eq} values for 0.25 μm technology ($W = L$):

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

How can R_{eq} be decreased?