

## Lecture #17 (cont'd from #16)

### OUTLINE

- MOSFET  $I_D$  vs.  $V_{GS}$  characteristic
- Circuit models for the MOSFET
  - resistive switch model
  - small-signal model


### Reading

- Rabaey *et al.*: Chapter 3.3.2
- Hambley: Chapter 12 (through 12.5)
 
## MOSFET $V_T$ Measurement

- $V_T$  can be determined by plotting  $I_D$  vs.  $V_{GS}$  using a low value of  $V_{DS}$ :

$$I_D = k'_n \frac{W}{L} \left[ V_{GS} - V_T - \frac{V_{DS}}{2} \right] V_{DS}$$




## MOSFET $I_D$ vs. $V_{GS}$ Characteristic

- Typically,  $V_{DS}$  is fixed when  $I_D$  is plotted as a function of  $V_{GS}$


### Long-channel MOSFET

$$V_{DS} = 2.5 V > V_{DSAT}$$

 


### Short-channel MOSFET

$$V_{DS} = 2.5 V > V_{DSAT}$$

 
 
## Subthreshold Conduction (Leakage Current)

- The transition from the ON state to the OFF state is gradual. This can be seen more clearly when  $I_D$  is plotted on a logarithmic scale:




- In the subthreshold ( $V_{GS} < V_T$ ) region,

$$I_D \propto \exp\left(\frac{qV_{GS}}{nkT}\right)$$

This is essentially the channel-source pn junction current. (Some electrons diffuse from the source into the channel, if this pn junction is forward biased.)
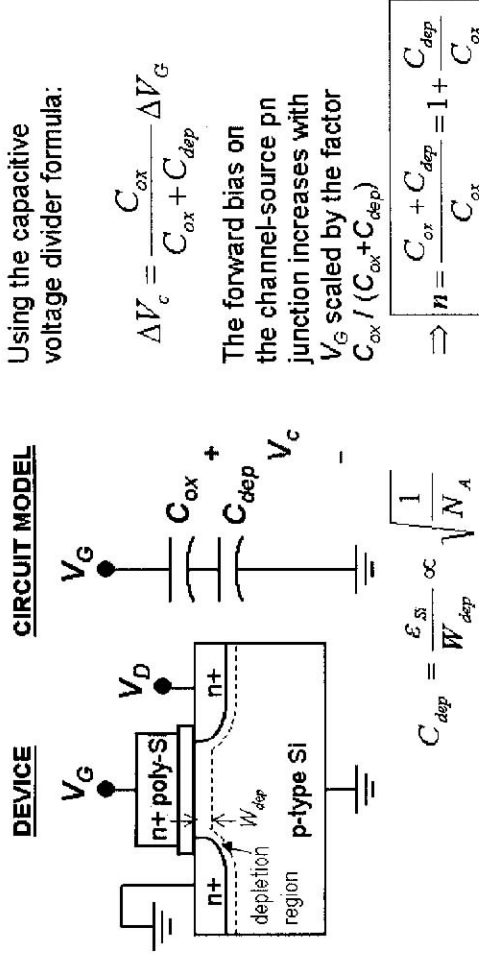
## Qualitative Explanation for Subthreshold Leakage

- The channel  $V_c$  (at the Si surface) is capacitively coupled to the gate voltage  $V_G$ :



EECS40, Spring 2004


Lecture 17, Slide 5

Prof. Sanders
 
## $V_T$ Design Trade-Off

(Important consideration for digital-circuit applications)

- Low  $V_T$  is desirable for high ON current  
 $I_{DSAT} \propto (V_{DD} - V_T)^\eta$      $1 < \eta < 2$   
 where  $V_{DD}$  is the power-supply voltage  
 ... but high  $V_T$  is needed for low OFF current




EECS40, Spring 2004

Lecture 17, Slide 7

Prof. Sanders
 
## Slope Factor (or Subthreshold Swing) $S$

- $S$  is defined to be the inverse slope of the log ( $I_D$ ) vs.  $V_{GS}$  characteristic in the subthreshold region:



$$S \equiv \eta \left( \frac{kT}{q} \right) \ln(10)$$

Units: Volts per decade

Note that  $S \geq 60$  mV/dec at room temperature:

$$\left( \frac{kT}{q} \right) \ln(10) = 60 \text{ mV}$$

EECS40, Spring 2004


Lecture 17, Slide 6

Prof. Sanders
 
## The MOSFET as a Resistive Switch

- For digital circuit applications, the MOSFET is either OFF ( $V_{GS} < V_T$ ) or ON ( $V_{GS} = V_{DD}$ ). Thus, we only need to consider two  $I_D$  vs.  $V_{DS}$  curves:

- the curve for  $V_{GS} < V_T$
- the curve for  $V_{GS} = V_{DD}$



EECS40, Spring 2004


Lecture 17, Slide 8

Prof. Sanders
 
## Equivalent Resistance $R_{eq}$

- In a digital circuit, an n-channel MOSFET in the ON state is typically used to discharge a capacitor connected to its drain terminal:

- gate voltage  $V_G = V_{DD}$
- source voltage  $V_S = 0$  V
- drain voltage  $V_D$  initially at  $V_{DD}$ , discharging toward 0 V



$$V_{DS} (V_{DD} - V_{DD} = 0)$$


$$I_{DSATn} = \frac{k'_n W}{2 L} (V_{DD} - V_{Th})^2$$

The value of  $R_{eq}$  should be set to the value which gives the correct propagation delay (time required for output to fall to  $\frac{1}{2}V_{DD}$ ):

$$R_{eq} \approx \frac{3}{4} \frac{V_{DD}}{I_{DSATn}} \left( 1 - \frac{5}{6} \lambda_n V_{DD} \right)$$
 
## P-Channel MOSFET Example

- In a digital circuit, a p-channel MOSFET in the ON state is typically used to charge a capacitor connected to its drain terminal:
  - gate voltage  $V_G = 0$  V
  - source voltage  $V_S = V_{DD}$  (power-supply voltage)
  - drain voltage  $V_D$  initially at 0 V, charging toward  $V_{DD}$



$$R_{eq} \approx \frac{3}{4} \frac{V_{DD}}{I_{DSATp}} \left( 1 - \frac{5}{6} \lambda_p V_{DD} \right)$$

$$I_{DSATp} = -\frac{k'_p W}{2 L} (V_{DD} - |V_{Tp}|)^2$$

## Typical MOSFET Parameter Values

- For a given MOSFET fabrication process technology, the following parameters are known:
  - $V_T$  ( $\sim 0.5$  V)
  - $C_{ox}$  and  $k'$  ( $< 0.001$   $\text{A/V}^2$ )
  - $V_{DSAT}$  ( $\leq 1$  V)
  - $\lambda$  ( $\leq 0.1$   $\text{V}^{-1}$ )


Example  $R_{eq}$  values for 0.25  $\mu\text{m}$  technology ( $W = L$ ):

$V_{DD}$ (V)	1	1.5	2	2.5
NMOS (k $\Omega$ )	35	19	15	13
PMOS (k $\Omega$ )	115	55	38	31

How can  $R_{eq}$  be decreased?
 
## Common-Source (CS) Amplifier


- The input voltage  $v_s$  causes  $v_{GS}$  to vary with time, which in turn causes  $i_D$  to vary.
  - The changing voltage drop across  $R_D$  causes an amplified (and inverted) version of the input signal to appear at the drain terminal.



## Notation

- Subscript convention:
  - $V_{DS} \equiv V_D - V_S$ ,  $V_{GS} \equiv V_G - V_S$ , etc.
- Double-subscripts denote DC sources:
  - $V_{DD}$ ,  $V_{CC}$ ,  $I_{SS}$ , etc.
- To distinguish between DC and incremental components of an electrical quantity, the following convention is used:
  - DC quantity: upper-case letter with upper-case subscript
    - $I_D$ ,  $V_{DS}$ , etc.
  - Incremental quantity: lower-case letter with lower-case subscript
    - $i_d$ ,  $v_{ds}$ , etc.
  - Total (DC + incremental) quantity: lower-case letter with upper-case subscript
    - $I_D$ ,  $V_{DS}$ , etc.


## Voltage Transfer Function

 

- (1): transistor biased in cutoff region
- (2):  $V_{IN} > V_T$ ; transistor biased in saturation region
- (3): transistor biased in saturation region
- (4): transistor biased in "resistive" or "triode" region
 
## Load-Line Analysis of CS Amplifier


- The operating point of the circuit can be determined by finding the intersection of the appropriate MOSFET  $i_D$  vs.  $v_{DS}$  characteristic and the load line:



## Quiescent Operating Point

- The operating point of the amplifier for zero input signal ( $v_s = 0$ ) is often referred to as the **quiescent operating point**. (Another word: **bias**.)
    - The bias point should be chosen so that the output voltage is approximately centered between  $V_{DD}$  and 0 V.
    - $v_s$  varies the input voltage around the input bias point.
- Note: The relationship between  $v_{OUT}$  and  $v_{IN}$  is not linear; this can result in a distorted output voltage signal. If the input signal amplitude is very small, however, we can have amplification with negligible distortion.


## Bias Circuit Example

 

## Rules for Small-Signal Analysis

- A DC supply voltage acts as a short circuit
  - Even if AC current flows through the DC voltage source, the AC voltage across it is zero.
- A DC supply current acts as an open circuit
  - Even if AC voltage is applied across the current source, the AC current through it is zero.

## NMOSFET Small-Signal Model

 


$$i_d = \frac{\partial i_D}{\partial V_{GS}} v_{gs} + \frac{\partial i_D}{\partial V_{DS}} v_{ds} = g_m v_{gs} + g_o v_{ds}$$

$$g_m \equiv \frac{\partial i_D}{\partial V_{GS}} \cong \frac{W}{L} k'(V_{GS} - V_T) \quad \text{transconductance}$$

$$g_o \equiv \frac{\partial i_D}{\partial V_{DS}} \cong \lambda I_D \quad \text{output conductance}$$

## Small-Signal Equivalent Circuit

 

$$v_{out} = -g_m v_{gs} (r_o \parallel R_D)$$

$$\text{voltage gain } A_v = \frac{v_{out}}{v_{in}} = -g_m (r_o \parallel R_D)$$