

## Lecture #7


### OUTLINE

- Thevenin/Norton Eq. Cont'd
- Max power transfer theorem
- The operational amplifier ("op amp")
- Feedback
- Comparator circuits
- Ideal op amp
- Unity-gain voltage follower circuit

### Reading

Complete Ch. 2, Begin Ch. 14, Look at Ch. 11

## Op Amp Circuit Symbol and Terminals

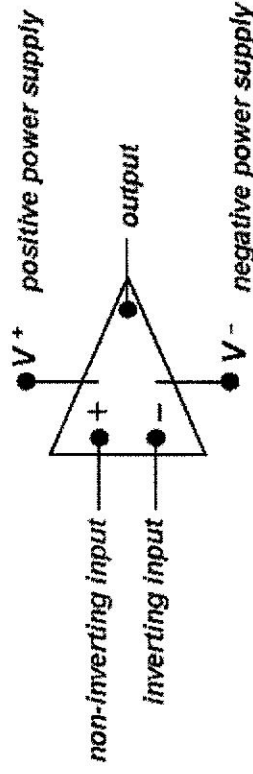

### The output voltage can range from $V^-$ to $V^+$


The positive and negative power supply voltages do not have to be equal in magnitude.

## The Operational Amplifier

- The **operational amplifier** ("**op amp**") is a basic building block used in analog circuits.
  - Its behavior is modeled using a dependent source.
  - When combined with resistors, capacitors, and inductors, it can perform various useful functions:
    - **amplification/scaling** of an input signal
    - **sign changing** (inversion) of an input signal
    - **addition** of multiple input signals
    - **subtraction** of one input signal from another
    - **integration** (over time) of an input signal
    - **differentiation** (with respect to time) of an input signal
    - **analog filtering**
    - **nonlinear functions** like exponential, log, sqrt, etc

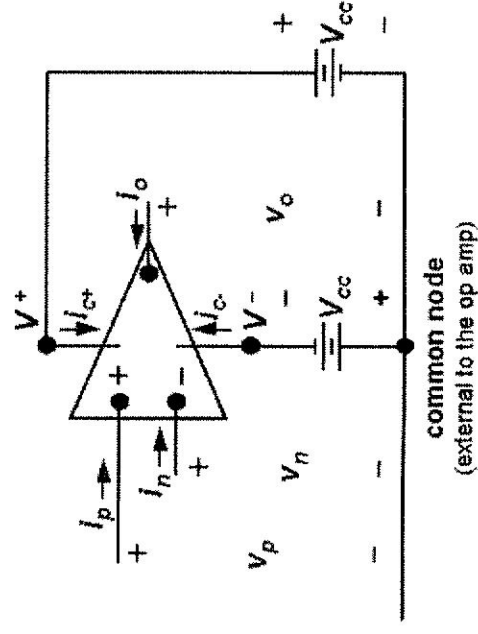
## Op Amp Terminal Voltages and Currents

- All voltages are referenced to a common node.
- Current reference directions are **into** the op amp.


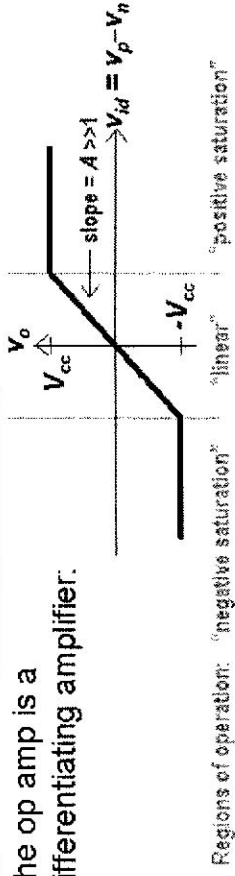
## Op Amp Voltage Transfer Characteristic

The op amp is a differentiating amplifier.



Regions of operation: "negative saturation", "linear", "positive saturation"

• In the **linear region**,  $V_o = A (V_p - V_n) = A V_{id}$  where **A is the open-loop gain**

• Typically,  $V_{cc} \leq 20 \text{ V}$  and  $A > 10^4$   
 $\rightarrow$  linear range:  $-2 \text{ mV} \leq V_{id} = (V_p - V_n) \leq 2 \text{ mV}$

Thus, for an op amp to operate in the linear region,

$$V_p \cong V_n$$

(i.e. there is a "virtual short" between the input terminals.)

## Negative vs. Positive Feedback

Familiar examples of negative feedback:

- Thermostat controlling room temperature
  - Driver controlling direction of automobile
  - Pupil diameter adjustment to light intensity
- Fundamentally pushes toward stability


Familiar examples of positive feedback:

- Microphone "squawk" in sound system
  - Mechanical bi-stability in light switches
- Fundamentally pushes toward instability or bi-stability
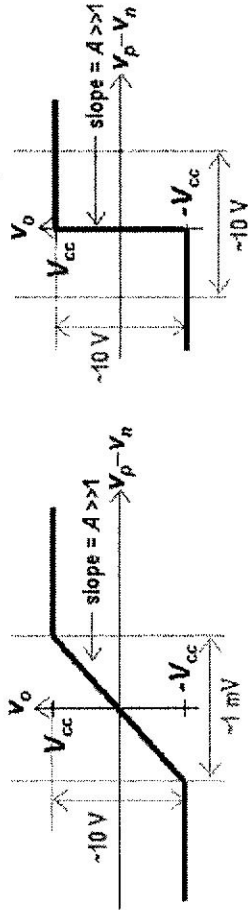
## Achieving a "Virtual Short"

- Recall the voltage transfer characteristic of an op amp:

Plotted using different scales for  $V_o$  and  $V_p - V_n$




**Q:** How does a circuit maintain a virtual short at the input of an op amp, to ensure operation in the linear region?

**A:** By using **negative feedback**. A signal is fed back from the output to the inverting input terminal, effecting a **stable** circuit connection. Operation in the **linear region** enforces the virtual short circuit.

## Op Amp Operation w/o Negative Feedback (Comparator Circuits for Analog-to-Digital Signal Conversion)

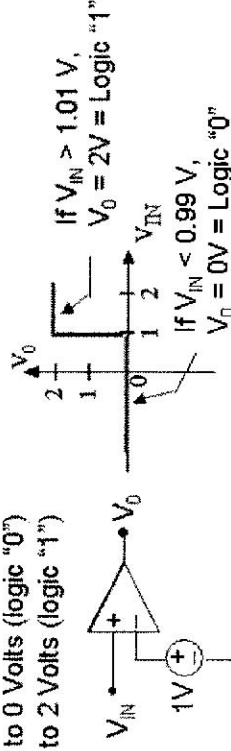
1. Simple comparator with 1 Volt threshold:

- $V^+$  is set to 0 Volts (logic "0")
- $V^+$  is set to 2 Volts (logic "1")
- $A = 100$



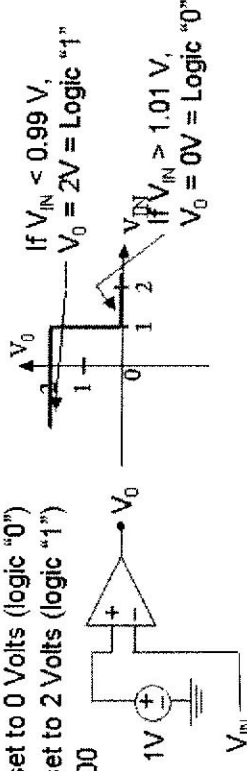2. Simple inverter with 1 Volt threshold:

- $V^+$  is set to 0 Volts (logic "0")
- $V^+$  is set to 2 Volts (logic "1")
- $A = 100$



## Op Amp Circuits with Negative Feedback

**Q:** How do we know whether an op amp is operating in the linear region?

**A:** We don't, *a priori*.

- Assume that the op amp is operating in the linear region and solve for  $v_o$  in the op-amp circuit.
  - If the calculated value of  $v_o$  is within the range from  $-V_{cc}$  to  $+V_{cc}$ , then the assumption of linear operation *might* be valid. We also need stability – usually assumed for negative feedback.
  - If the calculated value of  $v_o$  is greater than  $V_{cc}$ , then the assumption of linear operation was invalid, and the op amp output voltage is saturated at  $V_{cc}$ .
  - If the calculated value of  $v_o$  is less than  $-V_{cc}$ , then the assumption of linear operation was invalid, and the op amp output voltage is saturated at  $-V_{cc}$ .


## Ideal Op Amp

- Assumptions:

- $R_i$  is large ( $\geq 10^5 \Omega$ )
- $A$  is large ( $\geq 10^4$ )
- $R_o$  is small ( $< 100 \Omega$ )

$$\boxed{\begin{aligned} i_p &= -i_n = 0 \\ V_p &= V_n \end{aligned}}$$

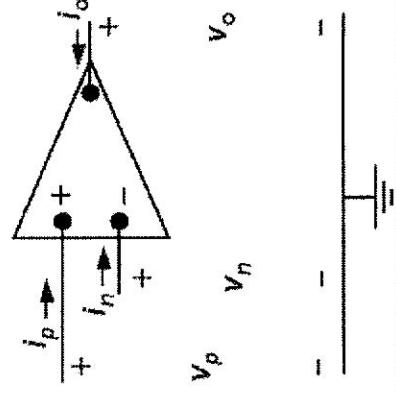- Simplified circuit symbol:
  - power-supply terminals and dc power supplies not shown




**Note:** The resistances used in an op-amp circuit must be much larger than  $R_o$  and much smaller than  $R_i$  in order for the ideal op amp equations to be accurate.

## Op Amp Circuit Model (Linear Region)

$R_i$  is the equivalent resistance “seen” at the input terminals, typically very large ( $> 1M\Omega$ ), so that the input current is usually very small:


$$i_p = -i_n \cong 0$$

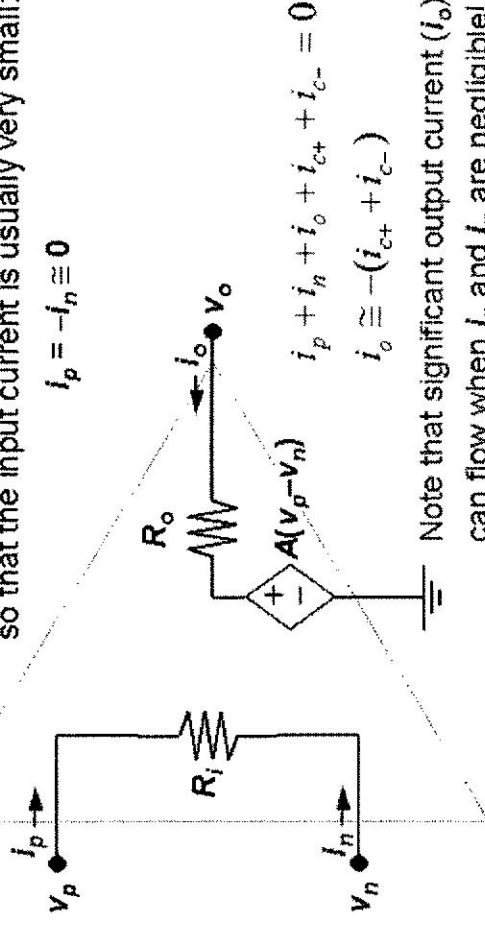

$$\begin{aligned} i_p + i_n + i_o + i_{c+} + i_{c-} &= 0 \\ i_o &\cong -(i_{c+} + i_{c-}) \end{aligned}$$


Note that significant output current ( $i_o$ ) can flow when  $i_p$  and  $i_n$  are negligible!

## Unity-Gain Voltage Follower Circuit

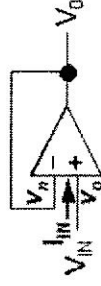

$$\boxed{V_p = V_n \rightarrow V_o = V_{IN}}$$

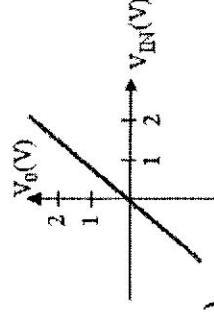(valid as long as  $V_- \leq V_o \leq V_+$ )



Note that the analysis of this simple (but important) circuit required only one of the ideal op-amp rules.

**Q:** Why is this circuit important (i.e. what is it good for)?

**A:** A “weak” source can drive a “heavy” load; in other words, the source  $V_{IN}$  only needs to supply a little power (since  $i_{IN} = 0$ ), whereas the output can drive a power-hungry load (with the op-amp providing the power).