

Lecture #8


OUTLINE

- Op-Amp ckt's continued: examples
- Inverting amplifier circuit
- Summing amplifier circuit
- Noninverting amplifier circuit
- Differential amplifier circuit

Reading

Chapter 14, also refer to Ch. 11

Inverting Amplifier Circuit

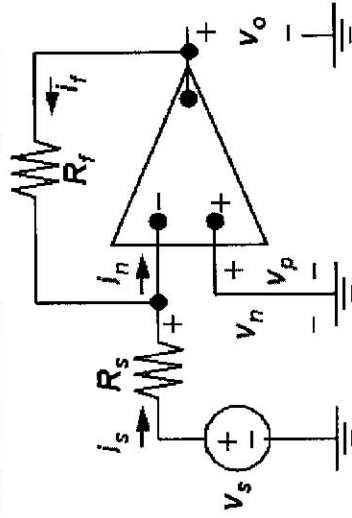

$$v_o = -\frac{R_f}{R_s} v_s$$



$$i_n = 0 \rightarrow i_s = -i_f$$

$$v_p = 0 \rightarrow v_n = 0$$



Review: Negative Feedback

- Negative feedback is used to "linearize" a high-gain differential amplifier.

Without feedback

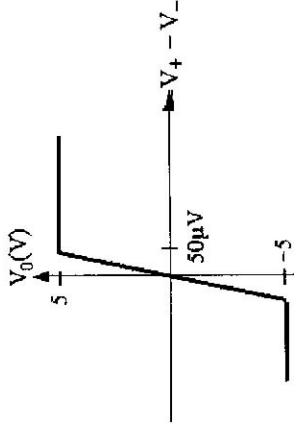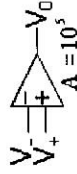

With feedback

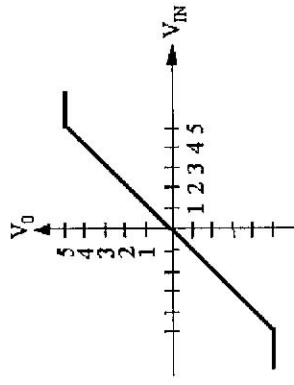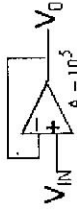


Analysis using Realistic Op Amp Model

- In the analysis on the previous slide, the op amp was assumed to be ideal, *i.e.*

$$R_i = \infty; A = \infty; R_o = 0$$
- In reality, an op amp has finite R_i , finite A , non-zero R_o , and usually is loaded at its output terminals with a load resistance R_L .


Summing Amplifier Circuit

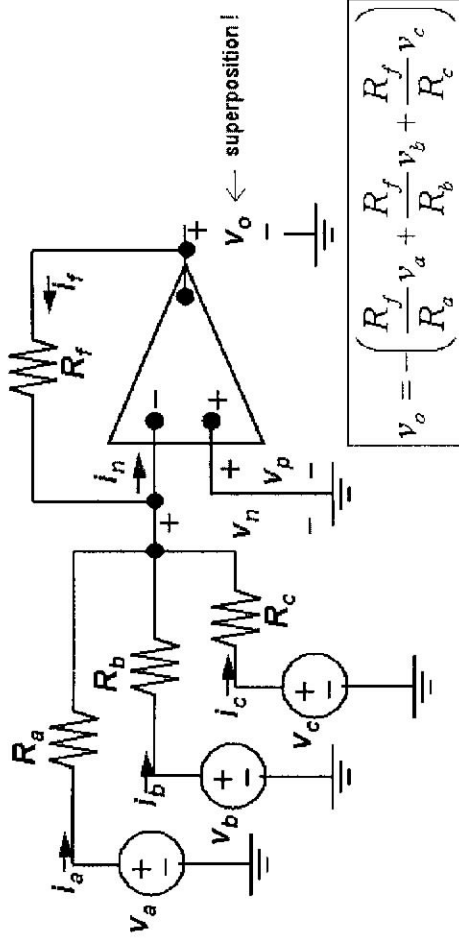

$$i_n = 0 \rightarrow i_a + i_b + i_c = -i_f$$

$$V_p = 0 \rightarrow V_n = 0$$


Characteristic of 4-Bit DAC

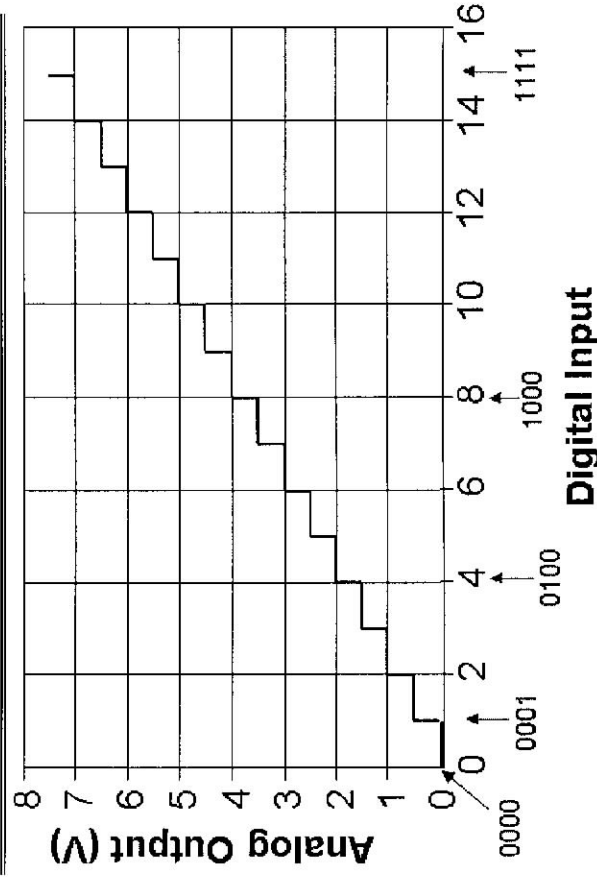

Application: Digital-to-Analog Conversion

A DAC can be used to convert the digital representation of an audio signal into an analog voltage that is then used to drive speakers -- so that you can hear it!

"Weighted-adder D/A converter"

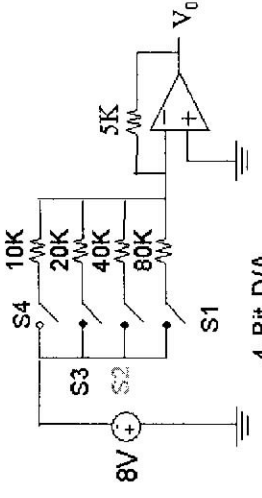


- S1 closed if LSB = 1
- S2 " " if next bit = 1
- S3 " " if " = 1
- S4 " " if MSB = 1

(Transistors are used as electronic switches)

MSB LSB

Binary number	Analog output (volts)
0000	0
0001	.5
0010	1
0011	1.5
0100	2
0101	2.5
0110	3
0111	3.5
1000	4
1001	4.5
1010	5
1011	5.5
1100	6
1101	6.5
1110	7
1111	7.5

Noninverting Amplifier Circuit

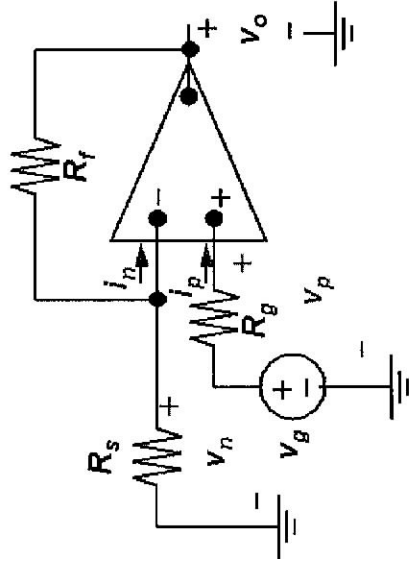


$$v_o = \frac{R_s + R_f}{R_g} v_g$$

$$i_p = 0 \rightarrow V_p = V_g \rightarrow V_n = V_g$$

$$i_n = 0 \rightarrow R_s \text{ \& \ } R_f \text{ form a voltage divider}$$

Differential Amplifier Circuit

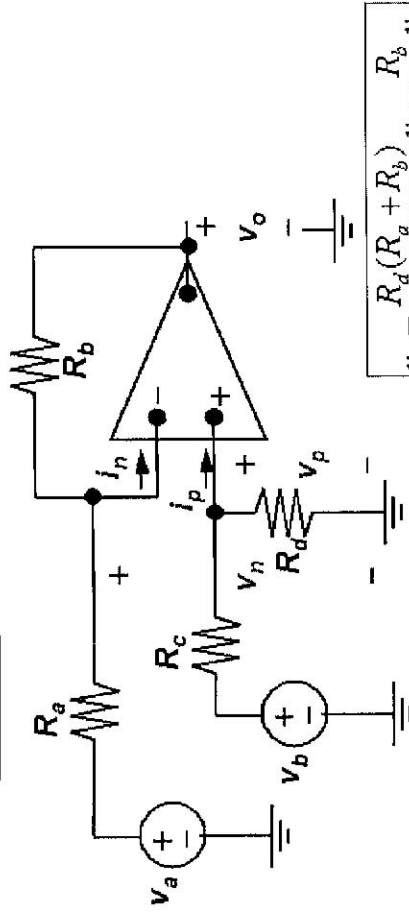

$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} v_b - \frac{R_b}{R_a} v_a$$

$$i_n = 0 \rightarrow \frac{v_n - v_a}{R_a} + \frac{v_n - v_o}{R_b} = 0$$

$$i_p = 0 \rightarrow v_p = \frac{R_d}{R_c + R_d} v_b = v_n \quad \text{If } \frac{R_a}{R_b} = \frac{R_c}{R_d}, \text{ then } v_o = \frac{R_b}{R_a} (v_b - v_a)$$

Differential Amplifier (cont'd)

$$\text{If } \frac{R_a}{R_b} = \frac{R_c}{R_d}, \text{ then } v_{cm} = 0 \text{ and } v_{dm} = \frac{R_b}{R_a} v_a$$

- An ideal differential amplifier amplifies only the differential mode portion of the input voltage, and eliminates the common mode portion.
 - provides immunity to noise (common to both inputs)
- If the resistors are not perfectly matched, the **common mode rejection ratio (CMRR)** is finite:

$$CMRR \equiv \left| \frac{A_{dm}}{A_{cm}} \right| \approx \frac{1 + R_b/R_c}{\epsilon} \text{ if } \frac{R_a}{R_b} = (1 - \epsilon) \frac{R_c}{R_d}$$

Differential Amplifier – Another Perspective

Redefine the inputs in terms of two other voltages:

- differential mode input** $v_{dm} \equiv v_b - v_a$
- common mode input** $v_{cm} \equiv (v_a + v_b)/2$

so that

$$v_a = v_{cm} - (v_{dm}/2) \text{ and } v_b = v_{cm} + (v_{dm}/2)$$

Then it can be shown that


$$v_o = A_{cm} v_{cm} + A_{dm} v_{dm}$$

$$\text{where } A_{cm} = \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)} \text{ and } A_{dm} = \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2 R_a (R_c + R_d)}$$

“common mode gain” “differential mode gain”

Summary

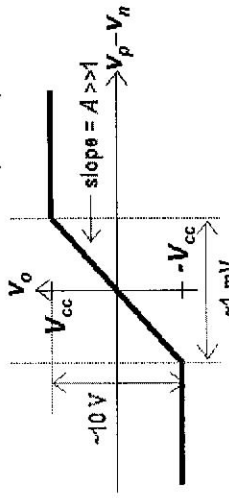• Voltage transfer characteristic of op amp:



- A feedback path between an op amp's output and its inverting input can force the op amp to operate in its linear region, where $v_o = A (v_p - v_n)$
- An ideal op amp has infinite input resistance R_i , infinite open-loop gain A , and zero output resistance R_o . As a result, the input voltages and currents are constrained: $v_p = v_n$ and $i_p = -i_n = 0$