

# Lecture #10

---

## OUTLINE

- Mutual inductance
- First-order circuits

## Reading

Chapter 3, begin Chapter 4

# Mutual Inductance


- Mutual inductance occurs when two windings are arranged so that they have a mutual flux linkage.
- The change in current in one winding causes a voltage drop to be induced in the other.

Example: Consider left-hand side of the diagram below

– self-induced voltage is  $L_1(di_1/dt)$


– mutually induced voltage is  $M(di_2/dt)$

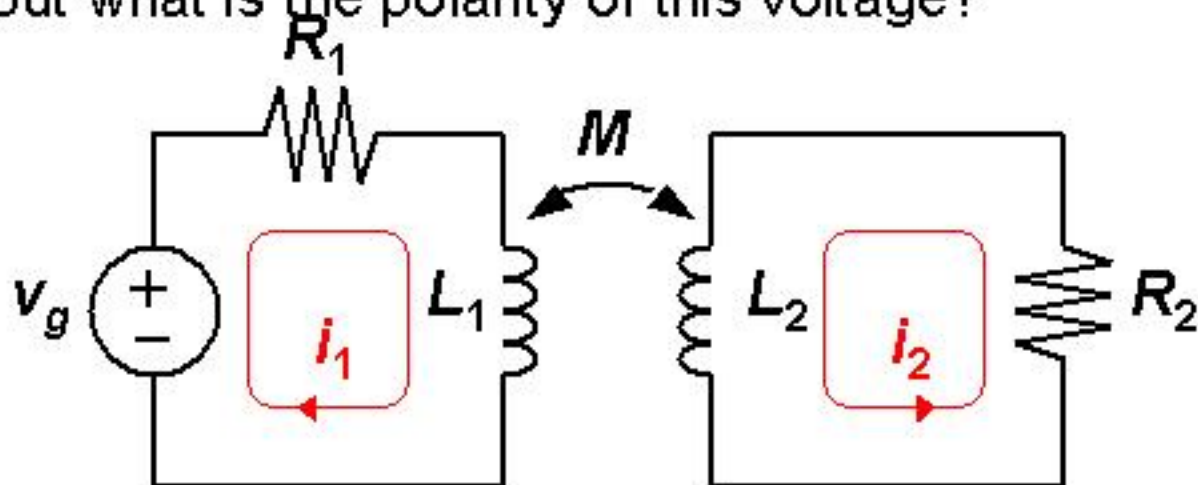...but what is the polarity of this voltage?



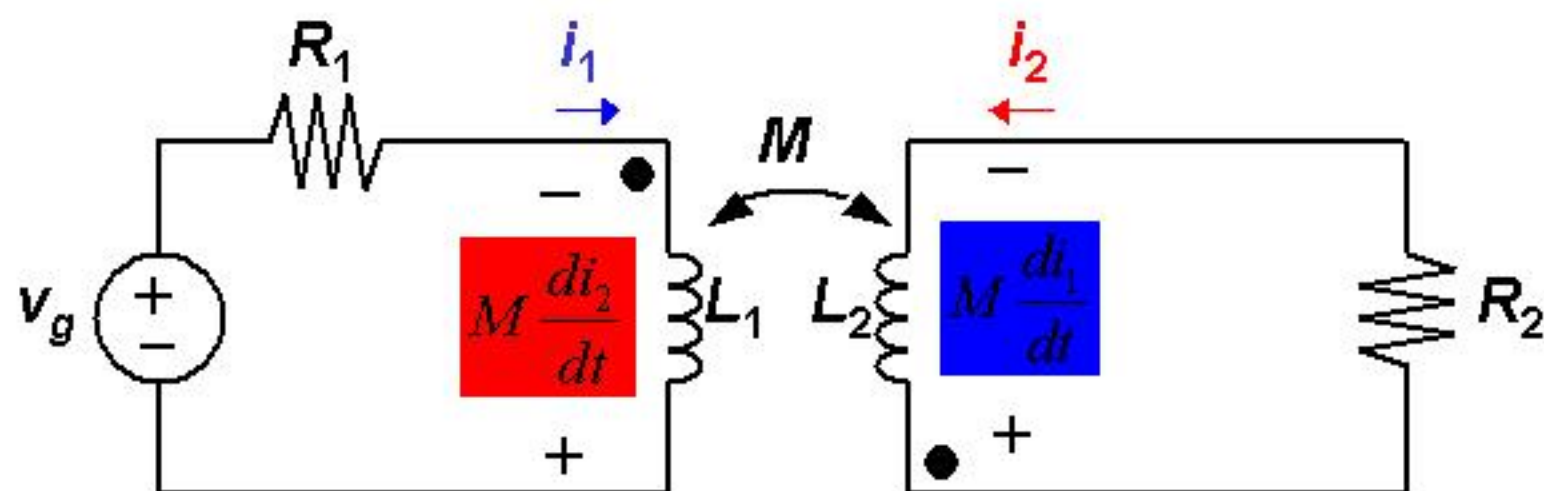
# The “Dot Convention”

- If a current “enters” the dotted terminal of a coil, the reference polarity of the voltage induced in the other coil is positive at its dotted terminal.
- If a current “leaves” the dotted terminal of a coil, the reference polarity of the voltage induced in the other coil is negative at its dotted terminal.


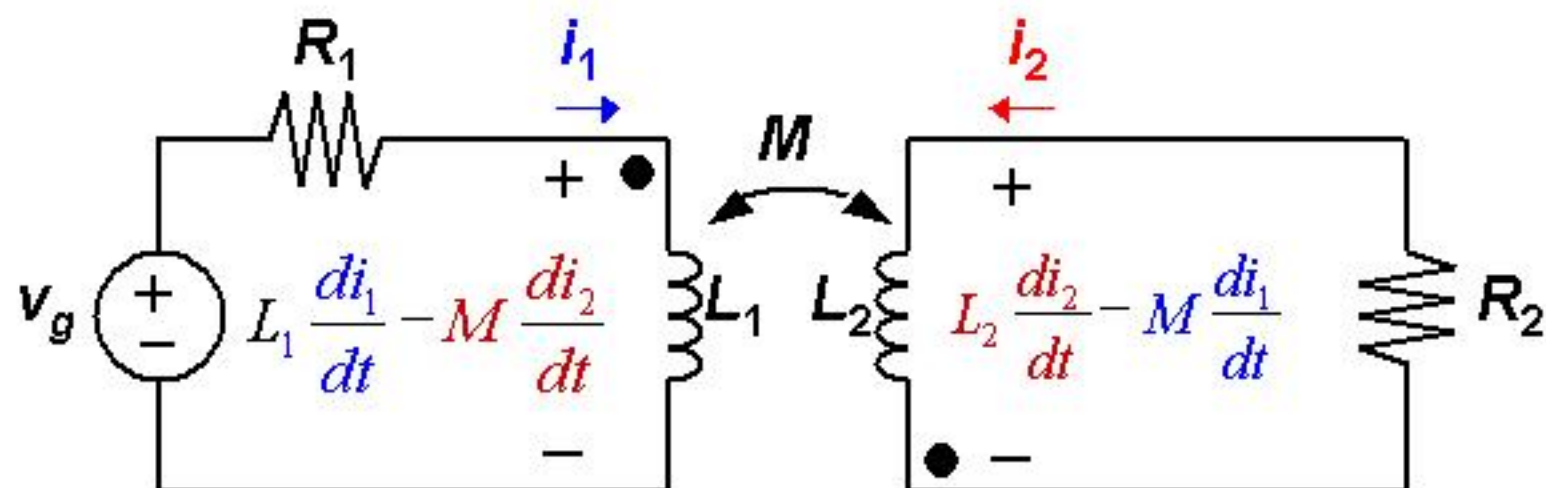
# Induced Voltage Drop

- The total induced voltage drop across a winding is equal to the sum of the self-induced voltage and the mutually induced voltage
- Example (cont'd): Apply KVL to loops





# Relationship between $M$ and $L_1, L_2$

---
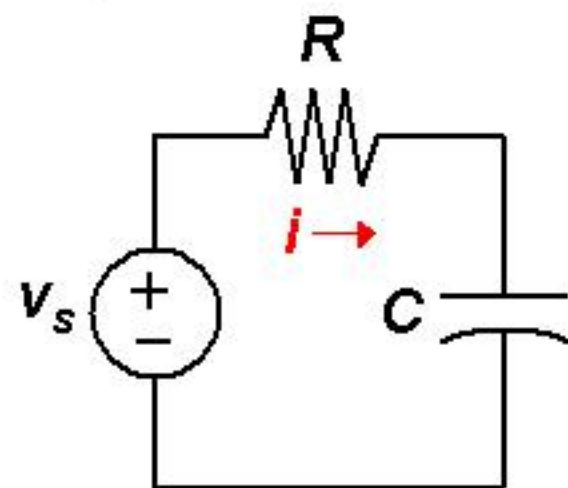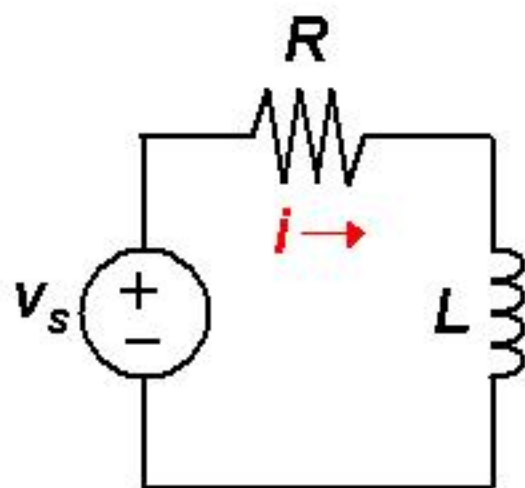
# First-Order Circuits

---

- A circuit which contains only sources, resistors and an inductor is called an **RL circuit**.
- A circuit which contains only sources, resistors and a capacitor is called an **RC circuit**.
- RL and RC circuits are called first-order circuits because their voltages and currents are described by first-order differential equations.




- 
- The ***natural response*** of an RL or RC circuit is its behavior (*i.e.* current and voltage) when stored energy in the inductor or capacitor is released to the resistive part of the network (containing no independent sources).
  
  - The ***step response*** of an RL or RC circuit is its behavior when a voltage or current source **step** is applied to the circuit, or immediately after a switch state is changed.
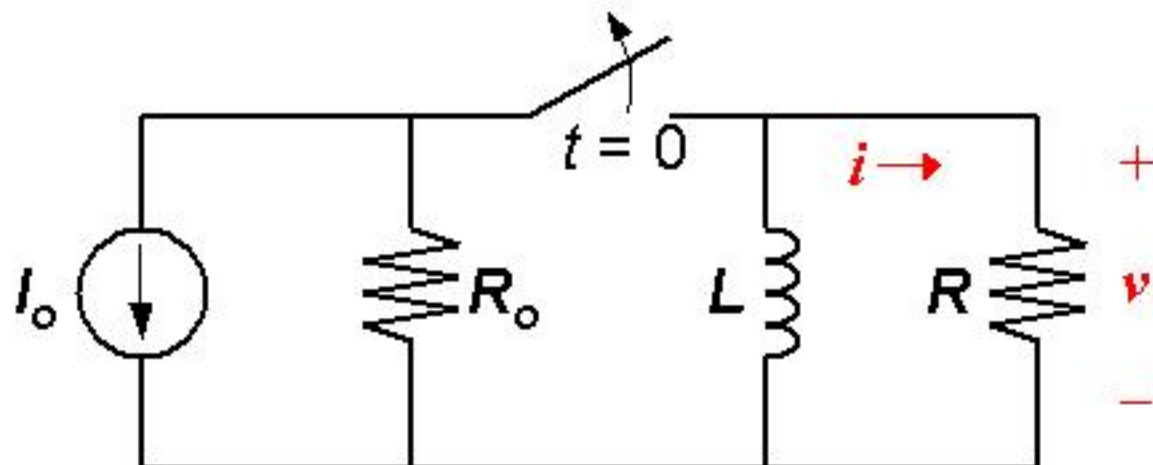
# Natural Response of an RL Circuit

---

- Consider the following circuit, for which the switch is closed for  $t < 0$ , and then opened at  $t = 0$ :



## Notation:

$0^-$  is used to denote the time just prior to switching

$0^+$  is used to denote the time immediately after switching


- The current flowing in the inductor at  $t = 0^-$  is  $I_0$ .



## Solving for the Current ( $t \geq 0$ )

---

- For  $t > 0$ , the circuit reduces to

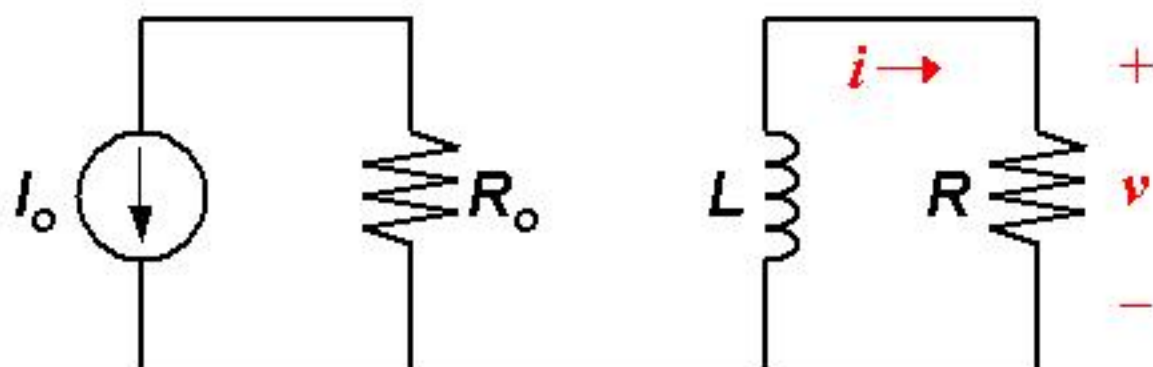


- Applying KVL to the LR circuit:

- Solution:  $i(t) = i(0)e^{-(R/L)t}$

## Solving for the Voltage ( $t > 0$ )

---

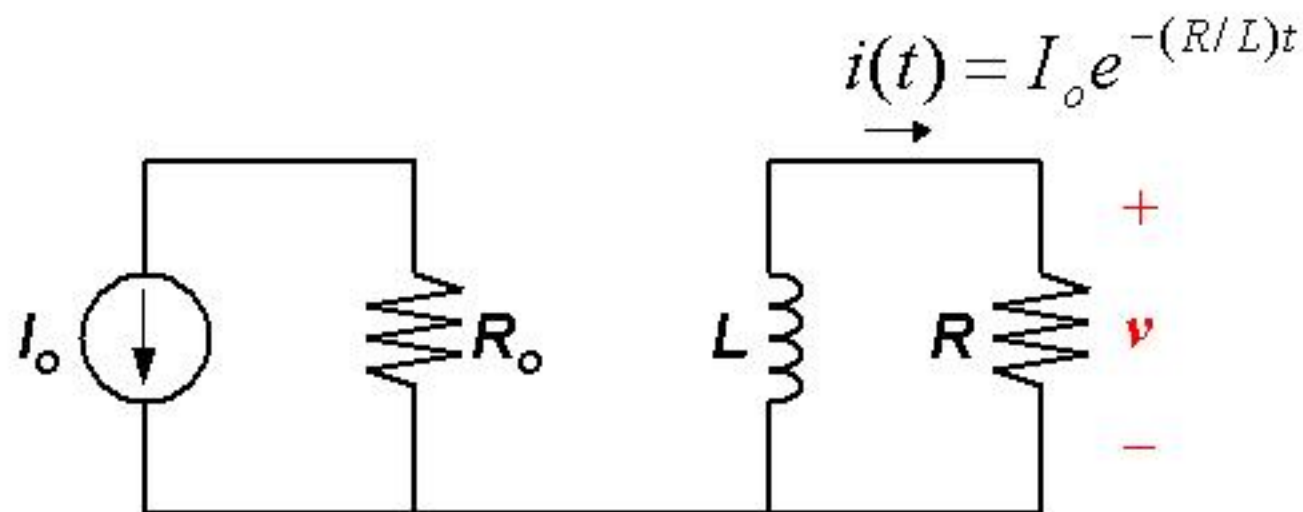

- Note that the voltage changes abruptly:

$$v(0^-) = 0$$

$$\text{for } t > 0, \quad v(t) = iR = I_o R e^{-(R/L)t}$$

$$\Rightarrow v(0^+) = I_o R$$

## Time Constant $\tau$

---

- In the example, we found that

$$i(t) = I_o e^{-(R/L)t} \quad \text{and} \quad v(t) = I_o R e^{-(R/L)t}$$

- Define the **time constant**

$$\tau = \frac{L}{R}$$

- At  $t = \tau$ , the current has reduced to  $1/e$  ( $\sim 0.37$ ) of its initial value.
- At  $t = 5\tau$ , the current has reduced to less than 1% of its initial value.

# Transient vs. Steady-State Response


---

- The momentary behavior of a circuit (in response to a change in stimulation) is referred to as its **transient response**.
  
  
  
  
  
  
  
  
  
  
- The behavior of a circuit a long time (many time constants) after the change in voltage or current is called the **steady-state response**.
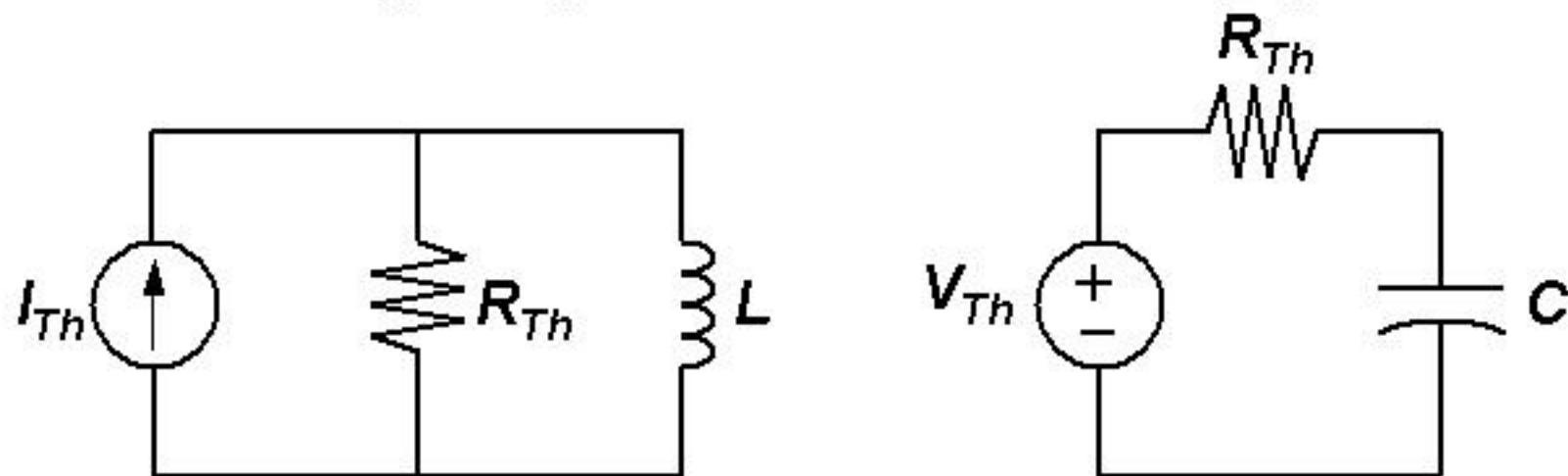
## Review (Conceptual)

---

- Any\* first-order circuit can be reduced to a Thévenin (or Norton) equivalent connected to either a single equivalent inductor or capacitor.




- In steady state, an inductor behaves like a short circuit
- In steady state, a capacitor behaves like an open circuit
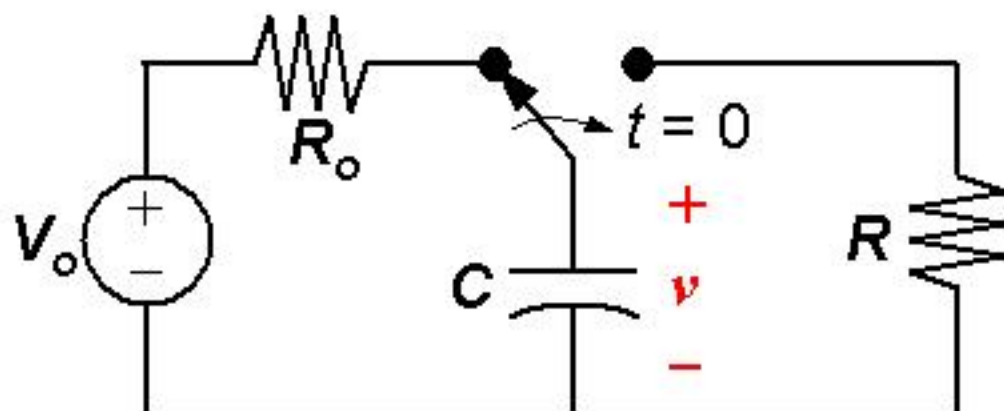
# Natural Response of an RC Circuit

---

- Consider the following circuit, for which the switch is closed for  $t < 0$ , and then opened at  $t = 0$ :



## Notation:

$0^-$  is used to denote the time just prior to switching


$0^+$  is used to denote the time immediately after switching

- The voltage on the capacitor at  $t = 0^-$  is  $V_0$

## Solving for the Voltage ( $t \geq 0$ )

---


- For  $t > 0$ , the circuit reduces to

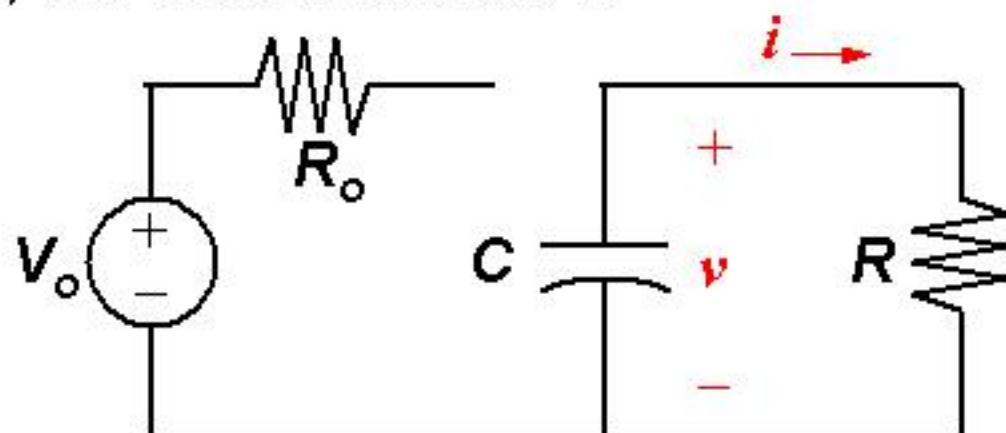

- Applying KCL to the RC circuit:

- Solution:  $v(t) = v(0)e^{-t/RC}$

## Solving for the Current ( $t > 0$ )

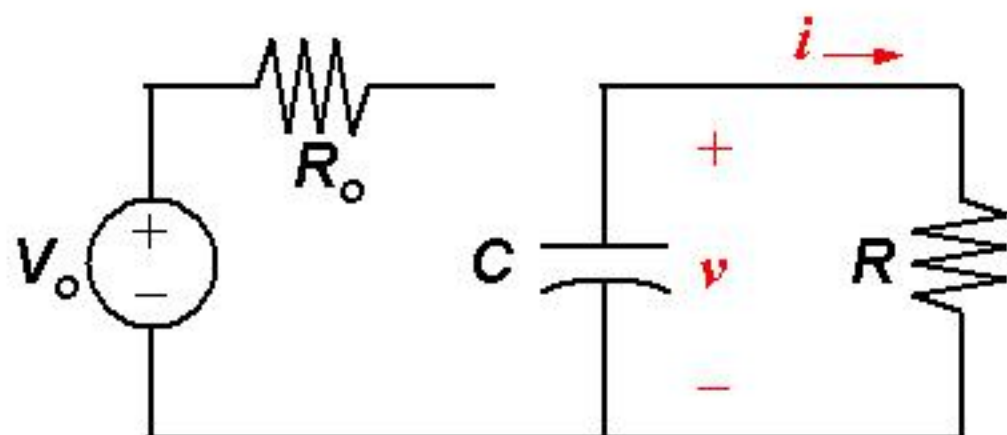

$$v(t) = V_o e^{-t/RC}$$

- Note that the current changes abruptly:

$$i(0^-) = 0$$

$$\text{for } t > 0, i(t) = \frac{v}{R} = \frac{V_o}{R} e^{-t/RC}$$

$$\Rightarrow i(0^+) = \frac{V_o}{R}$$



## Time Constant $\tau$

---


- In the example, we found that

$$v(t) = V_o e^{-t/RC} \quad \text{and} \quad i(t) = \frac{V_o}{R} e^{-t/RC}$$

- Define the **time constant**  $\tau = RC$ 
  - At  $t = \tau$ , the voltage has reduced to  $1/e$  ( $\sim 0.37$ ) of its initial value.
  - At  $t = 5\tau$ , the voltage has reduced to less than 1% of its initial value.

# Natural Response Summary

## RL Circuit

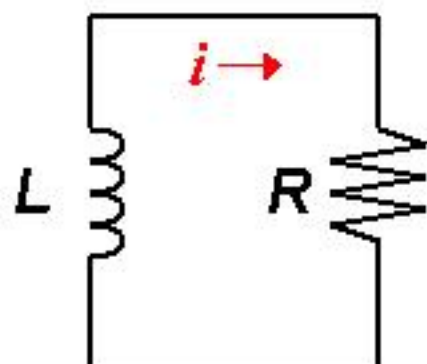


- Inductor current cannot change instantaneously

$$i(0^-) = i(0^+)$$

$$i(t) = i(0)e^{-t/\tau}$$

- time constant  $\tau = \frac{L}{R}$

## RC Circuit

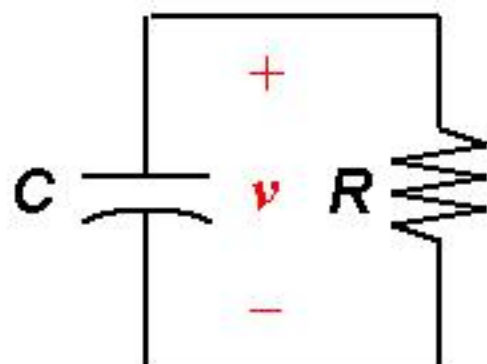

- Capacitor voltage cannot change instantaneously

$$v(0^-) = v(0^+)$$

$$v(t) = v(0)e^{-t/\tau}$$

- time constant  $\tau = RC$