

Lecture #18

OUTLINE


- Continue small signal analysis
- Logic functions
- NMOS logic gates
- The CMOS inverter

Reading

- Rabaey *et al.*: Chapter 5.2
- Hambley: Chapter 7.1-7.2

Digital Signals

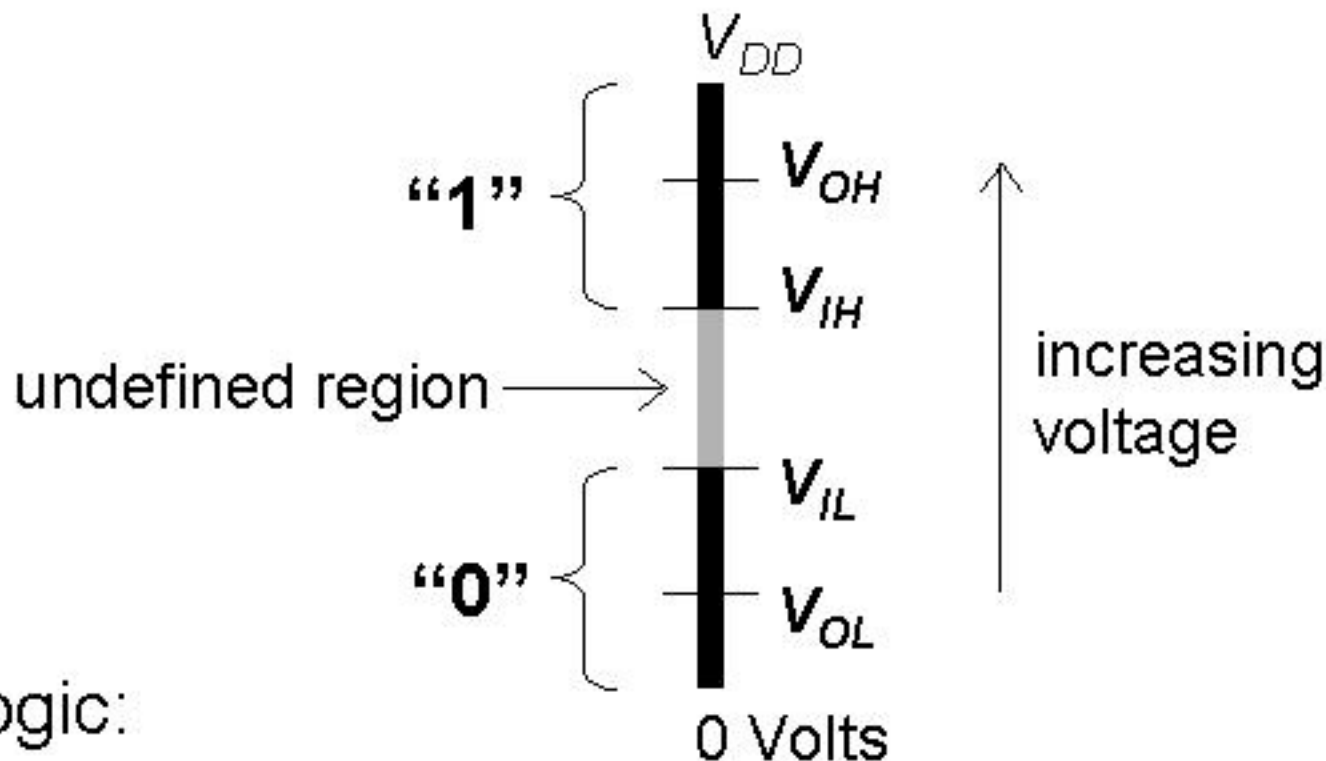- For a digital signal, the voltage must be within one of two ranges in order to be defined:



- Positive Logic:
 - "low" voltage \equiv logic state 0
 - "high" voltage \equiv logic state 1

Logic Functions, Symbols, & Notation


NAME

SYMBOL

NOTATION

TRUTH
TABLE

“NOT”

 

$$F = \bar{A}$$

A	F
0	1
1	0


“OR”



$$F = A + B$$

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

“AND”

 

$$F = A \cdot B$$

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1


“NOR”



$$F = \overline{A+B}$$

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

“NAND”

 

$$F = \overline{A \cdot B}$$

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

“XOR”
(exclusive OR)




$$F = A \oplus B$$



A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

NMOS Inverter ("NOT" Gate)

Circuit:

 

Voltage-Transfer Characteristic

  


increasing
 $v_{GS} = v_{IN} > V_T$


A	F
0	1
1	0

Noise Margins

Definition of Input Levels

 

Definition of Noise Margins

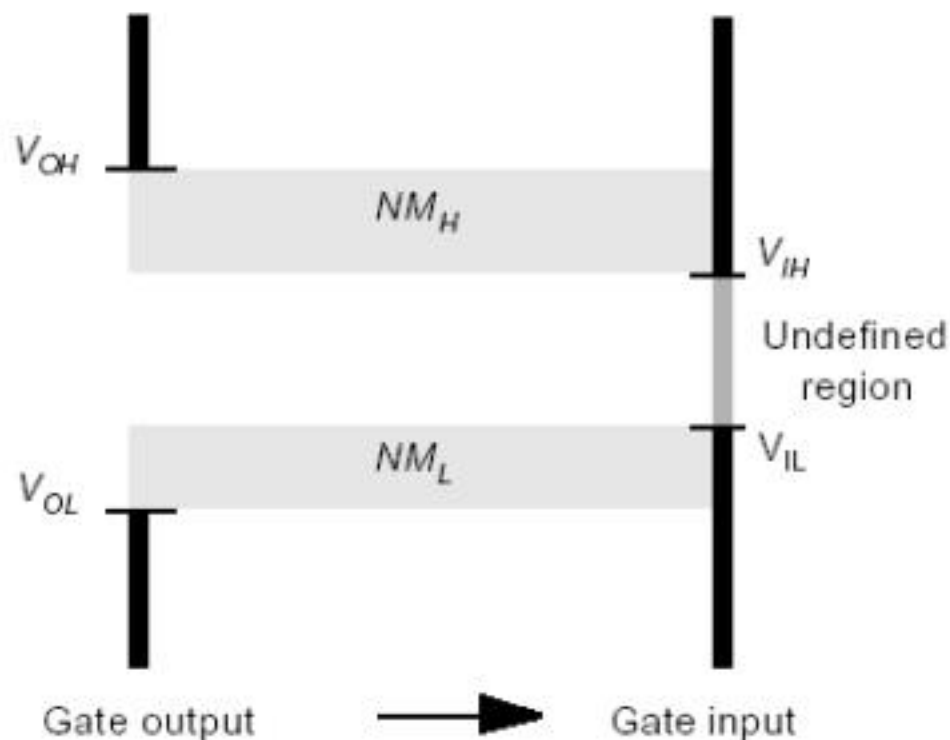


Noise margin high $NM_H = V_{OH} - V_{IH}$

Noise margin low $NM_L = V_{IL} - V_{OL}$

NMOS NAND Gate

 - Output is low only if both inputs are high




Truth Table

<u>A</u>	<u>B</u>	<u>F</u>
0	0	1
0	1	1
1	0	1
1	1	0

NMOS NOR Gate

- Output is low if either input is high

 

Truth Table

<u>A</u>	<u>B</u>	<u>F</u>
0	0	1
0	1	0
1	0	0
1	1	0


Disadvantages of NMOS Logic Gates

- Large values of R_D are required in order to
 - achieve a low value of V_{OL}
 - keep power consumption low

- Large resistors are needed, but these take up a lot of space.
 - One solution is to replace the resistor with an NMOSFET that is always on.


The CMOS Inverter: Intuitive Perspective

CIRCUIT

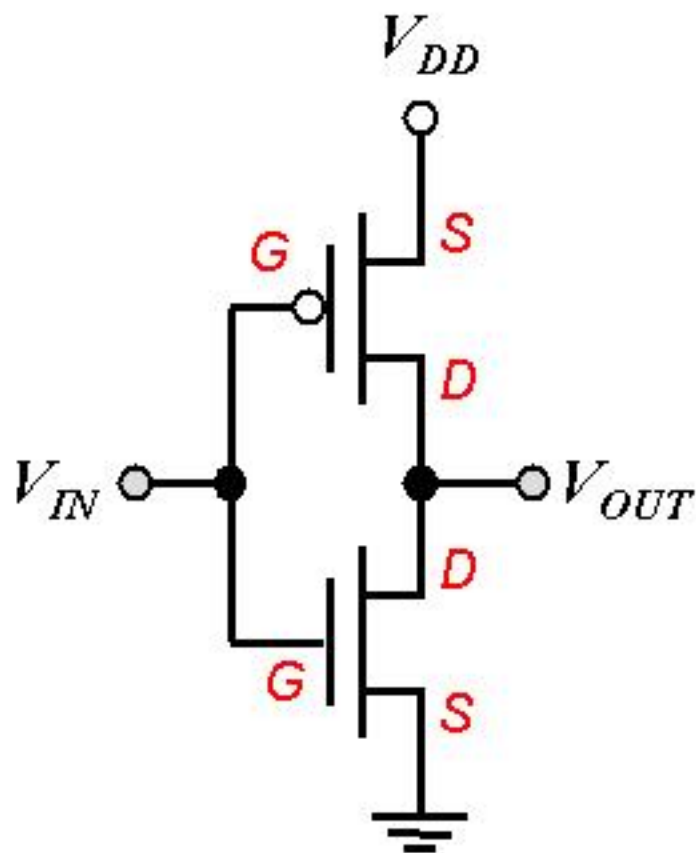

Low static power consumption, since one MOSFET is always off in steady state


SWITCH MODELS

 

$$V_{IN} = V_{DD}$$

$$V_{IN} = 0\text{ V}$$

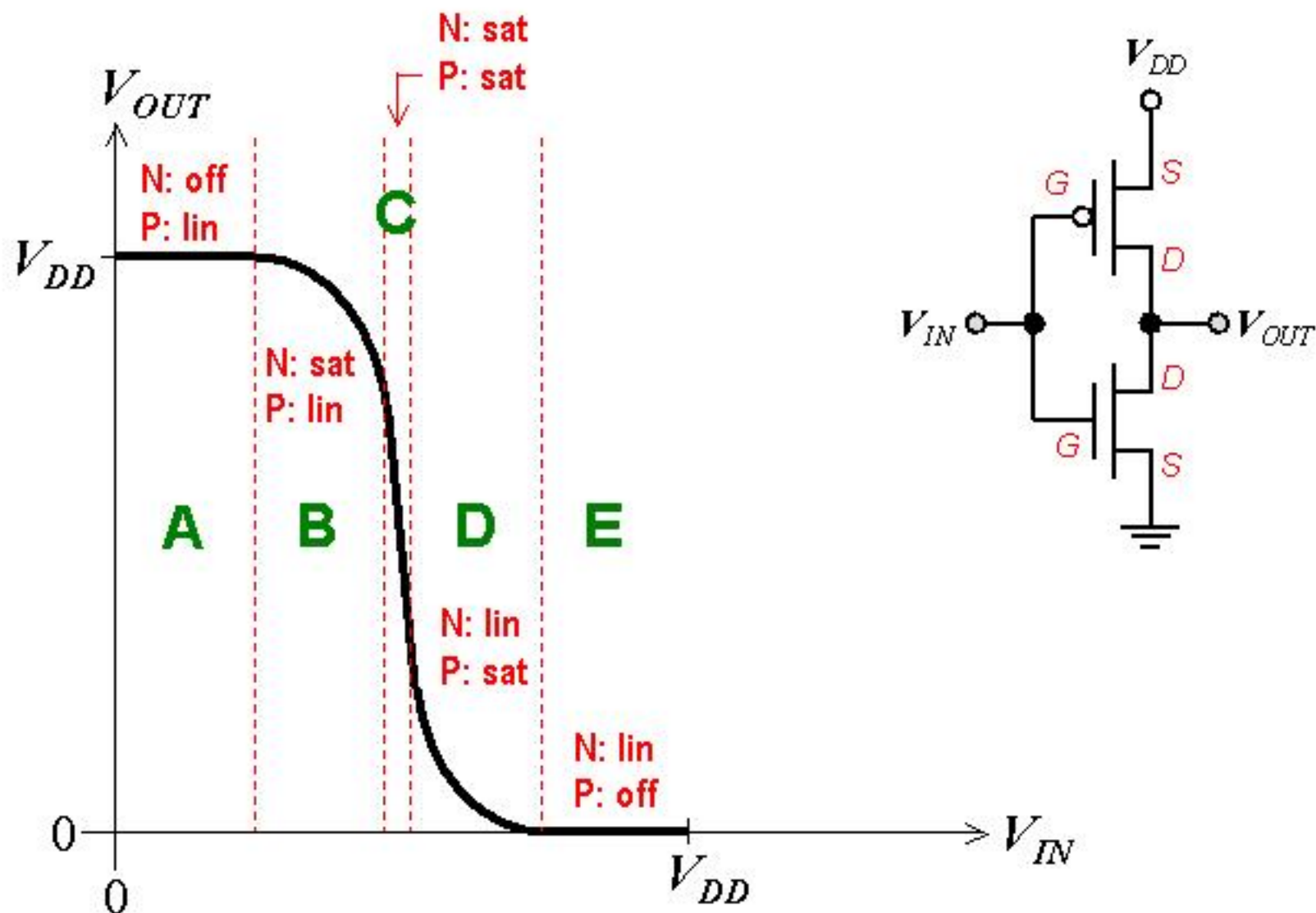
CMOS Inverter Voltage Transfer Characteristic



CMOS Inverter Load-Line Analysis



$$V_{IN} = V_{DD} + V_{GSp}$$

$$V_{OUT} = V_{DD} + V_{DSp}$$

 



CMOS Inverter Load-Line Analysis: Region A

$$V_{IN} \leq V_{Tn}$$

  



CMOS Inverter Load-Line Analysis: Region B

$$V_{DD}/2 > V_{IN} > V_{Tn}$$

  

CMOS Inverter Load-Line Analysis: Region D

$$V_{DD} - |V_{Tp}| > V_{IN} > V_{DD}/2$$

  

CMOS Inverter Load-Line Analysis: Region E

$$V_{IN} > V_{DD} - |V_{Tp}|$$

$$I_{Dn} = -I_{Dp}$$

