

# Lecture #21

---

## ANNOUNCEMENT

- Midterm 2 thurs. april 15, 9:40-11am.
- A-M initials in 10 Evans
- N-Z initials in Sibley auditorium
- Closed book, except for two 8.5 x 11 inch cheat sheets
- Comprehensive, but focuses on HW's 5-9; L's, C's, 1<sup>st</sup>-order ckts, semiconductor devices, diode ckts, mosfet model, common source amplifier
- extra office hour with Mervin in 297 Cory next Monday 6-7pm

## OUTLINE


- Sequential logic circuits
- Fan-out
- Propagation delay
- CMOS power consumption

Reading: Hambley Ch. 7; Rabaey et al. Secs. 5.2, 5.5, 6.2.1
 
# Flip-Flops

---


- One of the basic building blocks for sequential circuits is the **flip-flop**:
  - 2 stable operating states  $\rightarrow$  stores 1 bit of info.
  - A simple flip-flop can be constructed using two inverters:



# The S-R (“Set”-“Reset”) Flip-Flop

---


## S-R Flip-Flop Symbol:

 

- Rule 1:
  - If **S = 0** and **R = 0**, **Q** does not change.
- Rule 2:
  - If **S = 0** and **R = 1**, then **Q = 0**
- Rule 3:
  - If **S = 1** and **R = 0**, then **Q = 1**
- Rule 4:
  - **S = 1** and **R = 1** should never occur.

# Realization of the S-R Flip-Flop

---

 


R	S	$Q_n$
0	0	$Q_{n-1}$
0	1	1
1	0	0
1	1	<b>(not allowed)</b>
 
# Clock Signals

---


- Often, the operation of a sequential circuit is synchronized by a **clock signal** :



- The clock signal regulates when the circuits respond to new inputs, so that operations occur in proper sequence.
- Sequential circuits that are regulated by a clock signal are said to be **synchronous**.

# Clocked S-R Flip-Flop

---

 


- When **CK = 0**, the value of **Q** does not change
- When **CK = 1**, the circuit acts like an ordinary S-R flip-flop

# The D (“Delay”) Flip-Flop

---

## D Flip-Flop Symbol:

 


- The output terminals **Q** and **Q** behave just as in the S-R flip-flop.
- **Q** changes only when the clock signal **CK** makes a positive transition.

<b>CK</b>	<b>D</b>	<b>Q<sub>n</sub></b>
<b>0</b>	<b>x</b>	<b>Q<sub>n-1</sub></b>
<b>1</b>	<b>x</b>	<b>Q<sub>n-1</sub></b>
<b>↑</b>	<b>0</b>	<b>0</b>
<b>↑</b>	<b>1</b>	<b>1</b>


# D Flip-Flop Example (Timing Diagram)

---


CK

 

D

 

Q

 




# Registers

---

- A **register** is an array of flip-flops that is used to store or manipulate the bits of a digital word.

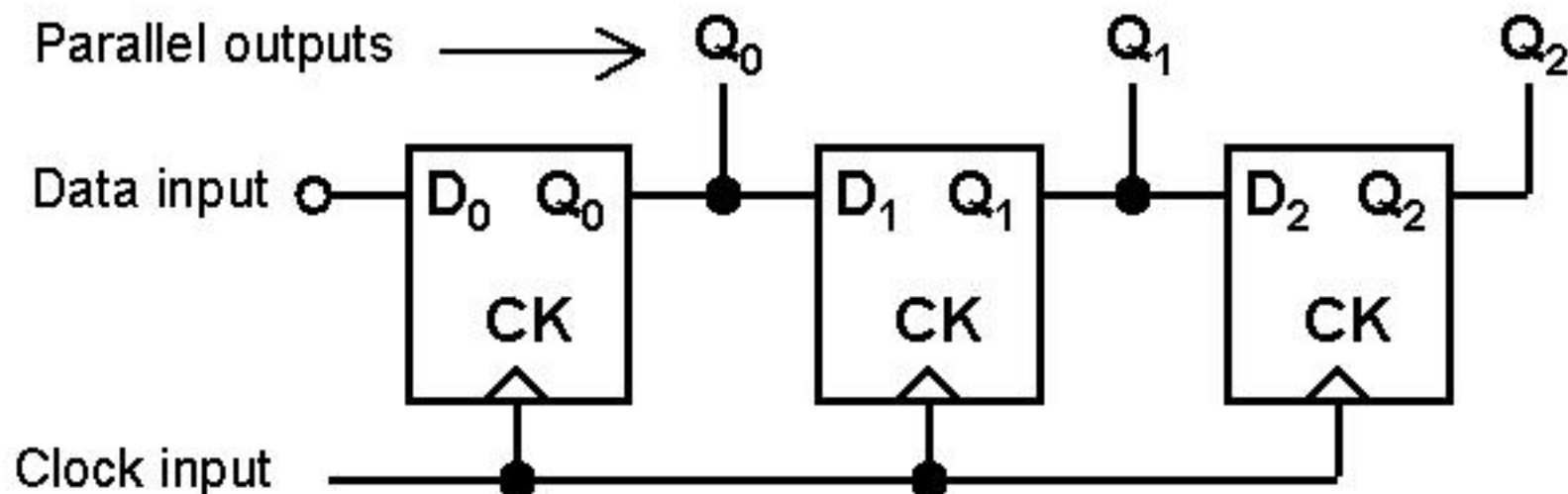Example: Serial-In, Parallel-Out Shift Register




## Conclusion (Logic Circuits)

---

- Complex combinational logic functions can be achieved simply by interconnecting NAND gates (or NOR gates).
- Logic gates can be interconnected to form flip-flops.
- Interconnections of flip-flops form registers.
- A complex digital system such as a computer consists of many gates, flip-flops, and registers. Thus, logic gates are the basic building blocks for complex digital systems.
 
# Fan-Out



- Typically, the output of a logic gate is connected to the input(s) of one or more logic gates
- The ***fan-out*** is the number of gates that are connected to the output of the driving gate:



- Fanout leads to increased capacitive load on the driving gate, and therefore longer propagation delay
  - The input capacitances of the driven gates sum, and must be charged through the equivalent resistance of the driver
  
# Effect of Capacitive Loading

- When an input signal of a logic gate is changed, there is a **propagation delay** before the output of the logic gate changes. This is due to capacitive loading at the output.



**The propagation delay is measured between the 50% transition points of the input and output signals.**

# Calculating the Propagation Delay

Model the MOSFET in the ON state as a resistive switch:


Case 1:  $V_{out}$  changing from High to Low  
(input signal changed from Low to High)

- NMOSFET(s) connect  $V_{out}$  to  $GND$

$$t_{pHL} = 0.69 \times R_n C_L$$

Pull-up network is modeled as an open switch  $\rightarrow$

 Pull-down network is modeled as a resistor  $\rightarrow$



# Calculating the Propagation Delay (cont'd)

Case 2:  $V_{out}$  changing from Low to High  
(input signal changed from High to Low)


- PMOSFET(s) connect  $V_{out}$  to  $V_{DD}$

$$t_{pLH} = 0.69 \times R_p C_L$$

Pull-up network is modeled as a resistor  $\rightarrow$

$V_{IN} = 0 \text{ V}$

 Pull-down network is modeled as an open switch  $\rightarrow$



# Output Capacitance of a Logic Gate


- The output capacitance of a logic gate is comprised of several components:

“intrinsic capacitance”

- pn-junction and gate-drain capacitance
  - both NMOS and PMOS transistors

“extrinsic capacitance”

- capacitance of connecting wires
- input capacitances of the fan-out gates

 

**Figure 5.14** The Miller effect—A capacitor experiencing identical but opposite voltage swings at both its terminals can be replaced by a capacitor to ground, whose value is two times the original value.

# Minimizing Propagation Delay


---

- A fast gate is built by
  - 1. Keeping the output capacitance  $C_L$  small**
    - Minimize the area of drain pn junctions.
    - Lay out devices to minimize interconnect capacitance.
    - Avoid large fan-out.
  - 2. Decreasing the equivalent resistance of the transistors**
    - Decrease  $L$
    - Increase  $W$ 
      - ... but this increases pn junction area and hence  $C_L$
  - 3. Increasing  $V_{DD}$** 
    - trade-off with power consumption & reliability



# Transistor Sizing for Performance


---

 

- Widening the transistors reduces resistance, but increases capacitance
- In order to have the on-state resistance of the PMOS transistor match that of the NMOS transistor (e.g. to achieve a symmetric voltage transfer curve), its  $W/L$  ratio must be larger by a factor of  $\sim 3$ . To achieve minimum propagation delay, however, **the optimum factor is  $\sim 2$ .**
 
# CMOS Energy Consumption (Review)

- The energy delivered by the voltage source in charging the load capacitance is  $C_L V_{DD}^2$ 
    - Half of this is stored in  $C_L$ ; the other half is absorbed by the resistance through which  $C_L$  is charged.
- In one complete cycle (charging and discharging), the total energy delivered by the voltage source is  $C_L V_{DD}^2$



# CMOS Power Consumption

---

- The total power consumed by a CMOS circuit is comprised of several components:
  - Dynamic power consumption due to charging and discharging capacitances\*:**

$$P_{dyn} = C_L V_{DD}^2 f_{0 \rightarrow 1} = C_{EFF} V_{DD}^2 f$$

$f_{0 \rightarrow 1}$  = frequency of 0  $\rightarrow$  1 transitions (“switching activity”)

$f$  = clock rate (maximum possible event rate)

**Effective capacitance  $C_{EFF}$**  = average capacitance charged every clock cycle

**\* This is typically by far the dominant component!**

# CMOS Power Consumption (cont'd)

2. Dynamic power consumption due to direct-path currents during switching


$$P_{dp} = C_{sc} V_{DD}^2 f$$

$C_{sc} = t_{sc} I_{peak} / V_{DD}$  is the equivalent capacitance charged every clock cycle due to "short-circuits" between  $V_{DD}$  & GND

(typically <10% of total power consumption)

3. Static power consumption due to transistor leakage and pn-junction leakage

$$P_{stat} = I_{stat} V_{DD}$$

 

# Low-Power Design Techniques

---

## 1. Reduce $V_{DD}$

→ quadratic effect on  $P_{dyn}$

Example: Reducing  $V_{DD}$  from 2.5 V to 1.25 V  
reduces power dissipation by factor of 4

– Lower bound is set by  $V_T$ :  $V_{DD}$  should be  $>2V_T$

## 2. Reduce load capacitance

→ Use minimum-sized transistors whenever possible

## 3. Reduce the switching activity

– involves design considerations at the architecture level (beyond the scope of this class!)

# NAND Gates vs. NOR Gates

---

- In order for a 2-input NAND gate to have the same pull-down delay ( $t_{pHL}$ ) as an inverter, the NMOS devices in the NAND gate must be made twice as wide.
    - This first-order analysis neglects the increase in capacitance which results from widening the transistors.
    - Note: The delay depends on the input signal pattern.
  - In order for a 2-input NOR gate to have the same pull-up delay ( $t_{pLH}$ ) as an inverter, the PMOS devices in the NOR gate must be made twice as wide.
    - Since hole mobility is lower than electron mobility (so that larger  $W/L$  ratios are needed for PMOS devices as compared with NMOS devices), stacking PMOS devices in series (as is done in a NOR gate) should be avoided as much as possible.
- **NAND gates are preferred for implementing logic!**