

Announcements

- Visit the class website to see updated TA section assignments
- Tuesday discussion section moved to Wednesday
- HW #1 due Friday, Jan. 30, in hw box in 240 Cory

<http://www-inst.eecs.berkeley.edu/~ee40>

Lecture #3

OUTLINE


- Circuit element I - V characteristics
- Construction of a circuit model
- Kirchhoff's laws – a closer look

Reading

(Chapter 1, begin Ch. 2)



Current vs. Voltage (I - V) Characteristic

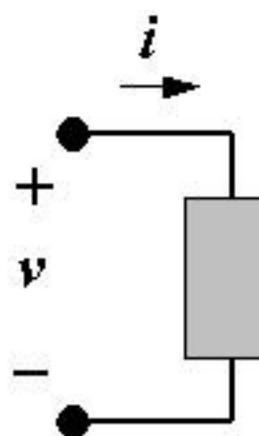- Voltage sources, current sources, and resistors can be described by plotting the current (i) as a function of the voltage (v)





- Later, we will see that the I - V characteristic of any circuit consisting only of sources and resistors is a straight line.

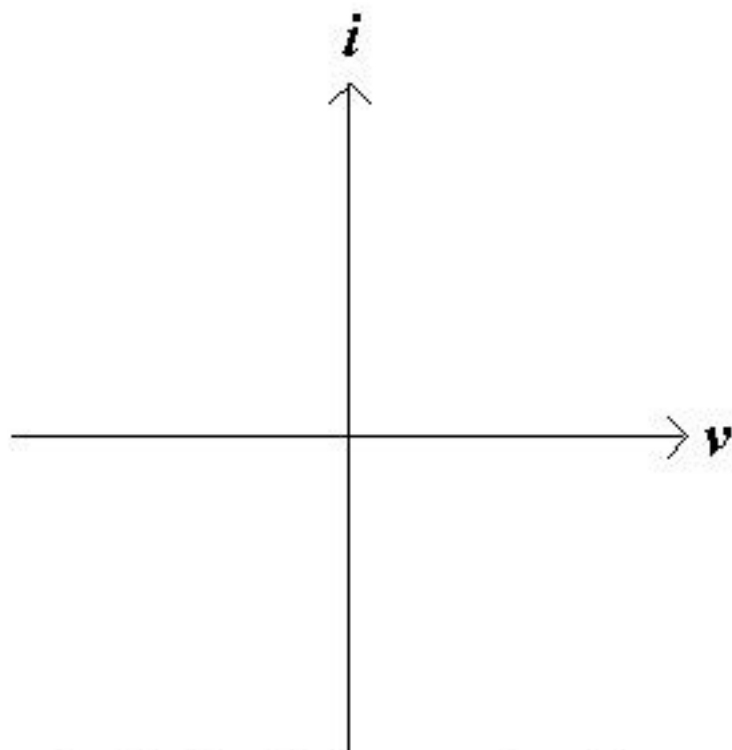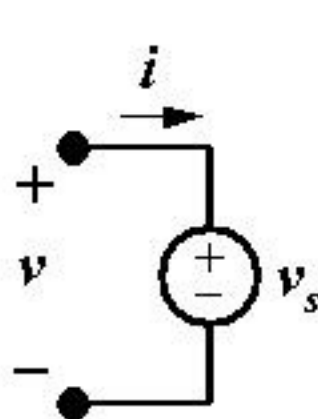***I-V* Characteristic of Ideal Voltage Source**





- 1. Plot the $I-V$ characteristic for $v_s > 0$. For what values of i does the source absorb power? For what values of i does the source release power?**
- 2. Repeat (1) for $v_s < 0$.**
- 3. What is the $I-V$ characteristic for an ideal wire?**

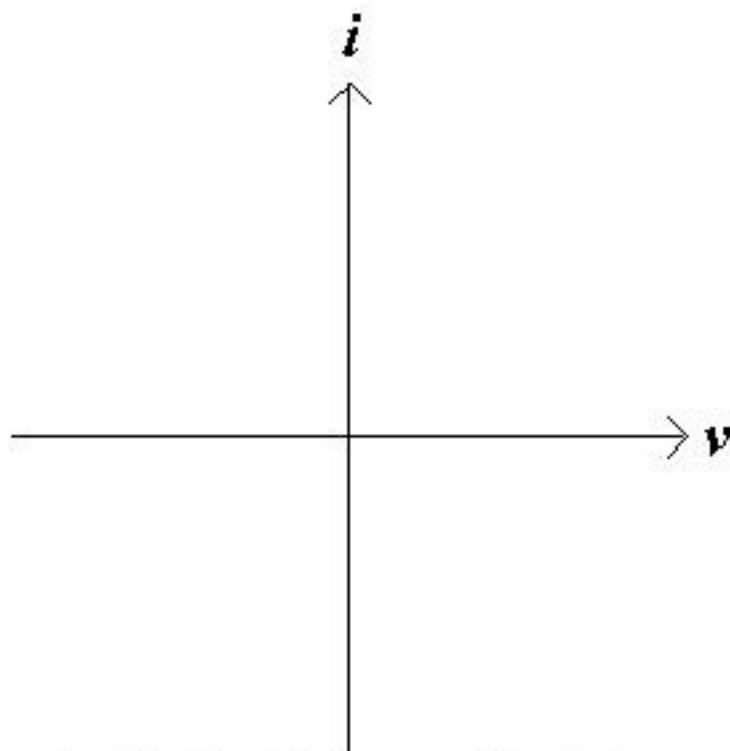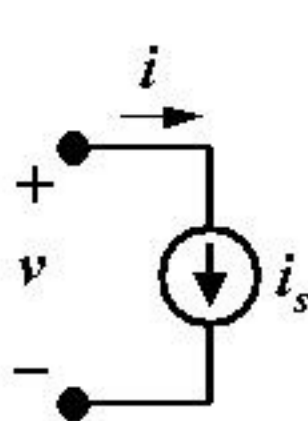***I-V* Characteristic of Ideal Current Source**



- 1. Plot the $I-V$ characteristic for $i_s > 0$. For what values of v does the source absorb power? For what values of v does the source release power?**
- 2. Repeat (1) for $i_s < 0$.**
- 3. What is the $I-V$ characteristic for an open circuit?**

I - V Characteristic of Ideal Resistor

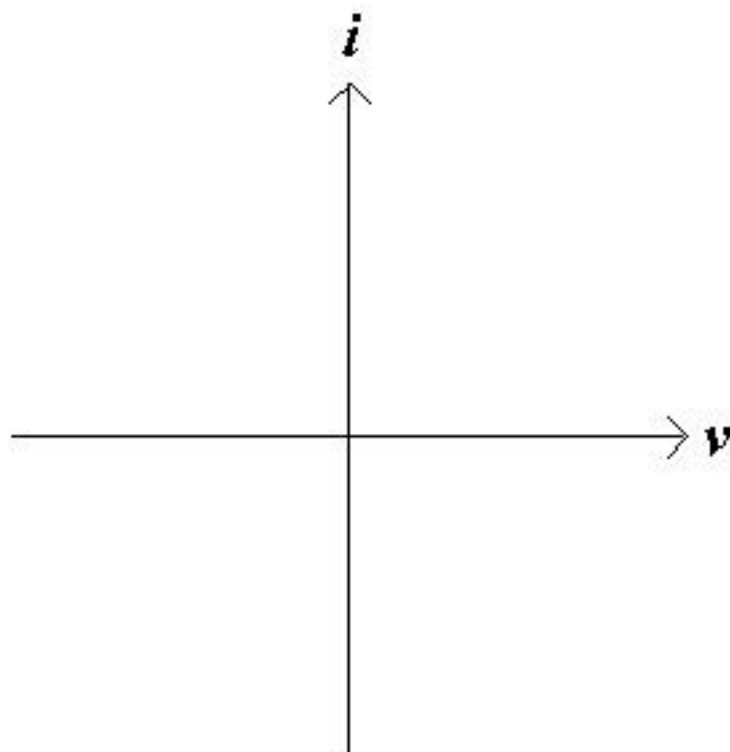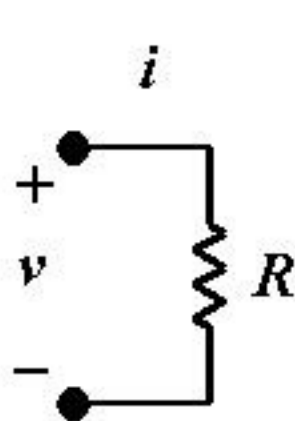

1. Plot the I - V characteristic for $R = 1 \text{ k}\Omega$. What is the slope?

“Lumped Element” Circuit Modeling

(Model = representation of a real system which simplifies analysis)

- In circuit analysis, important characteristics are grouped together in “lumps” (separate circuit elements) connected by perfect conductors (“**wires**”)
- An electrical system can be modeled by an **electric circuit** (combination of paths, each containing 1 or more **circuit elements**) if

$$\lambda = c/f \gg \text{physical dimensions of system}$$

Distance travelled by a particle travelling at the speed of light in one period

Example: $f = 60 \text{ Hz}$


$$\lambda = 3 \times 10^8 \text{ m/s} / 60 = 5 \times 10^6 \text{ m}$$

Construction of a Circuit Model



- The electrical behavior of each physical component is of primary interest.
- We need to account for undesired as well as desired electrical effects.
- Simplifying assumptions should be made wherever reasonable.

Terminology: Nodes and Branches

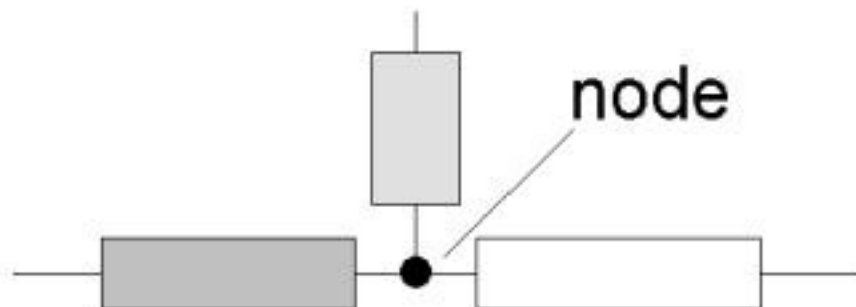Node: A point where two or more circuit elements are connected – **entire wire**




Branch: A path that connects two nodes

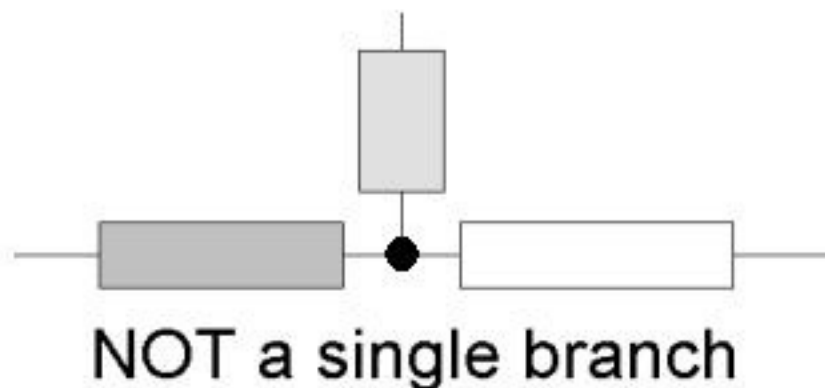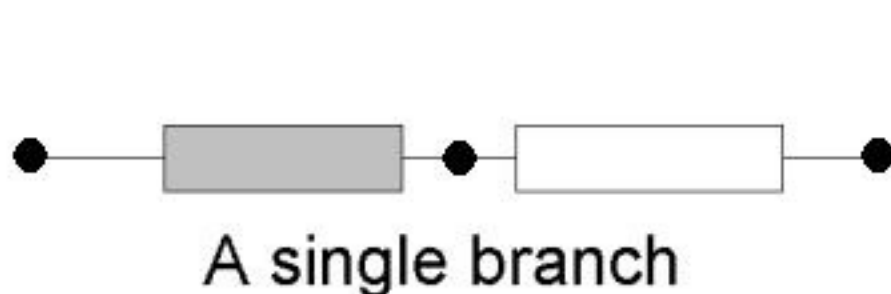

Notation: Node and Branch Voltages


- Use one node as the reference (the “common” or “ground” node) – label it with a symbol
- The voltage drop from node x to the reference node is called the **node voltage** v_x .
- The voltage across a circuit element is defined as the difference between the node voltages at its terminals

Example:

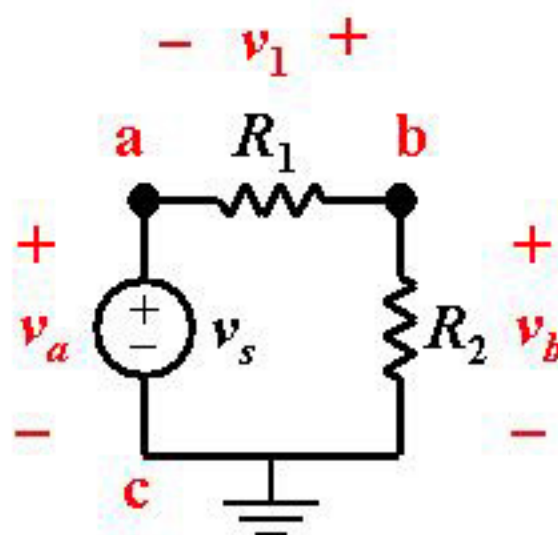

Using Kirchhoff's Current Law (KCL)

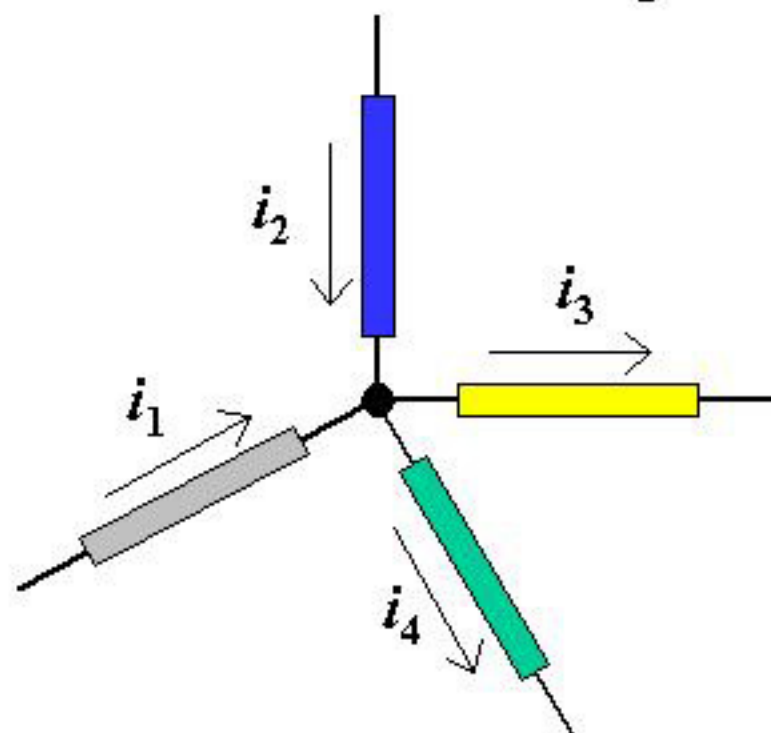Consider a node connecting several branches:



- Use **reference directions** to determine whether currents are “entering” or “leaving” the node – **with no concern about actual current directions**

Formulations of Kirchhoff's Current Law

(Charge stored **in node** is zero.)

Formulation 1:

Sum of currents entering node
= sum of currents leaving node

Formulation 2:

Algebraic sum of currents entering node = 0

- Currents leaving are included with a minus sign.


Formulation 3:

Algebraic sum of currents leaving node = 0

- Currents entering are included with a minus sign.

A Major Implication of KCL

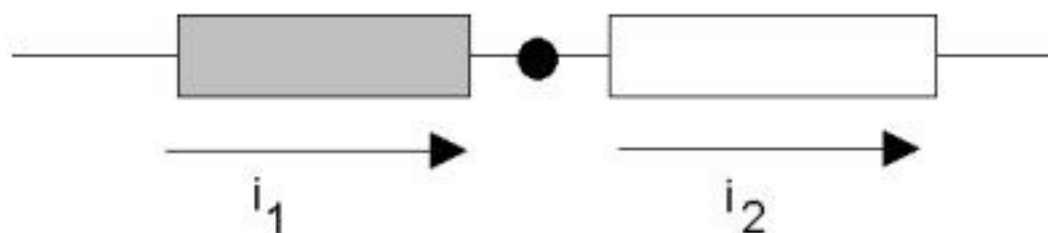
- KCL tells us that **all of the elements in a single branch carry the same current.**
- We say these elements are connected ***in series***.



Current entering node = Current leaving node

$$i_1 = i_2$$

KCL Example

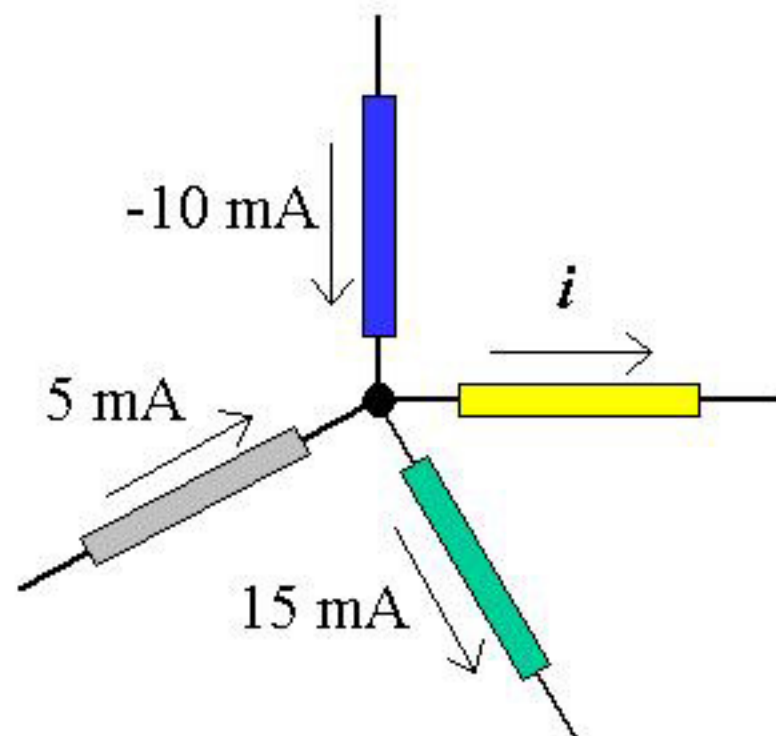

Currents entering the node:

Currents leaving the node:


3 formulations of KCL:

- 1.
- 2.
- 3.



Generalization of KCL

- The sum of currents entering/leaving a **closed surface** is zero. Circuit branches can be inside this surface, *i.e.* the surface can enclose more than one node!

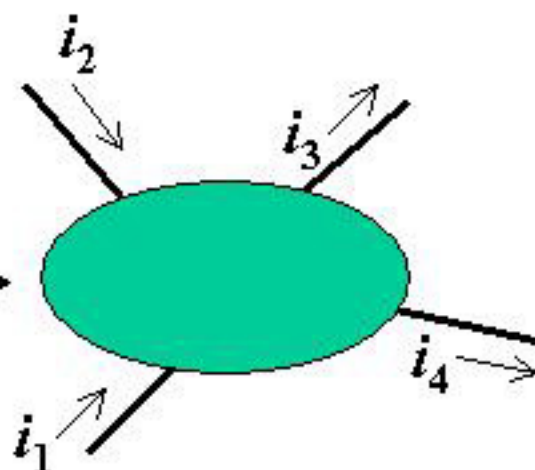This could be a big chunk of a circuit, e.g. a “black box”





Generalized KCL Examples

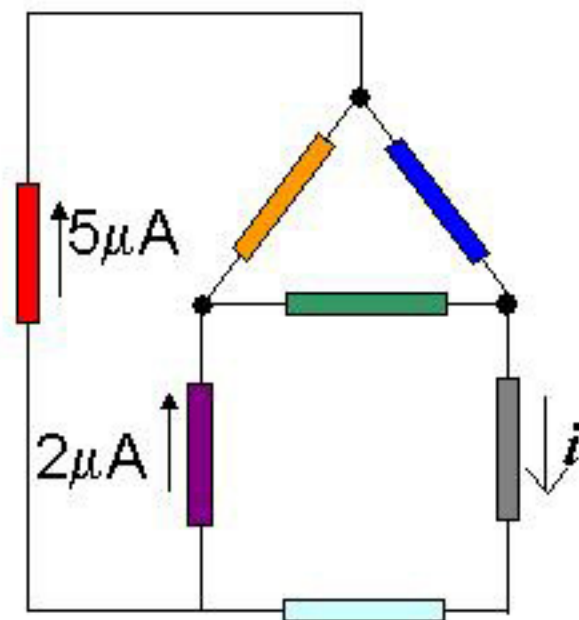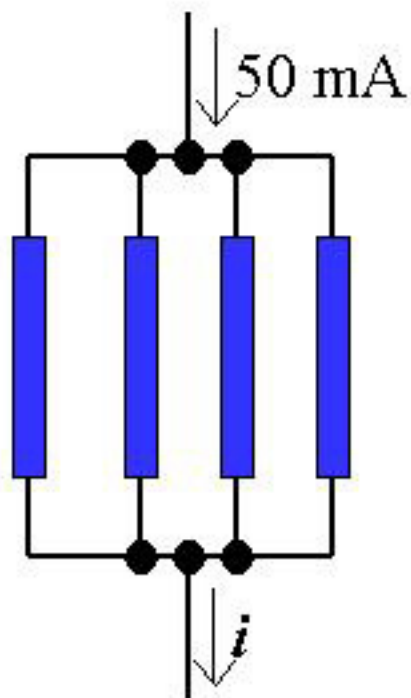

Using Kirchhoff's Voltage Law (KVL)

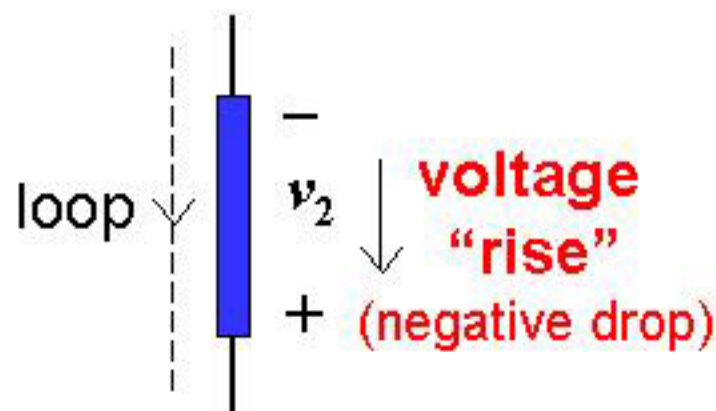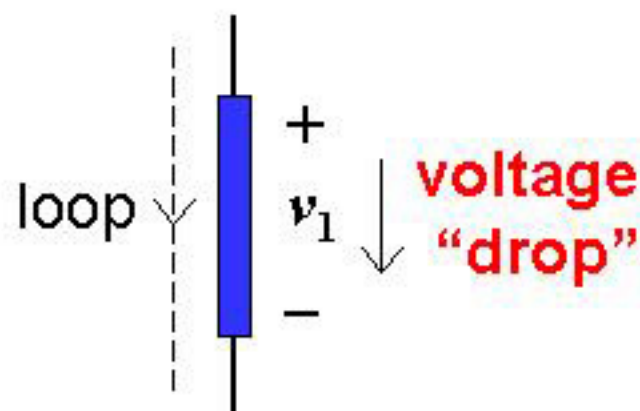Consider a branch which forms part of a loop:



- Use **reference polarities** to determine whether a voltage is dropped – **with no concern about actual voltage polarities**

Formulations of Kirchhoff's Voltage Law

(Conservation of energy)

Formulation 1:

Sum of voltage drops around loop
= sum of voltage rises around loop

Formulation 2:

Algebraic sum of voltage drops around loop = 0

- Voltage rises are included with a minus sign.

(Handy trick: Look at the first sign you encounter on each element when tracing the loop.)


Formulation 3:

Algebraic sum of voltage rises around loop = 0

- Voltage drops are included with a minus sign.

A Major Implication of KVL

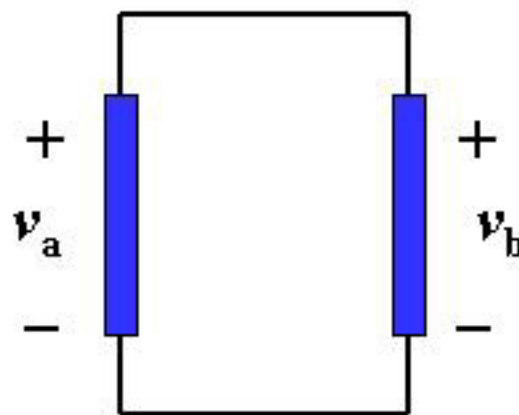- KVL tells us that **any set of elements which are connected at both ends carry the same voltage.**
- We say these elements are connected **in parallel.**




Applying KVL in the clockwise direction, starting at the top:

$$v_b - v_a = 0 \quad \rightarrow \quad v_b = v_a$$

KVL Example

Three closed paths:

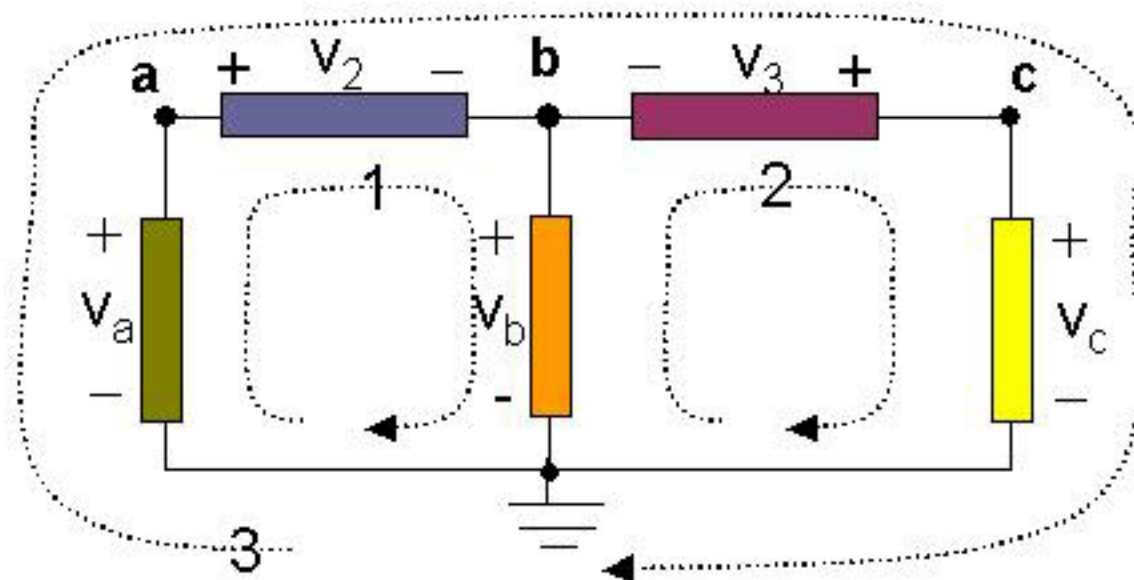

Path 1:


Path 2:

Path 3:

An Underlying Assumption of KVL

- No time-varying magnetic flux through the loop
Otherwise, there would be an induced voltage (Faraday's Law)
- Note: Antennas are designed to “pick up” electromagnetic waves; “regular circuits” often do so undesirably.

Avoid these loops!

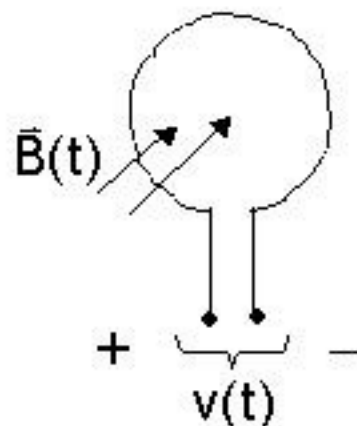


How do we deal with antennas (EECS 117A)?

Include a voltage source as the circuit representation of the induced voltage or “noise”.

(Use a lumped model rather than a distributed (wave) model.)

Resistors in Series

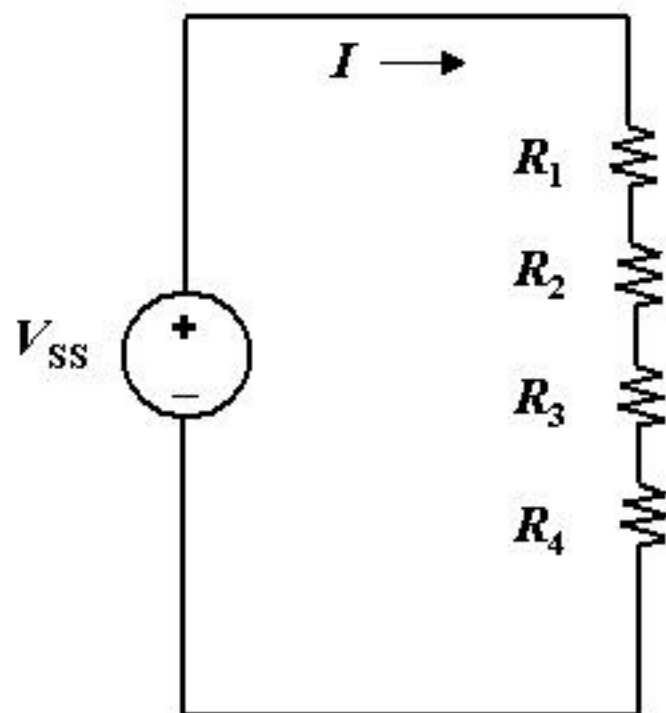
Consider a circuit with multiple resistors connected in series. Find their “equivalent resistance”.



- KCL tells us that the same current (I) flows through every resistor
- KVL tells us


Equivalent resistance of resistors in series is the sum

Voltage Divider

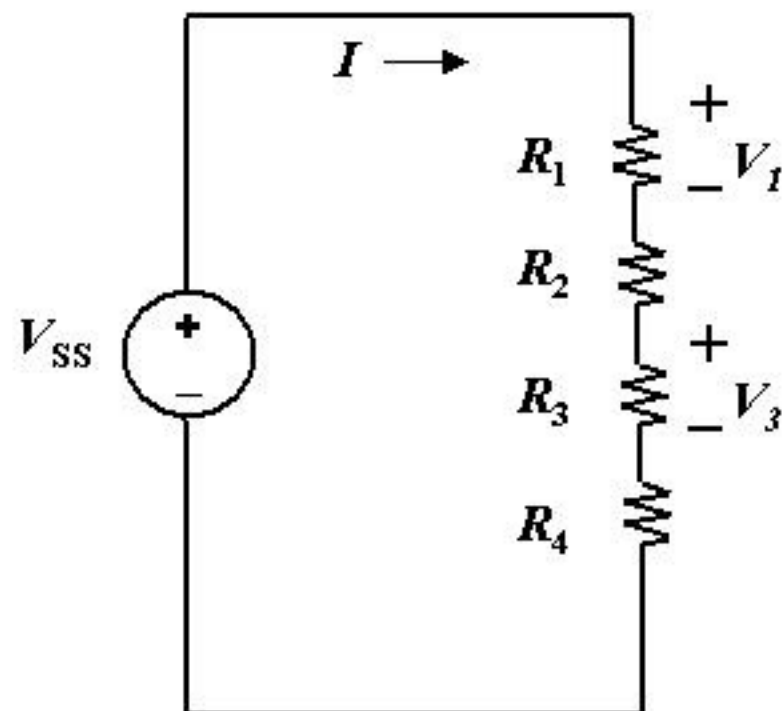


$$I = V_{SS} / (R_1 + R_2 + R_3 + R_4)$$

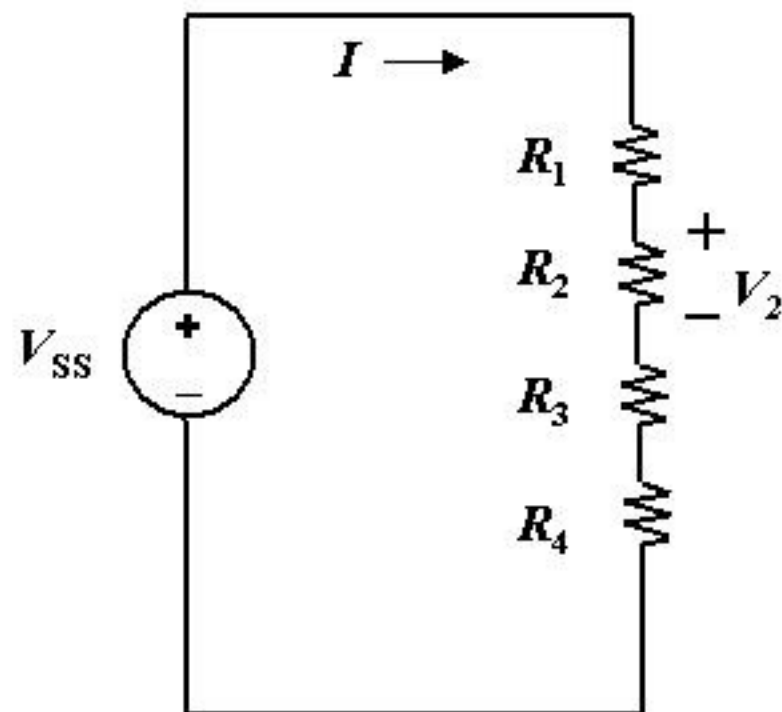When can the Voltage Divider Formula be Used?



$$V_2 = \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

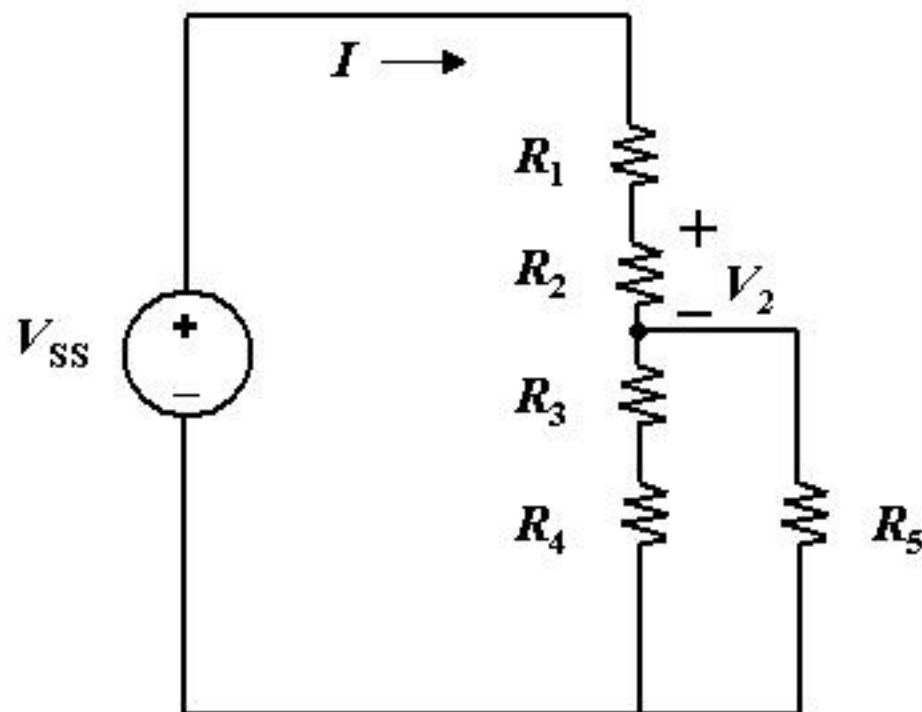Correct, if nothing else
is connected to nodes




$$V_2 \neq \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

because R_5 removes condition
of resistors in series

Resistors in Parallel

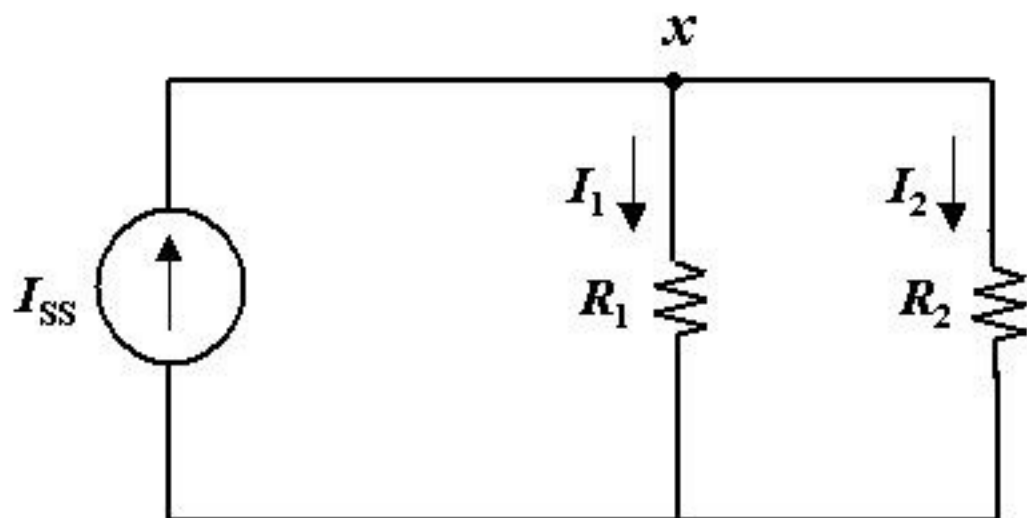Consider a circuit with two resistors connected in parallel. Find their “equivalent resistance”.




- KVL tells us that the same voltage is dropped across each resistor

$$V_x = I_1 R_1 = I_2 R_2$$

- KCL tells us


General Formula for Parallel Resistors

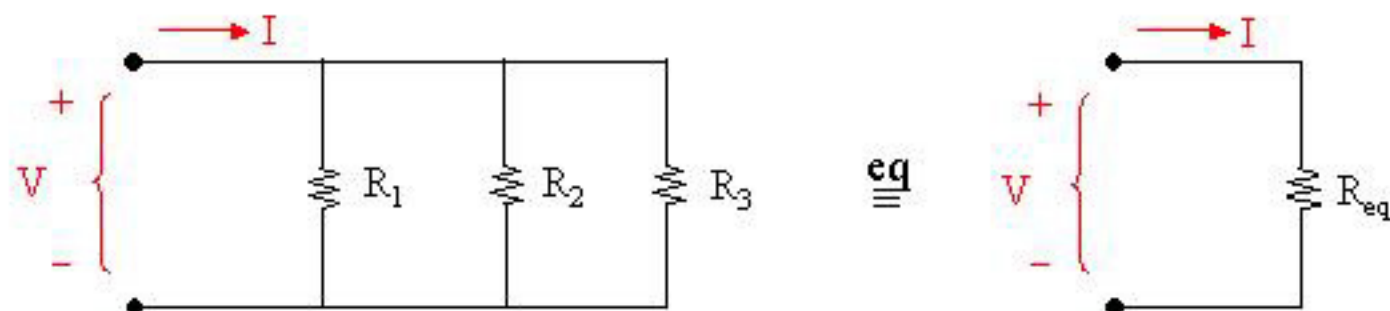What single resistance R_{eq} is equivalent to three resistors in parallel?



Equivalent conductance of resistors in parallel is the sum


Current Divider

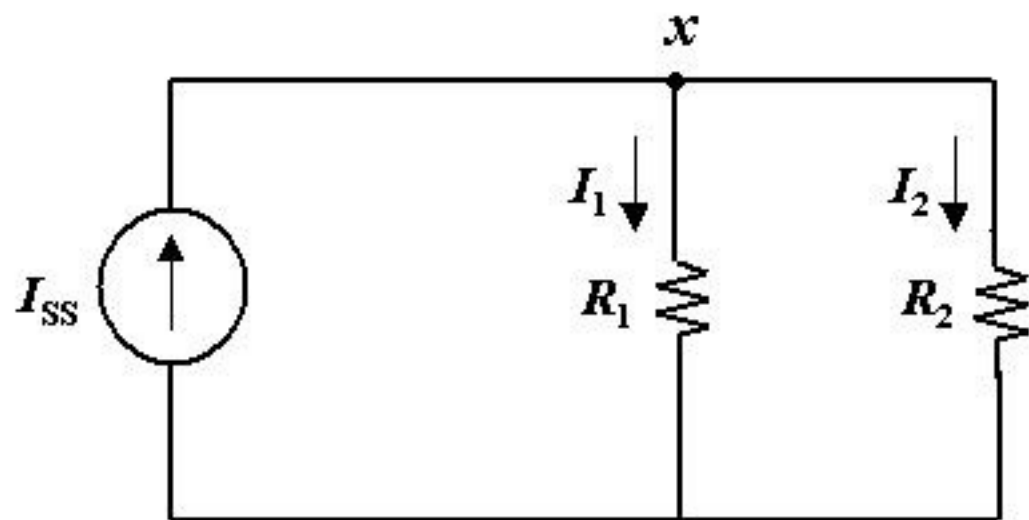

$$V_x = I_1 R_1 = I_{SS} R_{eq}$$

Generalized Current Divider Formula

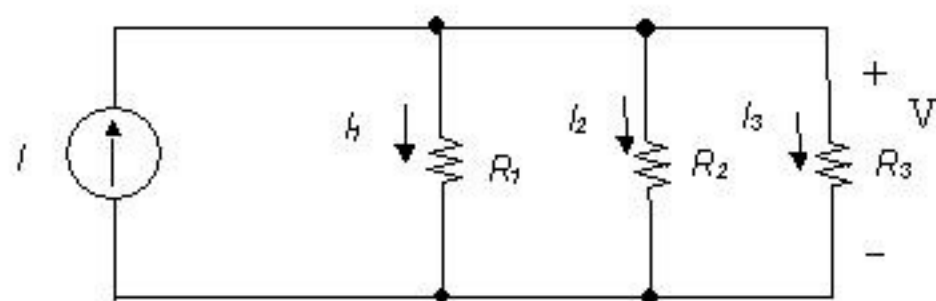Consider a current divider circuit with >2 resistors in parallel:



$$V = \frac{I}{\left(\frac{1}{R_1}\right) + \left(\frac{1}{R_2}\right) + \left(\frac{1}{R_3}\right)}$$

$$I_3 = \frac{V}{R_3} = I \left[\frac{1/R_3}{1/R_1 + 1/R_2 + 1/R_3} \right]$$

Summary

- An **ideal voltage source** maintains a prescribed voltage regardless of the current in the device.
- An **ideal current source** maintains a prescribed current regardless of the voltage across the device.
- A **resistor** constrains its voltage and current to be proportional to each other:

$$v = iR \quad (\text{Ohm's law})$$

- **Kirchhoff's current law** states that the algebraic sum of all currents at any node in a circuit equals zero.
- **Kirchhoff's voltage law** states that the algebraic sum of all voltages around any closed path in a circuit equals zero.

Summary (cont'd)

- Resistors in Series – Voltage Divider
- Conductances in Parallel – Current Divider