

# Lecture #7

---

## OUTLINE

- Thevenin/Norton Eq. Cont'd
- Max power transfer theorem
- The operational amplifier ("op amp")
- Feedback
- Comparator circuits
- Ideal op amp
- Unity-gain voltage follower circuit

## Reading

Complete Ch. 2, Begin Ch. 14, Look at Ch. 11


# The Operational Amplifier

---

- The ***operational amplifier*** (“***op amp***”) is a basic building block used in analog circuits.
  - Its behavior is modeled using a dependent source.
  - When combined with resistors, capacitors, and inductors, it can perform various useful functions:
    - **amplification/scaling** of an input signal
    - **sign changing** (inversion) of an input signal
    - **addition** of multiple input signals
    - **subtraction** of one input signal from another
    - **integration** (over time) of an input signal
    - **differentiation** (with respect to time) of an input signal
    - **analog filtering**
    - **nonlinear functions** like exponential, log, sqrt, etc

# Op Amp Circuit Symbol and Terminals

---

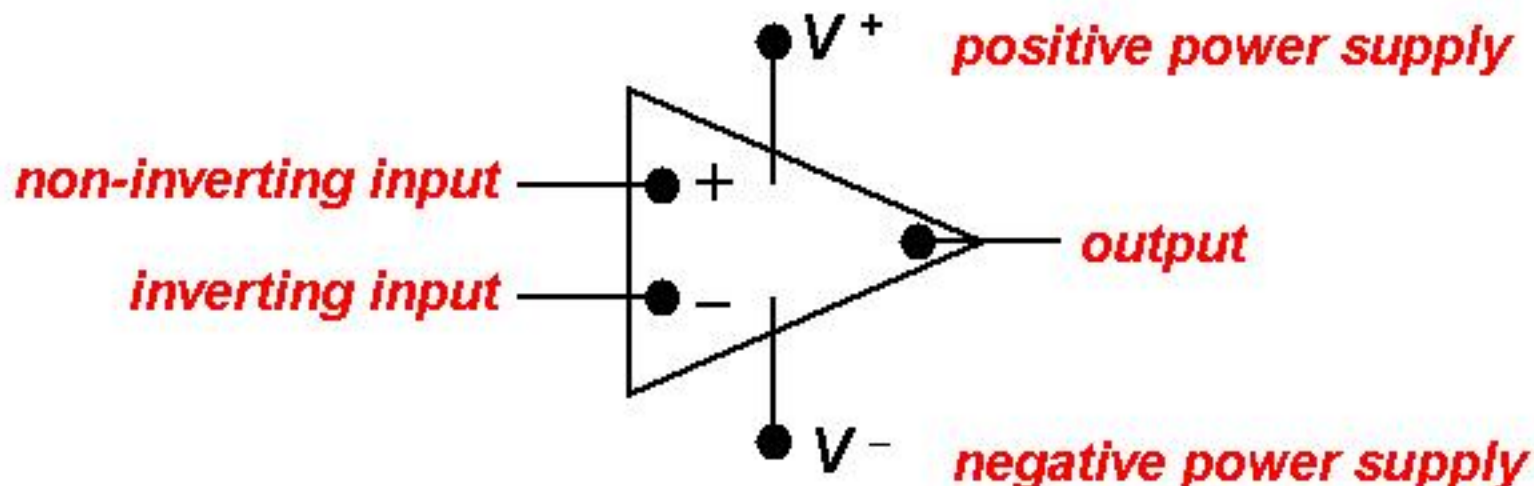


**The output voltage can range from  $V^-$  to  $V^+$**

The positive and negative power supply voltages do not have to be equal in magnitude.

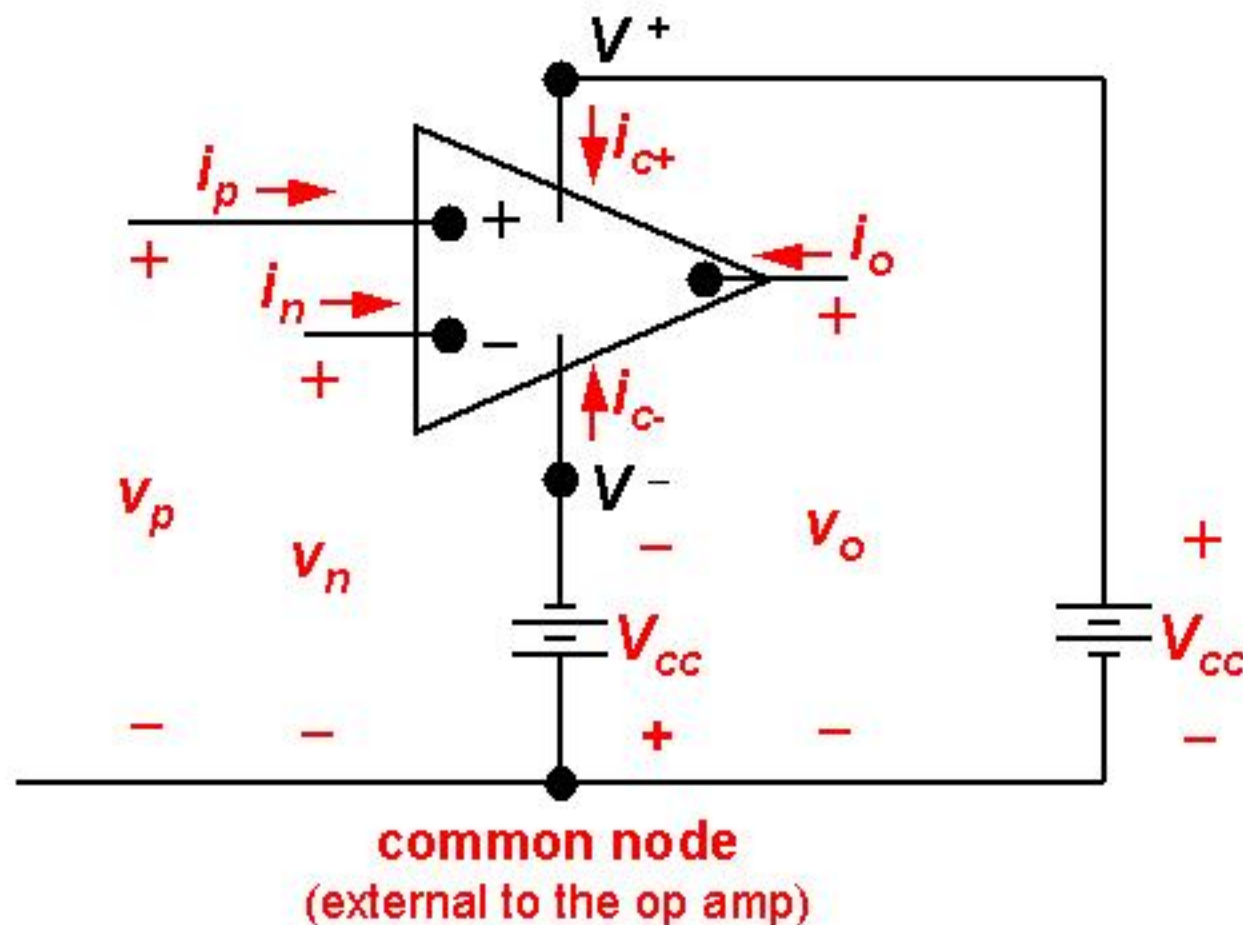
# Op Amp Terminal Voltages and Currents

- All voltages are referenced to a common node.
- Current reference directions are into the op amp.


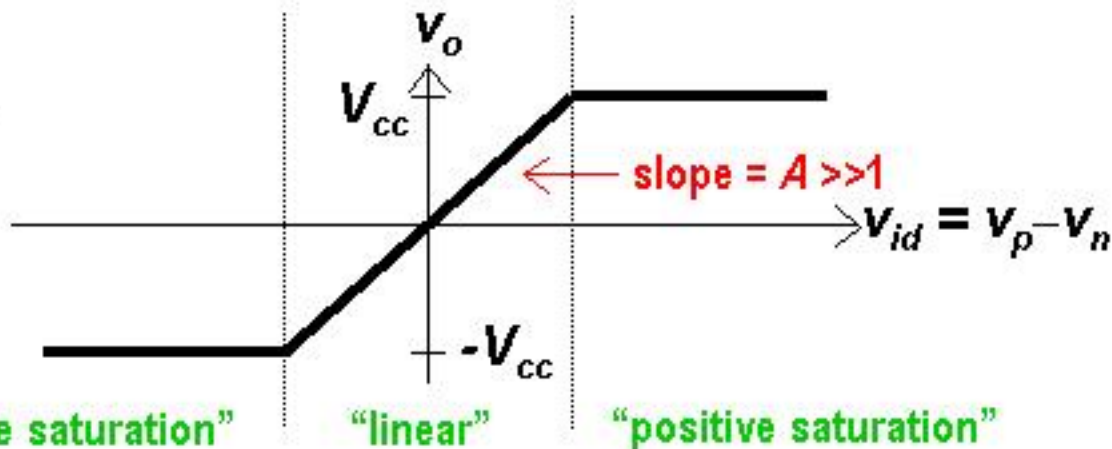
# Op Amp Voltage Transfer Characteristic

The op amp is a differentiating amplifier:



- In the **linear region**,  $v_o = A (v_p - v_n) = A v_{id}$   
where  **$A$  is the open-loop gain**

- Typically,  $V_{cc} \leq 20$  V and  $A > 10^4$   
→ linear range:  $-2$  mV  $\leq v_{id} = (v_p - v_n) \leq 2$  mV

Thus, for an op amp to operate in the linear region,


$$V_p \cong V_n$$

(i.e. there is a “virtual short” between the input terminals.)

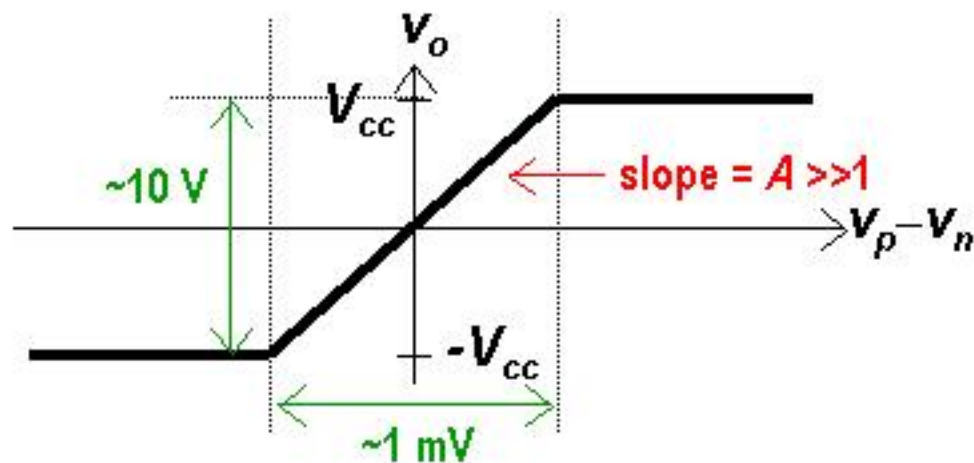
# Achieving a “Virtual Short”

- Recall the voltage transfer characteristic of an op amp:

Plotted using different scales  
for  $v_o$  and  $v_p - v_n$



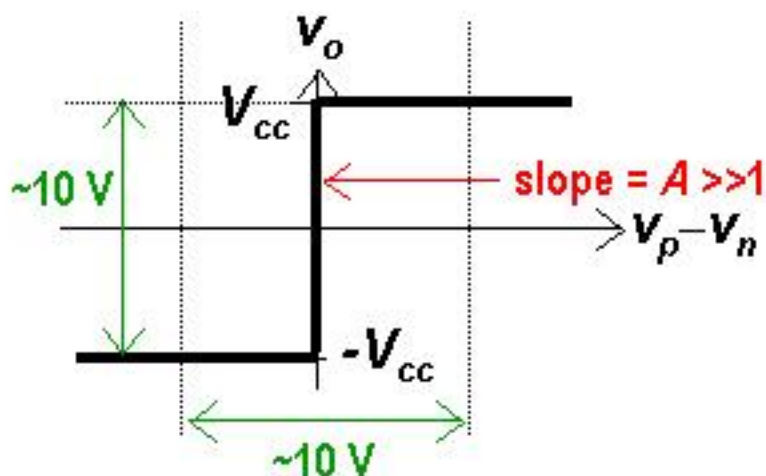Plotted using similar scales  
for  $v_o$  and  $v_p - v_n$



**Q:** How does a circuit maintain a virtual short at the input of an op amp, to ensure operation in the linear region?

**A:** By using **negative feedback**. A signal is fed back from the output to the **inverting input terminal**, effecting a **stable** circuit connection. Operation in the **linear region** enforces the virtual short circuit.

# Negative vs. Positive Feedback

---

Familiar examples of negative feedback:

- Thermostat controlling room temperature
  - Driver controlling direction of automobile
  - Pupil diameter adjustment to light intensity
- Fundamentally pushes toward stability**

Familiar examples of positive feedback:



- Microphone “squawk” in sound system
  - Mechanical bi-stability in light switches
- Fundamentally pushes toward instability or bi-stability**

# Op Amp Operation w/o Negative Feedback

## (Comparator Circuits for Analog-to-Digital Signal Conversion)

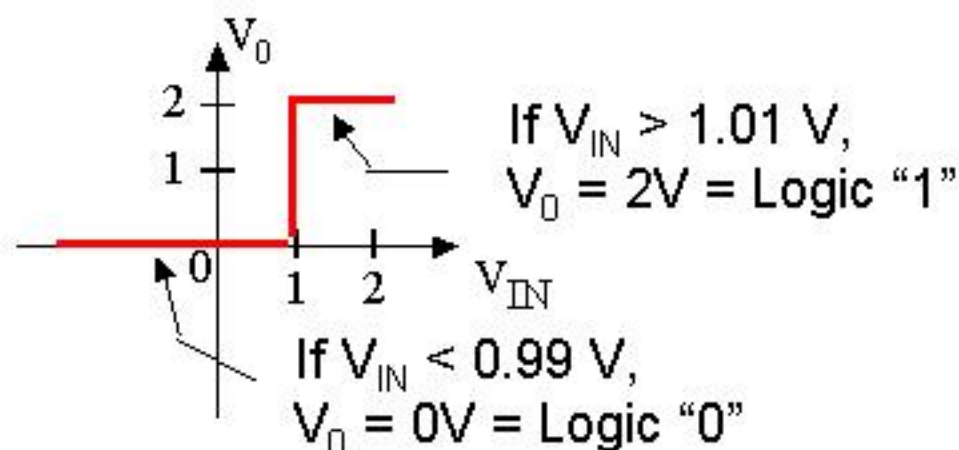
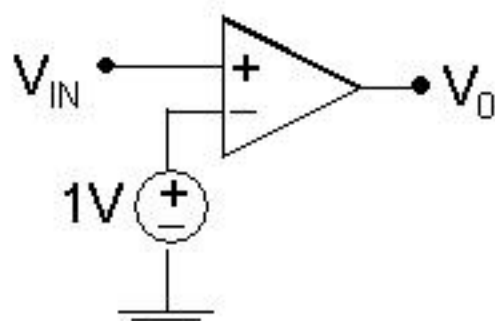
### 1. Simple comparator with 1 Volt threshold:

- $V^-$  is set to 0 Volts (logic "0")
- $V^+$  is set to 2 Volts (logic "1")
- $A = 100$


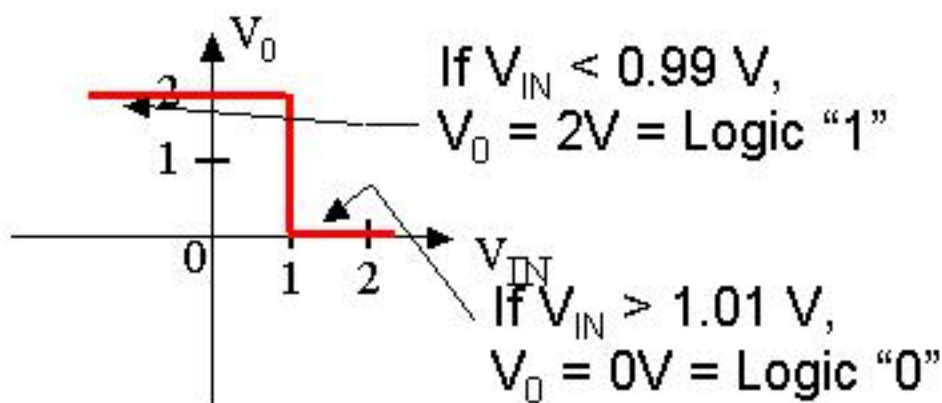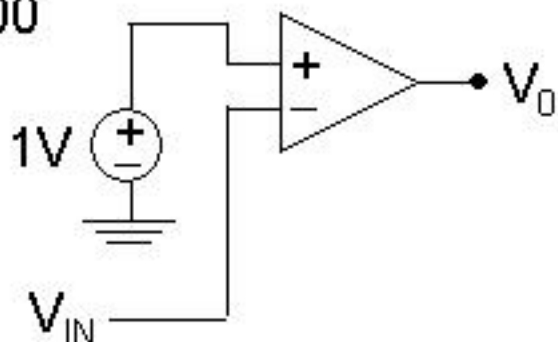
### 2. Simple inverter with 1 Volt threshold:

- $V^-$  is set to 0 Volts (logic "0")
- $V^+$  is set to 2 Volts (logic "1")
- $A = 100$





# Op Amp Circuits with Negative Feedback

---

**Q:** How do we know whether an op amp is operating in the linear region?


**A:** We don't, *a priori*.

- Assume that the op amp is operating in the linear region and solve for  $v_o$  in the op-amp circuit.
  - If the calculated value of  $v_o$  is within the range from  $-V_{cc}$  to  $+V_{cc}$ , then the assumption of linear operation *might* be valid. We also need stability – usually assumed for negative feedback.
  - If the calculated value of  $v_o$  is greater than  $V_{cc}$ , then the assumption of linear operation was invalid, and the op amp output voltage is saturated at  $V_{cc}$ .
  - If the calculated value of  $v_o$  is less than  $-V_{cc}$ , then the assumption of linear operation was invalid, and the op amp output voltage is saturated at  $-V_{cc}$ .

# Op Amp Circuit Model (Linear Region)

$R_i$  is the equivalent resistance "seen" at the input terminals, typically very large ( $>1\text{M}\Omega$ ), so that the input current is usually very small:

$$i_p = -i_n \cong 0$$

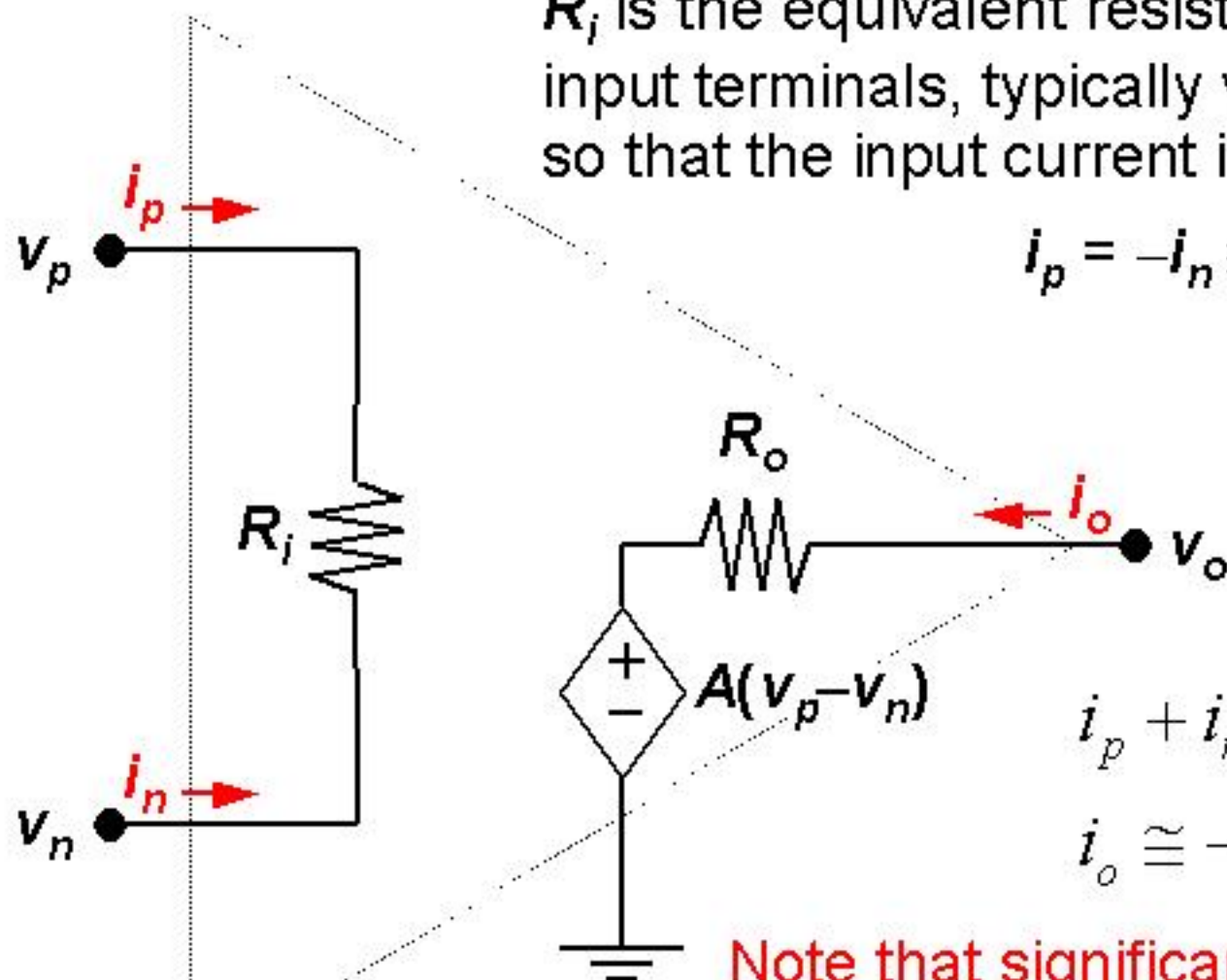

$$i_p + i_n + i_o + i_{c+} + i_{c-} = 0$$


$$i_o \cong -(i_{c+} + i_{c-})$$

Note that significant output current ( $i_o$ ) can flow when  $i_p$  and  $i_n$  are negligible!

# Ideal Op Amp


- Assumptions:
  - $R_i$  is large ( $\geq 10^5 \Omega$ )
  - $A$  is large ( $\geq 10^4$ )
  - $R_o$  is small ( $< 100 \Omega$ )
- Simplified circuit symbol:
  - power-supply terminals and dc power supplies not shown

$$i_p = -i_n = 0$$
$$V_p = V_n$$

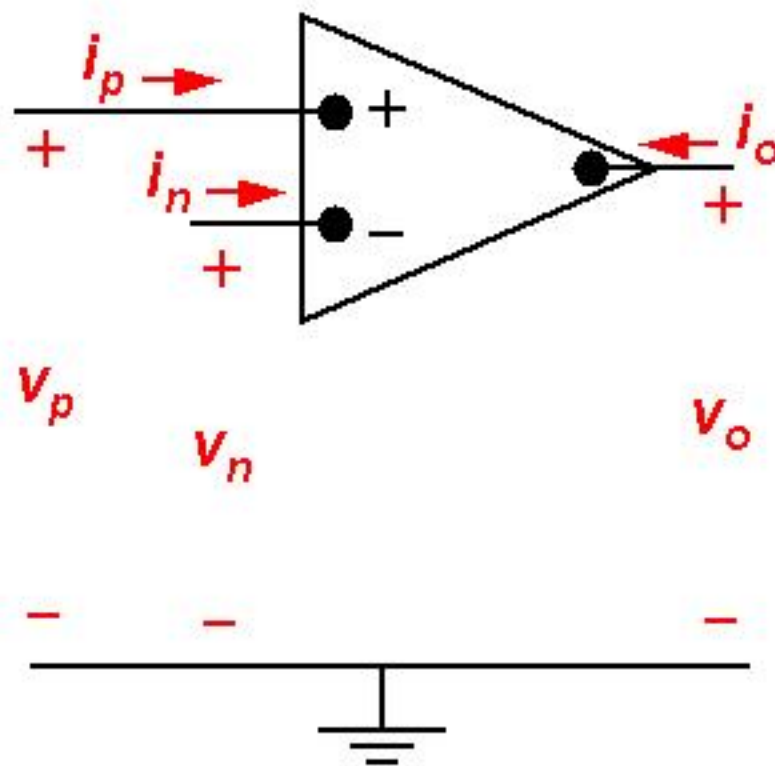


**Note:** The resistances used in an op-amp circuit must be much larger than  $R_o$  and much smaller than  $R_i$  in order for the ideal op amp equations to be accurate.

# Unity-Gain Voltage Follower Circuit

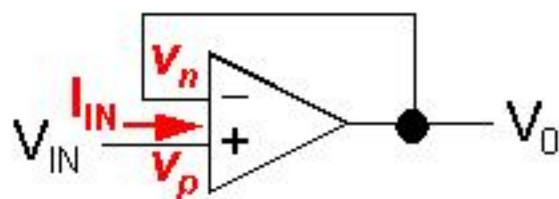

$$V_p = V_n \rightarrow V_0 = V_{IN}$$

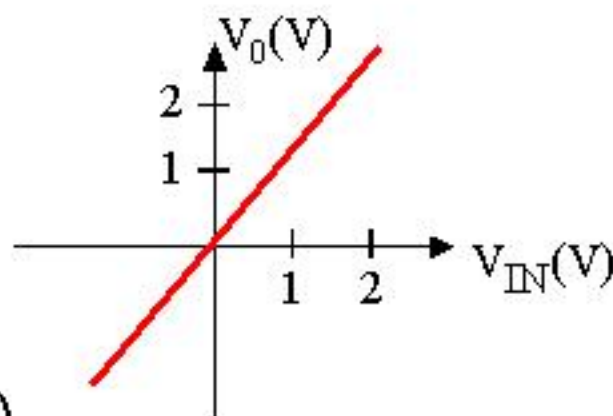( valid as long as  $V^- \leq V_0 \leq V^+$  )



Note that the analysis of this simple (but important) circuit required only one of the ideal op-amp rules.

Q: Why is this circuit important (*i.e.* what is it good for)?

A: A “weak” source can drive a “heavy” load; in other words, the source  $V_{IN}$  only needs to supply a little power (since  $I_{IN} = 0$ ), whereas the output can drive a power-hungry load (with the op-amp providing the power).