

Lecture #8

OUTLINE

- Op-Amp ckts continued: examples
- Inverting amplifier circuit
- Summing amplifier circuit
- Noninverting amplifier circuit
- Differential amplifier circuit



Reading

Chapter 14, also refer to Ch. 11



Review: Negative Feedback

- Negative feedback is used to “linearize” a high-gain differential amplifier.


Without feedback

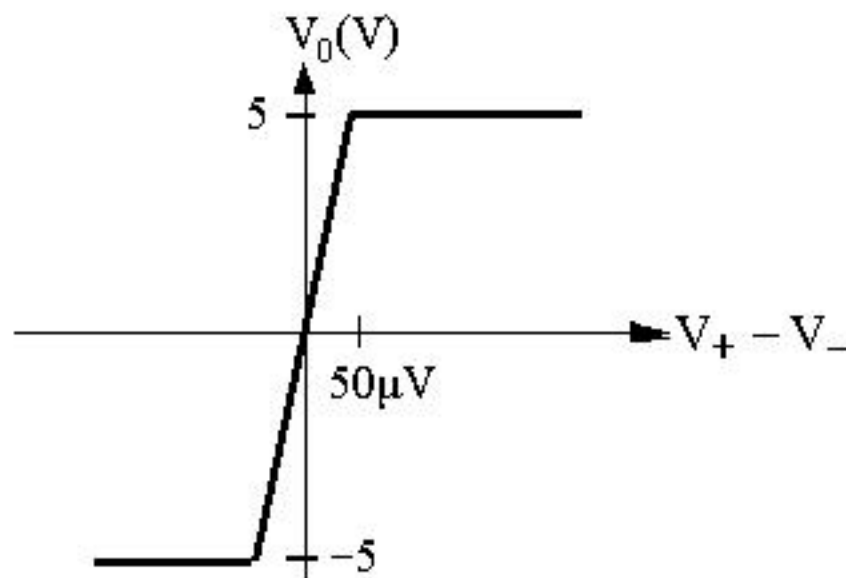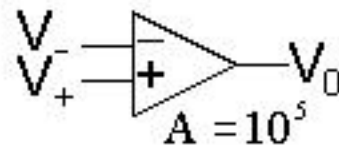

With feedback

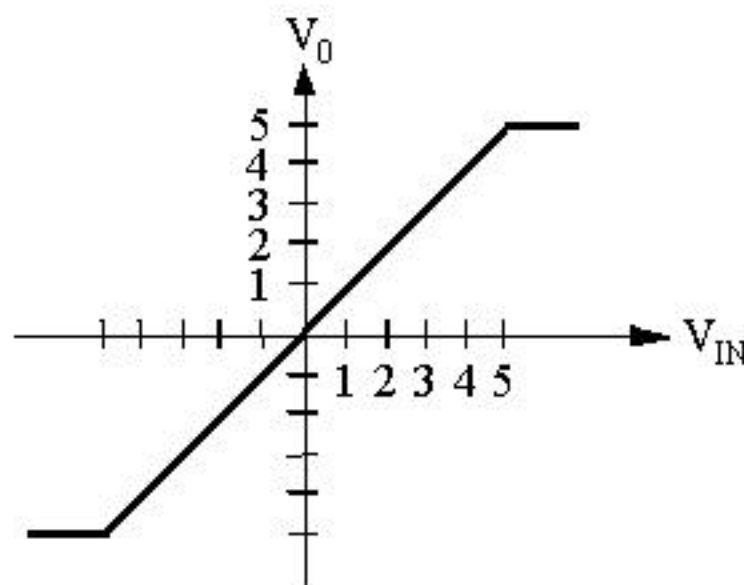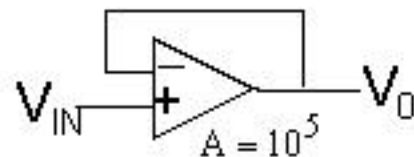

Inverting Amplifier Circuit

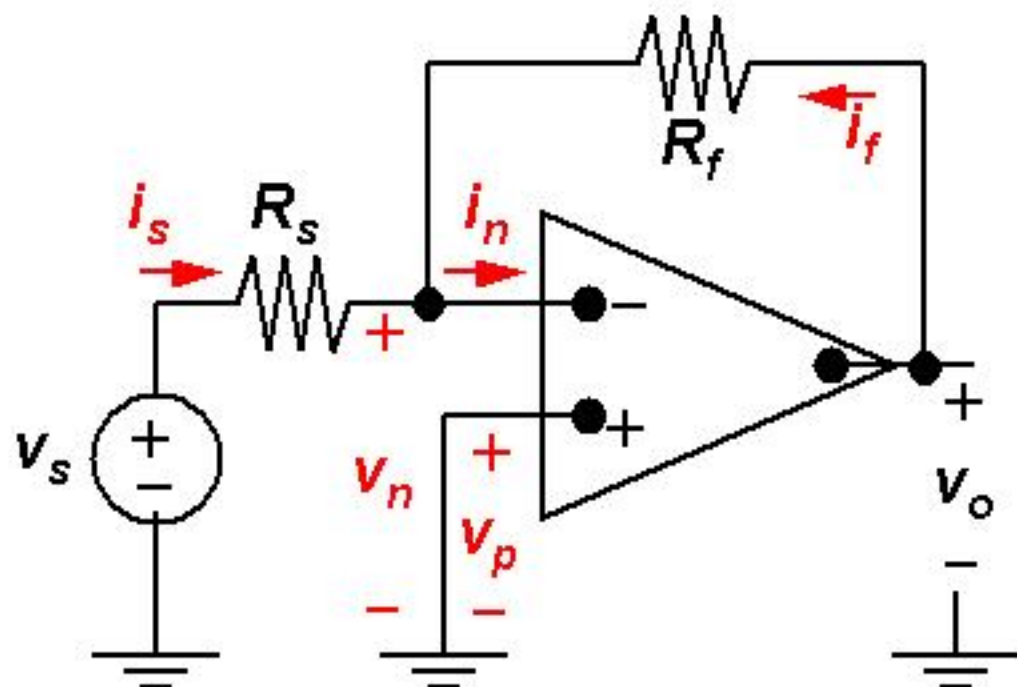

$$v_o = -\frac{R_f}{R_s} v_s$$

$$i_n = 0 \rightarrow i_s = -i_f$$

$$v_p = 0 \rightarrow v_n = 0$$


Analysis using Realistic Op Amp Model

- In the analysis on the previous slide, the op amp was assumed to be ideal, *i.e.*

$$\mathbf{R}_i = \infty; \mathbf{A} = \infty; \mathbf{R}_o = 0$$

- In reality, an op amp has finite \mathbf{R}_i , finite \mathbf{A} , non-zero \mathbf{R}_o , and usually is loaded at its output terminals with a load resistance \mathbf{R}_L .

Summing Amplifier Circuit

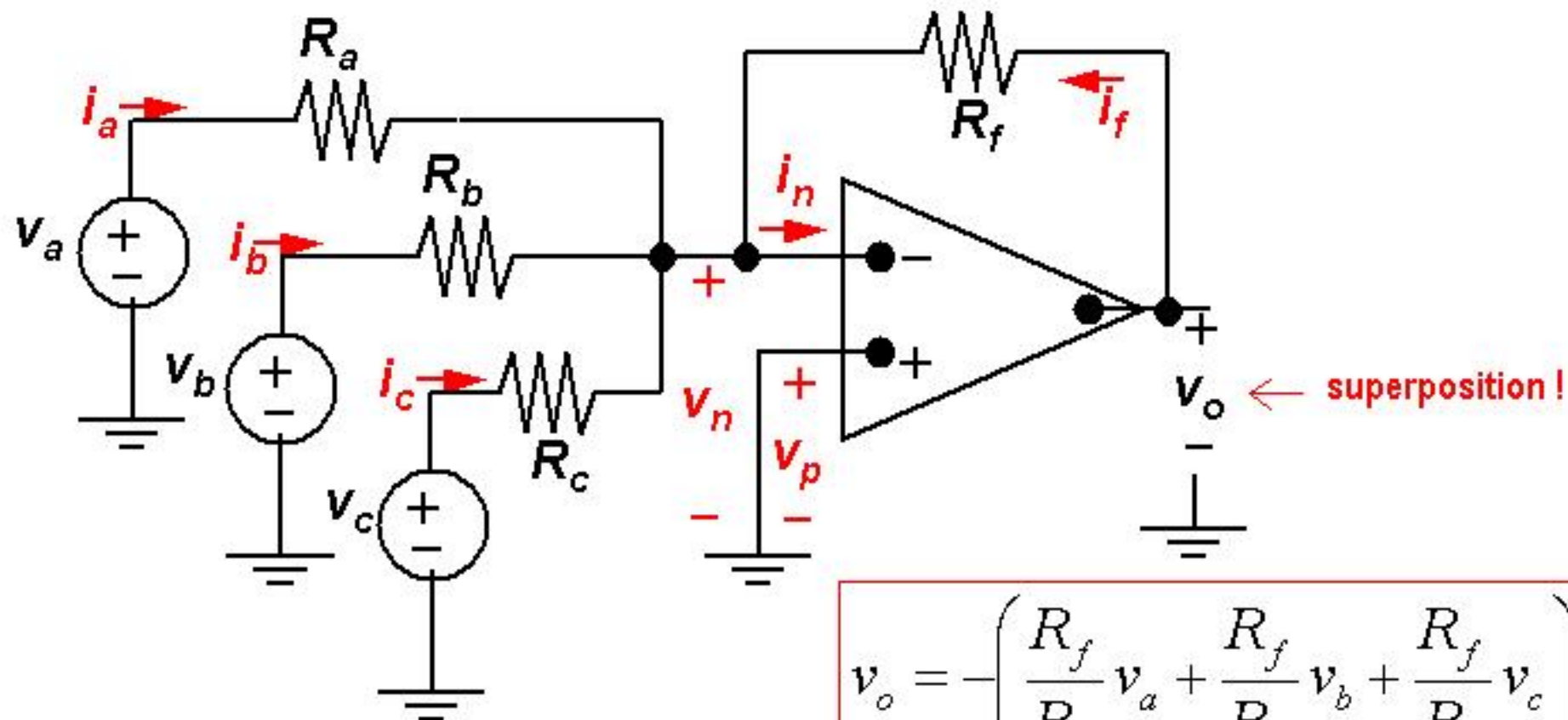

$$v_o = - \left(\frac{R_f}{R_a} v_a + \frac{R_f}{R_b} v_b + \frac{R_f}{R_c} v_c \right)$$


$$i_n = 0 \rightarrow i_a + i_b + i_c = -i_f$$

$$v_p = 0 \rightarrow v_n = 0$$

Application: Digital-to-Analog Conversion

A DAC can be used to convert the digital representation of an audio signal into an analog voltage that is then used to drive speakers -- so that you can hear it!

“Weighted-adder D/A converter”

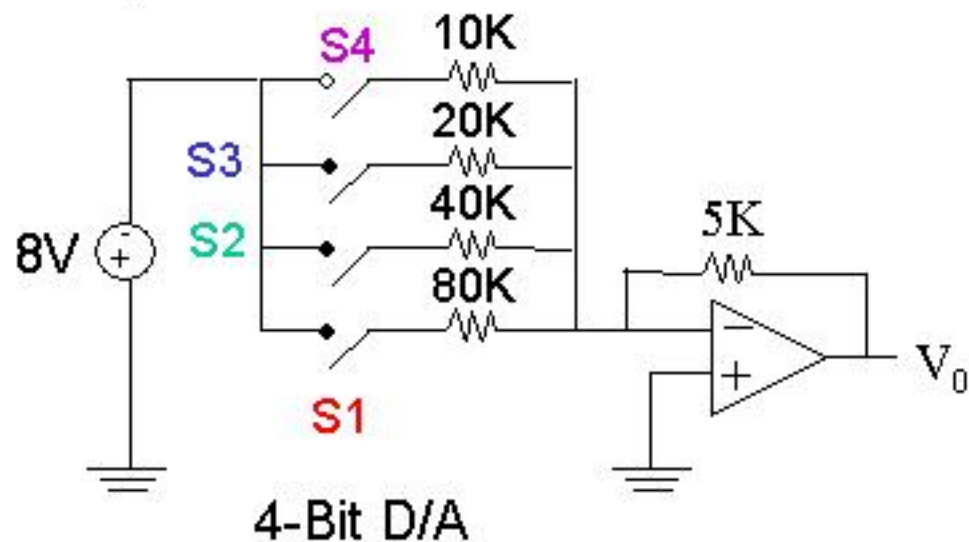

(Transistors are used as electronic switches)


S1 closed if LSB = 1
 S2 " if next bit = 1
 S3 " if " " = 1
 S4 " if MSB = 1

Binary number	Analog output (volts)
---------------	-----------------------


0 0 0 0	0
0 0 0 1	.5
0 0 1 0	1
0 0 1 1	1.5
0 1 0 0	2
0 1 0 1	2.5
0 1 1 0	3
0 1 1 1	3.5
1 0 0 0	4
1 0 0 1	4.5
1 0 1 0	5
1 0 1 1	5.5
1 1 0 0	6
1 1 0 1	6.5
1 1 1 0	7
1 1 1 1	7.5

↑ ↑
 MSB LSB

Characteristic of 4-Bit DAC

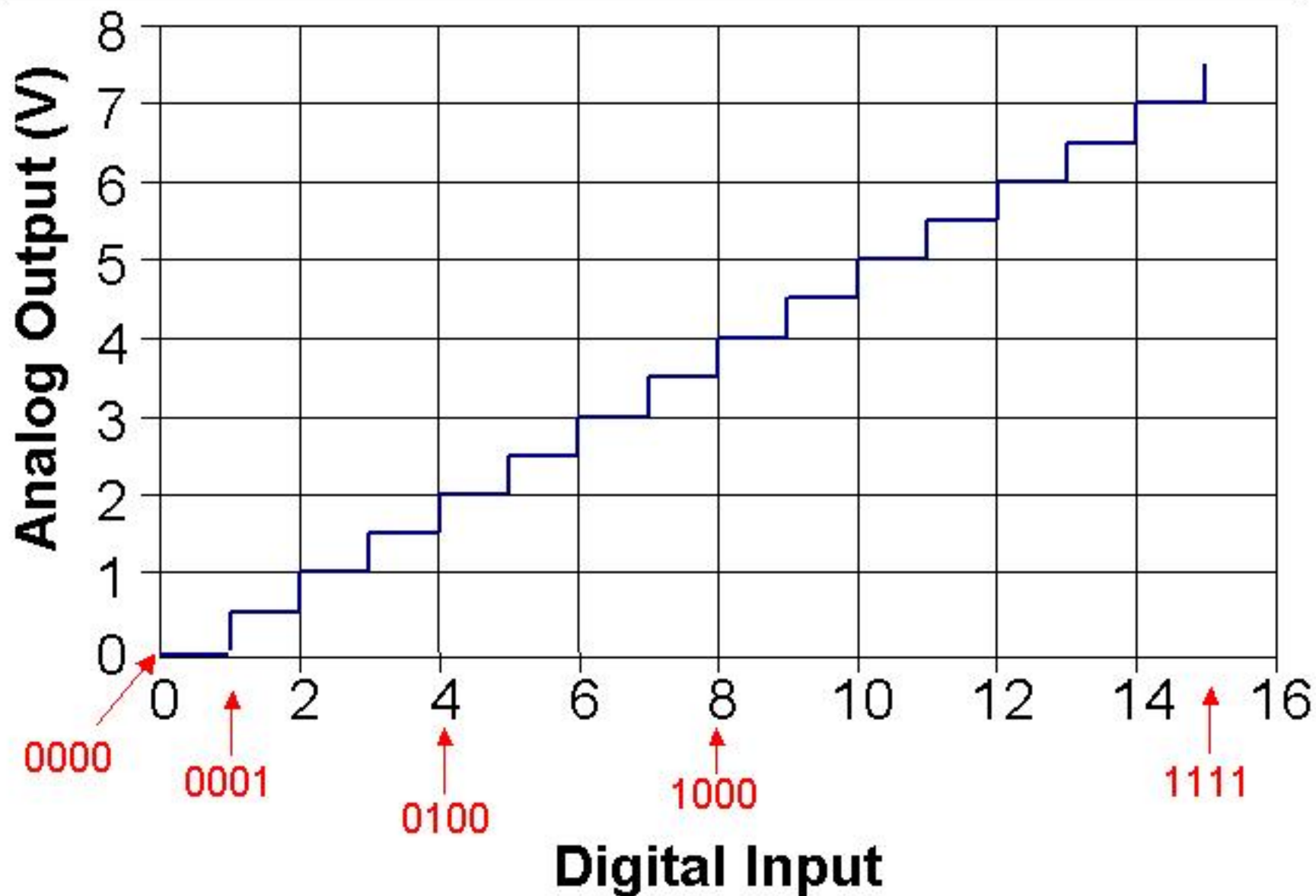

Noninverting Amplifier Circuit

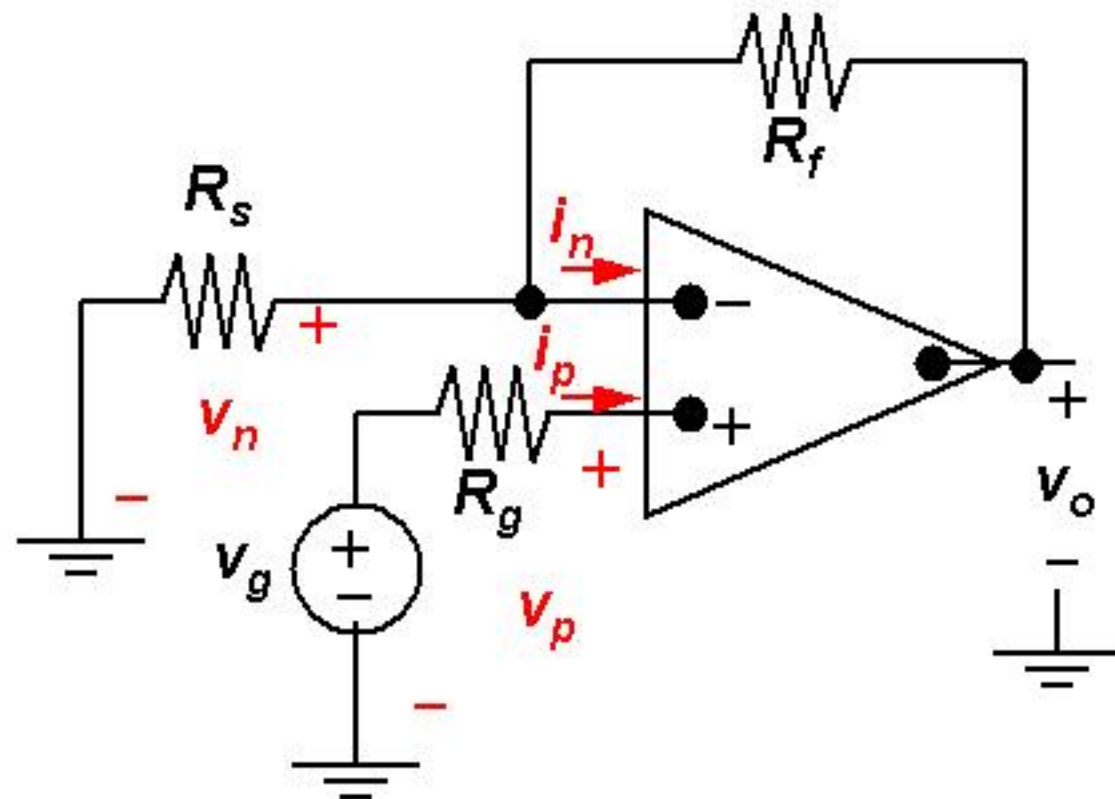


$$v_o = \frac{R_s + R_f}{R_s} v_g$$

$$i_p = 0 \rightarrow v_p = v_g \rightarrow v_n = v_g$$

$$i_n = 0 \rightarrow R_s \text{ \& \ } R_f \text{ form a voltage divider}$$

Differential Amplifier Circuit

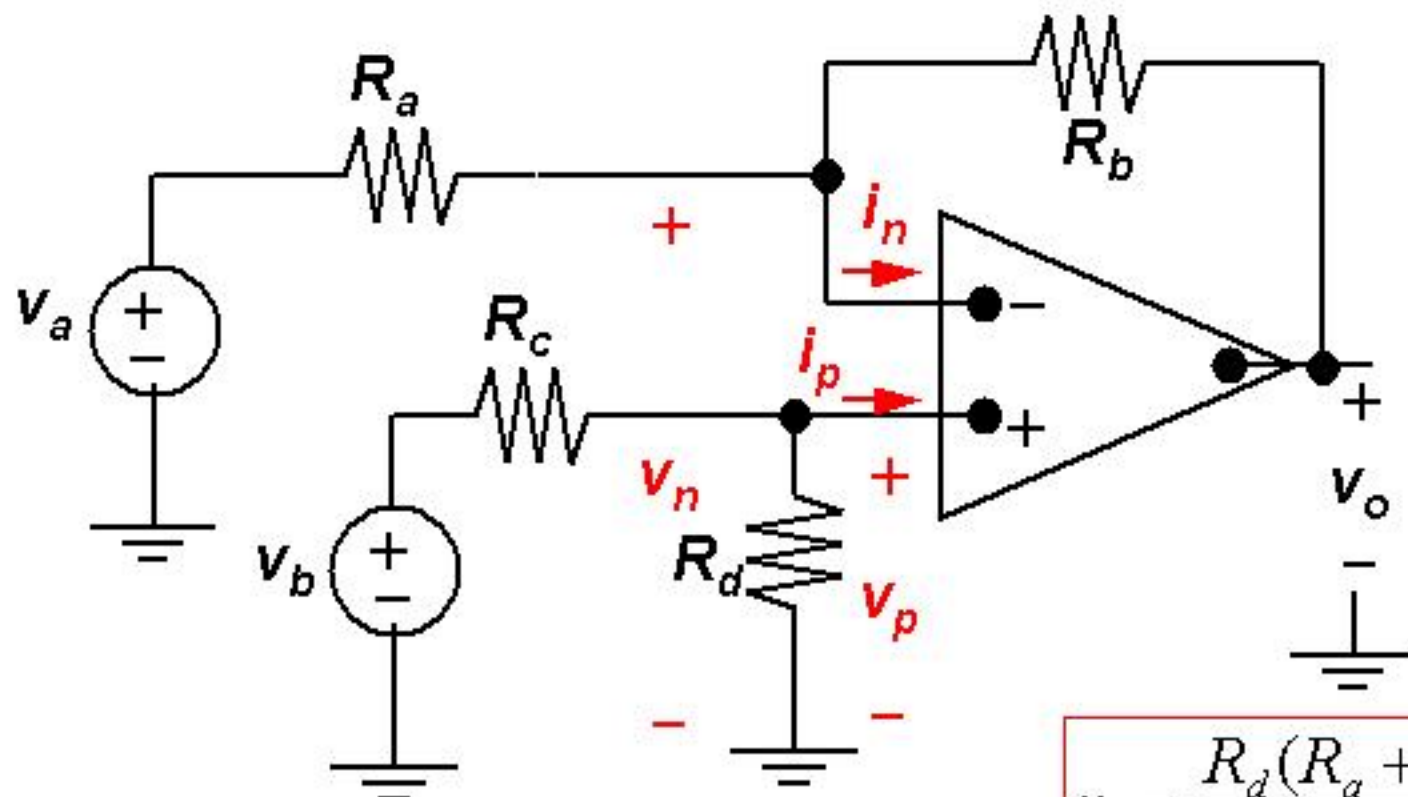

$$v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)} v_b - \frac{R_b}{R_a} v_a$$

$$i_n = 0 \rightarrow \frac{v_n - v_a}{R_a} + \frac{v_n - v_o}{R_b} = 0$$

$$i_p = 0 \rightarrow v_p = \frac{R_d}{R_c + R_d} v_b = v_n$$

$$\text{If } \frac{R_a}{R_b} = \frac{R_c}{R_d}, \text{ then } v_o = \frac{R_b}{R_a} (v_b - v_a)$$

Differential Amplifier – Another Perspective

Redefine the inputs in terms of two other voltages:

1. **differential mode input** $v_{dm} \equiv v_b - v_a$

2. **common mode input** $v_{cm} \equiv (v_a + v_b)/2$

so that

$$v_a = v_{cm} - (v_{dm}/2) \quad \text{and} \quad v_b = v_{cm} + (v_{dm}/2)$$

Then it can be shown that

$$v_o = A_{cm} v_{cm} + A_{dm} v_{dm}$$

where $A_{cm} = \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)}$ and $A_{dm} = \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2R_a (R_c + R_d)}$

“common mode gain”

“differential mode gain”

Differential Amplifier (cont'd)


$$\text{If } \frac{R_a}{R_b} = \frac{R_c}{R_d}, \text{ then } v_{cm} = 0 \text{ and } v_{dm} = \frac{R_b}{R_a}$$

- An ideal differential amplifier amplifies only the differential mode portion of the input voltage, and eliminates the common mode portion.
 - provides immunity to noise (common to both inputs)
- If the resistors are not perfectly matched, the **common mode rejection ratio** (CMRR) is finite:

$$CMRR \equiv \left| \frac{A_{dm}}{A_{cm}} \right| \approx \frac{1 + R_b / R_a}{\varepsilon} \text{ if } \frac{R_a}{R_b} = (1 - \varepsilon) \frac{R_c}{R_d}$$

Summary

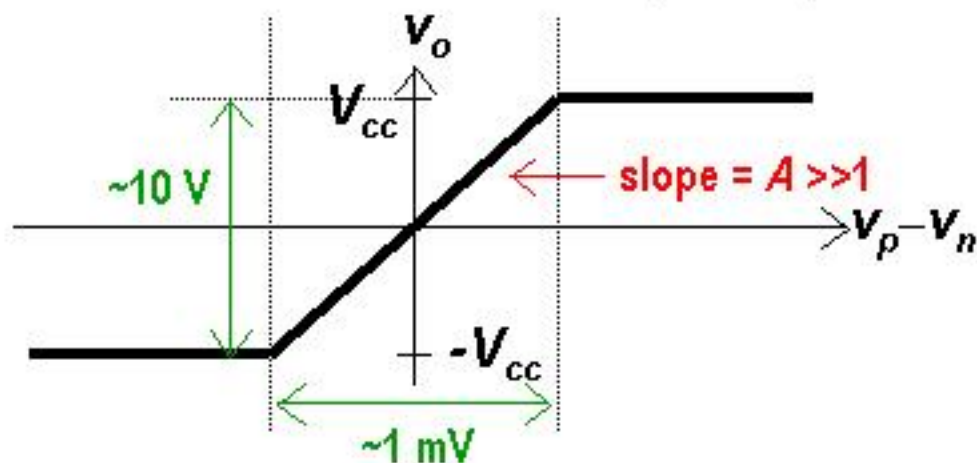- Voltage transfer characteristic of op amp:



- A feedback path between an op amp's output and its inverting input can force the op amp to operate in its linear region, where $v_o = A (v_p - v_n)$
- An **ideal op amp** has infinite input resistance R_i , infinite **open-loop gain** A , and **zero output resistance** R_o . As a result, the input voltages and currents are constrained:

$$v_p = v_n \text{ and } i_p = -i_n = 0$$