

EE43/EE100 — LAB REPORT #4
Op Amps

Name: _____

TA: _____

Section: _____

Part 2: The Voltage Follower

Step 4: Measured v_{in} : _____

v_{out} : Theoretical _____

Measured _____

Part 3: The Inverting Amplifier

Step 6: Measured **R**: _____

v_{out} : Theoretical _____

Measured _____

Gain: _____

Step 7: Measured **R**: _____


v_{out} : Theoretical _____

Measured _____

Gain: _____

Step 8: v_{in} : Measured _____ V_{pp}

v_{out} : Theoretical _____

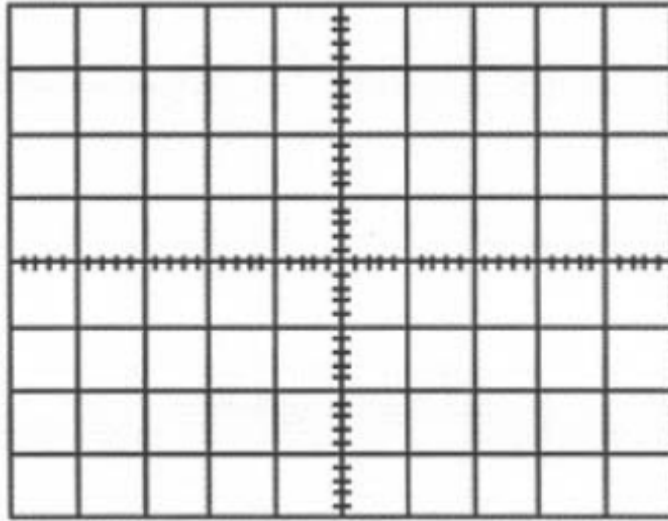

Gain: _____

Part 4: The Non-inverting Amplifier

Step 10: Measured **R**: _____

v_{out}: Theoretical _____

Measured _____

Gain: _____

Step 11: Measured **R**: _____


v_{out}: Theoretical _____

Measured _____

Gain: _____

Step 12: **v_{in}**: Measured _____ **V_{pp}**

v_{out}: Theoretical _____

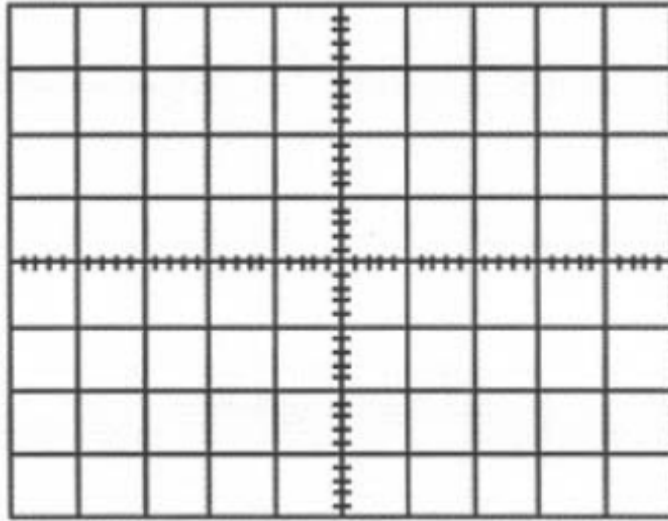

Gain: _____

Part 5: The Summing Amplifier

Step 14:

V_{out} : Theoretical _____

Measured _____

Step 15:

V_{out} : Theoretical _____

Measured _____

Step 16:

V_{out} : Theoretical _____

Measured _____

Part 6: The Non-Ideal Op Amp

Step 18: Measured **R**: _____

V_{in} : Theoretical _____

Measured _____

V_{out} : Theoretical _____

Measured _____

Step 19: Measured **R**: _____

v_{in} : Theoretical _____

Measured _____

v_{out} : Theoretical _____

Measured _____

Reason for difference between theoretical v_{out} and measured v_{out} :

Part 7: The Differential Amplifier

Step 21: v_{out} : Theoretical _____

Step 22: Measured v_{out} :

