

Name: _____
Student ID: _____
Name: _____
Student ID: _____
Section: _____
Date: _____

UNIVERSITY OF CALIFORNIA, BERKELEY
EE40: Introduction to Microelectronic Circuits

Diodes Report

Half Wave Rectifier

2a) Measure V_T when the input is Frequency = 1KHz, $V_{pp} = 5V$, Offset = 0.

2b) What happens when you lower V_{pp} ?

2c) What happens if you use a negative offset?

2d) What happens to the output if you make the input $V_{pp} = 0.5V$ and you increase the offset = 0.5V.

2e) What happens if you lower the frequency of the function generator?

2f) What happens as you vary the resistance on the rheostat?

2g) Do different color LED's have different threshold voltages?

3) Replace the LED with a 1N914 diode and measure the new threshold voltage. Is it different?

Diode Logic

2) $R_s =$

3) OR Gate

A (V)	B (V)	C (V)
0	0	
0	5	
5	0	
5	5	

4) AND Gate

A (V)	B (V)	C (V)
0	0	
0	5	
5	0	
5	5	

5) Chained

A_{OR} (V)	B_{OR} (V)	B_{AND} (V)	C (V)
0	0	0	
0	0	5	
0	5	0	
0	5	5	
5	0	0	
5	0	5	
5	5	0	
5	5	5	

6) Does it still perform normally? Why or why not?