


**EECS 40/42/100, Spring 2007****Prof. Chang-Hasnain****Homework #5**

Due at 6 pm in 240 Cory on Wednesday, 2/28/07

Total Points: 100

- Put (1) your name and (2) **discussion section number** on your homework.
- You need to put down all the derivation steps to obtain full credits of the problems. Numerical answers alone will at best receive low percentage partial credits.
- No late submission will be accepted expect those with prior approval from Prof. Chang-Hasnain.

1. Consider the following circuit:

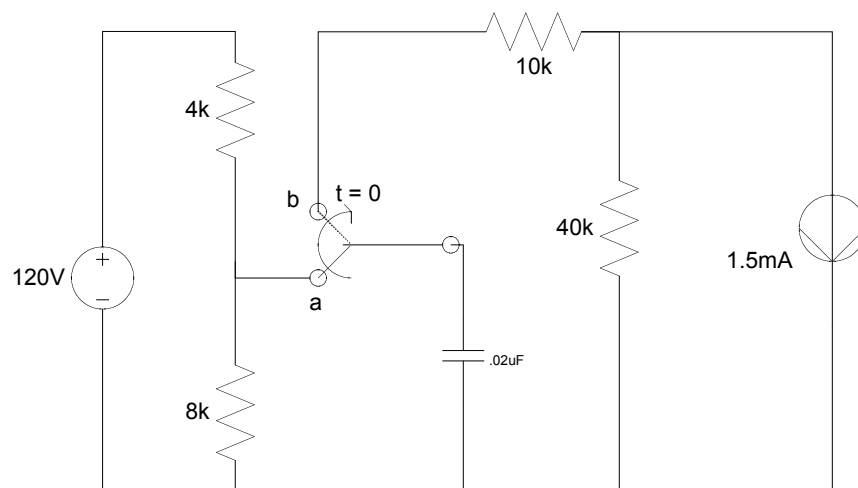

The switch in the circuit shown has been in position a for a long time, At  $t = 0$  the switch is moved to position b. Calculate:

- The initial voltage on the capacitor
- The final voltage on the capacitor
- The time constant for  $t > 0$
- The length of time required for capacitor voltage to reach zero after the switch is moved to position b.

- Hambley, P4.33
- Hambley, P4.35
- Hambley, P4.39
- Hambley, P4.41
- Hambley, P4.48
- Hambley, P5.19
- Hambley, P5.22
- Hambley, P5.24
- Hambley, P5.30