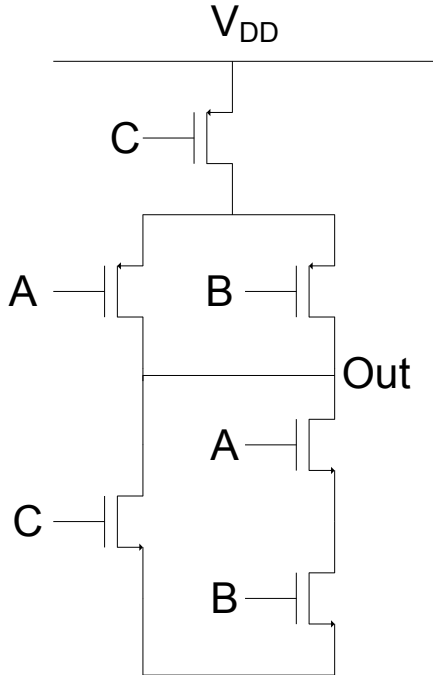


EE40/42/100 Practice MOSFET Problems

(Problems 4 ~ 6 are for EE40 only, though EE42/100 students may want to try to find the Q-point for each of these questions)

1.




What logic function does this CMOS gate perform? (Draw a truth table, and write an expression in sum-of-products form.)

2. Draw a CMOS circuit for the function: $\text{Out} = (AB)' + A'C$


Where X' means the inversion of X .

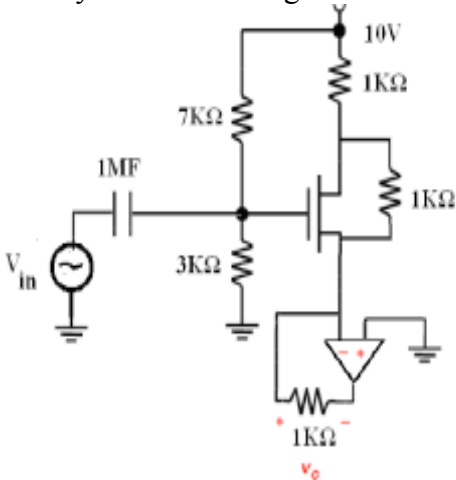3. Analyze the following NMOS circuit. $K = 1\text{mA/V}^2$ and $V_{t0} = 1\text{V}$




a. Using KVL, write the equation of I_{ds} as a function of V_{ds} .

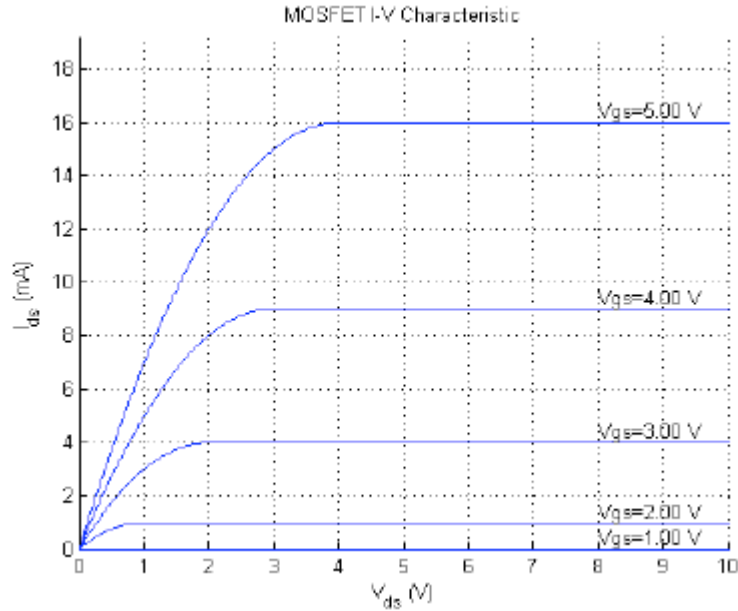b. Draw the load line on the following diagram:



c. Using equations for a NMOS transistor, find V_{GSQ} , I_{DSQ} , and V_{DSQ} . Confirm answers through the load line above.

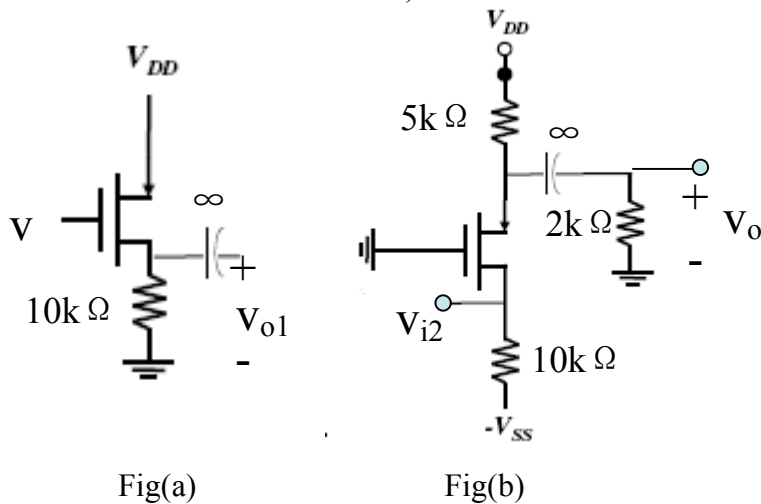4. (a) The NMOS transistor in the source follower circuit of Fig(a) has $g_m=5\text{mA/V}$ and r_d is infinity. Find the open-circuit voltage gain and the output resistance.
 (b) The NMOS transistor in the common-gate amplifier of Fig(b) has $g_m=5\text{mA/V}$ and r_d is infinity. Find the input resistance and voltage gain.
 (c) If the output of the source follower in (a) is connected to the input of the common-gate amplifier in (b), use the results of (a) and (b) to obtain the over all voltage gain. (Hint: Voltage gain is affected by the load resistance. Consider the load effect for cascaded circuits.)



- 6 Hambley, P12.45. But use $10\text{M}\Omega$ for both R_1 and R_2 , and $20\text{k}\Omega$ for R_L . r_d is not equal to infinity anymore. Do consider the effect caused by r_d .
(Hint: The transistor might not operated in the saturaion regime. Think about how you can find out r_d from the definition(eq. 12.31).