

3. What did you see on the oscilloscope when you change the frequency of the signal? Qualitatively draw graphs at $f = 100$ Hz, $f = 1$ kHz, $f = 10$ kHz of square wave. Explain why they look different.

4. Attach your LabVIEW measurement print-outs for high-pass filter and low-pass filter. Compare it with your manual plots. Are they in a good agreement in terms of shapes, amplitudes and 3 dB points? If not, try to explain the reason. What are the advantages you think of using LabVIEW rather than doing it manually?

5. Construct the RLC filter and connect the multimeter across the resistor. Using prelab values, note down the resonant frequency, the quality factor, Q , and the width of the passband?

6. Use LabView to plot the frequency response, sampling at 5 steps / decade. Find the half-power frequencies by stretching the graph. What are the 2 half-power frequencies, and what is the width of the passband?

Are your findings consistent with the equation relating quality factor, bandwidth and resonant frequency? Explain.