

UNIVERSITY OF CALIFORNIA, BERKELEY


EE40: Introduction to Microelectronic Circuits Lab 1

Introduction to Circuits and Instruments Prelab

Name _____

Session/TA _____

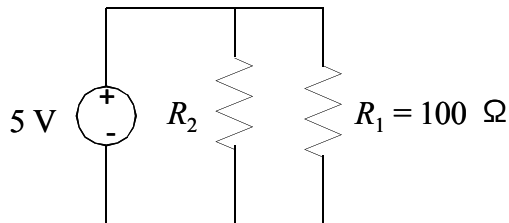1. Two resistors are connected in parallel to an ideal voltage source of 5 V. Choose the value of R_2 so that the total current going through R_1 and R_2 is 100 mA.



2. The examples given in the chart on page 4 are a $560 \text{ k}\Omega \pm 5\%$ 4-band resistor and a $237 \square \pm 1\%$ 5-band resistor. Try to verify the values yourself using the steps described there.

$$R = \frac{V_R R_m}{V_{test} - V_R}$$

3. Derive the equation shown in Figure 12 (a).

4. If R_L is 150Ω , and the signal generator display shows $V_{pp} = 1 \text{ V}$, what is the actual peak to peak amplitude of the signal across R_L ?

