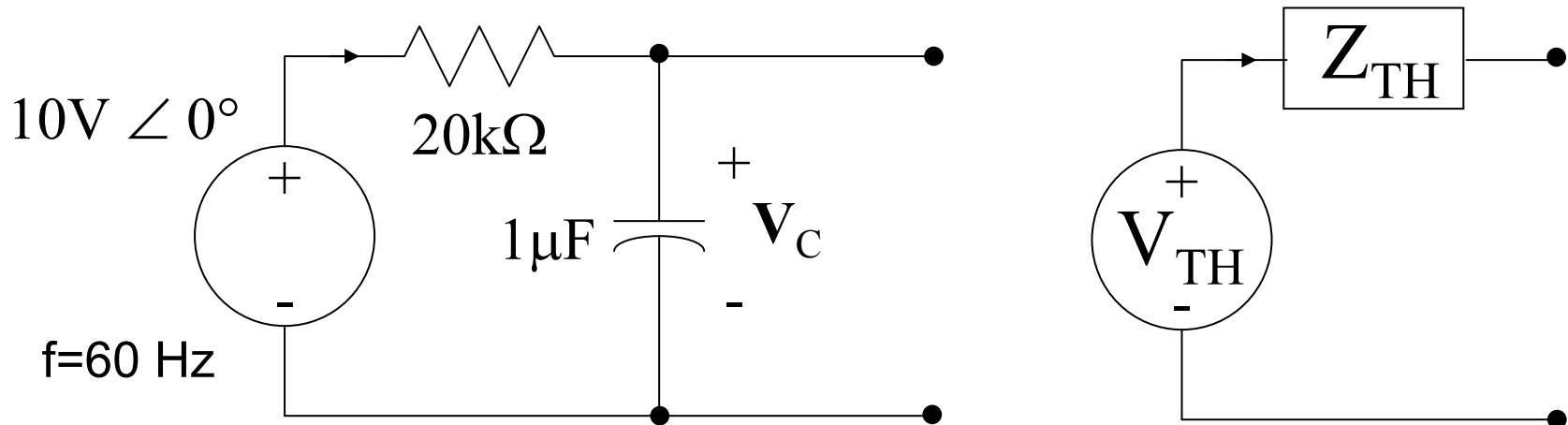

EE40
Lecture 17
Venkat Anantharam

3/05/08

Reading: Chap. 5: phasors.
Chap. 6: Bode plots.

Thevenin Equivalent



$$\mathbf{Z}_R = R = 20\text{k}\Omega = 20\text{k}\Omega \angle 0^\circ$$

$$\mathbf{Z}_C = 1/j(2\pi f \times 1\mu\text{F}) = 2.65\text{k}\Omega \angle -90^\circ$$

$$\mathbf{V}_{TH} = \mathbf{V}_{OC} = 10\text{V} \angle 0^\circ \left(\frac{2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 1.31 \angle -82.4$$

$$\mathbf{Z}_{TH} = \mathbf{Z}_R \parallel \mathbf{Z}_C = \left(\frac{20\text{k}\Omega \angle 0^\circ \cdot 2.65\text{k}\Omega \angle -90^\circ}{2.65\text{k}\Omega \angle -90^\circ + 20\text{k}\Omega \angle 0^\circ} \right) = 2.62 \angle -82.4$$

Root Mean Square (rms) Values

- rms value defined as

$$v_{RMS} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \quad T = \text{period}$$

- Assuming a sinusoid gives

$$v_{RMS} = \sqrt{\frac{1}{T} \int_0^T v_m^2 \cos^2(\omega t + \theta) dt}$$

- Using a trigonometric identity gives

$$v_{RMS} = \sqrt{\frac{v_m^2}{2T} \int_0^T [1 + \cos(2\omega t + 2\theta)] dt}$$

- Evaluating at limits gives

$$v_{RMS} = \sqrt{\frac{v_m^2}{2T} \left[T + \frac{1}{2\omega} \sin(2\omega T + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \right]} \quad v_{RMS} = \frac{v_m}{\sqrt{2}}$$

Power: Instantaneous and Time-Average

For a Resistor

- The instantaneous power is
$$p(t) = v(t)i(t) = \frac{v(t)^2}{R}$$

- The time-average power is

$$P_{AVE} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{v(t)^2}{R} dt = \frac{1}{R} \left[\frac{1}{T} \int_0^T v(t)^2 dt \right] = \frac{v_{rms}^2}{R}$$

For an Impedance

- The instantaneous power is

$$p(t) = v(t)i(t)$$


- The time-average power is

$$P_{AVE} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T v(t)i(t) dt = \text{Re} \{ \mathbf{V}_{rms} \cdot \mathbf{I}_{rms}^* \}$$

- The reactive power at 2ω is

$$Q = \text{Im} \{ \mathbf{V}_{rms} \cdot \mathbf{I}_{rms}^* \} \qquad P_{AVE}^2 + Q^2 = (V_{rms} \cdot I_{rms})^2$$

Maximum Average Power Transfer

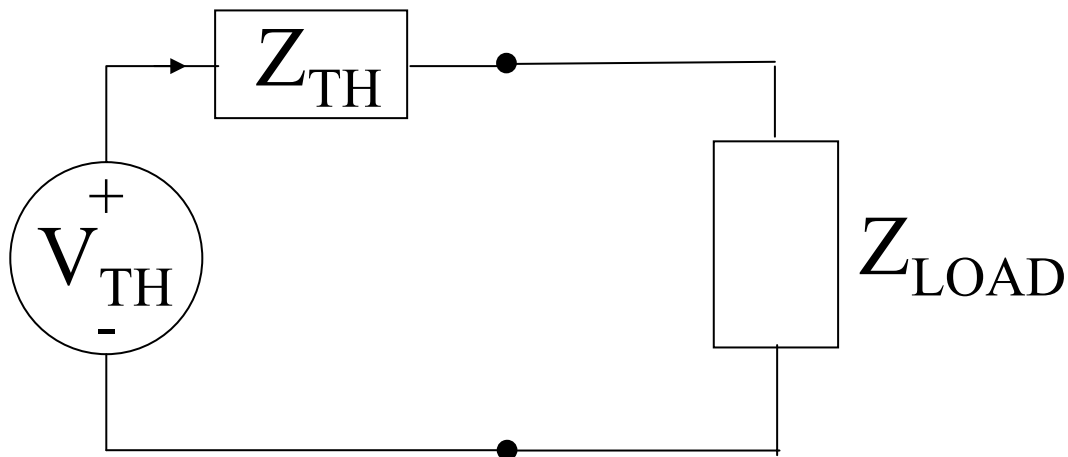

- Maximum time average power occurs when

$$\mathbf{Z}_{LOAD} = \mathbf{Z}_{TH}^*$$

- This presents a resistive impedance to the source

$$\mathbf{Z}_{total} = \mathbf{Z}_{TH} + \mathbf{Z}_{TH}^*$$

- Power transferred is

$$P_{AVE} = \text{Re}\{\mathbf{V}\mathbf{I}^*\} = \text{Re}\left\{\mathbf{V} \frac{\mathbf{V}^*}{2R}\right\} = \frac{1}{2} \frac{V_{rms}^2}{R}$$