
EE40
Lecture 19
Venkat Anantharam

3/10/08

Reading: Chap. 6: Filters, two-terminal elements, Bode plots.

Bel and Decibel (dB)

- A **bel** is a unit of measure of ratios of power levels, i.e. relative power levels.
 - The name was coined in the early 20th century in honor of Alexander Graham Bell, a telecommunications pioneer.
 - The bel is a logarithmic measure. The number of bels for a given ratio of power levels is calculated by taking the logarithm, to the base 10, of the ratio.
 - one bel corresponds to a ratio of 10:1.
- The bel is too large for everyday use, so the **decibel (dB)**, is more commonly used.
 - $10 \log_{10}(P_1/P_2)$ is the power ratio measure in decibels
- dB are used to measure
 - Electric power, Gain or loss of amplifiers, Insertion loss of filters.

Logarithmic Measure for Power

- To express a power in terms of decibels, one starts by choosing a reference power, $P_{\text{reference}}$, and writing

$$\text{Power } P \text{ in decibels} = 10 \log_{10}(P/P_{\text{reference}})$$

- Exercise:
 - Express a power of 50 mW in decibels relative to 1 watt.
 - $P \text{ (dB)} = 10 \log_{10}(50 \times 10^{-3}) = -13 \text{ dB}$
- Exercise:
 - Express a power of 50 mW in decibels relative to 1 mW.
 - $P \text{ (dB)} = 10 \log_{10}(50) = 17 \text{ dB}$.
- One uses dBm to express **absolute** values of power relative to a milliwatt.
 - $\text{dBm} = 10 \log_{10}(\text{power in milliwatts} / 1 \text{ milliwatt})$
 - $100 \text{ mW} = 20 \text{ dBm}$
 - $10 \text{ mW} = 10 \text{ dBm}$

Logarithmic Measures for Voltage or Current

From the expression for power ratios in decibels, we can readily derive the corresponding expressions for voltage or current ratios.

Suppose that the voltage V (or current I) appears across (or flows in) a resistor whose resistance is R . The corresponding power dissipated, P , is V^2/R (or I^2R). We can similarly relate the reference voltage or current to the reference power, as

$$P_{\text{reference}} = (V_{\text{reference}})^2/R \text{ or } P_{\text{reference}} = (I_{\text{reference}})^2R.$$

Hence,

$$\begin{aligned} \text{Voltage, } V \text{ in decibels} &= 20\log_{10}(V/V_{\text{reference}}) \\ \text{Current, } I, \text{ in decibels} &= 20\log_{10}(I/I_{\text{reference}}) \end{aligned}$$

Logarithmic Measures for Voltage or Current

Note that the voltage and current expressions are just like the power expression except that they have **20** as the multiplier instead of **10** because power is proportional to the square of the voltage or current.

Exercise: How many decibels larger is the voltage of a 9-volt transistor battery than that of a 1.5-volt AA battery? Let $V_{\text{reference}} = 1.5$. The ratio in decibels is

$$20 \log_{10}(9/1.5) = 20 \log_{10}(6) = 16 \text{ dB.}$$

Logarithmic Measures for Voltage or Current

The gain produced by an amplifier or the loss of a filter is often specified in decibels.

The input voltage (current, or power) is taken as the reference value of voltage (current, or power) in the decibel defining expression:

$$\text{Voltage gain in dB} = 20 \log_{10}(V_{\text{output}}/V_{\text{input}})$$

$$\text{Current gain in dB} = 20 \log_{10}(I_{\text{output}}/I_{\text{input}})$$

$$\text{Power gain in dB} = 10 \log_{10}(P_{\text{output}}/P_{\text{input}})$$


Example: The voltage gain of an amplifier whose input is 0.2 mV and whose output is 0.5 V is

$$20 \log_{10}(0.5/0.2 \times 10^{-3}) = 68 \text{ dB.}$$

Bode Plot

- Plot of magnitude of transfer function vs. frequency
 - Both x and y scale are in log scale
 - Y scale in dB
- Log Frequency Scale
 - Decade \rightarrow Ratio of higher to lower frequency = 10
 - Octave \rightarrow Ratio of higher to lower frequency = 2

Bode Plot: Label as dB

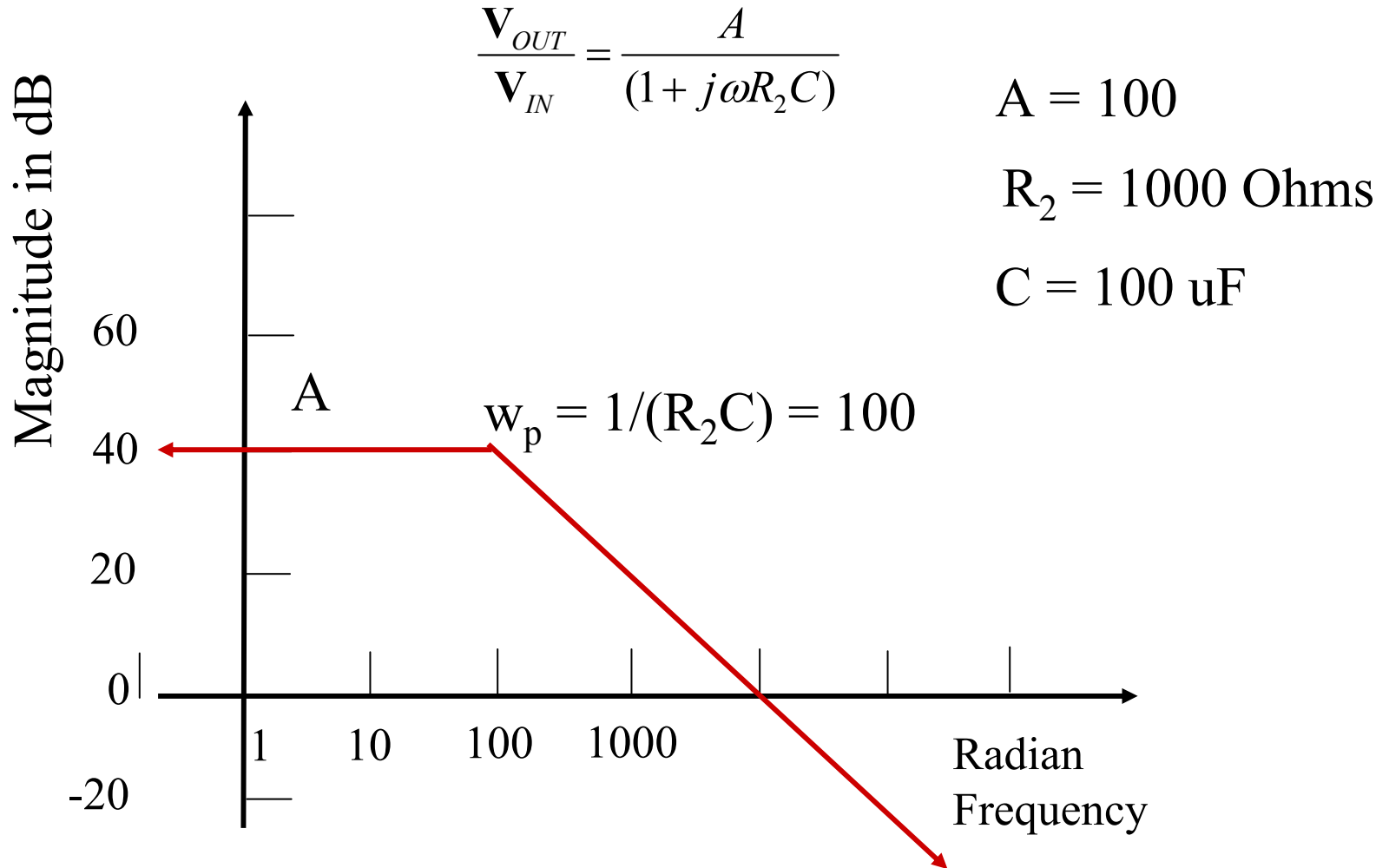

Note: Magnitude in dB = $20 \log_{10}(V_{OUT}/V_{IN})$

First-Order Lowpass Filter

$$\mathbf{H}(\mathbf{f}) = \frac{\mathbf{V}_C}{\mathbf{V}} = \frac{1/(j\omega C)}{1/(j\omega C) + R} = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} \angle -\tan^{-1}(\omega RC)$$


$$\text{Let } \omega_B = \frac{1}{RC} \text{ and } f_B = \frac{1}{2\pi RC}$$

$$\mathbf{H}(\mathbf{f}) = H(f) \angle \theta$$

$$H(f) = \frac{1}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}, \theta = -\tan^{-1}\left(\frac{f}{f_B}\right)$$

$$H(f_B) = \frac{1}{\sqrt{2}} = 2^{-1/2}$$
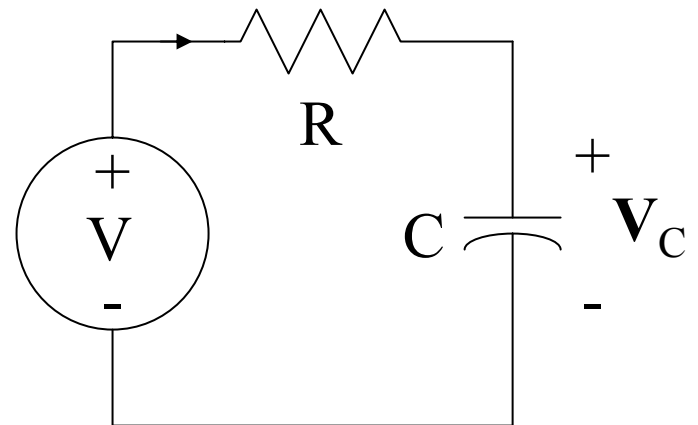
$$20 \log_{10} \frac{H(f_B)}{H(0)} = 20 \left(-\frac{1}{2}\right) \log_{10} 2 = -3 \text{ dB}$$



High-frequency asymptote of Lowpass filter

The high frequency asymptote of magnitude Bode plot assumes -20dB/decade slope

As $f \rightarrow \infty$

$$H(f) = \left(\frac{f}{f_B} \right)^{-1}$$

$$20 \log_{10} \frac{H(10f_B)}{H(f_B)} = -20dB$$

