

---


**EE40**  
**Lecture 2**  
**Venkat Anantharam**

1/25/08

Reading: Chap. 1

# The Ideal Basic Circuit Element

---

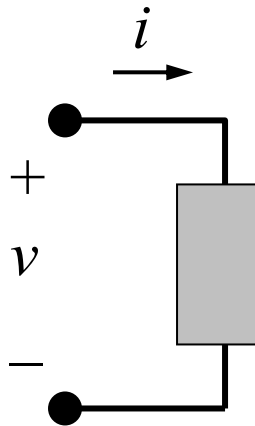

- Polarity reference for voltage can be indicated by plus and minus signs
- Reference direction for the current is indicated by an arrow

## Attributes:

- Two terminals (points of connection)
- Mathematically described in terms of current and/or voltage
- Cannot be subdivided into other elements

# Electric Power

---

- **Definition**: transfer of energy per unit time
- **Symbol**:  $p$
- **Units**: Joules per second  $\equiv$  Watts (W)

$$p = dw/dt = (dw/dq)(dq/dt) = vi$$

- **Concept**:

As a positive charge  $q$  moves through a drop in voltage  $v$ , it loses energy

- energy change =  $qv$
- rate is proportional to # charges/sec




James Watt  
1736 - 1819

# Passive Sign Convention

---

$$p = vi$$

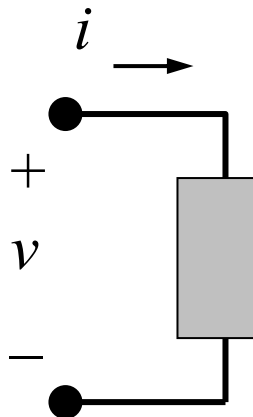


- If  $p > 0$ , power is being delivered to the box.
  - The element is a passive element.
- If  $p < 0$ , power is being generated from the box.
  - The element is an active element.
- How can a circuit element absorb power?
  - By converting electrical energy into heat (resistors in toasters), light (light bulbs), or acoustic energy (speakers); by storing energy (charging a battery).

# Sign Convention for Power


## Passive sign convention

$$p = vi$$

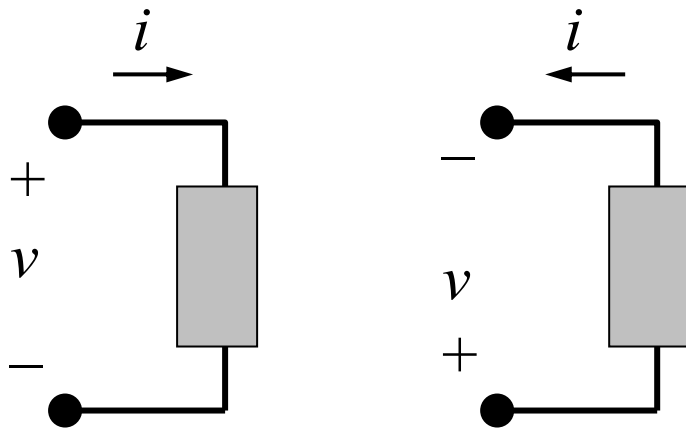

## Active sign convention

$$p = -vi$$

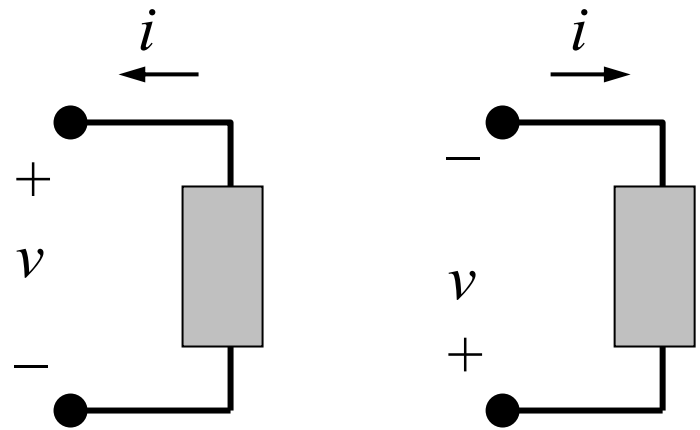

## Irrespective of the sign convention

- If  $p > 0$ , power is being delivered to the box.
- If  $p < 0$ , power is being extracted from the box.

# Electrical Resistance

---

- **Resistance:** the ratio of voltage drop and current. The circuit element used to model this behavior is the **resistor**.

Circuit symbol:



Units: Volts per Ampere  $\equiv$  ohms ( $\Omega$ )

- The current flowing in the resistor is proportional to the voltage across the resistor:

$$v = i R \quad (\text{Ohm's Law})$$

where  $v$  = voltage (V),  $i$  = current (A), and  $R$  = resistance ( $\Omega$ )





Georg Simon Ohm  
1789-1854
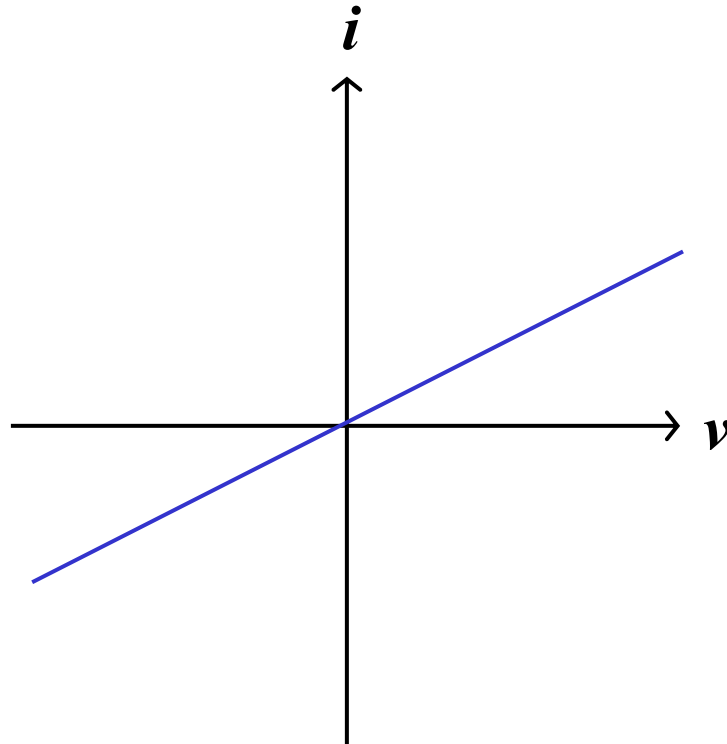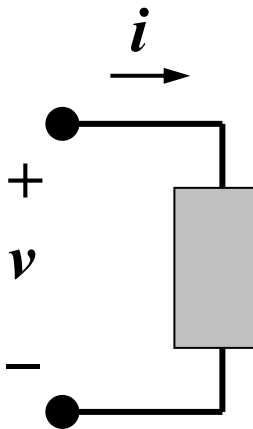
# Current vs. Voltage ( $I$ - $V$ ) Characteristic

---

What is the  $I$ - $V$  characteristic for an ideal resistor?



The slope must be positive and the characteristic must go through the origin.

# Electrical Conductance

---

- **Conductance** is the reciprocal of resistance.

**Symbol:**  $G$

**Units:** siemens (S) or mhos ( $\bar{\Omega}$ )

**Example:**

Consider an  $8 \Omega$  resistor. *What is its conductance?*



Werner von Siemens  
1816-1892





# Electrical Sources

---

- An ***electrical source*** is a device that is capable of converting non-electric energy to electric energy and *vice versa*.

## Examples:

- battery: chemical  $\longleftrightarrow$  electric
- dynamo (generator/motor): mechanical  $\longleftrightarrow$  electric  
(Ex. gasoline-powered generator, Bonneville dam)


→ Electrical sources can either deliver or absorb power

# Ideal Voltage Source


---

- Circuit element that maintains a prescribed voltage across its terminals, **regardless of the current flowing in those terminals.**
  - Voltage is known, but current is determined by the circuit to which the source is connected.
- The voltage can be either **independent** or **dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.


## Device symbols:

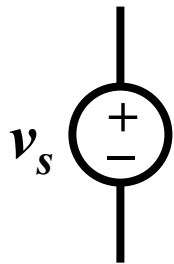

independent


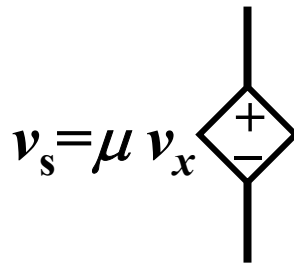


voltage-controlled

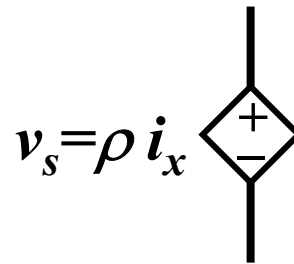

current-controlled
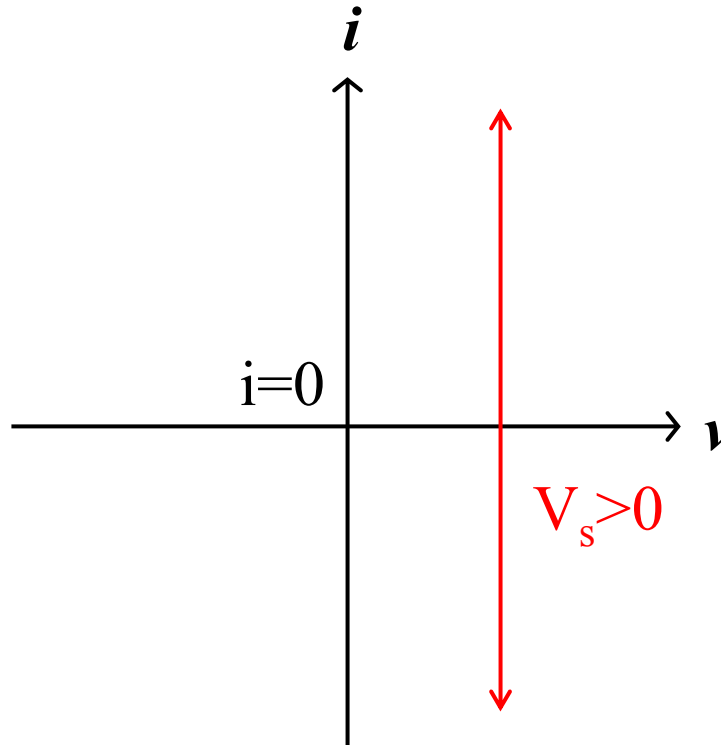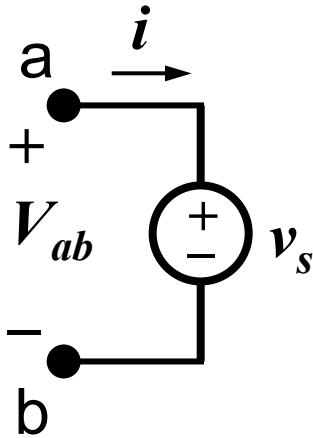
# I-V Characteristic of Ideal Voltage Source



1. Plot the  $I$ - $V$  characteristic for  $v_s > 0$ . For what values of  $i$  does the source absorb power? For what values of  $i$  does the source release power?


$V_s > 0 \rightarrow i < 0$  release power;  $i > 0$  absorb power

# Ideal Current Source


---

- Circuit element that maintains a prescribed current through its terminals, **regardless of the voltage across those terminals.**
  - Current is known, but voltage is determined by the circuit to which the source is connected.
- The current can be either **independent or dependent** on a voltage or current elsewhere in the circuit, and can be constant or time-varying.


## Device symbols:

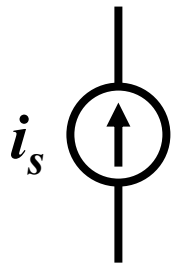

independent

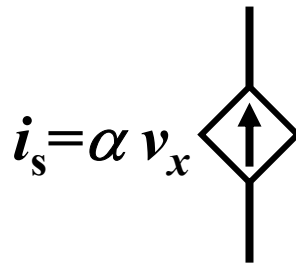



voltage-controlled

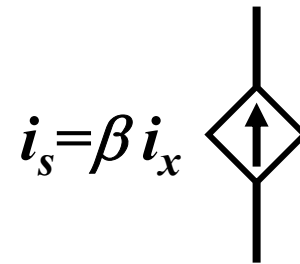

current-controlled

# I-V Characteristic of Ideal Current Source

---

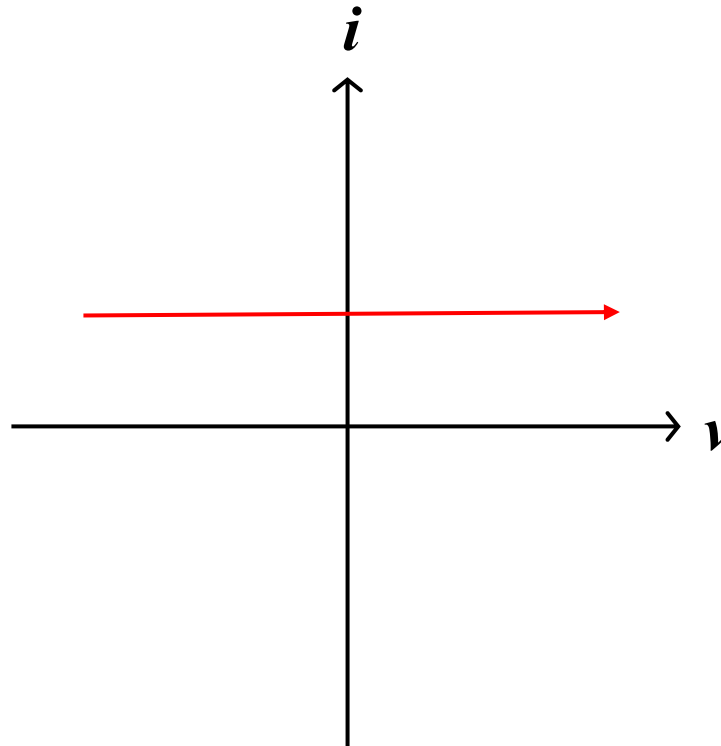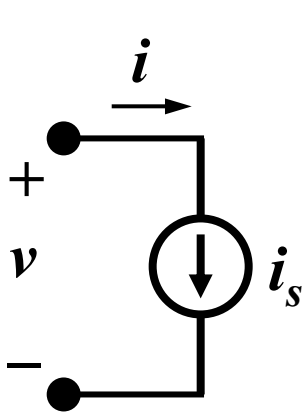

1. Plot the  $I$ - $V$  characteristic for  $i_s > 0$ . For what values of  $v$  does the source absorb power? For what values of  $v$  does the source release power?

$V > 0$  absorb power;  $V < 0$  release power