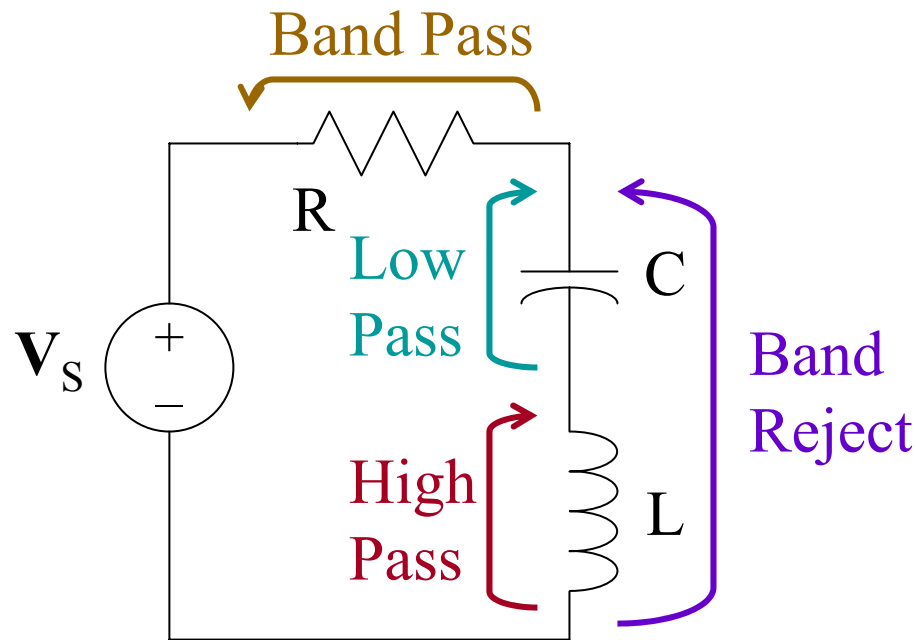

EE40
Lecture 21
Venkat Anantharam

3/14/08

Reading: Chap. 6: Bode plots for
second order systems.

Second-Order Filter Circuits



$$\mathbf{Z} = R + 1/j\omega C + j\omega L$$


$$\mathbf{H}_{BP} = R / \mathbf{Z}$$

$$\mathbf{H}_{LP} = (1/j\omega C) / \mathbf{Z}$$

$$\mathbf{H}_{HP} = j\omega L / \mathbf{Z}$$

$$\mathbf{H}_{BR} = \mathbf{H}_{LP} + \mathbf{H}_{HP}$$

Series Resonance

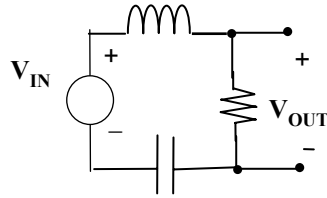

Voltage divider

$$\frac{V_{OUT}}{V_{IN}} = \frac{Z_R}{Z_L + Z_R + Z_C}$$

Substitute branch elements

$$\frac{V_{OUT}}{V_{IN}} = \frac{R}{j\omega L + R + 1/j\omega C}$$

Rearrange:


$$\frac{V_{OUT}}{V_{IN}} = \frac{R}{R + j(\omega L - 1/\omega C)}$$

Resonance quality factor

$$Q = \frac{\omega_0 L}{R}$$

Bandwidth is f_0/Q in Hz.

Parallel Resonance

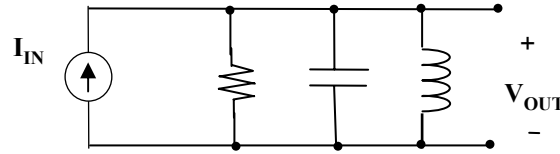

Admittance

$$V_{OUT} = \frac{I_S}{Y_L + Y_R + Y_C}$$

Substitute branch elements

$$V_{OUT} = \frac{I_S}{1/j\omega L + 1/R + j\omega C}$$

Rearrange:

$$V_{OUT} = \frac{I_S}{1/R + j(\omega C - 1/\omega L)}$$

Resonance quality factor

$$Q = \frac{\omega_0 L}{R}$$

Bandwidth is f_0/Q in Hz.