
EE40
Lecture 25
Venkat Anantharam

4/02/08

Reading: Chap. 14: Operational
Amplifiers+ Chap. 10: Diodes


Ideal Op-Analysis: Non-Inverting Amplifier

Yes Negative Feedback is present in this circuit!

Assumption 1: The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

Assumption 2: The **currents** flowing into the op-amp's two input terminals both equal **zero**.

KCL with currents in only two branches

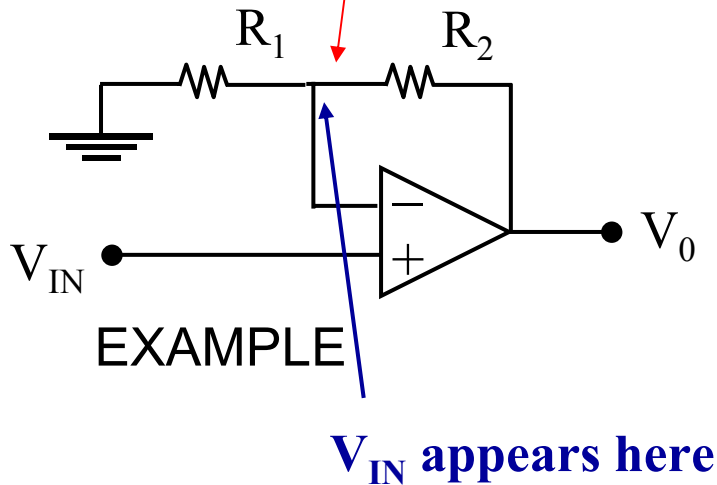


$$\frac{v_{in}}{R_1} + \frac{v_{in} - v_{out}}{R_2} = 0$$
$$v_{out} = \frac{R_1 + R_2}{R_1} v_{in}$$

Non-inverting Amplifier

Non-Inverting Amplifier

- Ideal voltage amplifier

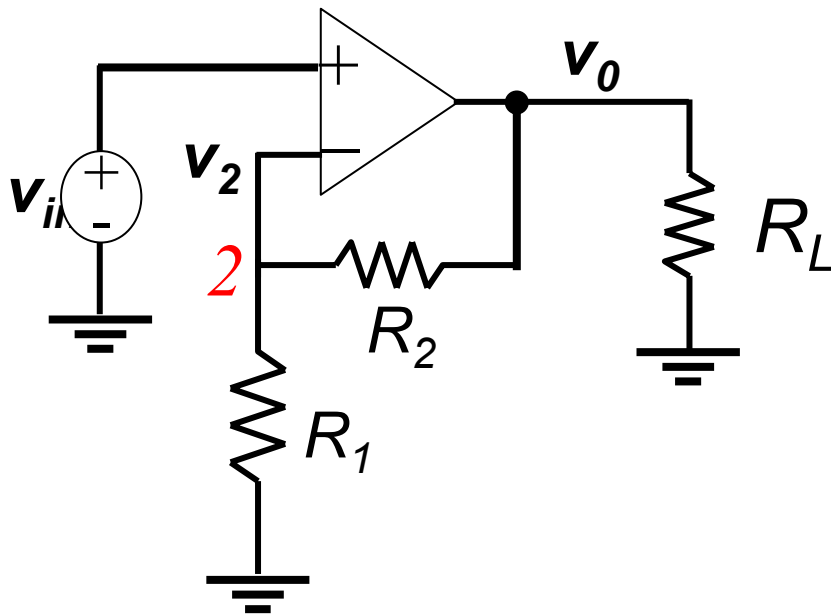

$$\text{Closed loop gain} = A_v = \frac{v_o}{v_{in}}$$

$$v_1 = v_2 = v_{in}, i_1 = i_2 = 0$$


Use KCL At Node 2.

$$i = \frac{(v_o - v_2)}{R_2} = \frac{(v_2 - 0)}{R_1}$$


$$A = \frac{v_o}{v_{in}} = \frac{(R_1 + R_2)}{R_1}$$

$$\text{Input impedance} = \frac{v_{in}}{i} \rightarrow \infty$$

Summing Amplifier

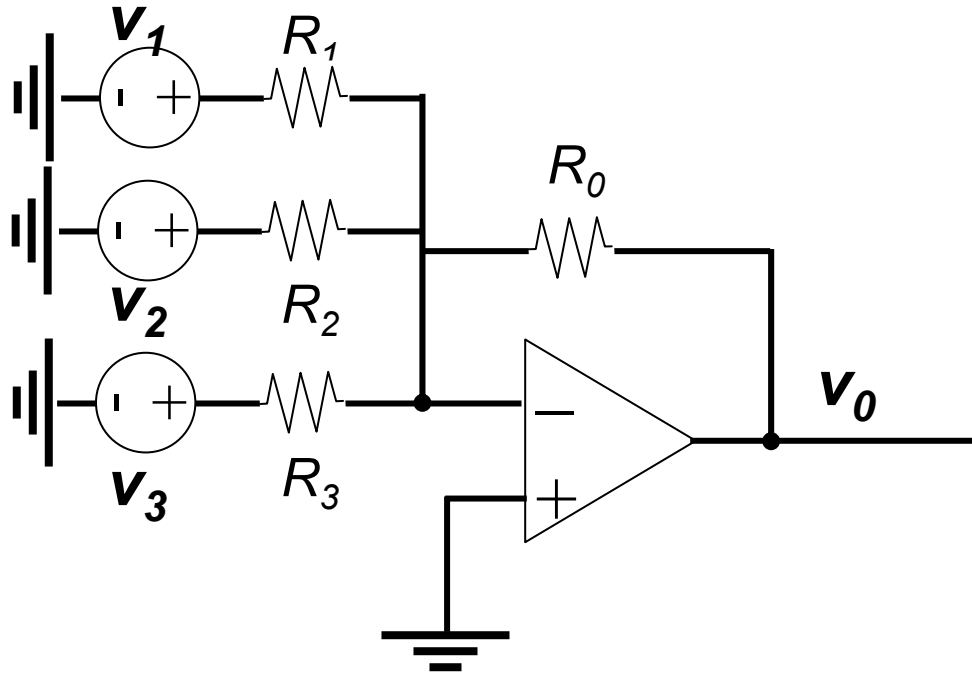


Difference Amplifier

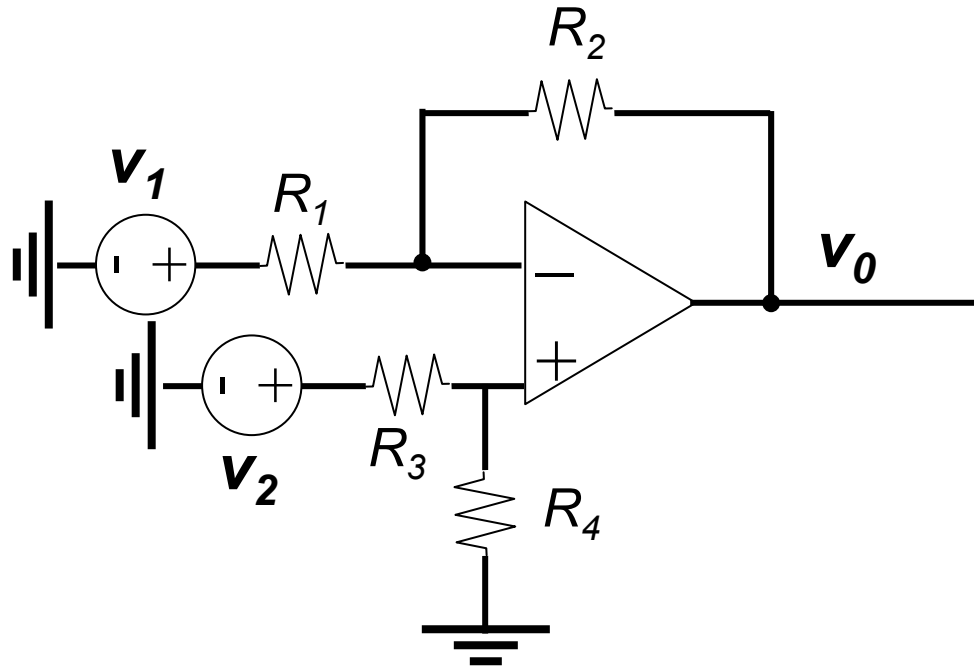


Integrator


- Want $v_o = K \int v_{in} dt$

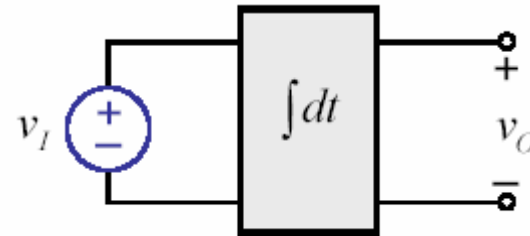

- What is the difference between:

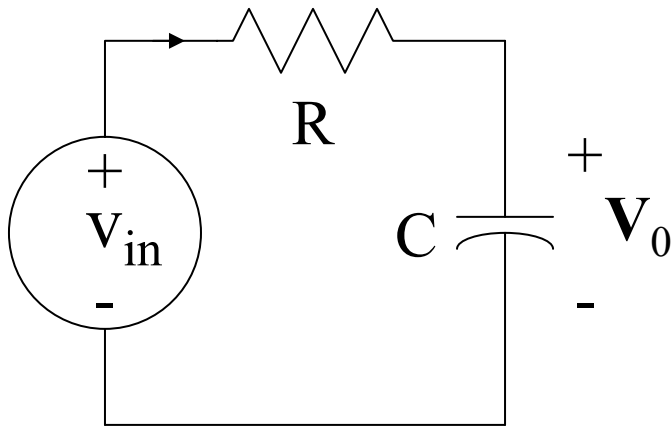

$$v_o \approx \frac{1}{RC} \int v_I dt$$

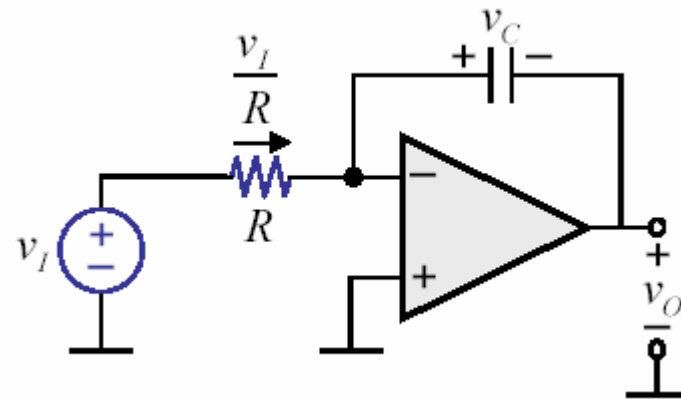

$$v_o = -\frac{1}{C} \int \frac{v_I}{R} dt$$

Differentiator

- Want

