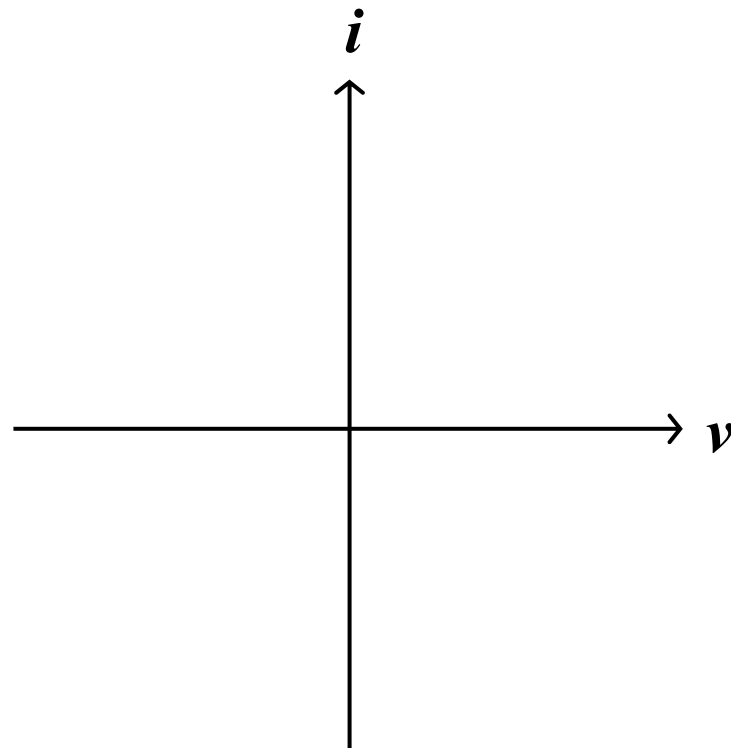
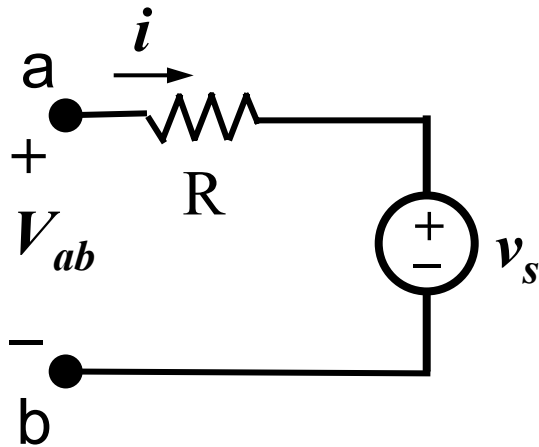

EE40
Lecture 3
Venkat Anantharam

1/28/08

Reading: Chap. 2

I-V Characteristic of Elements

Find the I-V characteristic.



Short Circuit and Open Circuit

- Short circuit
 - $R = 0 \rightarrow$ no voltage difference exists
 - all points on the wire are at the same potential.
 - Current can flow, as determined by the circuit
- Open circuit
 - $R = \infty \rightarrow$ no current flows
 - Voltage difference can exist, as determined by the circuit


Short Circuit and Open Circuit

Wire (“short circuit”):

- $R = 0 \rightarrow$ no voltage difference exists
(all points on the wire are at the same potential)
- Current can flow, as determined by the circuit

Air (“open circuit”):

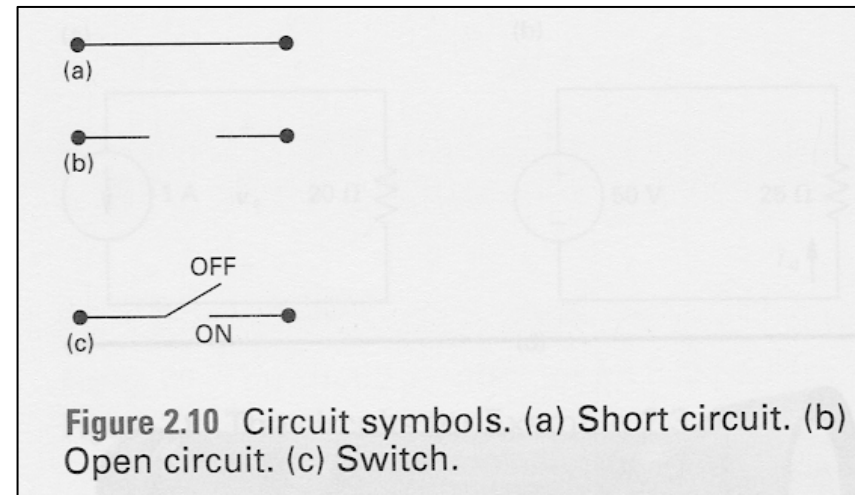- $R = \infty \rightarrow$ no current flows
- Voltage difference can exist, as determined by the circuit



Example: Power Absorbed by a Resistor


$$p = vi = (iR)i = i^2R$$

$$p = vi = v(v/R) = v^2/R$$

Note that $p > 0$ always, for a resistor \rightarrow a resistor dissipates electric energy

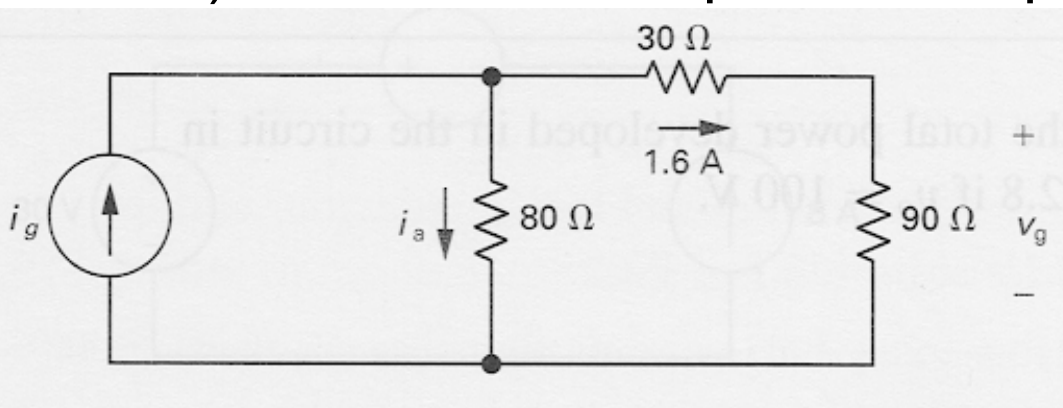
Example:

- Calculate the voltage v_g and current i_a .
- Determine the power dissipated in the 80Ω resistor.




Terminology: Nodes and Branches

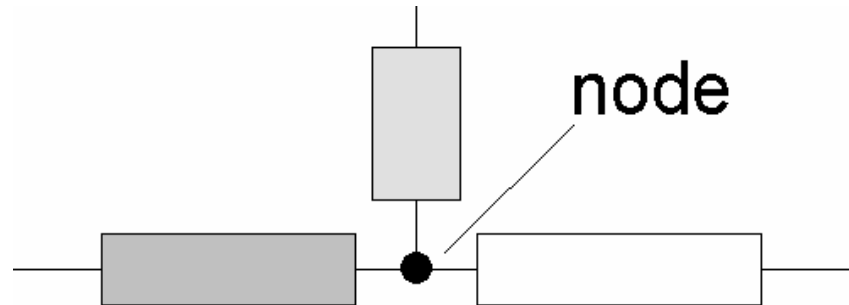
Node: A point where two or more circuit elements are connected



Branch:

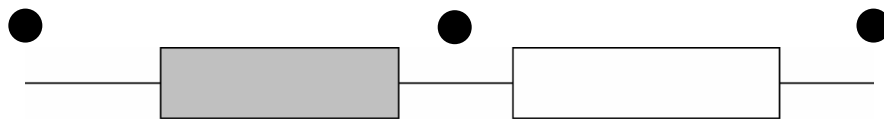

A single branch

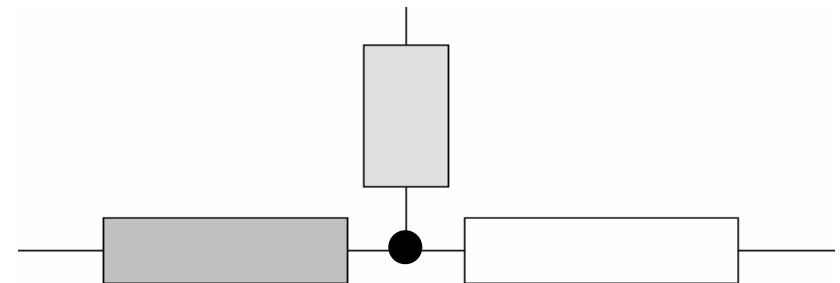

NOT a single branch

Graph associated to a circuit

- First determine all the nodes in the circuit.
- Draw a line diagram where every pair of nodes that is connected by a circuit element in the circuit is connected by an edge in your diagram.
- This is called the **graph** of the circuit.

Circuit Nodes and Loops

- A **node** is a point where two or more circuit elements are connected.
- A **loop** is formed by tracing a closed path in a circuit through selected basic circuit elements without passing through any intermediate node more than once