



Figure 0.1 Battery and resistor circuits with (a) forward- and (b) reverse-biased diodes.

© 2001 by Prentice Hall
 Prentice-Hall, Inc.
 Upper Saddle River, New Jersey 07458

All rights reserved. No part of this book may be reproduced in any form or by any means, without permission in writing from the publisher.