

Lecture 4: September 10th, 2001

Circuit Elements and Equivalent Circuits

A) Capacitors

B) Inductors

C) I versus V & Simplest Equivalent
Circuit

Reading:

Schwarz and Oldham 5.1, 2.2, 3.1

Summary 1

- Capacitors: two plate example $Q = CV$, $I = C dV/dt$
and $V = (1/C)$ integral of voltage
- Computer example 1 mA current charging 1 pF
 $V(t) = (I/C)t = (10^{-3} \text{ A}/10^{-12} \text{ F}) t = 10^9 \text{ V/s } t$
- At D.C. time derivatives are zero $\Rightarrow C$ is open circuit
- C in parallel add; series $1/C = \text{sum } (1/C_i)$; short together
(infinite current but conserve charge)
- Inductors: coil example Flux = LI, $V = L dI/dt$
and $I = (1/L)$ (integral of voltage)
- At D.C. time derivatives are zero $\Rightarrow L$ is short circuit
- L in parallel $1/L = \text{sum } (1/L_i)$; series add; connect in series
when have different currents $\Rightarrow L_1 I_1 + L_2 I_2 = (L_1 + L_2) I_{\text{NEW}}$

Summary 2

- I vs. V for ideal voltage source is a vertical line at $V = V_{SV}$
- I vs. V for ideal current source is a horizontal line at $I = I_{SC}$
- I vs. V for a circuit made up of ideal independent sources and resistors is a straight line.
- The simplest circuit for a straight line is an ideal voltage source and a resistor (Thevenin) or a current source and a parallel resistor (Norton)
- The easiest way to find the I vs. V line is to find the intercepts where $I = 0$ (open circuit voltage V_T) and where $V = 0$ (Short circuit current I_N)
- The short-cut for finding the $(\text{slope})^{-1} = R_T = R_N$ is to turn off all of the dependent sources to zero and find the remaining equivalent resistance between the terminals of the elements.