

Lecture 5: September 12th, 2001

Graphical Solutions and Power

- A) Load line method
- B) Power
- C) Nonlinear elements

Reading:

Schwarz and Oldham 3.2-3.3

Summary

- Load line method uses I vs. V for the element and finds the curve of I vs. V that satisfies the element.
- The circuit in which the element is to function is then characterized by a plot of I_{LOAD} vs. V_{LOAD} on the same axes by looking back into the circuit from the element and representing it as a Thevenin or Norton equivalent circuit.
- The intersection of these two curves gives a point or points that simultaneously meet the constraints of the element and the constraints of the circuit.
- Example: see 3.1 in text pp. 89 for an element; circuit is ideal voltage source and series resistor
 - **Case 1: 3V source and 100 ohms series resistor => 2.5V and 5 mA**
 - **Case2: 1V source and 100 ohms series resistor => 1.5V and -5 mA**

Summary

- **Power into the element is $I_E V_E$ and is given by the rectangular area between the intersection point and the horizontal and vertical axes.**
 - **Case 1: $(5 \text{ MA})(2.5\text{V}) = 12.5 \text{ mW}$**
 - **Case 2: $(-5\text{mA})(1.5\text{V}) = -7.5 \text{ mW}$**
- **Power from the source is $I_S V_S = I_E V_S$**
 - **Case 1: $(5 \text{ MA})(3\text{V}) = 15 \text{ mW}$ (rest is into resistor)**
 - **Case 2: $(-5\text{mA})(1\text{V}) = -5 \text{ mW}$ (rest is into resistor)**
- **Nonlinear elements have I vs. V curves that are not straight but the procedure is the same**
- **Example: Light Emitting Diode – design a bias to produce 20 mA at 4 V**
 - **Three 1.5V batteries plus total of 25 ohms resistance**
 - **9V battery plus 250 ohms of resistance**
 - **The former has better battery power to light efficiency but the latter is better in case high temperatures occur as the current versus voltage tends to double for every 5 degrees C.**