

Lecture 6: September 17th, 2001

Charging and Discharging of RC Circuits (Transients)

- A) Digital pulse environment
- B) RC response
- C) Review of simple exponentials

Reading:

Schwarz and Oldham 8.1+ Handout

The following slides were derived
from those prepared by Professor
Oldham For EE 40 in Fall 01


Review of charging and discharging in RC Circuits (an enlightened approach)

- *Before* we continue with formal circuit analysis - lets review RC circuits
- Rationale: Every node in a circuit has capacitance to ground, like it or not, and it's the charging of these capacitances that limits real circuit performance (speed)


Relevance to digital circuits:

We communicate with pulses

We send beautiful pulses out

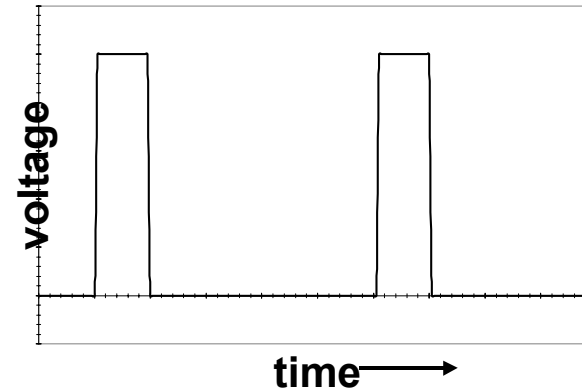

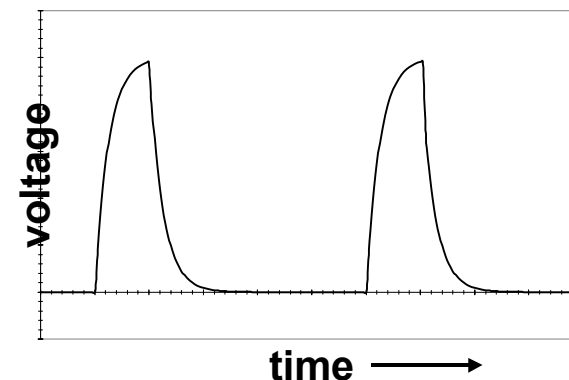But we receive lousy-looking pulses
and must restore them





RC charging effects are responsible So lets review them.

Simplification for time behavior of RC Circuits

- Before any input change occurs we have a dc circuit problem (that is we can use dc circuit analysis to relate the output to the input).
- Long after the input change occurs things “settle down” Nothing is changing So again we have a dc circuit problem.


We call the time period during which the output changes the *transient*

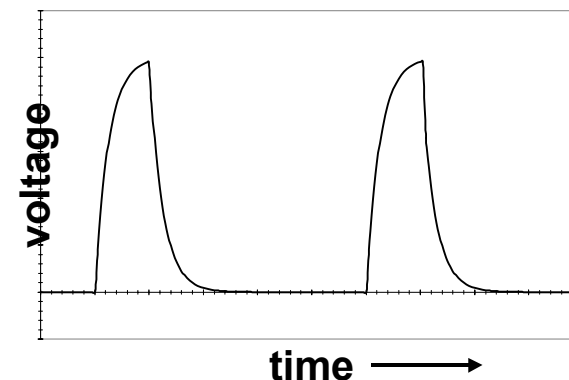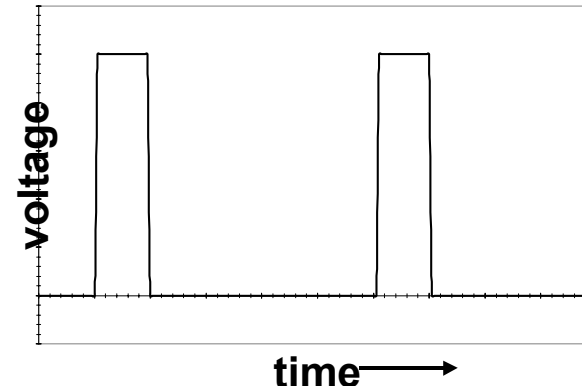We can predict a lot about the transient behavior from the pre- and post-transient dc solutions



What environment do pulses face?

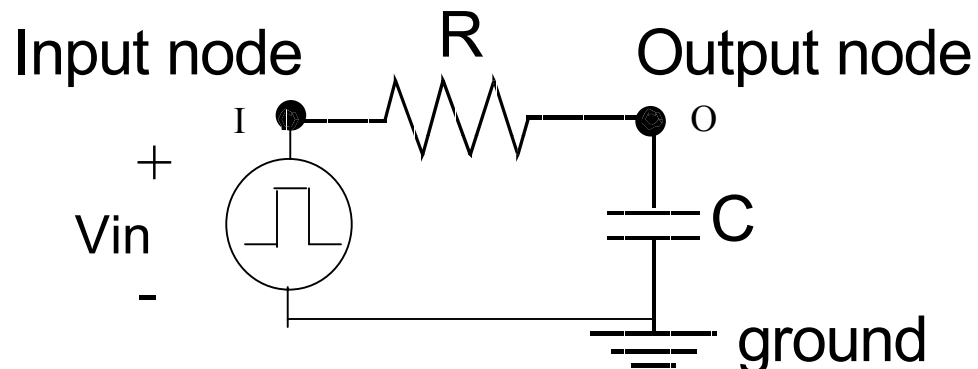- Every wire in a circuit has resistance.
- Every junction (called *nodes*) has capacitance to ground and other nodes.
- The active circuit elements (transistors) add additional resistance in series with the wires, and additional capacitance in parallel with the node capacitance.




A pulse originating at **node I** will arrive delayed and distorted at **node O** because it takes time to charge C through R

If we focus on the circuit which distorts the pulses produced by V_{in} , it consists simply of R and C . (V_{in} is just the time-varying source which produces the input pulse.)

The RC Circuit to Study

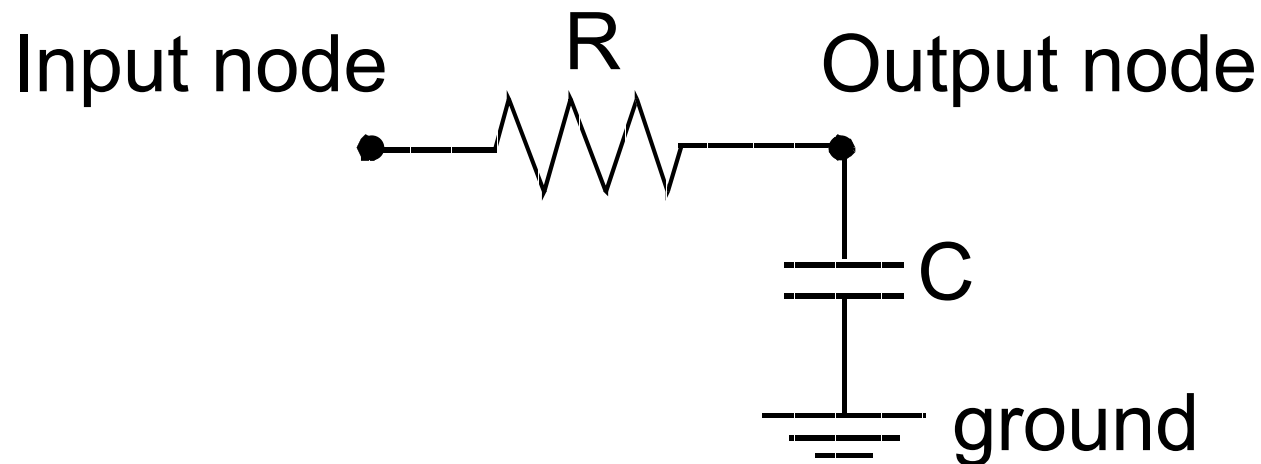(All single-capacitor circuits reduce to this one)



- R represents total resistance (wire plus whatever drives the input node)
- C represents the total capacitance from node to the outside world (from devices, nearby wires, ground etc)

SWITCHING PROPERTIES OF L, C

Rule: The voltage across a capacitor must be continuous and differentiable. For an inductor the current must be continuous and differentiable.

Basis: The energy cannot “jump” because that would require infinite energy flow (power) and of course neither the current or voltage can be infinite. For a capacitor this demands that V be continuous (no jumps in V); for an inductor it demands i be continuous (no jumps in i).

Capacitor

v is continuous

I can jump

Do not short circuit a charged capacitor

(produces ∞ current)

Inductor

i is continuous

V can jump



Do not open an inductor with current flowing

(produces ∞ voltage)

RC RESPONSE EXAMPLE

Version Date 9/17/01

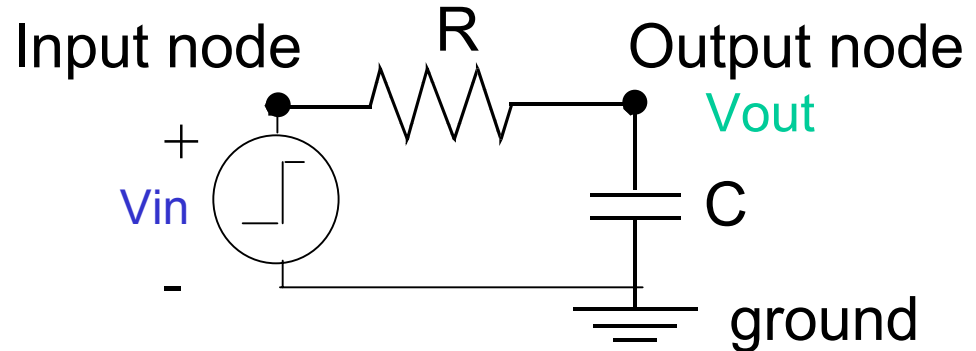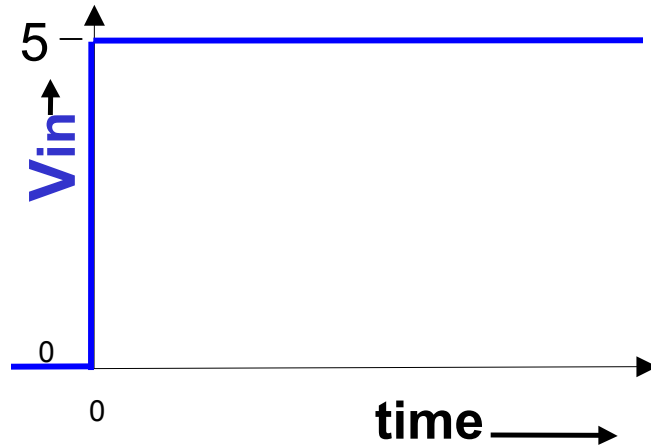
Case 1 Capacitor uncharged: Apply + voltage step of 2V



The capacitor voltage, V_{out} , is initially zero and rises in response to the step in input.

Its initial value, just after the step, is still zero WHY?

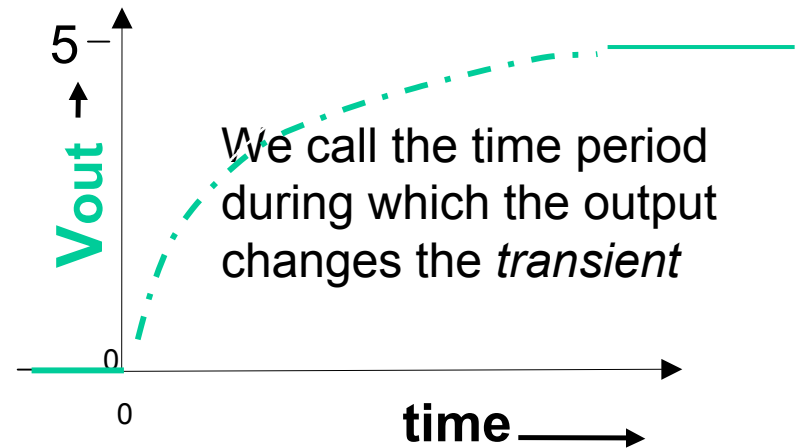
Its final value, long after the step is is 5V WHY?



We call the time period during which the output changes the *transient*

We need to find the solution during the transient.

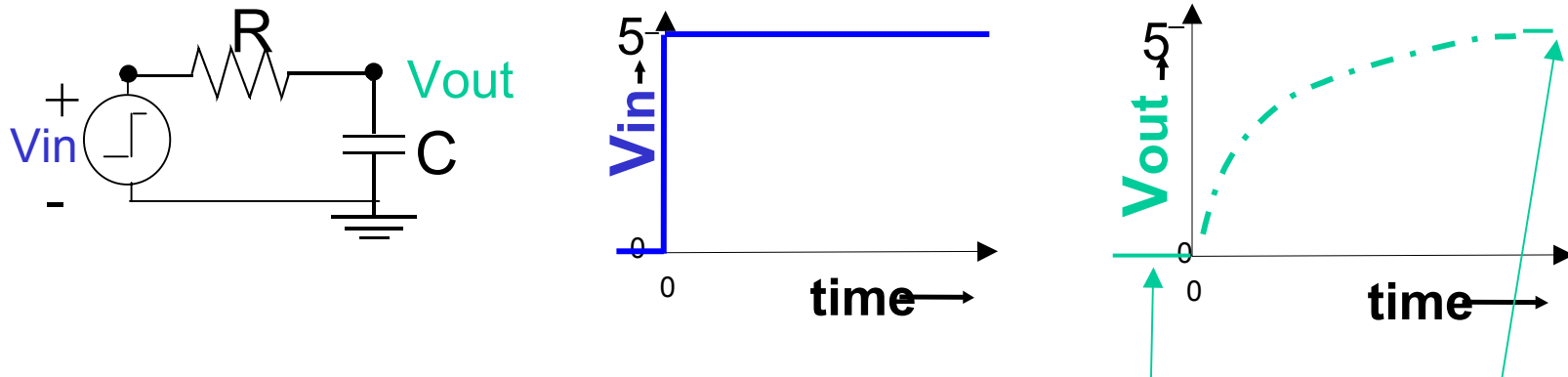Simplification for time behavior of RC Circuits





Before any input change occurs (before the transient) we have a dc circuit problem (that is we can use dc circuit analysis to relate the output to the input). That's because the capacitor current is zero.

Long after the input change occurs (i.e. after the transient is over) nothing is changing So again we have a dc circuit problem. Again that simply because d/dt is zero, hence the capacitor current is zero.

We can predict a lot about the transient behavior from the pre- and post-transient dc solutions

RC RESPONSE

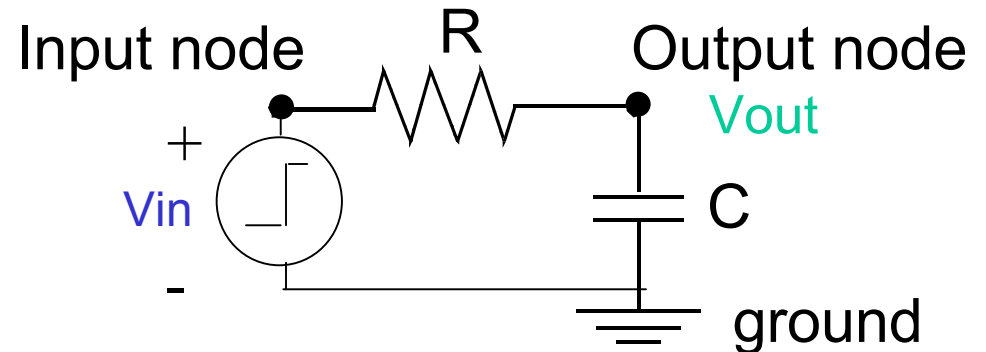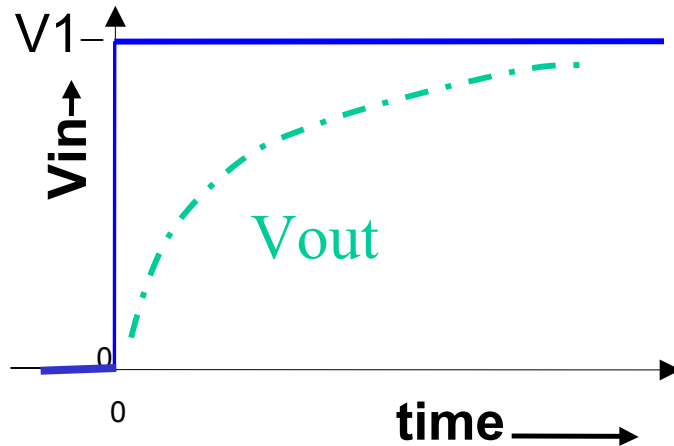Case 1 – Rising voltage. Capacitor uncharged: Apply + voltage step



- V_{in} “jumps” at $t=0$, but V_{out} cannot “jump” like V_{in} . Why not?

☞ Because an instantaneous change in a capacitor voltage would require instantaneous increase in energy stored ($1/2CV^2$), that is, infinite power. (Mathematically, V must be differentiable: $I=CdV/dt$)



V does not “jump” at $t=0$, i.e. $V(t=0^+) = V(t=0^-)$

Therefore the dc solution before the transient tells us the capacitor voltage at the beginning of the transient.

RC RESPONSE

Version Date 9/17/01

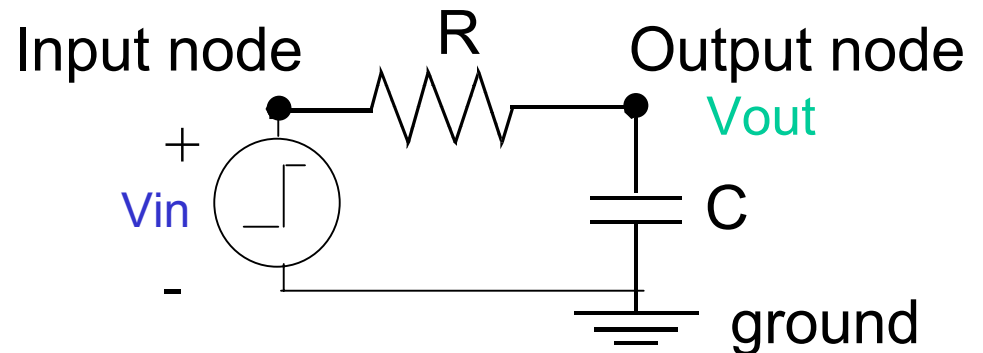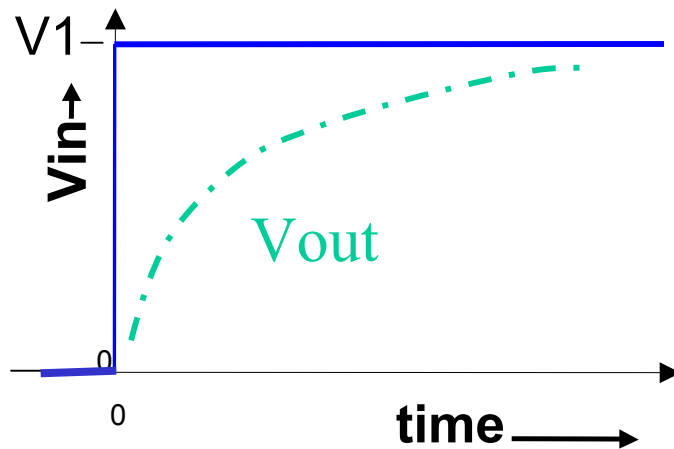Case 1 – Capacitor uncharged: Apply voltage step



- V_{out} approaches its final value asymptotically (It never quite gets to V_1 , but it gets arbitrarily close). Why?

After the transient is over (nothing changing anymore) it means $d(V)/dt = 0$; that is all currents must be zero. From Ohm's law, the voltage across R must be zero, i.e. $V_{in} = V_{out}$.



☞ That is, $V_{out} \rightarrow V_1$ as $t \rightarrow \infty$. (Asymptotic behavior)

Again the dc solution (after the transient) tells us (the asymptotic limit of) the capacitor voltage during the transient.

RC RESPONSE

Version Date 9/17/01

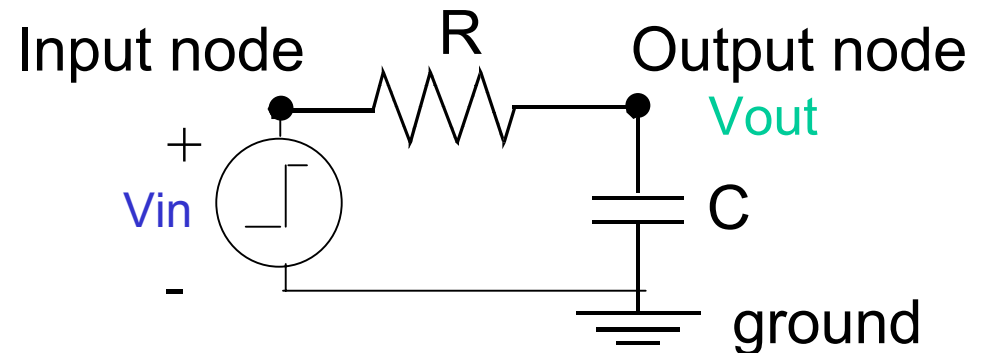
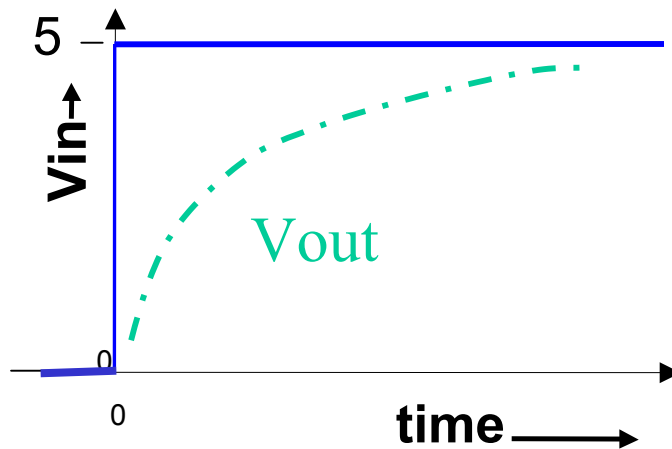
Example – Capacitor uncharged: Apply voltage step of 5 V



- Clearly V_{out} starts out at 0V (at $t = 0^+$) and approaches 5V.
- We know this because of the pre-transient dc solution ($V=0$) and post-transient dc solution ($V=5V$).

So we know a lot about V_{out} during the transient - namely its initial value, its final value , *and we know the general shape* .



RC RESPONSE: Case 1 (cont.)

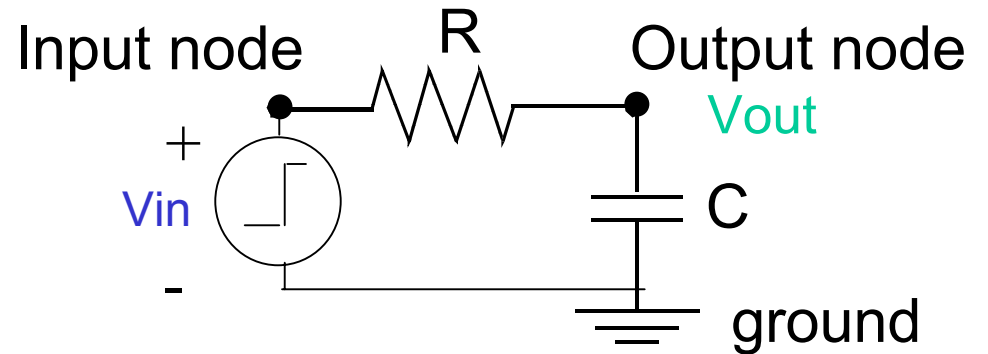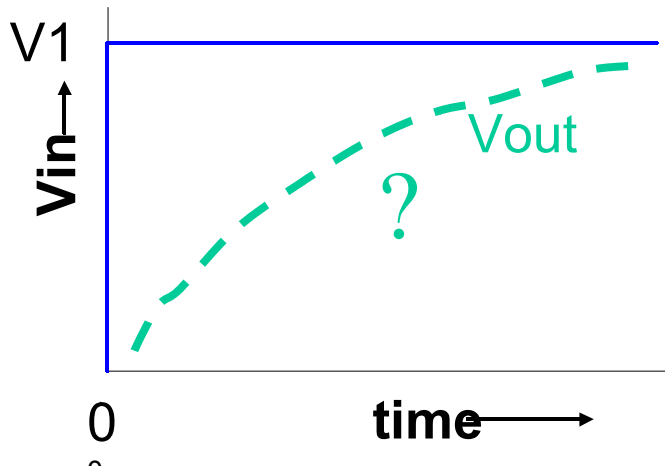

Equation for V_{out} : Do you remember general form?

$$V_{out} = V_1(1 - e^{-t/\tau})$$

Exact form of V_{out} ?

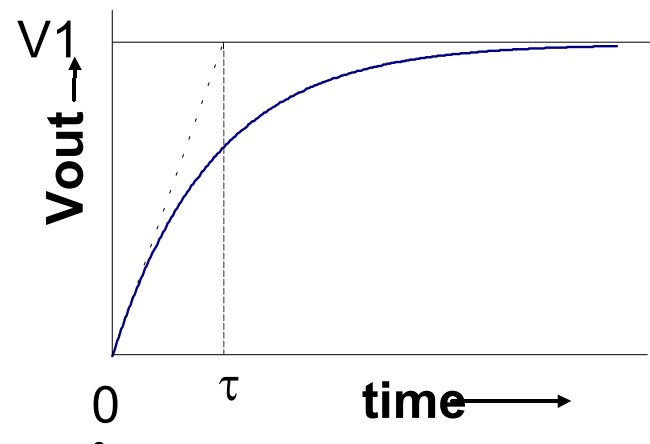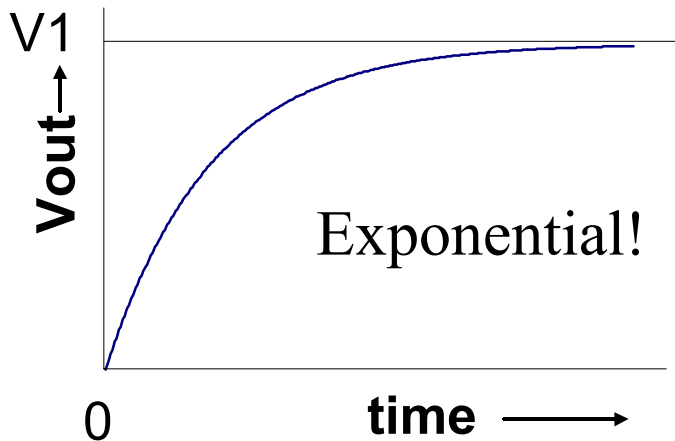


Review of simple exponentials.

Rising Exponential from Zero

$$V_{\text{out}} = V_1(1 - e^{-t/\tau})$$

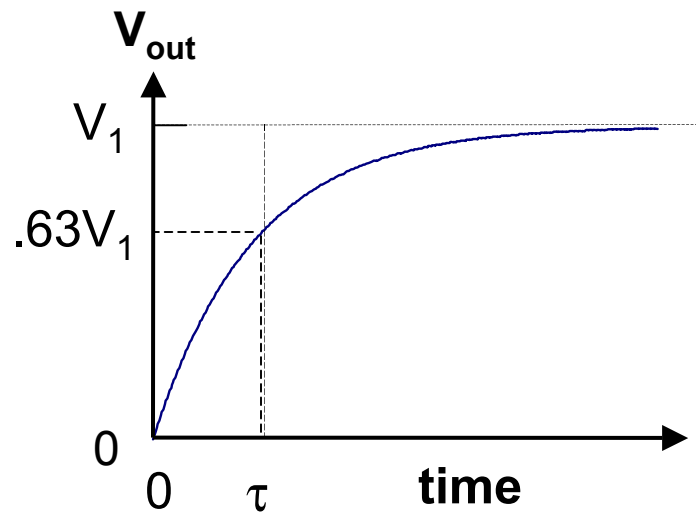
at $t = 0$, $V_{\text{out}} = 0$, and
 at $t \rightarrow \infty$, $V_{\text{out}} \rightarrow V_1$ also
 at $t = \tau$, $V_{\text{out}} = 0.63 V_1$



Falling Exponential to Zero

$$V_{\text{out}} = V_1 e^{-t/\tau}$$

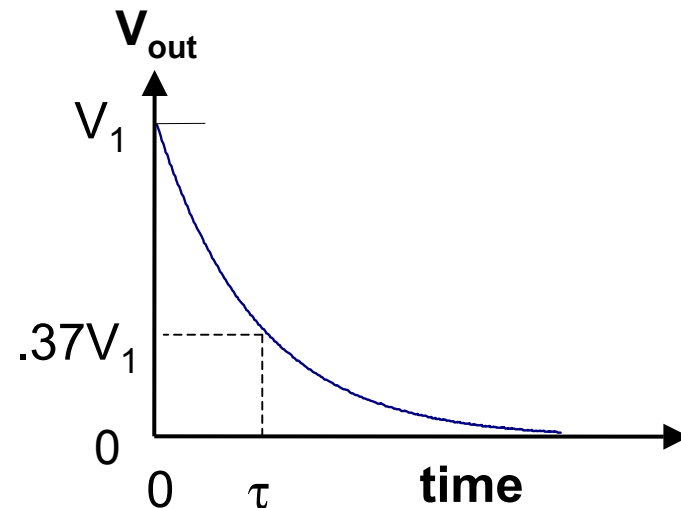at $t = 0$, $V_{\text{out}} = V_1$, and
 at $t \rightarrow \infty$, $V_{\text{out}} \rightarrow 0$, also
 at $t = \tau$, $V_{\text{out}} = 0.37 V_1$




Further Review of simple exponentials. Version Date 9/17/01

Rising Exponential from Zero

$$V_{out} = V_1(1 - e^{-t/\tau})$$

We can add a constant (positive or negative)


$$V_{out} = V_1(1 - e^{-t/\tau}) + V_2$$

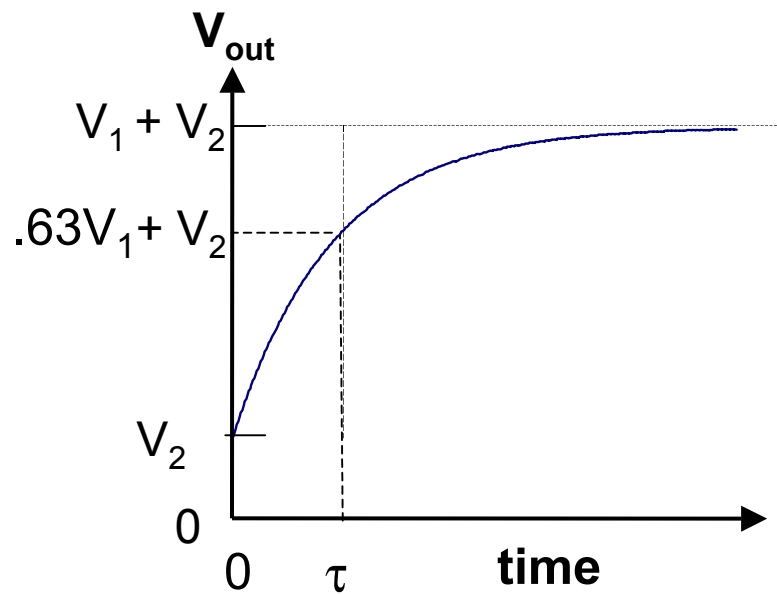

Falling Exponential to Zero

$$V_{out} = V_1 e^{-t/\tau}$$

$$V_{out} = V_1 e^{-t/\tau} + V_2$$

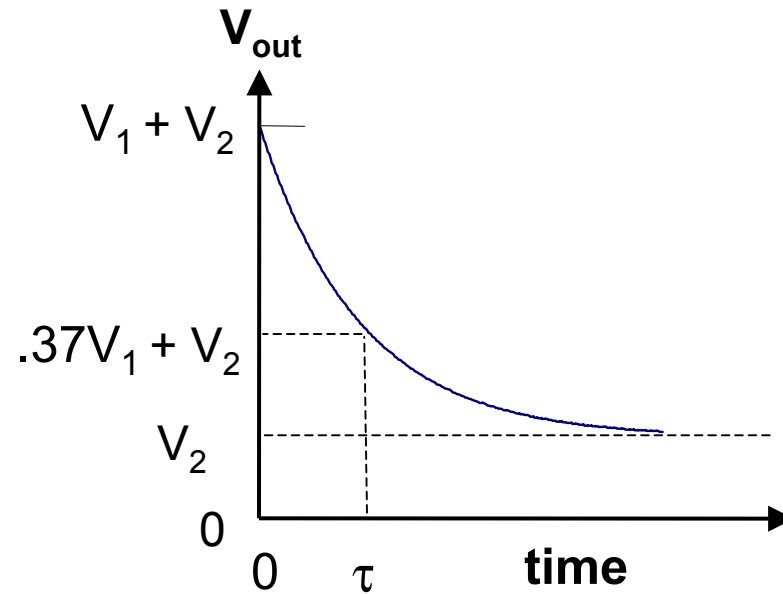

Further Review of simple exponentials. Version Date 9/17/01

Rising Exponential

$$V_{\text{out}} = V_1(1 - e^{-t/\tau}) + V_2$$



Falling Exponential

$$V_{\text{out}} = V_1 e^{-t/\tau} + V_2$$


Both equations can be written in one simple form: $V_{\text{out}} = A + B e^{-t/\tau}$

Initial value ($t=0$): $V_{\text{out}} = A + B$. Final value ($t \gg \tau$): $V_{\text{out}} = A$

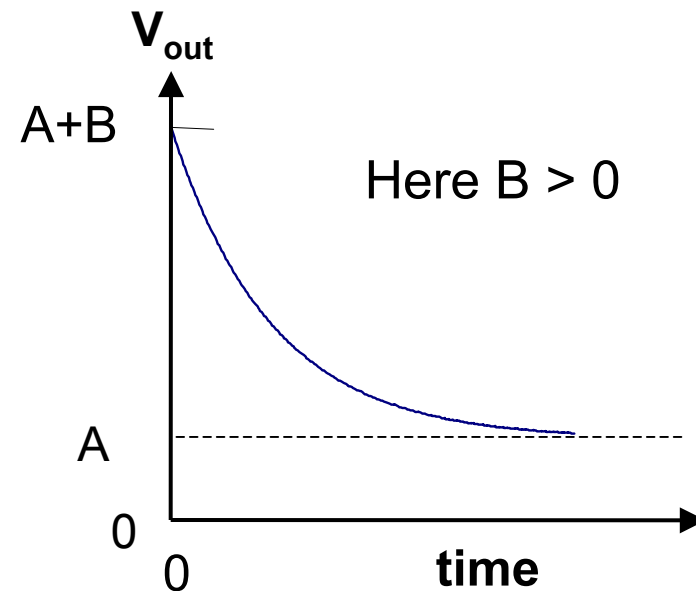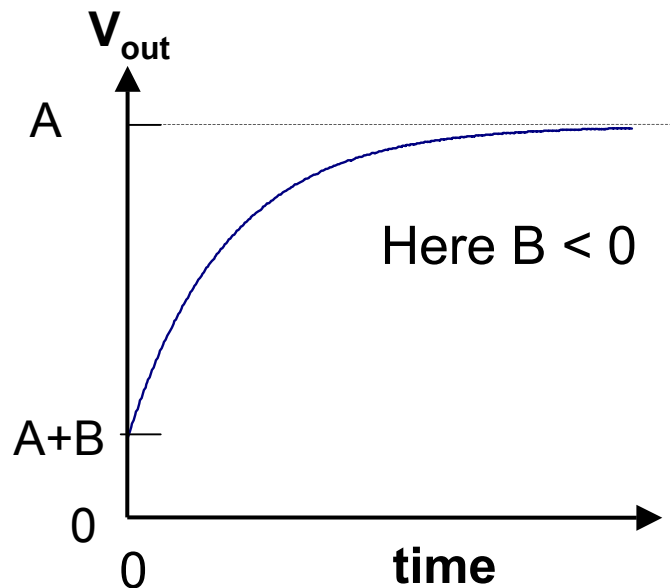Thus: if $B < 0$, rising exponential; if $B > 0$, falling exponential



RC RESPONSE: Case 1 (Rising exponential)

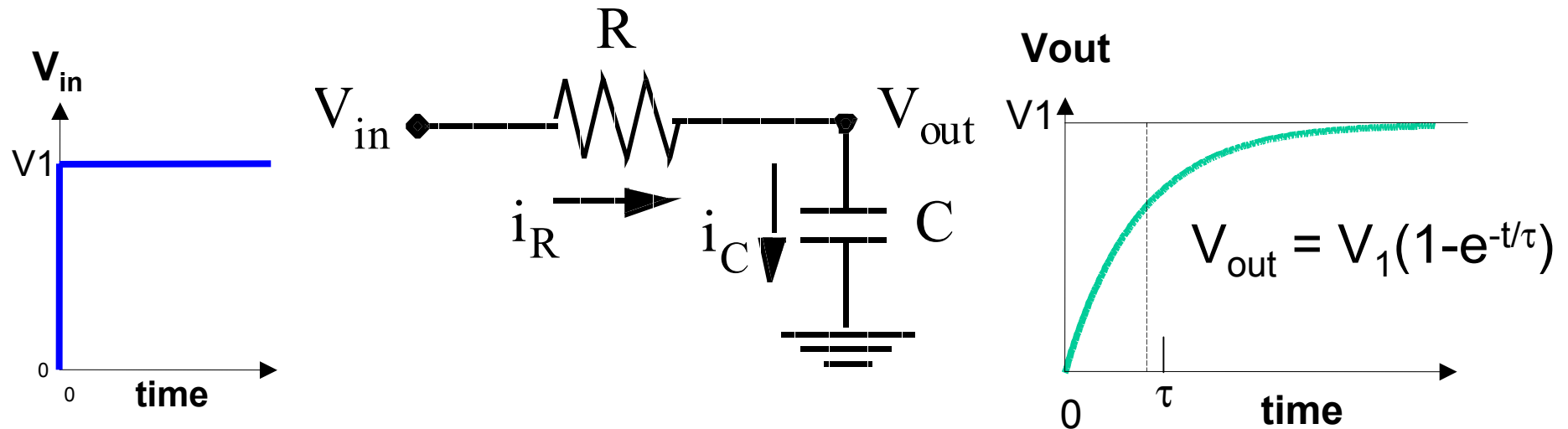

- How is τ related to R and C ?
 - If C is bigger, it takes longer ($\tau \uparrow$).
 - If R is bigger, it takes longer ($\tau \uparrow$).

~~✍~~ Thus, τ is proportional to RC .

☞ In fact, $\tau = RC$!

~~✍~~ Thus, $V_{out} = V_1(1 - e^{-t/\tau})$