

Lecture 7: September 19th, 2001

Charging and Discharging of RC Circuits (Transients)

A) Mathematical Method

B) EE42 Easy Method

C) Logic

D) Generalizations

E) Pulse Distortion

The following slides were
derived from those
prepared by Professor
Oldham for EE40 in Fall 01

Reading:

**Schwarz and Oldham 8.1 +
Handouts**

Charging and discharging in RC Circuits (continued)



Last Time:

We learned that simple the simple RC circuit with a step input has a universal exponential solution of the form:

$$V_{\text{out}} = A + Be^{-t/RC}$$


Example: $R = 1\text{K}$, $C = 1\text{pF}$, V_{in} steps from zero to 10V at $t=0$:

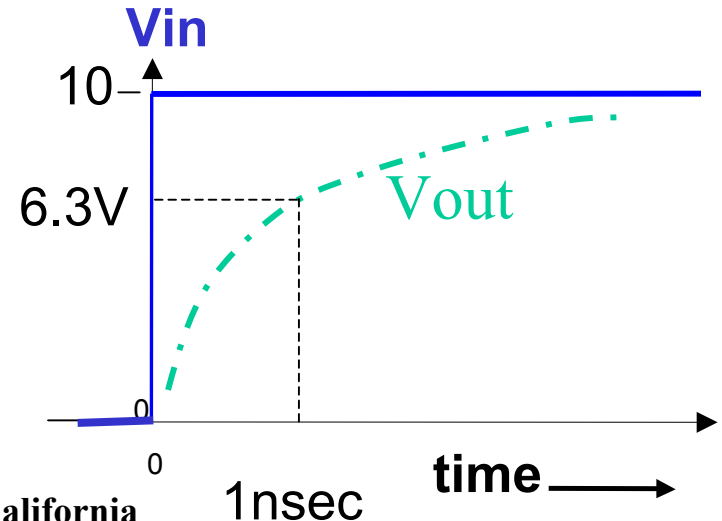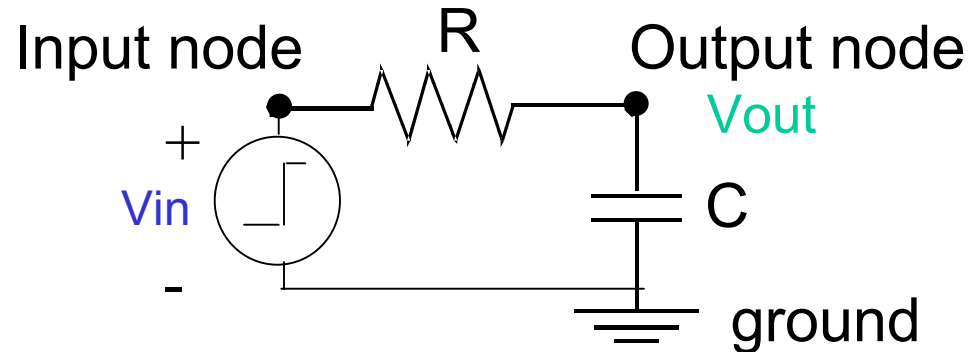- 1) Initial value of V_{out} is 0
- 2) Final value of V_{out} is 10V
- 3) Time constant is 10^{-9} sec
- 4) V_{out} reaches 0.63×10 in 10^{-9} sec



RC RESPONSE: Case 1 (cont.) Version Date 9/19/01

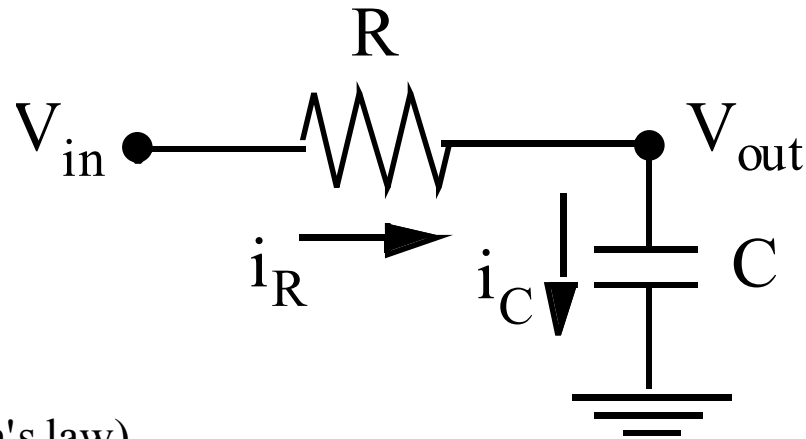Proof that $V_{out} = V_1(1 - e^{-t/RC})$



$$i_R = \frac{V_{in} - V_{out}}{R} \quad (\text{Ohm's law})$$

$$i_C = C \frac{dV_{out}}{dt} \quad (\text{capacitance law})$$

But $i_R = i_C$!

$$\text{Thus, } \frac{V_{in} - V_{out}}{R} = C \frac{dV_{out}}{dt}$$

or

$$\frac{dV_{out}}{dt} = \frac{1}{RC} (V_{in} - V_{out})$$

RC RESPONSE Case 1 (cont.)

Proof that $V_{\text{out}} = V_1(1 - e^{-t/RC})$

We have: $\frac{dV_{\text{out}}}{dt} = \frac{1}{RC}(V_{\text{in}} - V_{\text{out}})$

Proof by substitution:

But $V_{\text{in}} = V_1 = \text{constant}$

$$\frac{dV_{\text{out}}}{dt} \stackrel{?}{=} \frac{1}{RC}(V_{\text{in}} - V_{\text{out}})$$

and $V_{\text{out}} = 0$ at $t = 0^+$

Exp. Term gives the value of τ .

I claim that the solution to this first-order linear differential equation is:

$$\cancel{\frac{V_1}{RC}} e^{-t/RC} \stackrel{?}{=} \frac{1}{RC} (V_1 + \cancel{V_1} (1 - \cancel{e^{-t/RC}}))$$

Constant gives A.

$$V_{\text{out}} = V_1(1 - e^{-t/RC})$$


Initial condition gives A+B.

$$V_{\text{out}} = 0 \text{ at } t = 0^+ \quad \text{OK}$$

RC RESPONSE (cont.)

Version Date 9/19/01

Generalization

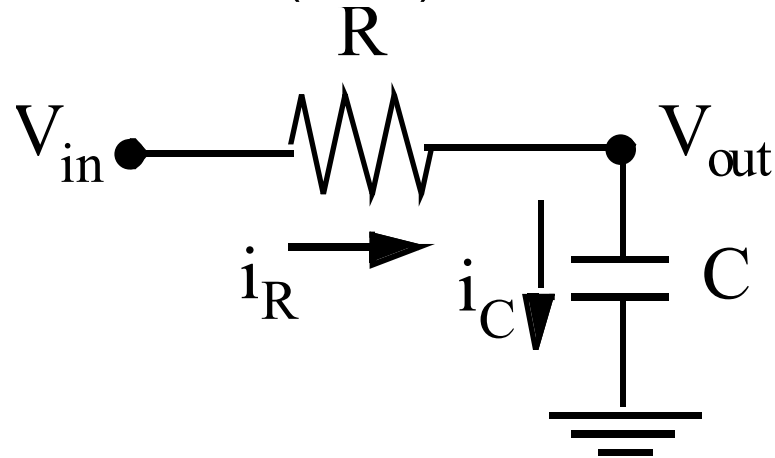

V_{in} switches at $t = 0$; then for any time interval $t > 0$, in which V_{in} is a constant, V_{out} is **always** of the form:

$$V_{out} = A + Be^{-t/\tau}$$

We determine A and B from the initial voltage on C , and the value of V_{in} . Assume V_{in} “switches” at $t=0$ from V_{co} to V_1 :

First, at $t = 0$ $V_C \equiv V_{co}$ initial voltage



➡ Thus, $A + B = V_{co}$

as $t \rightarrow \infty$, $V_C \rightarrow V_1$

➡ Thus, $A = V_1 \Rightarrow B = V_{co} - V_1$

Charging and discharging in RC Circuits

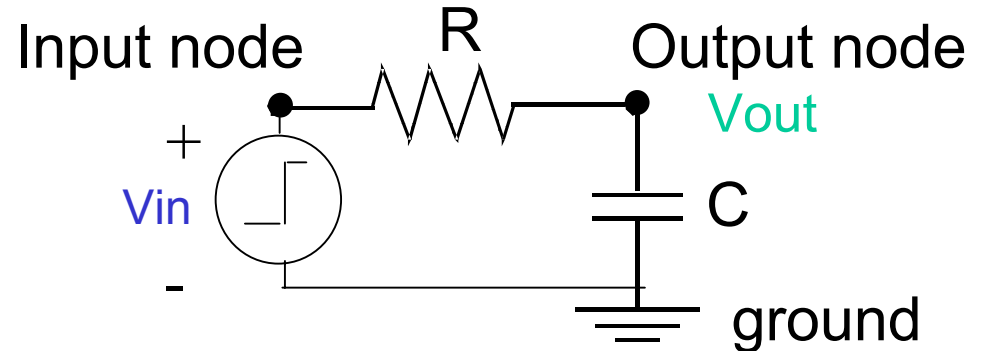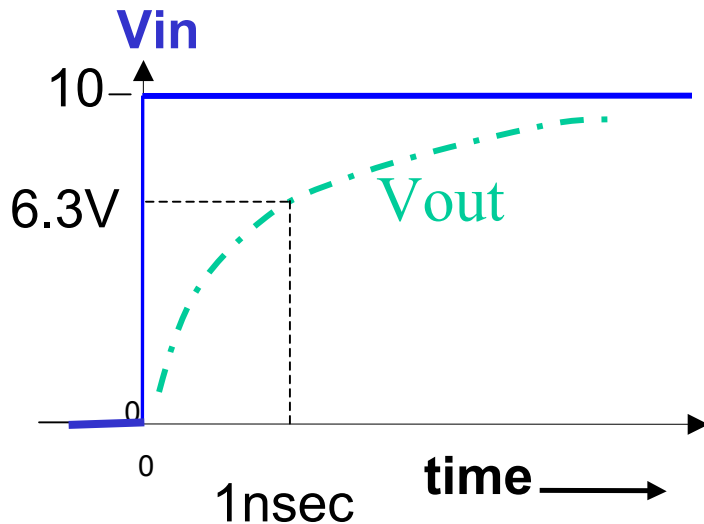For this example: $R = 1\text{K}$, $C = 1\text{pF}$,
 V_{in} steps from zero to 10V at $t=0$:



Note that we found this graph without even using the equation

$$V_{out} = A + Be^{-t/RC} \quad (\text{That is we did not try to evaluate } A \text{ and } B).$$

We simply used the dc solution for $t < 0$ and the dc solution for $t \gg 0$ to get the limits and we used the time constant to get the horizontal scale. We only need the equation to remind us the solution is an exponential. So this will be the basis of our **easy method**.

Charging and discharging in RC Circuits

(The official EE40/EE42 Easy Method)

01

Method of solving for any node voltage in a single capacitor circuit.

1) Simplify the circuit so it looks like one resistor, a source, and a capacitor (it will take another two weeks to learn all the tricks to do this.) But then the circuit looks like this:


2) The time constant of the transient is $\tau = RC$.

3) Solve the dc problem for the capacitor voltage before the transient. This is the starting value (initial value) for the transient voltage.

4) Solve the dc problem for the capacitor voltage after the transient is over. This is the asymptotic value.

5) Sketch the Transient. It is 63% complete after one time constant.

6) Write the equation by inspection.

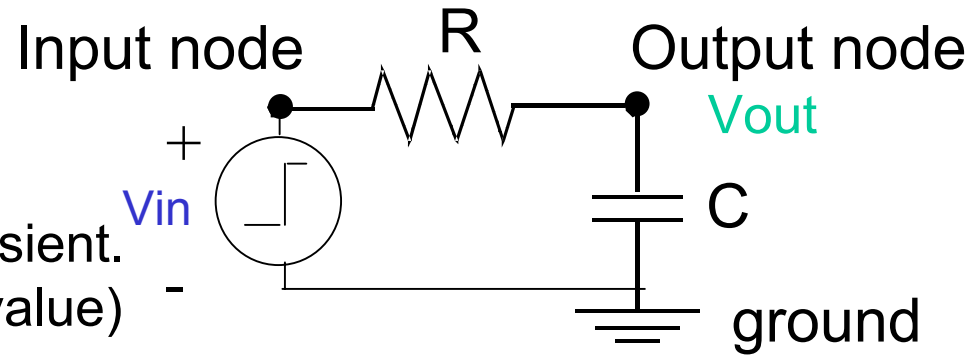


Charging and discharging in RC Circuits

(Example 1 of the EE42 Easy Method)


01

Find $V_c(t)$ for the following circuit: (input switches from 2V to -1V at $t = 0$)


1) Simplify the circuit :

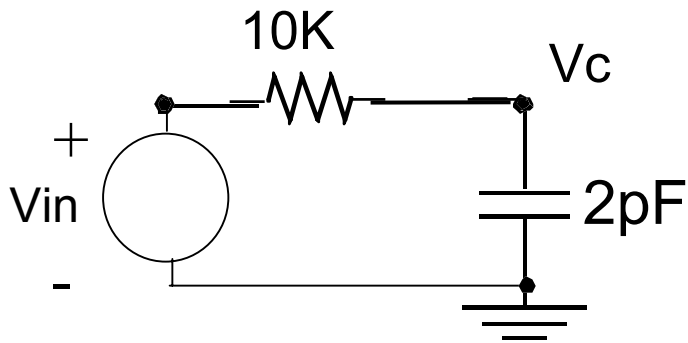

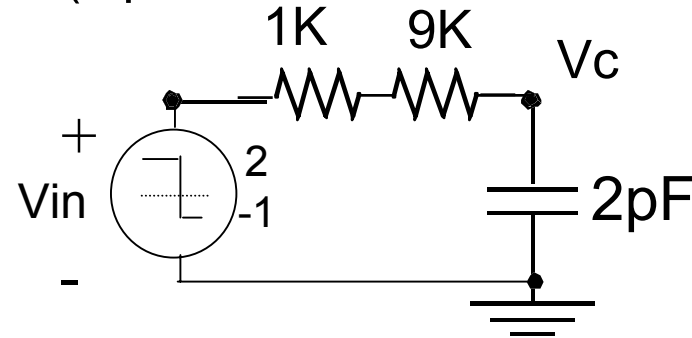
2) The time constant of the transient is $\tau = RC = 20\text{nsec}$



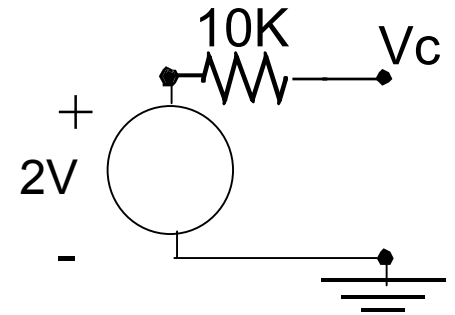3) Before the transient $V_{in} = 2\text{V}$ so $V_c = 2\text{V}$



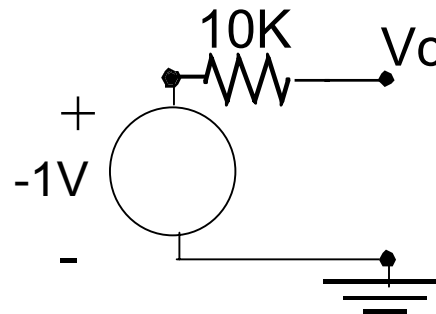4) After the transient is over $V_{in} = -1\text{V}$ so $V_c = -1\text{V}$. This is the asymptotic value.



Charging and discharging in RC Circuits


(Example 1 of the EE42 Easy Method)

01


Find $V_c(t)$ for the following circuit: (input switches from 2V to -1V at $t = 0$)

We have : Initial value of V_c is 2V,
final value is -1V and $\tau = 20\text{nsec}$

5) Sketch $V_c(t)$:

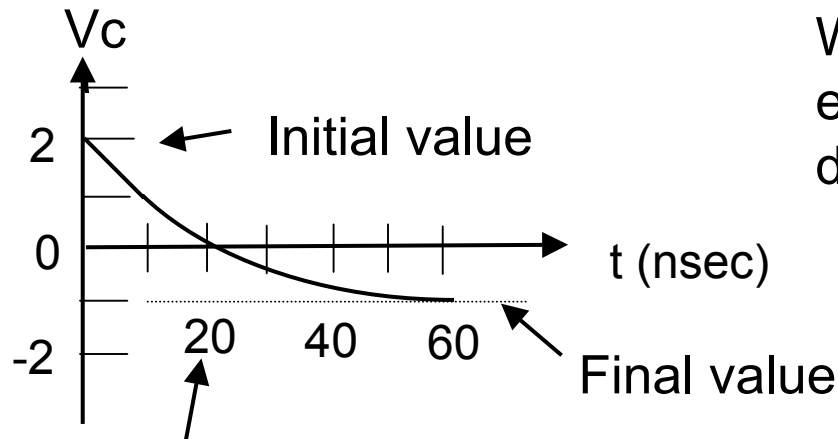

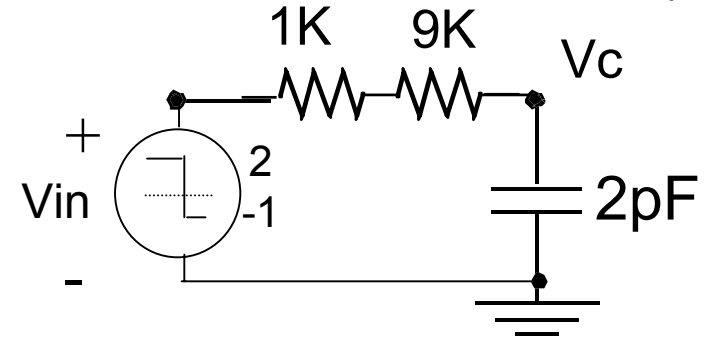37% of transient
remaining at one
time constant







What is the equation for an exponential beginning at 2V, decaying to -1V, with $\tau = 20\text{nsec}$?

$$V_c(t) = -1 + 3e^{-t/\tau}$$


OUR METHOD AVOIDS ALL MATH!

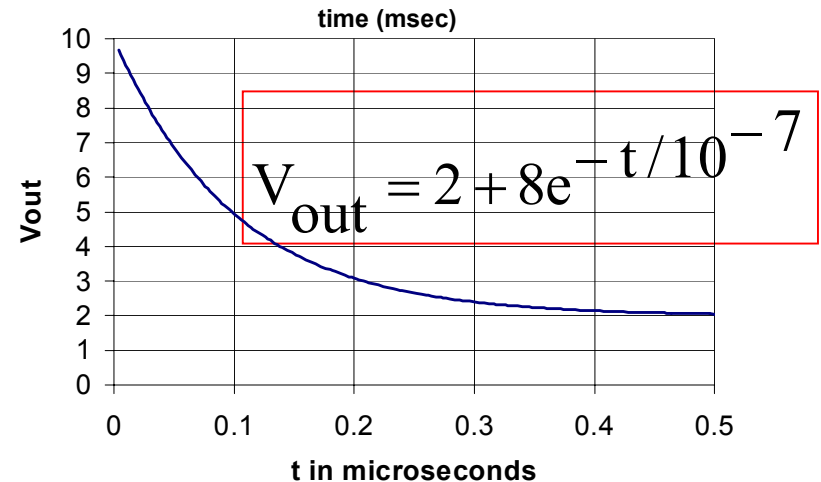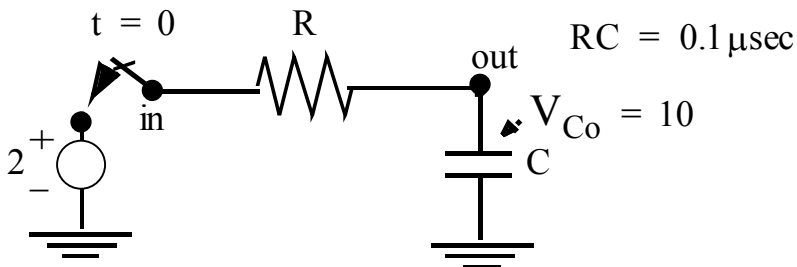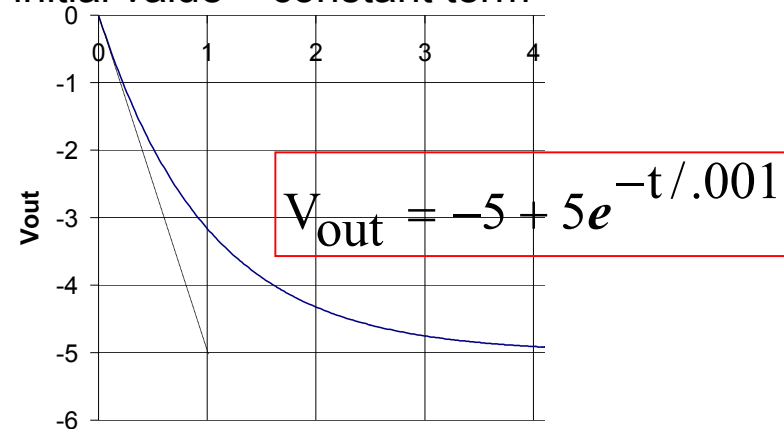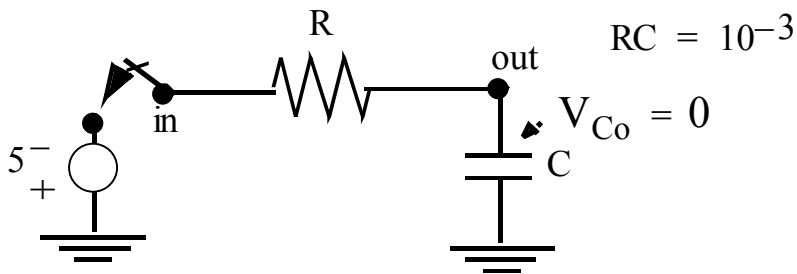- ★ Sketch waveform (starts at V_{Co} , ends asymptotically at V_1 , initial slope intersects at $t = RC$ or transient is 63% complete at $t=RC$)
- ★ Write equation: **2a.** constant term $A = \text{limit of } V \text{ as } t \rightarrow \infty$
2b. pre-exponent $B = \text{initial value} - \text{constant term}$



4 Examples


Version Date 9/19/01

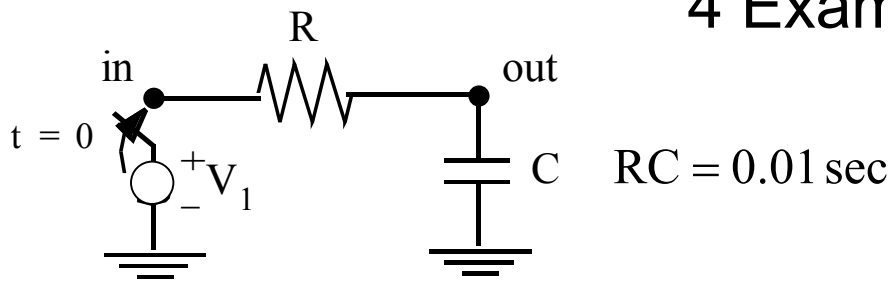


$$V_{out} = A + Be^{-t/RC}$$

$V_{C0} = 0$



$V_1 = 10$

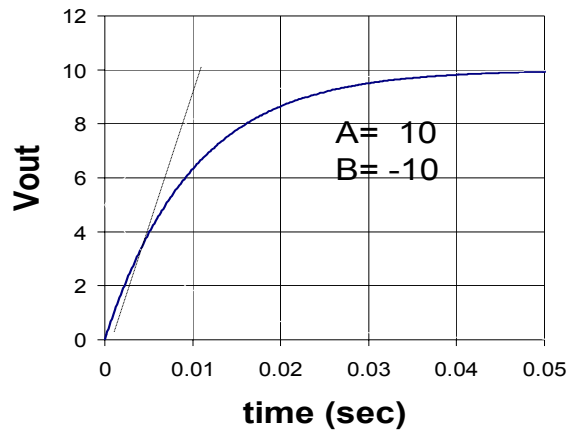

$V_{C0} = 5\text{ V}$

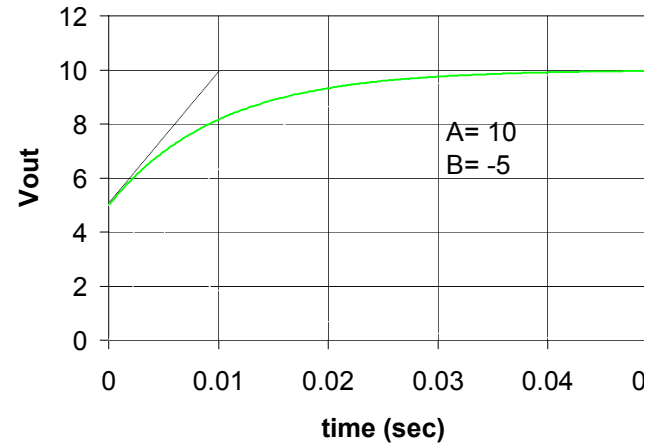

$V_1 = 0$

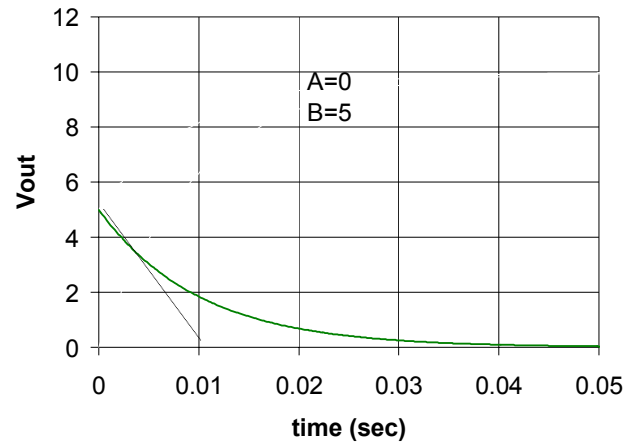
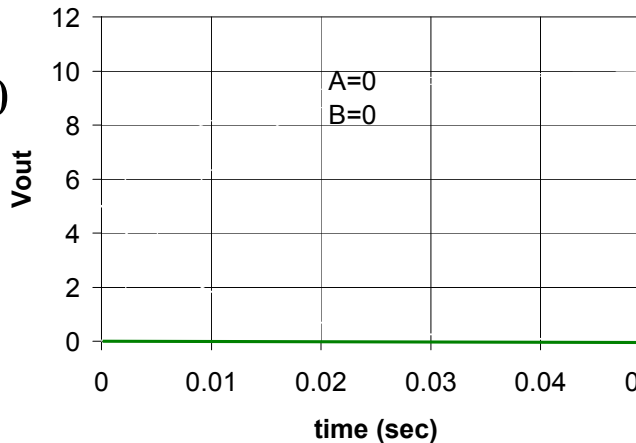


COMPLICATION: Event Happens at $t \neq 0$

(Solution: Shift reference time to time of event)

Version Date 9/19/01

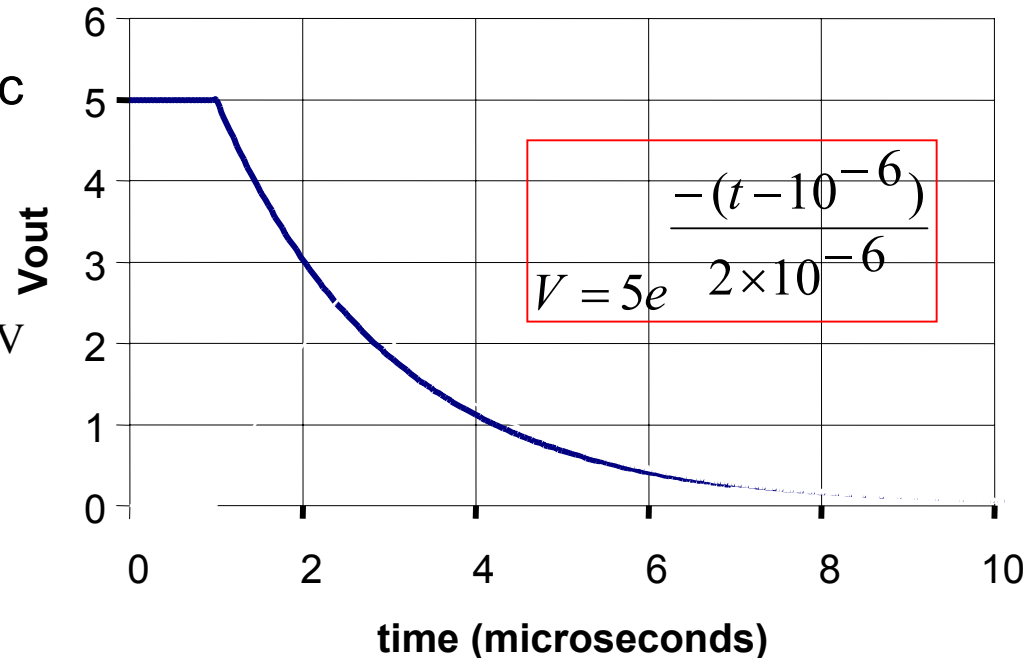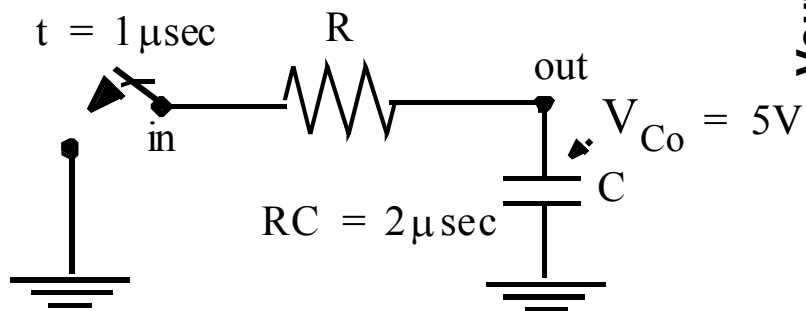Example: switch closes at $1\mu\text{sec}$





We shift the time axis here by one microsecond, i.e. imagine a new time coordinate $t^* = t - 1\mu\text{sec}$ so that in the new time domain, the event happens at $t^* = 0$ and our standard solution applies. Of course we replace t^* by $t - 1\mu\text{sec}$ in the equations and plots. Thus instead of $t^* = 0$ we have $t = 1\mu\text{sec}$, etc.

FINAL EXAMPLE

Your photo flash charges a $1000\mu\text{F}$ capacitor from a 50V source through a 2K resistor. If the capacitor is initially uncharged, how long must you wait for it to reach 95% charged (47.5 V)?

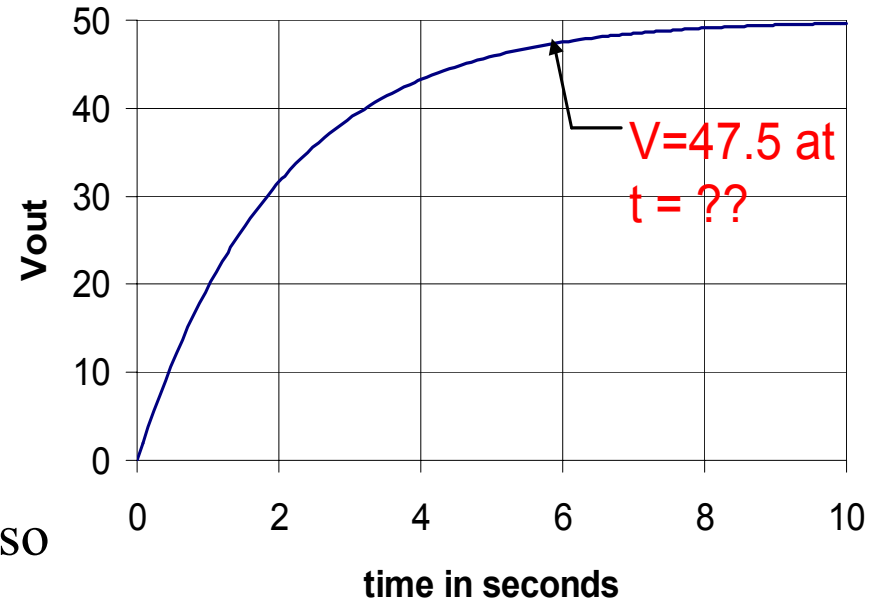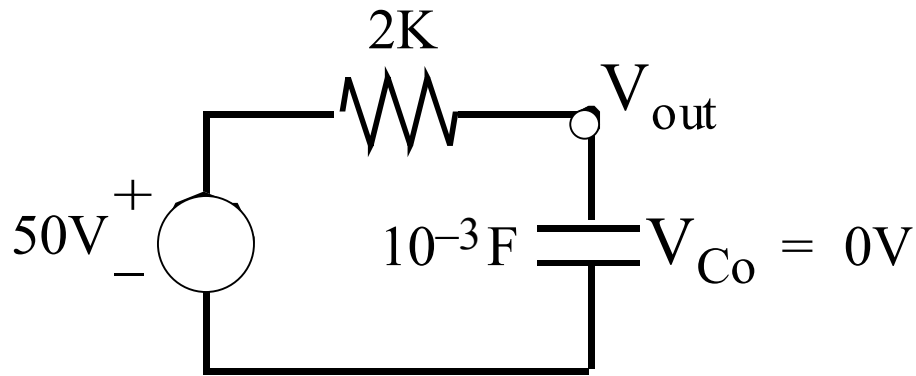Solution: $RC = 2\text{K} \times 10^{-3} = 2\text{ sec}$



By inspection: $V_o = 50 - 50e^{-t/2}$, so

$$47.5 = 50(1 - e^{-\frac{t_x}{2}}) \Rightarrow e^{-\frac{t_x}{2}} = \left(1 - \frac{47.5}{50}\right) \Rightarrow \boxed{t_x = 6\text{ sec}}$$


Generalizations

- Switching of circuits with multiple resistors and sources
 - use R_T seen looking back into the circuit from the terminals of the capacitor **after the switching changes conditions.**
- **Inductor** circuits use $\tau = L / R_T$

Pulse Distortion

Version Date 9/19/01

An example of RC analysis

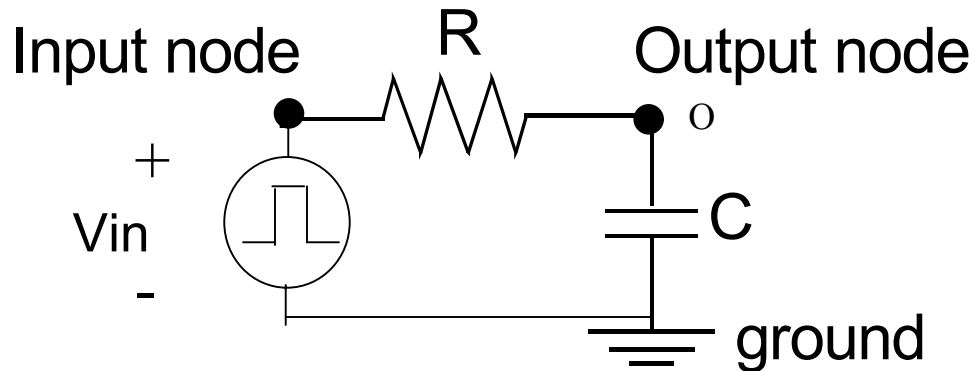

Rule: The pulse width must be **wider** than RC to avoid severe pulse distortion.

Example: Lets find the shape of the output pulse for pulse width of 0.1, 1, and 10 RC


Method: Use 5V pulse height. Let $RC = 1\mu\text{sec}$. Replace voltage source with a switch which shorts the input to ground for $t < 0$, switches to 5V at $t = 0$, and switches back to ground at $t = 0.1\mu\text{sec}$, or $t = 1\mu\text{sec}$, $t = 10\mu\text{sec}$.

Thus we have two problems: #1: V_{out} rising from zero and #2: V_{out} falling back toward zero. **Cascade solutions!**

PULSE: Output is Rising exponential then Falling exponential

Version Date 9/19/01

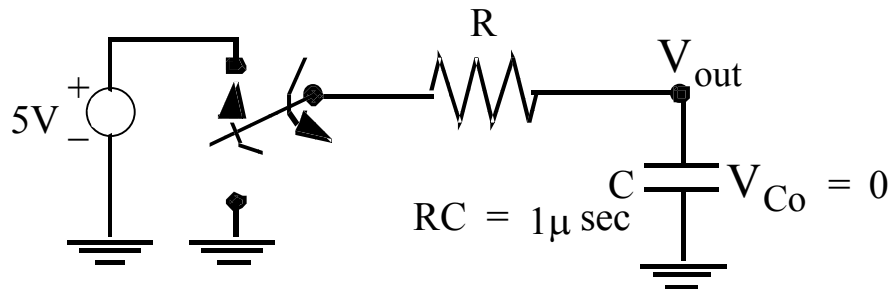Example: Switch rises at $t = 0$, falls at $t = 0.1, 1$ or $10 \mu\text{sec}$ (Do $1 \mu\text{sec}$ case)



Solution: for $RC = 1 \mu\text{sec}$:
during the first rise V obeys:


$$V = 5 \left[1 - e^{-\frac{t}{10^{-6}}} \right]$$

Thus at $t = 1 \mu\text{sec}$, rising voltage reaches

$$5 \left[1 - e^{-1} \right] = 3.16 \text{V}$$

Now starting at $1 \mu\text{sec}$ we are discharging the capacitor so the form is a falling exponential with initial value 3.16V :


What is equation?

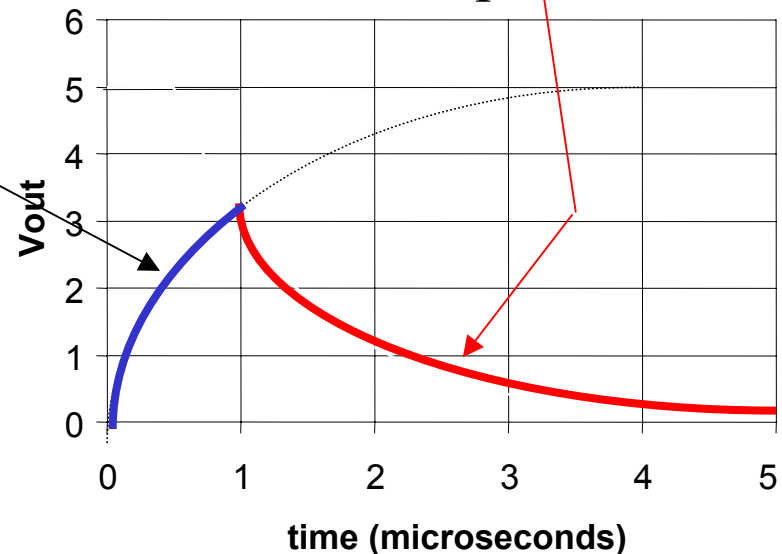

PULSE DISTORTION – other cases

Version Date 9/19/01

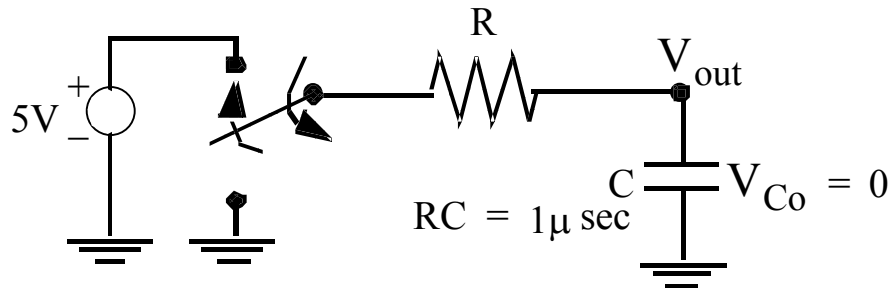Switch rises at $t = 0$, falls at $t = 0.1$ or $10 \mu\text{sec}$ (i.e. 0.1 or $10 \mu\text{sec}$ pulse widths)





Solve for V_{out} in the other two cases (0.1 or $10 \mu\text{sec}$) just as for $1 \mu\text{sec}$

At $t = 0.1 \mu\text{sec}$ the output has only risen to $0.5V$!

Whereas for $10 \mu\text{sec}$ pulse width, output reaches to within 0.995% of $5V$.


You need to verify the numbers!

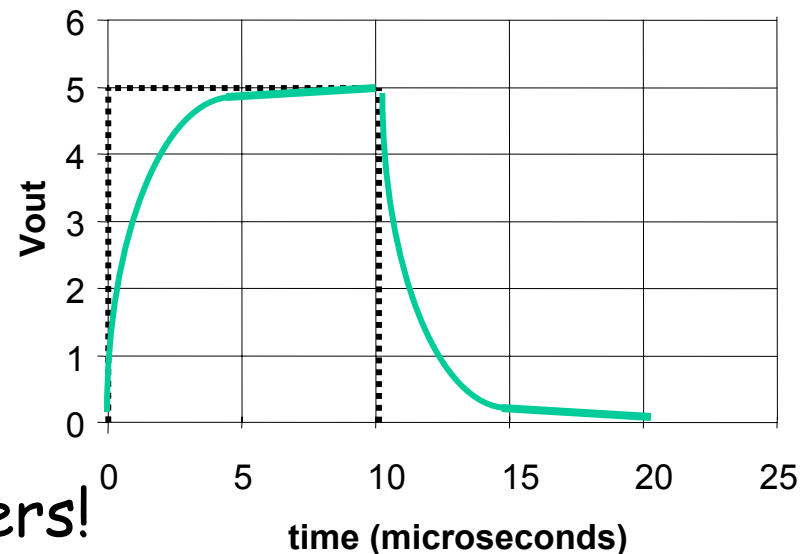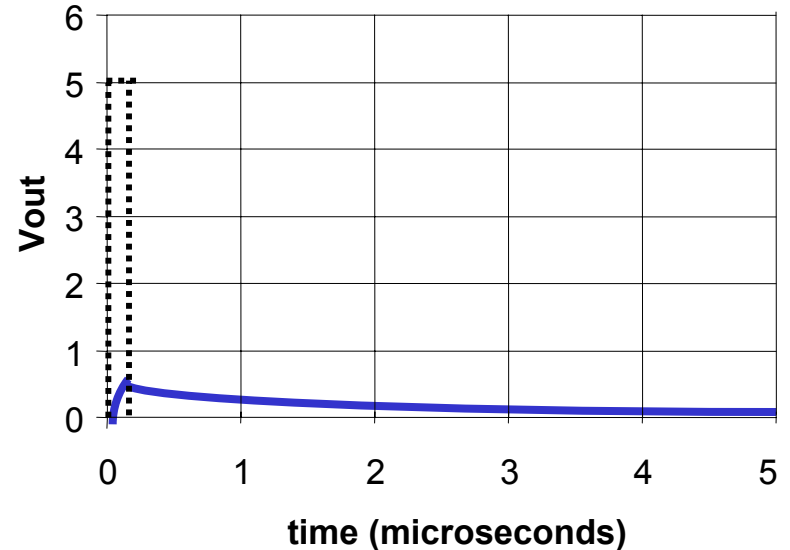


Pulse Distortion

Version Date 9/19/01


An example of RC analysis

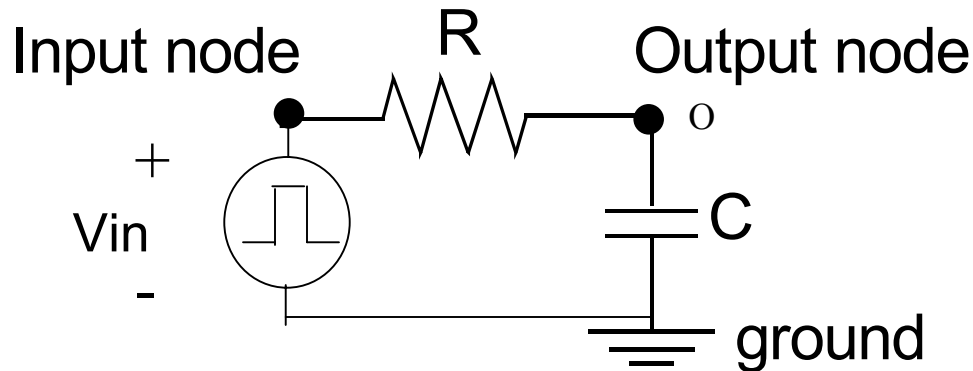

$$PW = 10RC$$

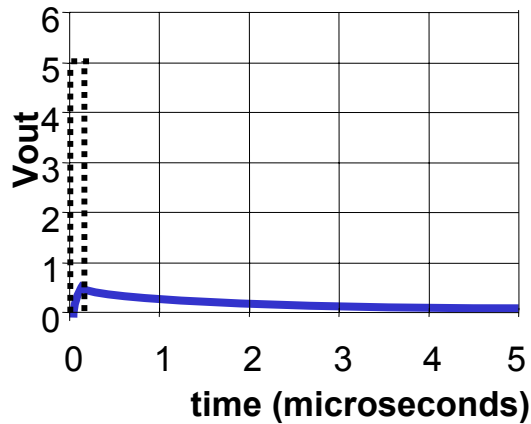

$$PW = RC$$

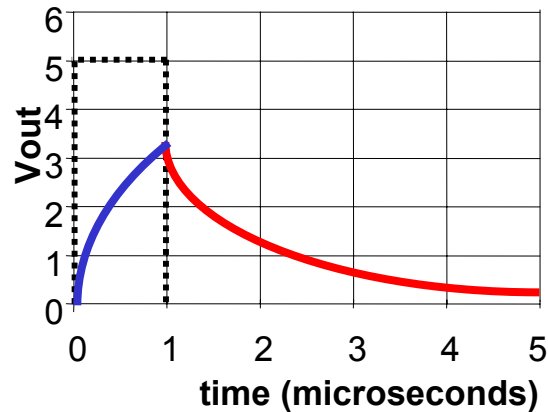

$$PW = 0.1RC$$

