

Lecture 14: October 17, 2001

Op-Amp Circuits and Comparators

A) Cascade Op-Amps

B) Integration/Differentiation Op-Amps

C) I vs. V of Op-Amps – Source Limits

D) Comparator Circuits


E) D to A Converters

Reading:

The following slides were derived from those prepared by Professor Oldham For EE 40 in Fall 01

Schwarz and Oldham 4.3-4.4 (light on non-ideal) and comparator viewgraphs

CASCADE OP-AMP CIRCUITS

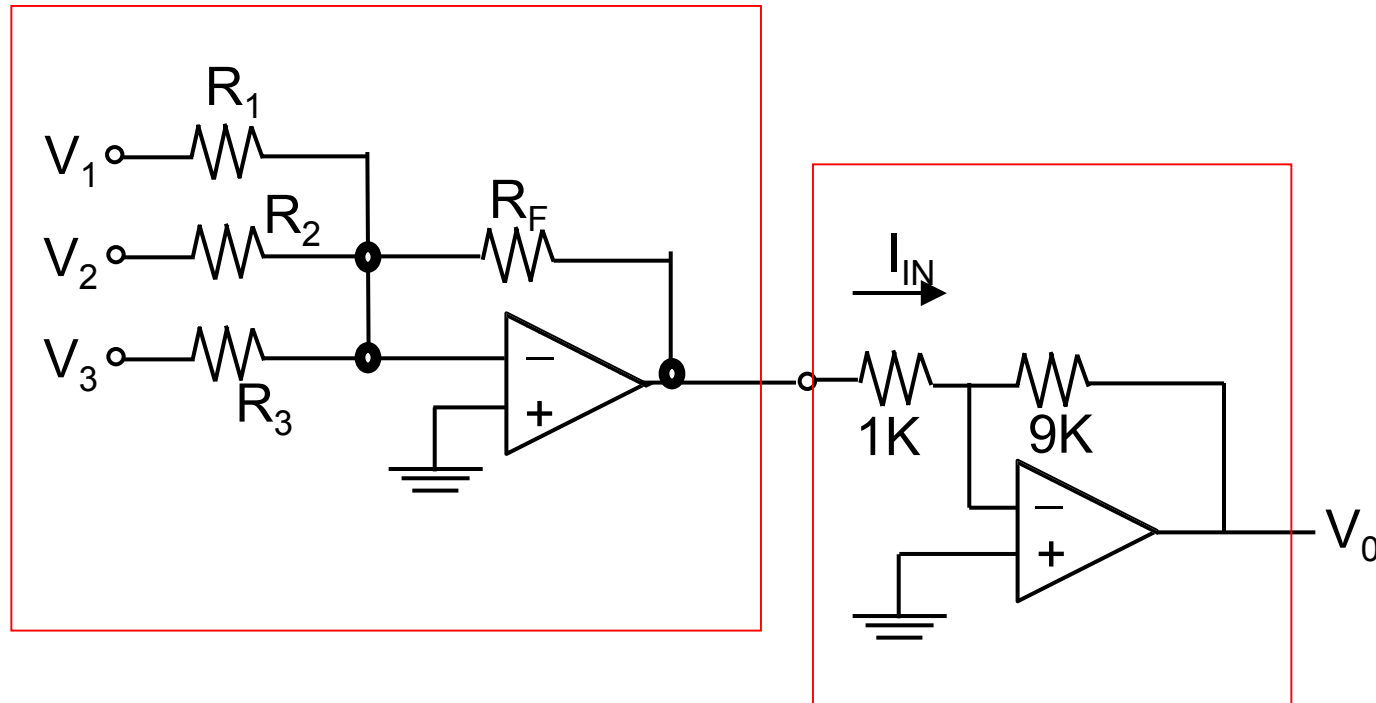


How do you get started on finding V_O ?

Hint: Identify Stages

Hint: I_{IN} does not affect V_{O1}

See the further examples of op-amp circuits in the reader

INTEGRATING OP-AMP

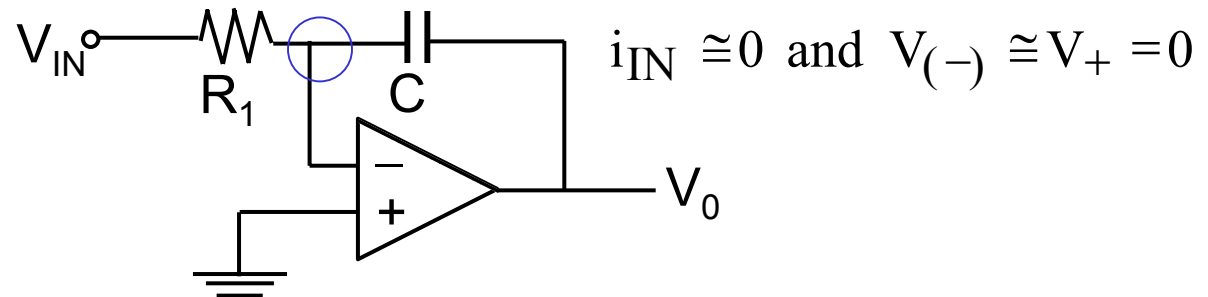


How do you get started on finding V_O ?

Hint: $i_{IN} \cong 0$ and $V_{(-)} \cong V_{+} = 0$


Hint: **KCL at V_- node with $I_{IN-} = 0$**

OP-AMP I-V CHARACTERISTICS WITH RAILS

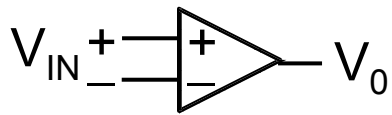

- Circuit model (ideal op-amp) gives the essential linear part
- But V_0 cannot rise above some physical voltage related to the positive power supply V_{CC} ("upper rail") $V_0 < V_{+RAIL}$
- And V_0 cannot go below most negative power supply, V_{EE} i.e., limited by lower "rail" $V_0 > V_{-RAIL}$

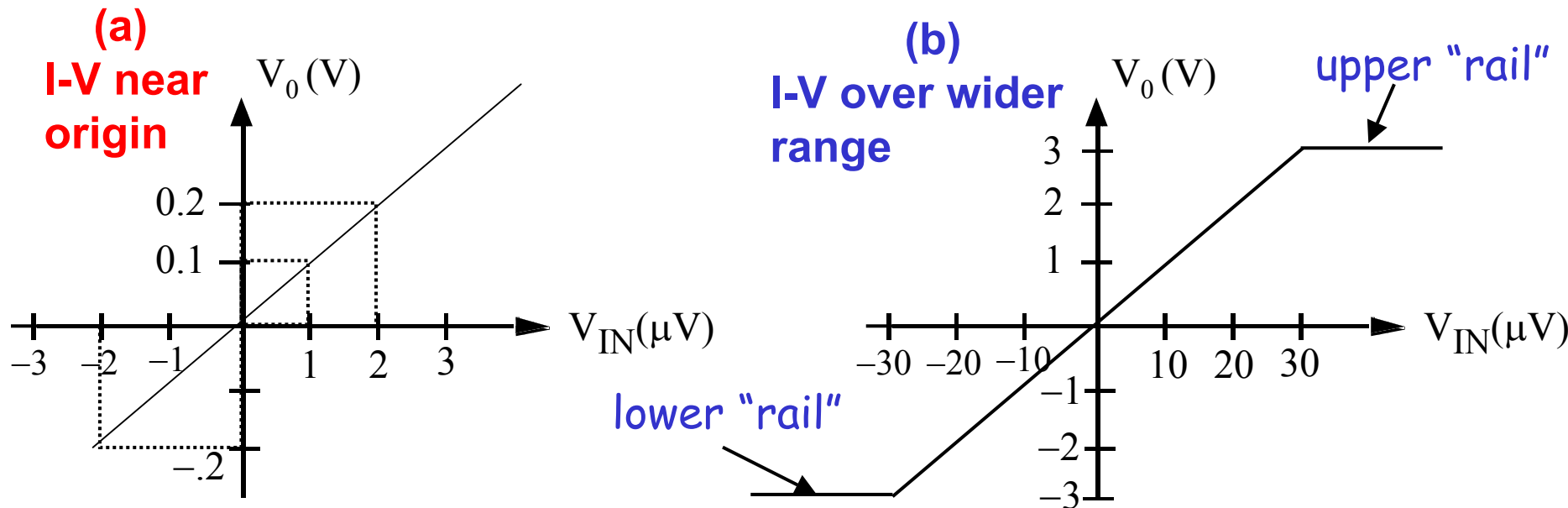Example: Amplifier with gain of 10^5 , with max V_0 of 3V and min V_0 of -3V.




OP-AMP I-V CHARACTERISTICS WITH RAILS (cont.)

Example: Amplifier with gain of 10^5 , with upper rail of 3V and lower rail of -3V. We plot the V_0 vs V_{IN} characteristics on two different scales



(c)

Same V_0 vs V_{IN} over even wider range

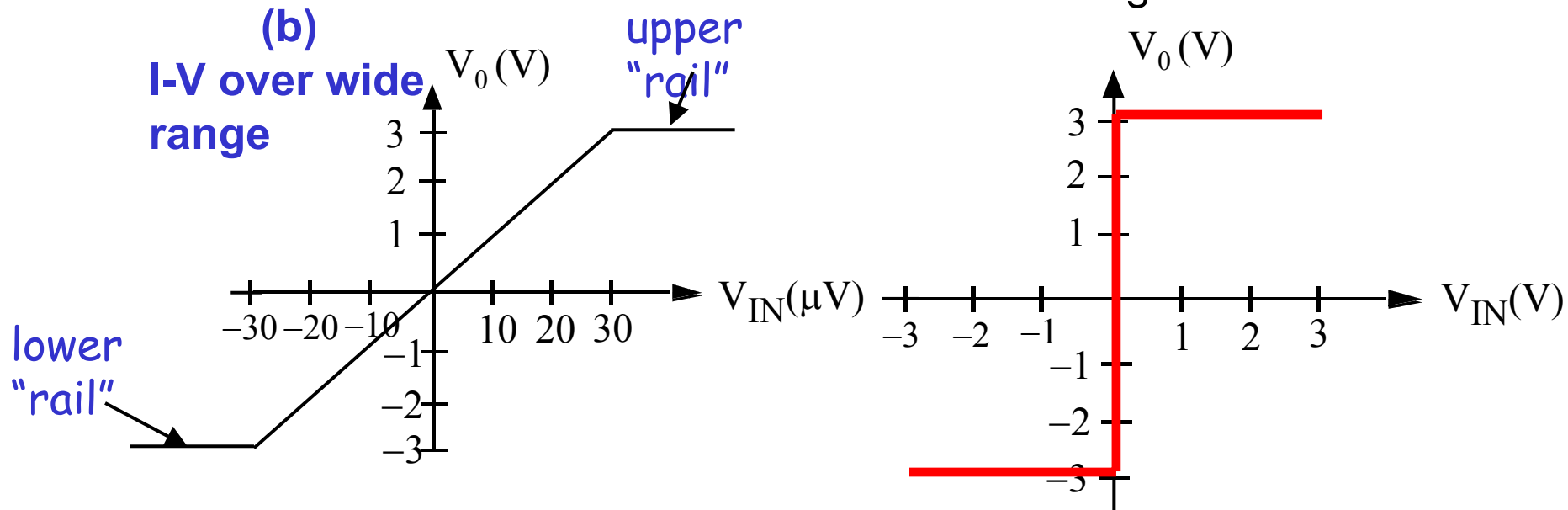

SIMPLE A/D CONVERTER

I-V with equal X and Y axes

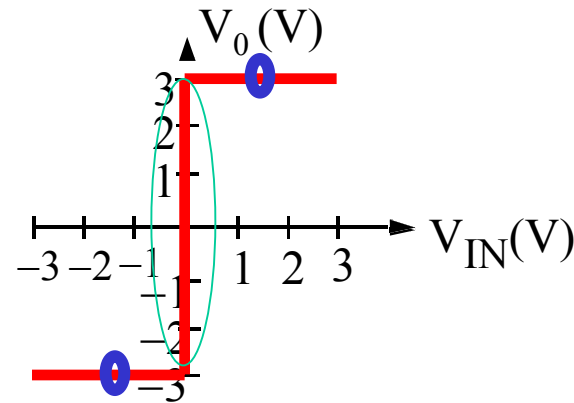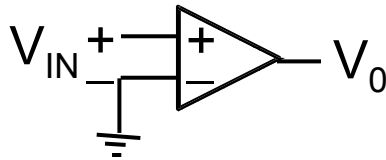


Note:


- (a) displays **linear amplifier behavior** ($|V_{IN}| < 30 \mu\text{V}$) and stops at rails
- (b) shows **comparator decision function** (1 bit A/D converter centered at $V_{IN} = 0$) where lower rail = logic “0” and upper rail = logic “1”

OP-AMP USE AS COMPARATOR (A/D) MODE

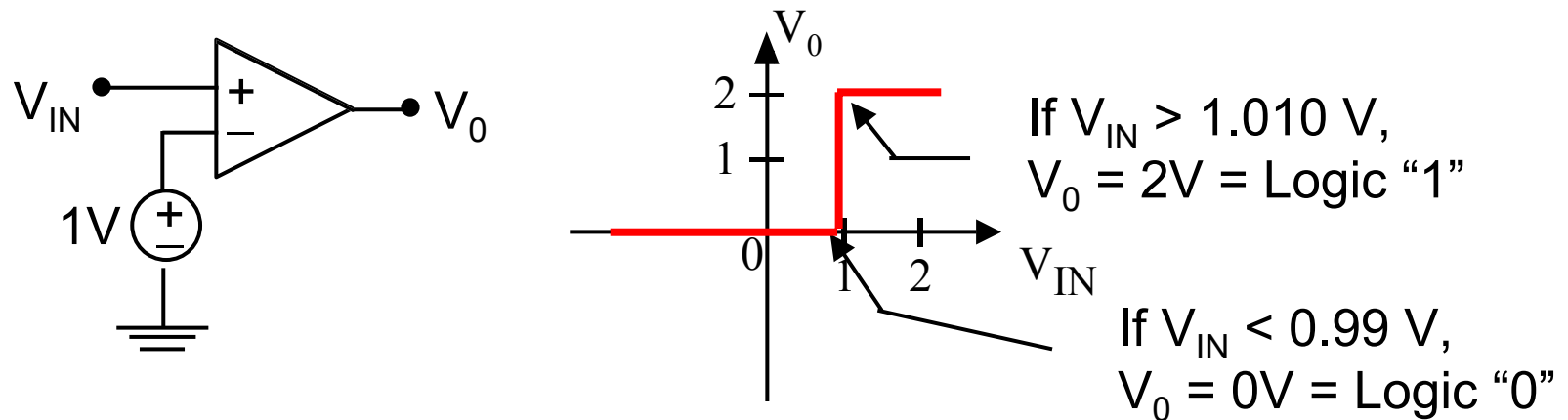
Simple comparator with threshold at 1V. Design lower rail at 0V and upper rail at 2V (logic "1"). $A = \text{large}$ (e.g. 10^2 to 10^5)



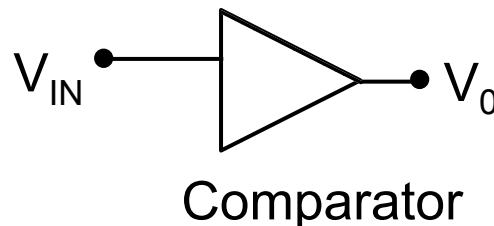NOTE: The actual diagram of a comparator would not show an amplifier with "offset" power supply as above. It would be a simple triangle, perhaps with the threshold level (here 1V) specified.




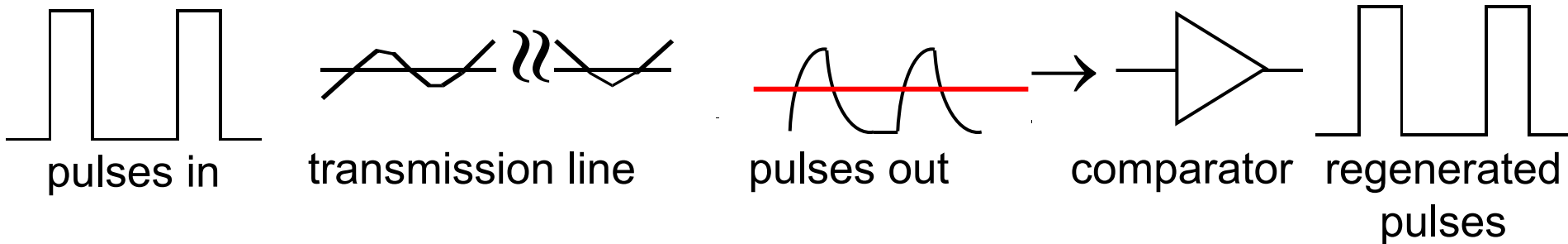ONE-BIT A/D CONVERSION REQUIRED IN DIGITAL SYSTEMS



As we saw, we set comparator **threshold** at a suitable value (e.g., halfway between rails) and comparator output goes to +rail if $V_{IN} > V_{THRESHOLD}$ and to -rail if $V_{IN} < V_{THRESHOLD}$.

What would this circuit do?

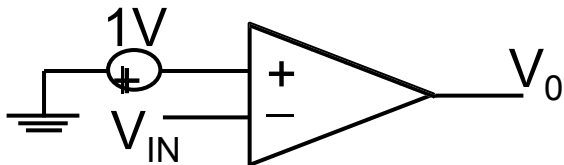


The **inverse** pulse shaped function is generated by applying the input voltage to V_- and setting V_+ to the threshold voltage.

D/A CONVERSION

Version Date 10/16/01

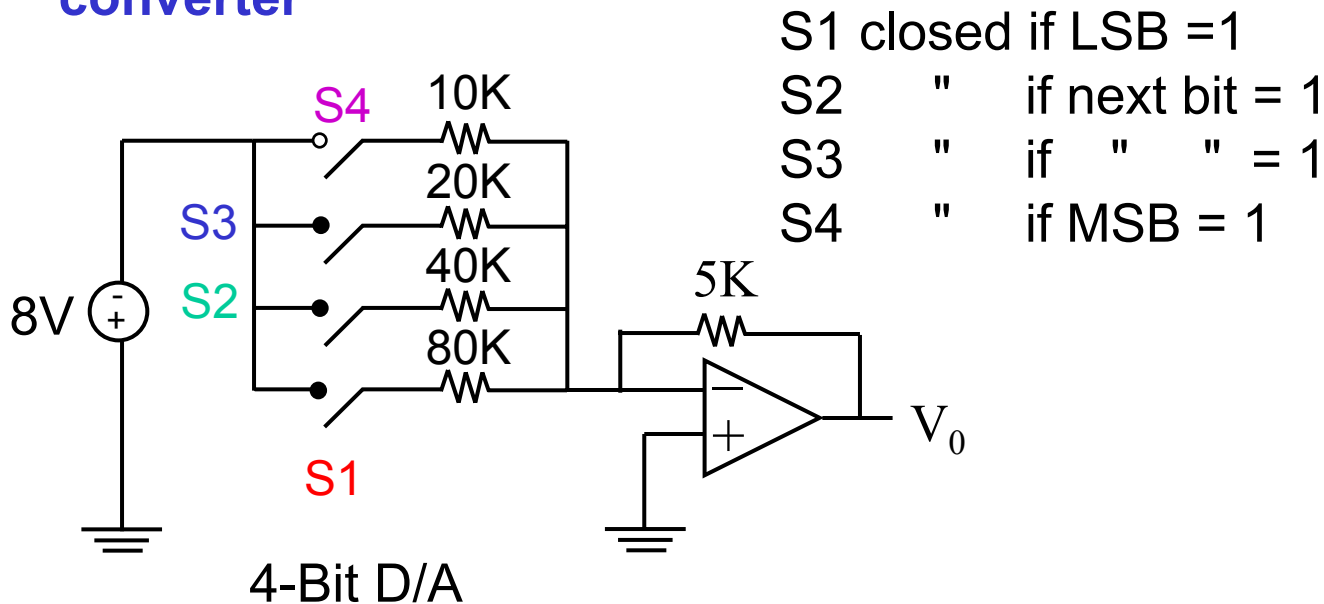Example: Digital representation of sound to analog
(so you can hear it!) → D/A conversion

The summing junction op-amp provides a simple means of D/A conversion via **weighted-adder D/A converter**



Another way (not shown) is to sum **charges** instead of current with capacitor networks

Binary number	Analog output (volts)
0 0 0 0	0
0 0 0 1	.5
0 0 1 0	1
0 0 1 1	1.5
0 1 0 0	2
0 1 0 1	2.5
0 1 1 0	3
0 1 1 1	3.5
1 0 0 0	4
1 0 0 1	4.5
1 0 1 0	5
1 0 1 1	5.5
1 1 0 0	6
1 1 0 1	6.5
1 1 1 0	7
1 1 1 1	7.5

↑ ↑
MSB LSB

CHARACTERISTIC OF A 4-BIT DAC

