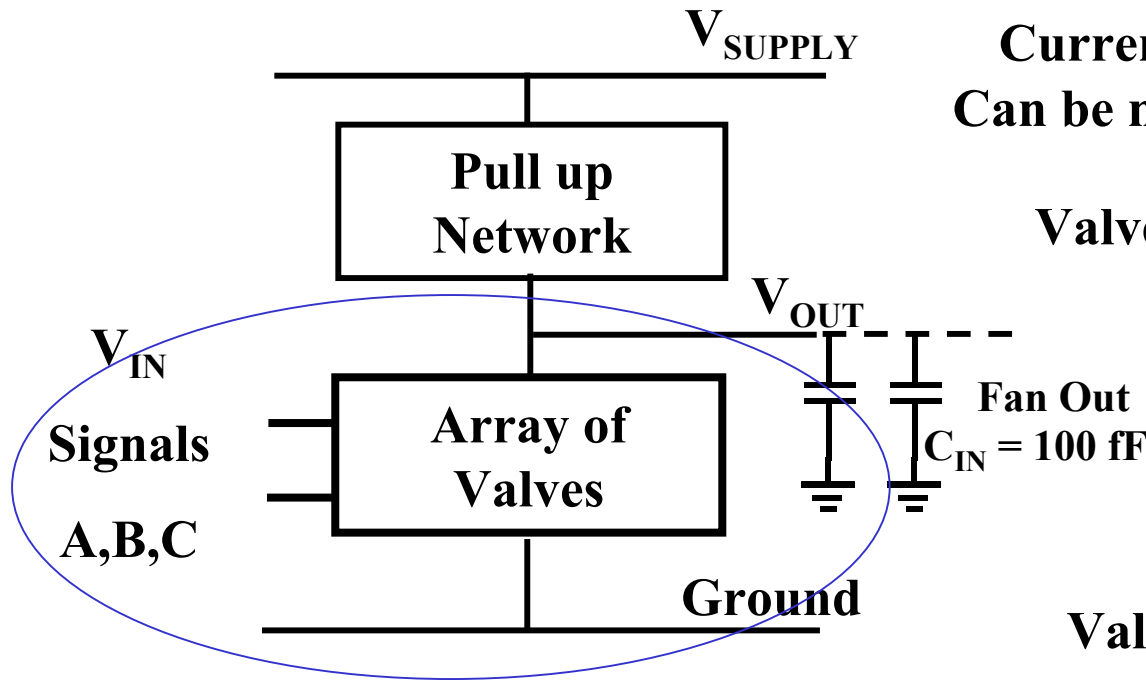


Lecture 15: October 22, 2001**Reminder:****20 Minute Quiz Wed. Oct. 31 in class****2nd Midterm Wed. Nov. 7 in class****Logic with a State Dependent Device****A) State Dependent Device I_{OUT} vs. V_{OUT}** **B) Load Line Analysis for Logic Levels****C) Voltage Transfer Characteristics****VTC = plot of V_{OUT} vs. V_{IN}** **D) 42 Pull Down (42PD) Device and Logic****Reading:****Schwarz and Oldham pp. 593-595, 604-606****(read for graphs and not physics)**


Logic Gates – How are they built in practice?




Current flows when V_{IN} is high
 Can be modeled by a $10k\Omega$ resistor



Valves in Series => NAND

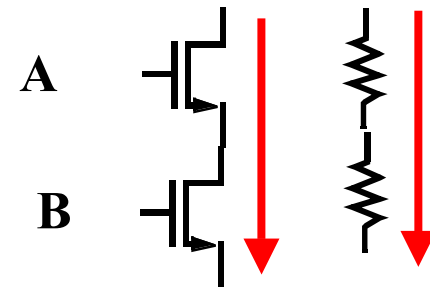

Valves in Parallel => NOR

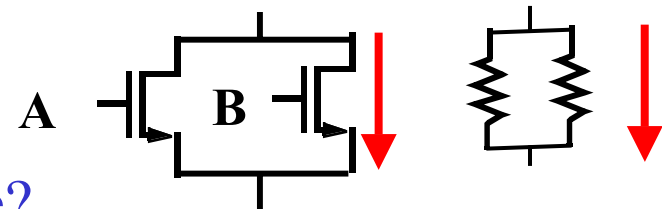

What goes in this box?

How does it affect digital performance?


Digital Logic from State-Dependent Three-Terminal Devices

Three-terminal devices such as MOS transistors have characteristics (such as I_{OUT} vs. V_{OUT} curves) on the output side that can be programmed by changing signals on the input side (such as the input voltage).


The input can thus be viewed as changing or programming the 'State' of the output of the device.

Three-terminal devices whose 'State' can be programmed can be used to make digital logic devices for computers that respond to input signals.

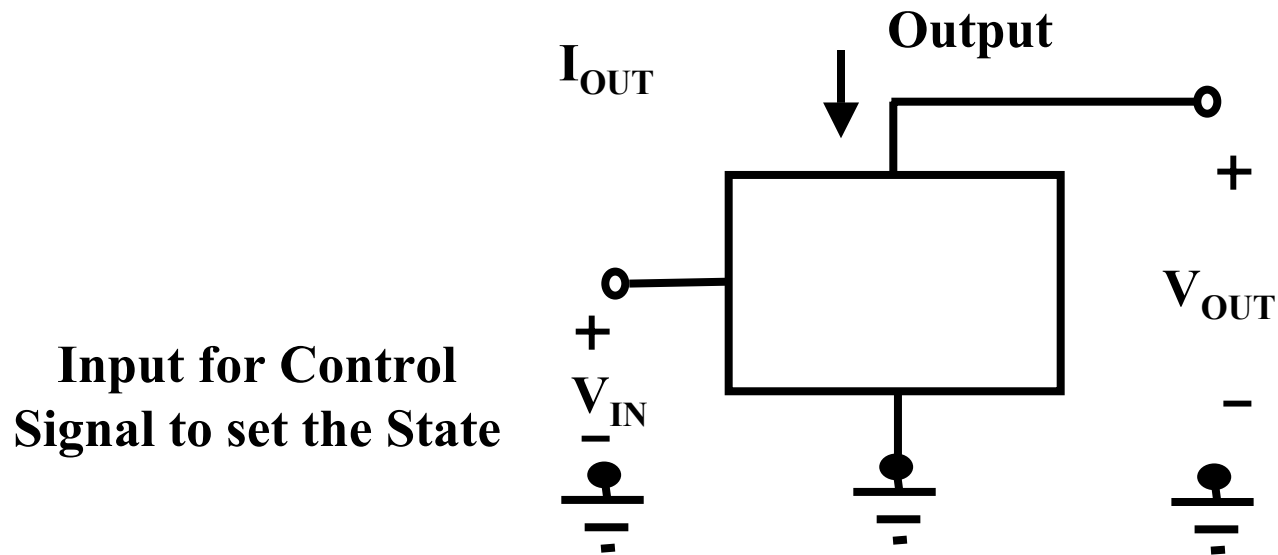
State-Dependent Three-Terminal Device Element



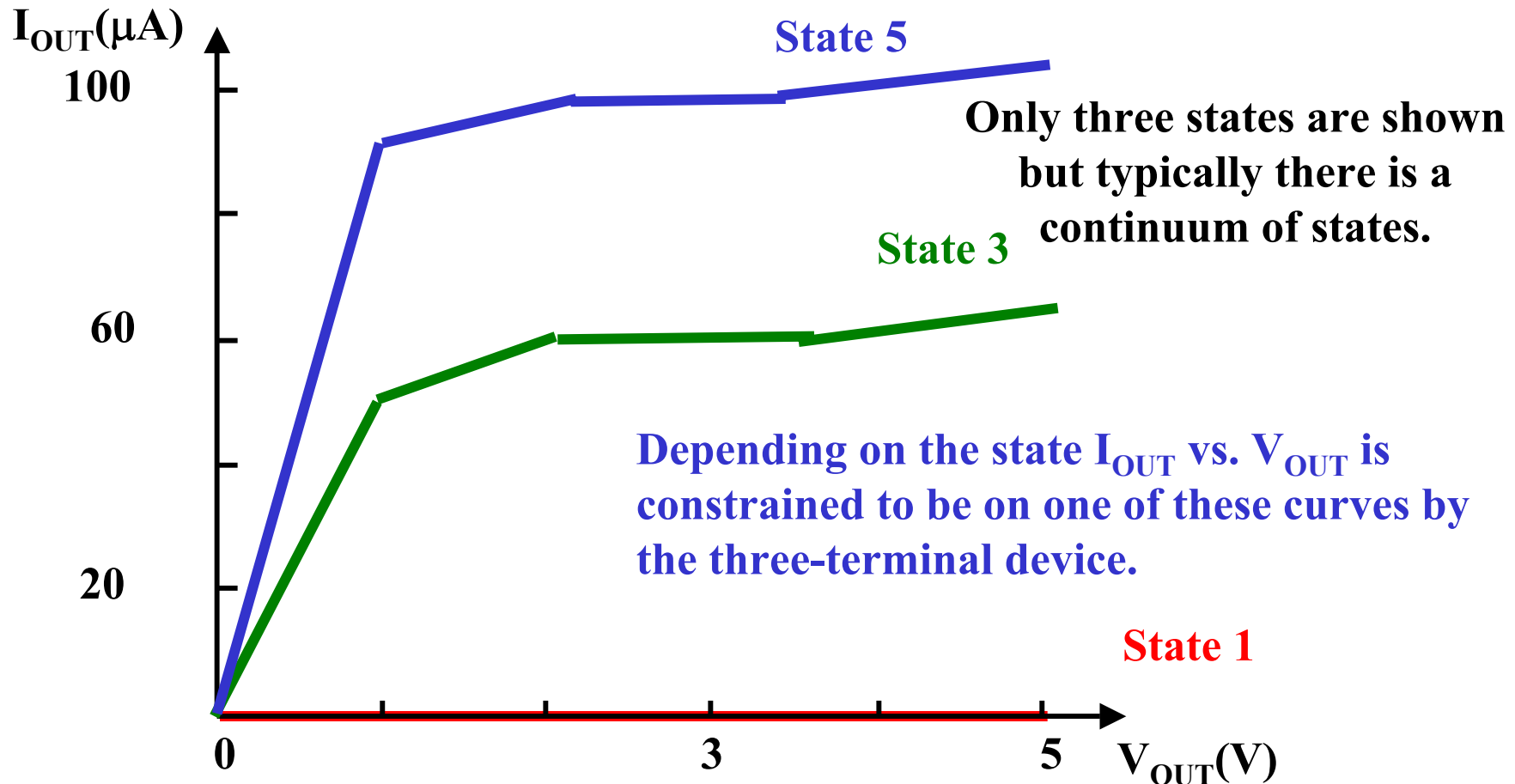
State-Dependent Device I_{OUT} vs. V_{OUT}



Three-Terminal Device Logic Circuit

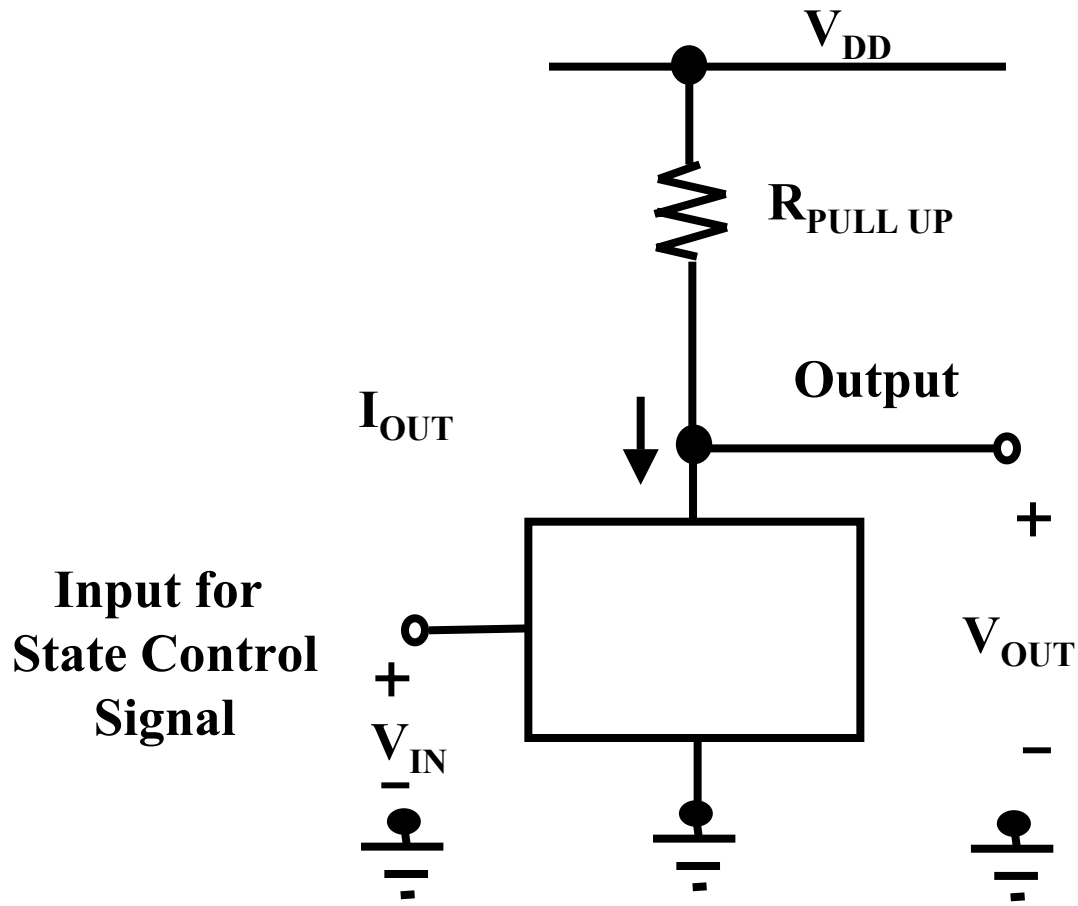

Thevenin Model For Pull-Up Device

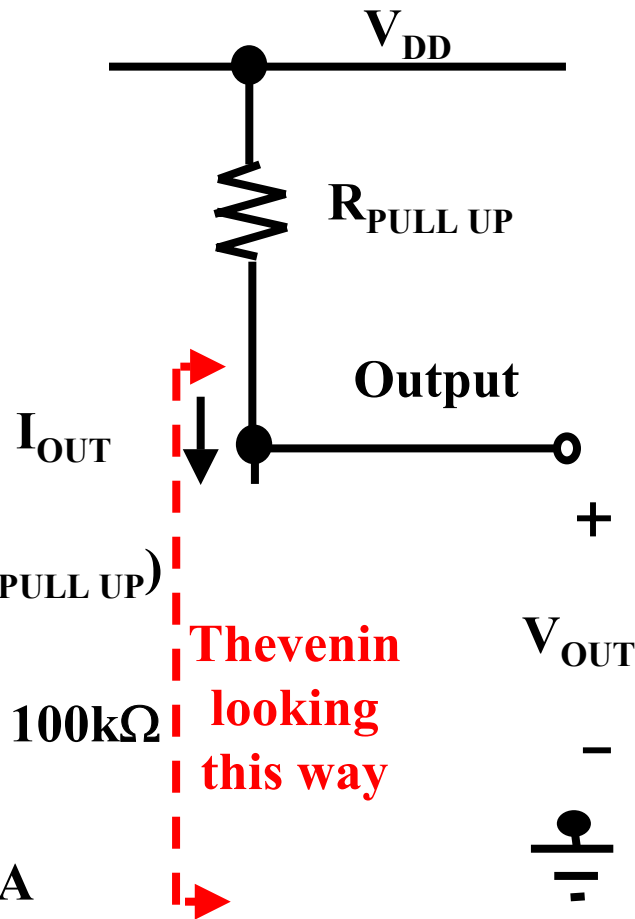

$$V_{\text{THEVENIN}} = V_{\text{DD}}$$

$$I_{\text{OUT SHORT CIRCUIT}} = (V_{\text{DD}}/R_{\text{PULL UP}})$$

Example:


$$V_{\text{DD}} = 5\text{V and } R_{\text{PULL UP}} = 100\text{k}\Omega$$

$$V_{\text{THEVENIN}} = 5\text{V}$$

$$I_{\text{OUT SHORT CIRCUIT}} = 50 \mu\text{A}$$

Thevenin Model For Pull-Up Device

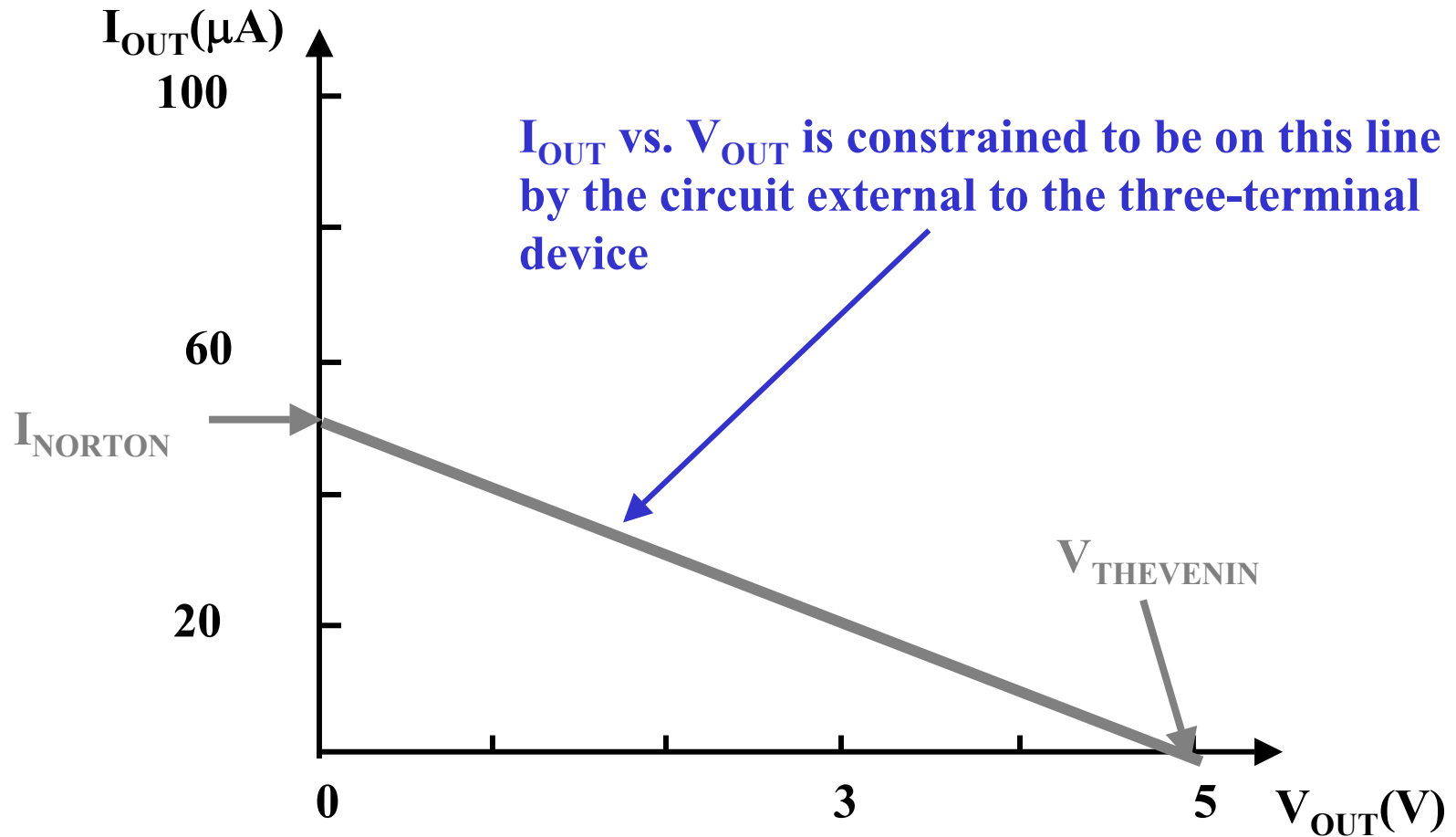
I_{OUT} vs. V_{OUT}
For the Pull-Up Resistor and V_{DD}



Composite Current Plot for the Logic Circuit

Three-Terminal Device


Plus Load Line for the Pull-Up Device

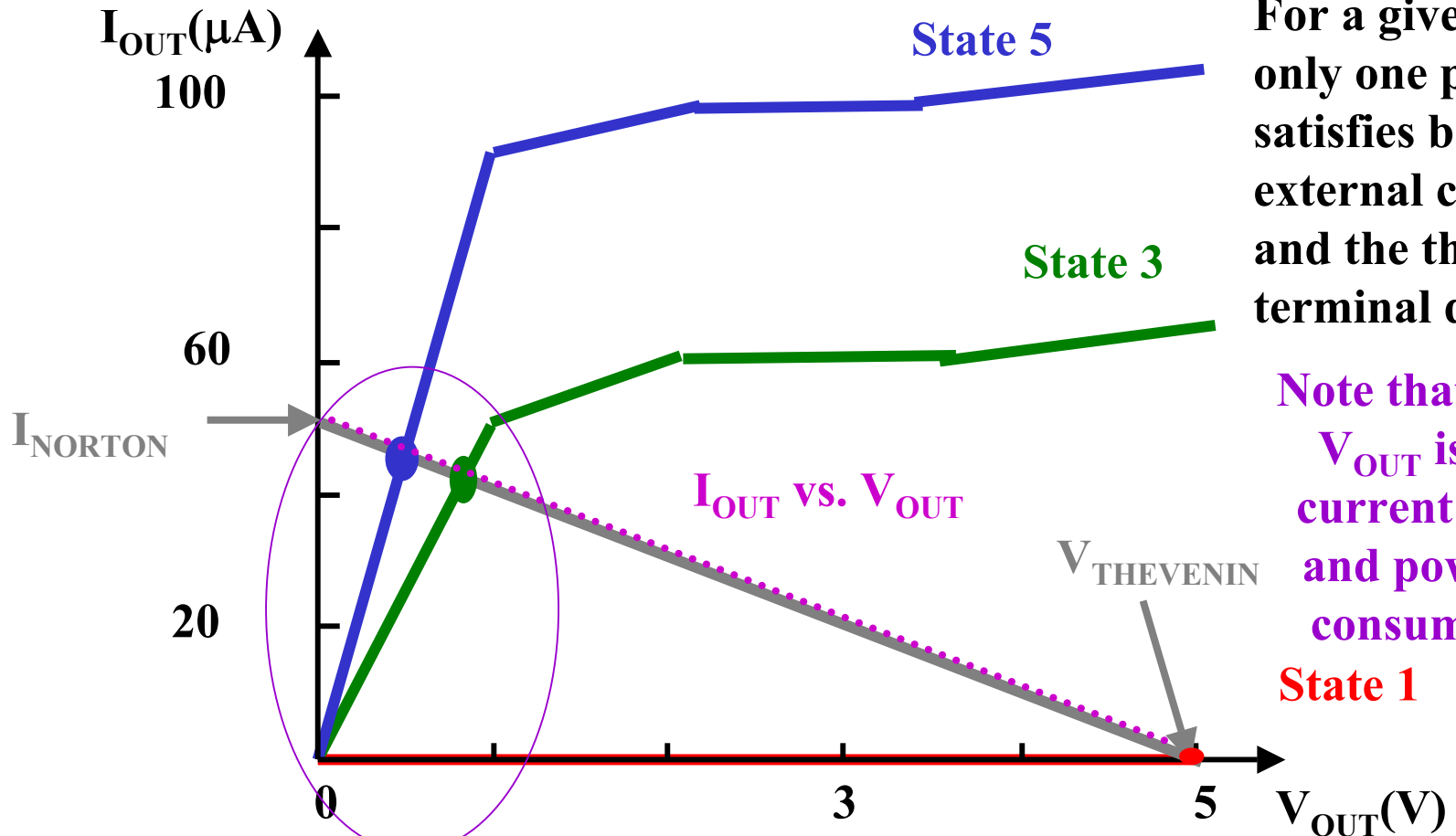


Voltage Transfer Function: V_{OUT} vs. V_{IN}

The V_{OUT} vs. V_{IN} characteristic is another view of the logic gate that is used to determine the inverting and noninverting nature of a gate.


Inverting type

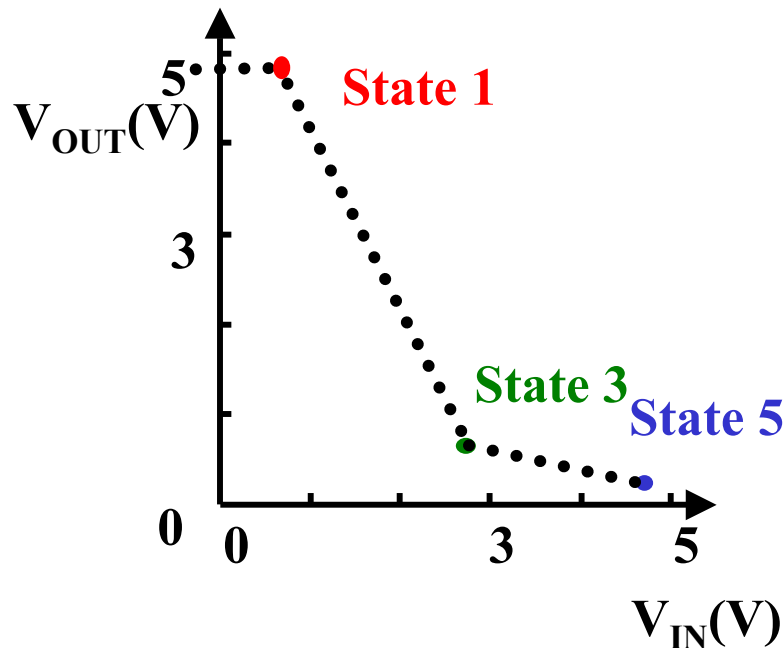

Noninverting type

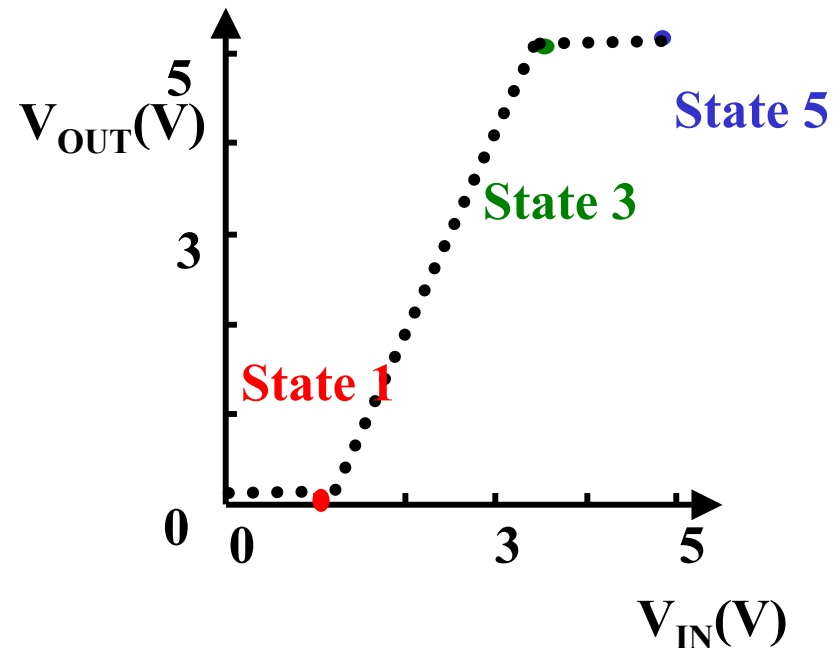


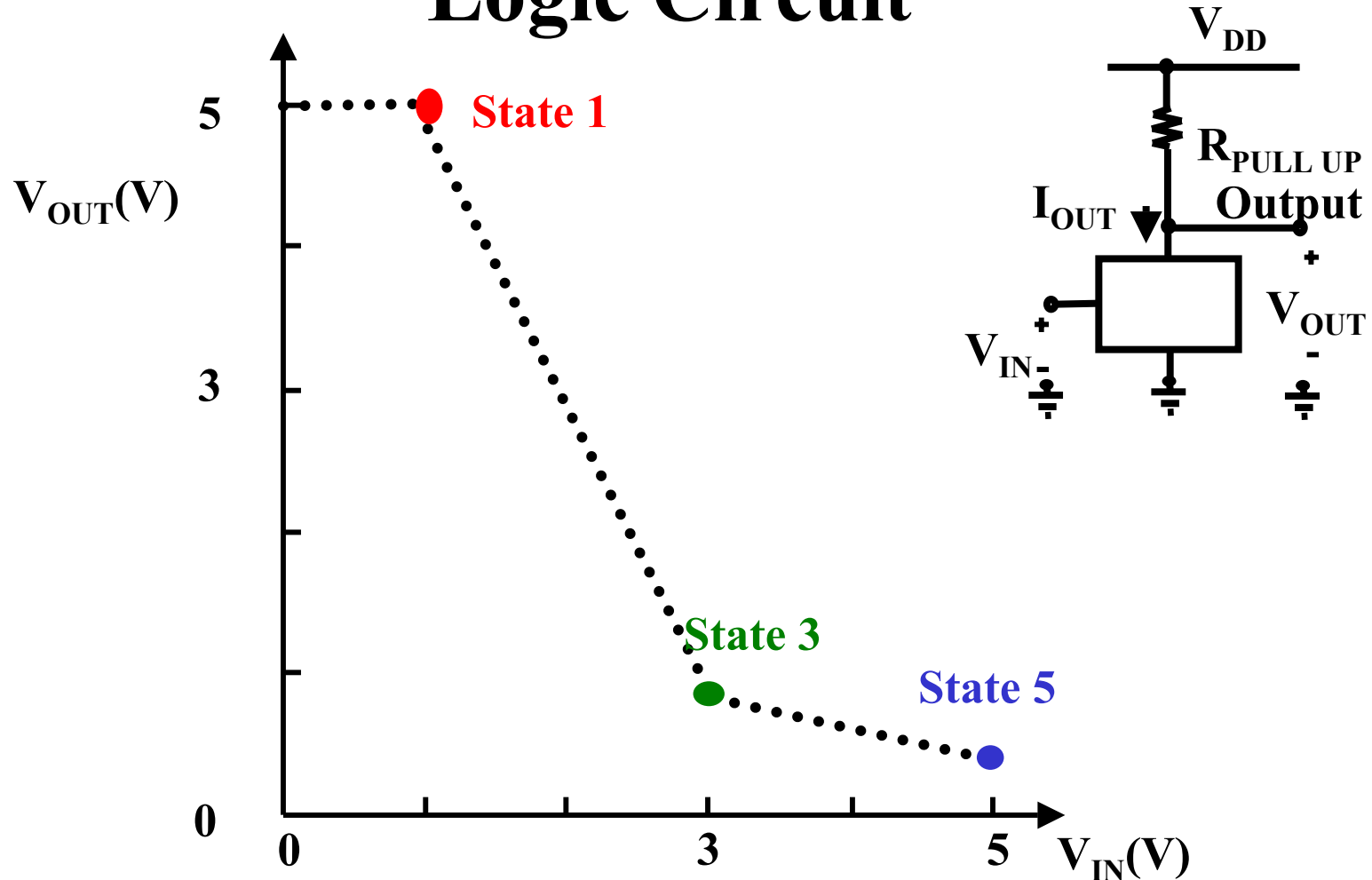Voltage Transfer Function for the Logic Circuit



42Pull-Down Device Model

I_{OUT} vs. V_{OUT}

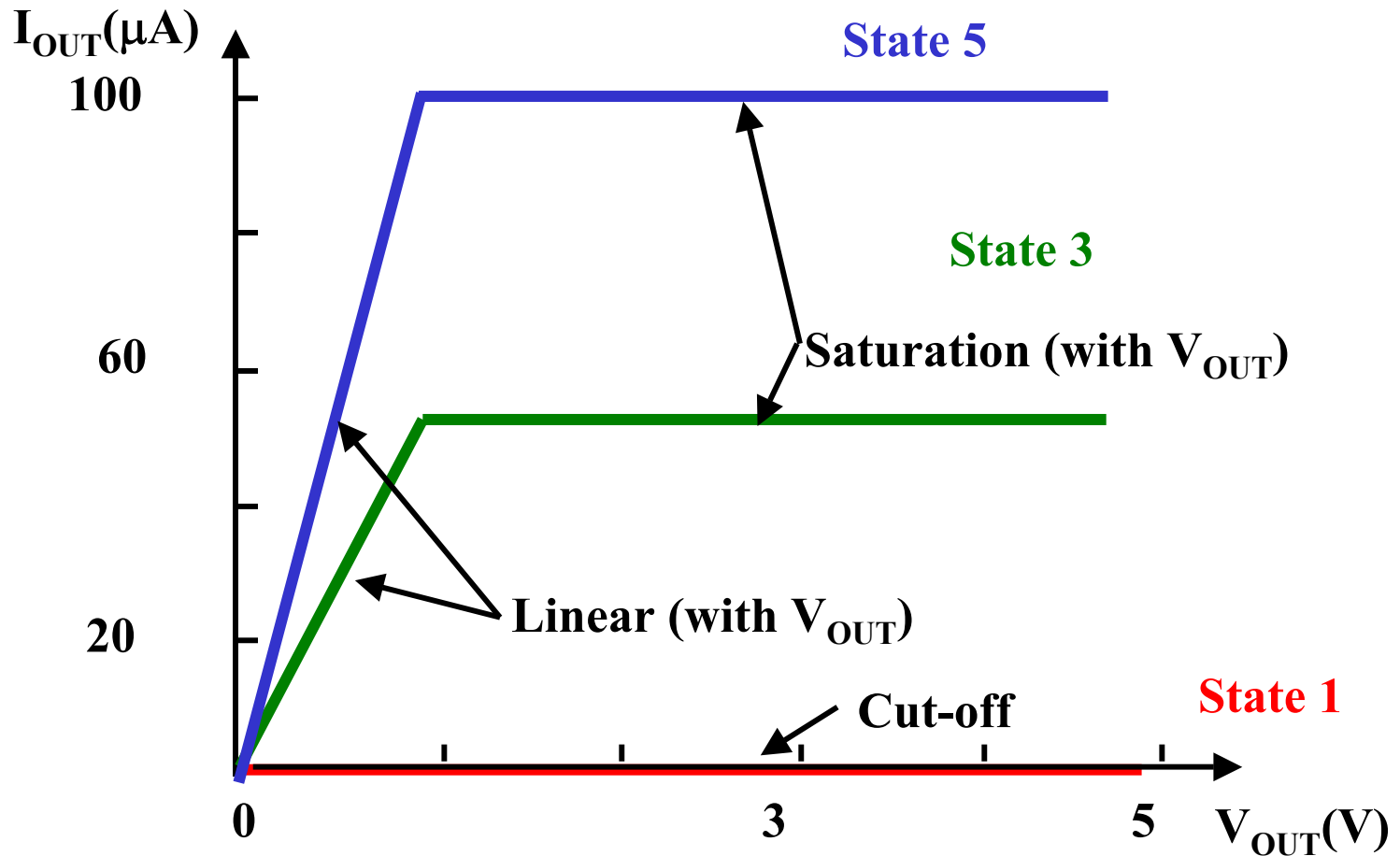

42 Pull-Down Device Equations

Describe I_{OUT} as function of V_{IN} and V_{OUT}

Cut-off $V_{IN} \leq V_T = 1V$

Values shown for $V_T = 1V$ and $k = 25 \mu A/V^2$

$$I_{OUT} = 0$$


Linear (with V_{OUT}) $V_{IN} \leq V_T = 1V$ $V_{OUT} \leq V_T = 1V$

$$I_{OUT} = k(V_{IN} - V_T)V_{OUT} = 25 \frac{\mu A}{V^2} (V_{IN} - 1)V_{OUT}$$


Saturation (with V_{OUT}) $V_{IN} \leq V_T = 1V$ $V_{OUT} \geq V_T = 1V$

$$I_{OUT} = k(V_{IN} - V_T)V_T = 25 \frac{\mu A}{V} (V_{IN} - 1)V_T$$

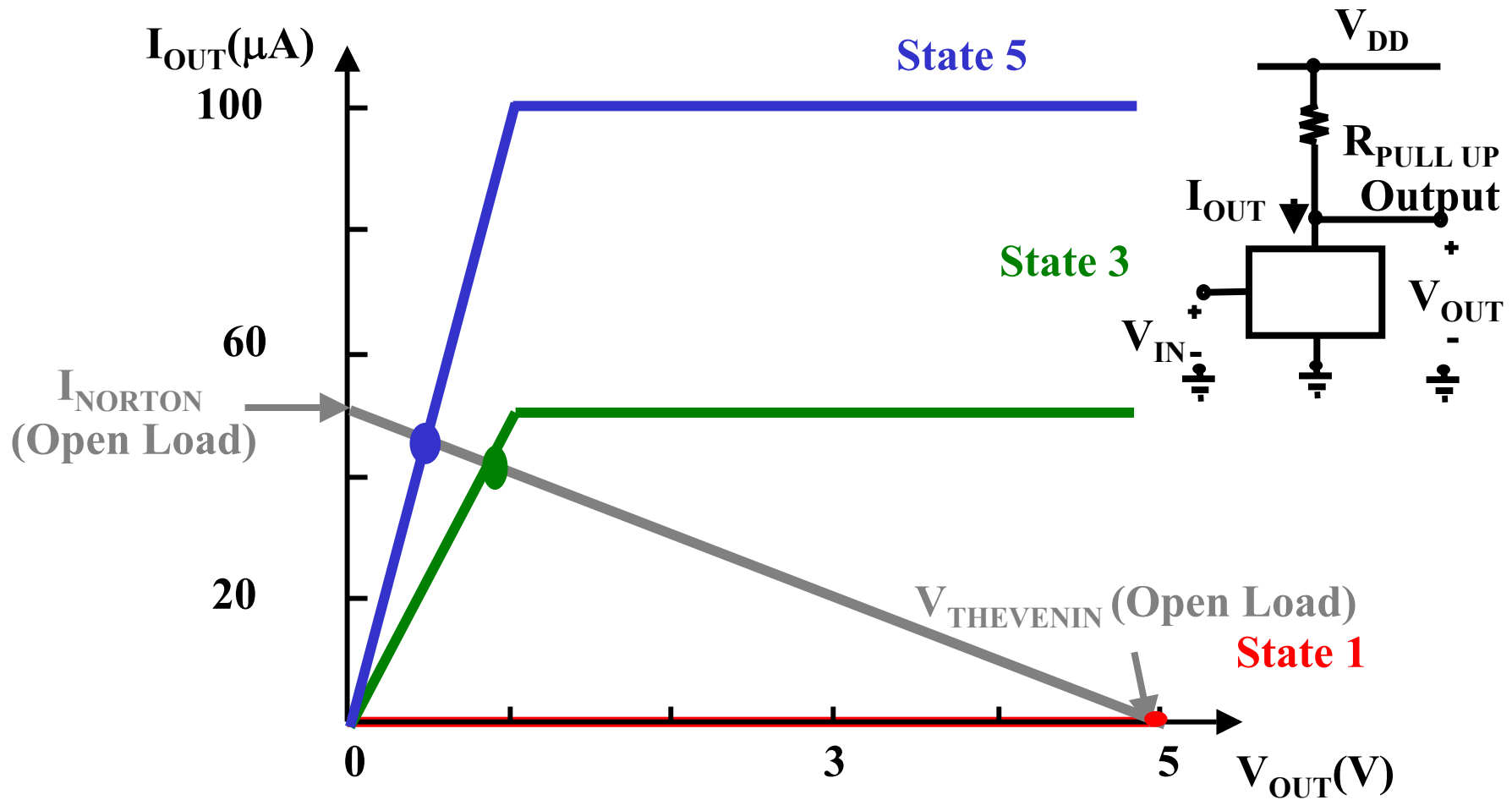Composite Current Plot for the 42PD Circuit



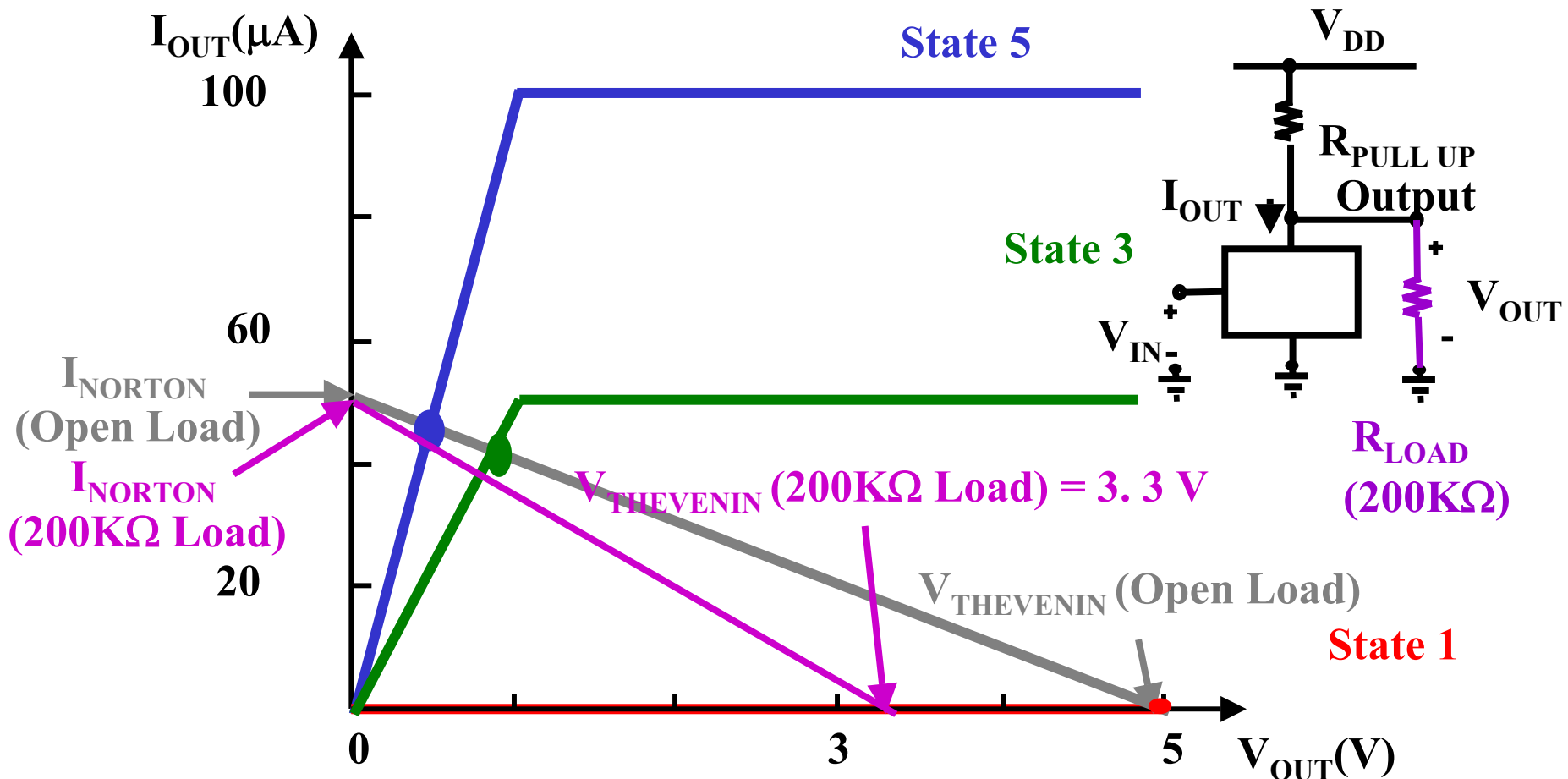Composite Current Plot for the 42PD Circuit with 200k Ω Load to Ground



Voltage Transfer Function for the 42PD Logic Circuit w/wo Load

