

## Lecture 18: October 31, 2001


### Logic Switched Resistor Model

- A) Worst Case Input Scenario
- B) Cascade Stages for Many Inputs
- C) Typical 0.25  $\mu\text{m}$  Device Parameters


### Reading:

lecture viewgraphs
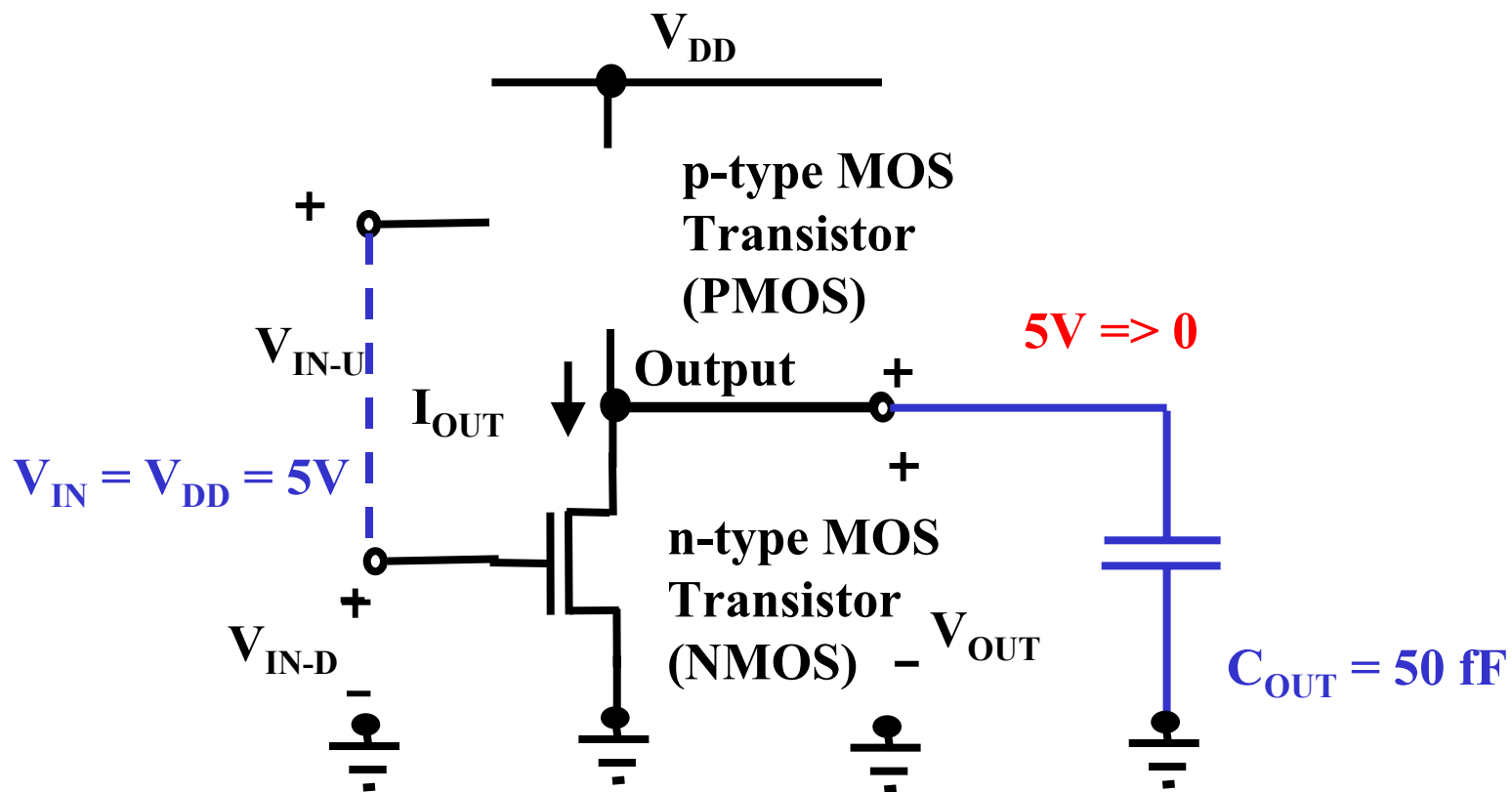
# Transient Gate Problem: Discharging and Charging Capacitance on the Output



# Output Capacitance Voltage vs. Time

 

When  $V_{OUT} > V_{OUT-SAT-D}$  the available current is  $I_{OUT-SAT-D}$

Assume that the necessary voltage swing to cause the next downstream gate to begin to switch is  $V_{DD}/2$  or 2.5V. The **propagation delay** is thus

$$\Delta t = \frac{C_{OUT} \Delta V}{I_{OUT-SAT-D}} = \frac{C_{OUT} V_{DD}}{2I_{OUT-SAT-D}} = \frac{50 \text{ fF} \cdot 2.5V}{100 \mu A} = 1.25 \text{ ns}$$

# Switched Equivalent Resistance Model

The above model assumes the device is an ideal constant current source.


- 1) This is not true below  $V_{OUT-SAT-D}$  and leads to inaccuracies.
- 2) Combining ideal current sources in networks with series and parallel connections is problematic.

Instead define an equivalent resistance for the device by setting  $0.69R_D C$  equal to the  $\Delta t$  found above

$$\Delta t = \frac{C_{OUT} V_{DD}}{2I_{OUT-SAT-D}} = 0.69R_D C_{OUT}$$



This gives
 
$$R_D = \frac{V_{DD}}{2 \cdot (0.69)I_{OUT-SAT-D}} \approx \frac{3}{4} \frac{V_{DD}}{I_{OUT-SAT-D}} = \frac{3}{4} \frac{5V}{100\mu A} = 37.5k\Omega$$



Each device can now be replaced by this equivalent resistor.

# Switched Equivalent Resistance Network

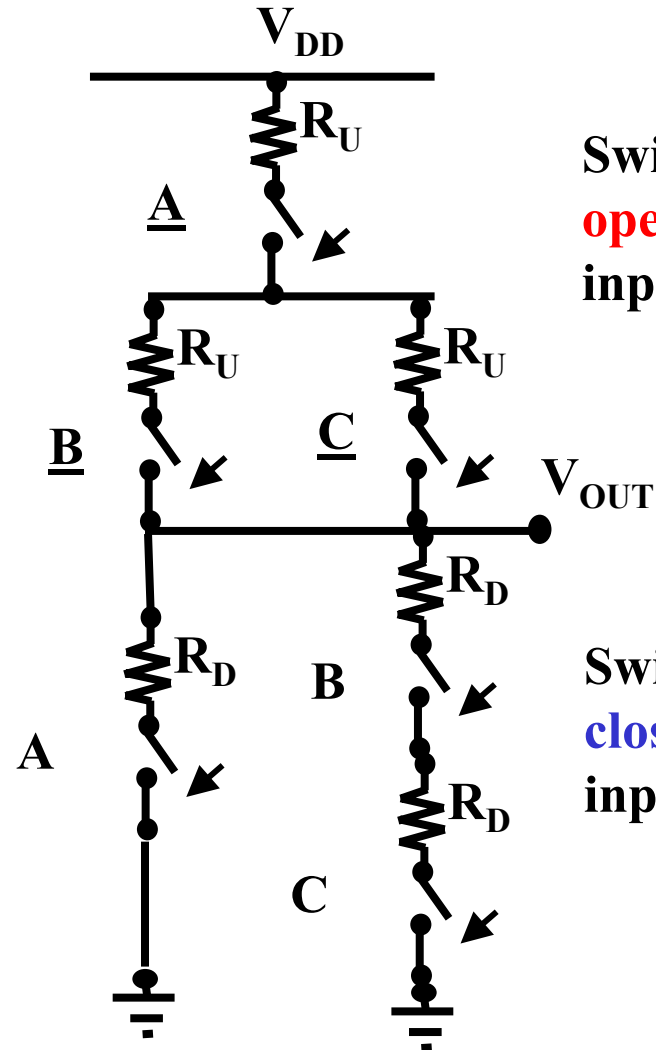 



Switches **open** when input is **high**.

Switches **close** when input is **high**.

**For convenience in EE 42 we assume  $R_D = R_U = 10 \text{ k}\Omega$**

# Inverter Propagation Delay

Discharge (pull-down)

  


$$\Delta t = 0.69R_D C_{OUT} = 0.69(10\text{k}\Omega)(50\text{fF}) = 345 \text{ ps}$$

Discharge (pull-up)

$$\Delta t = 0.69R_U C_{OUT} = 0.69(10\text{k}\Omega)(50\text{fF}) = 345 \text{ ps}$$
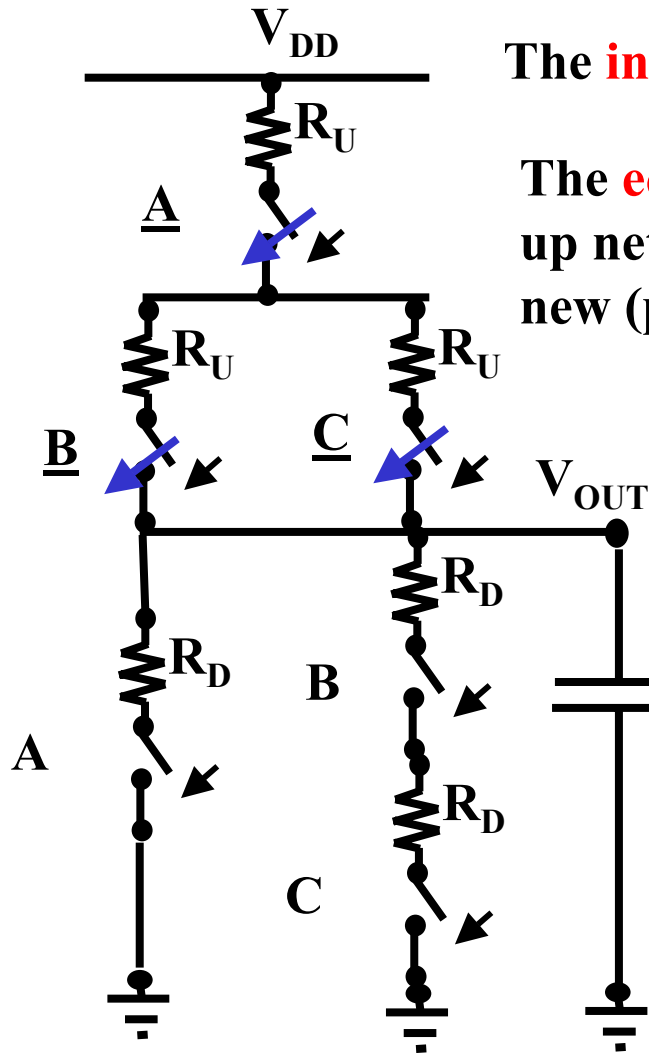
# Logic Gate Propagation Delay: Initial State




The **initial state** depends on the old (previous) inputs.

The **equivalent resistance** of the pull-down or pull-up network for the transient phase depends on the new (present) input state.

Example:  $A=0, B=0, C=0$  for a long time.

These inputs provided a path to  $V_{DD}$  for a long time and the capacitor has precharged up to  $V_{DD} = 5V$ .
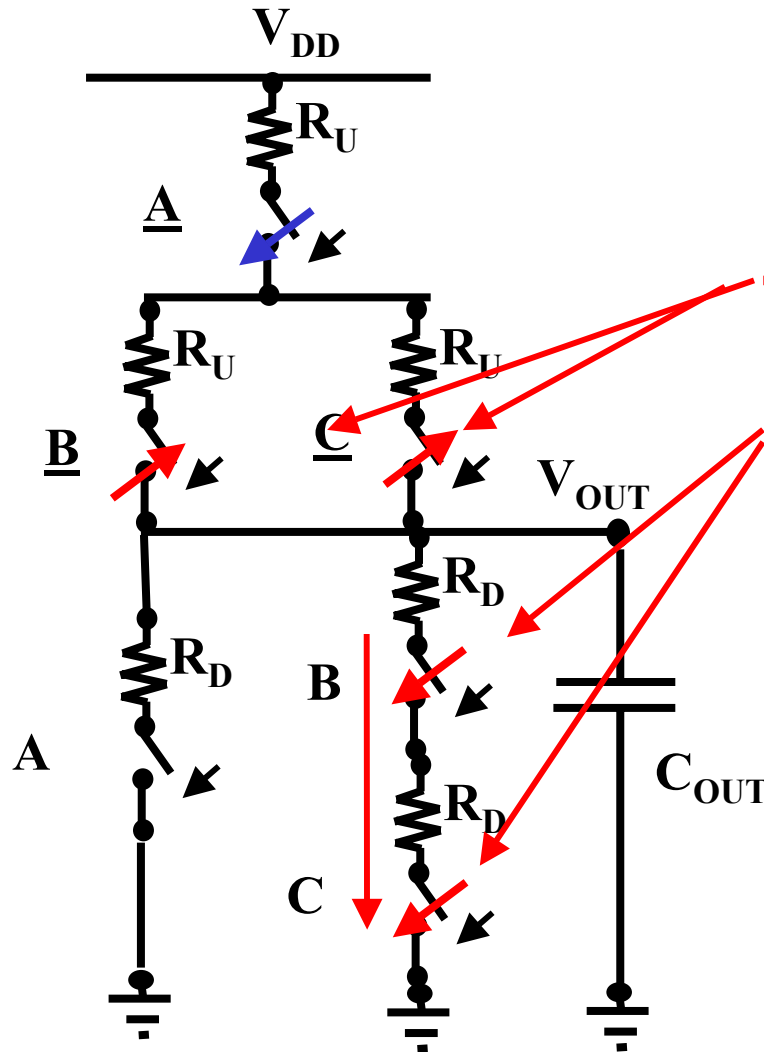
# Logic Gate Propagation Delay: Transient



At t=0, B and C switch from low to high (V<sub>DD</sub>) and A remains low.

This breaks the path from V<sub>OUT</sub> to V<sub>DD</sub>

And opens a path from V<sub>OUT</sub> to GND

C<sub>OUT</sub> discharges through the pull-down resistance of gates B and C in series.


$$\Delta t = 0.69(R_{DB} + R_{DC})C_{OUT}$$

$$= 0.69(20\text{k}\Omega)(50\text{fF}) = 690 \text{ ps}$$

The propagation delay is **two times longer** than that for the inverter!



# Logic Gate: Worst Case Scenarios

 

What combination of previous and present logic inputs will make the Pull-Up the **fastest**?

What combination of previous and present logic inputs will make the Pull-Up the **slowest**?

What combination of previous and present logic inputs will make the Pull-Down the **fastest**?


What combination of previous and present logic inputs will make the Pull-Down the **slowest**?

**Fastest overall?**

**Slowest overall?**
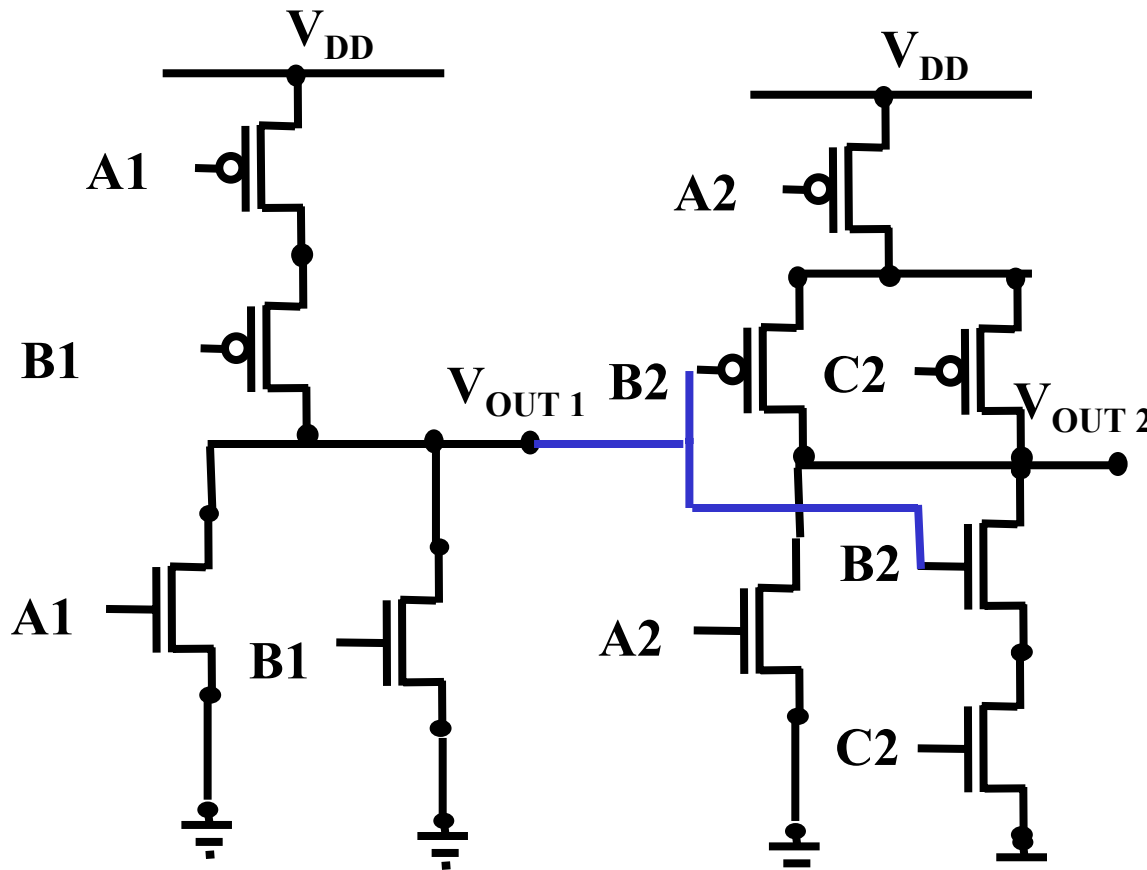
# Logic Gate Cascade

To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.



$$B2 = V_{OUT1}$$

The four independent input are A1, B1, A2 and C2.

A2 high discharges gate 2 without even waiting for the output of gate 1.

C2 high and A2 low makes gate 2 wait for Gate 1 output

# Switched Equivalent Resistance Values

**The resistor values depend on the properties of silicon, geometrical layout, design style and technology node.**

**n-type silicon has a carrier mobility that is 2 to 3 times higher than p-type.**

**The resistance is inversely proportion to the gate width/length in the geometrical layout.**

**Design styles may restrict all NMOS and PMOS to be of a predetermined fixed size.**

**The current per unit width of the gate increases nearly inversely with the linewidth.**

# CMOS Device Parameters at 0.25 $\mu\text{m}$

Gate length is 0.25  $\mu\text{m}$  = 250 nm

$$V_{DD} = 2.5V$$

A minimum sized device has  $W = 0.5 \mu\text{m}$   
and  $L = 0.25 \mu\text{m}$  so  $W/L=2$

$$k = k' \frac{(W/L)}{(W/L)_{\min}}$$

	$V_T(V)$	$V_{OUT-SAT}(V)$	$k' (\mu A/V^2)$
NMOS	0.43	0.63	115
PMOS	0.4	1	30

$$I_{OUT-SAT-D} = \left(115 \mu A/V^2\right) \left(\frac{2}{2}\right) (2.5V - 0.43V)(0.63V) = 150 \mu A$$