

Lecture 19: November 5, 2001

Midterm in Class Wed. Nov 7th

Covers Material 6th-10th week including HW#10

**Closed Book, Closed Notes, Bring Calculator, Paper Provided
Last Name A-K 2040 Valley LSB; Last Name L-Z in 10 Evans**

Review Session: Sat 1-2:30 (241 Cory); Tu 5-6:00 (241 Cory)

EE 43 Labs Are **Not Cancelled:**


Flip-Flops

- A) Synchronization: Clocks and Latches**
- B) Two Stage Latch**
- C) Memory Requires Feedback**
- D) Simple Flip-Flop Gate**

**Reading:
Schwarz and
Oldham
11.3 and
lecture
viewgraphs**

Logic Gate Cascade

 To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.



$$B2 = V_{OUT1}$$

The four independent input are A1, B1, A2 and C2.


A2 high discharges gate 2 without even waiting for the output of gate 1.

C2 high and A2 low makes gate 2 wait for Gate 1 output

Data Synchronization problem

- Combinatorial logic gates can give incorrect answers prematurely and may take several gate propagation delays produce an answer.
- Clocks (signals as to when to proceed) and latches (which capture and hold the correct outputs) can provide synchronization.

Latch Controlled by a Clock

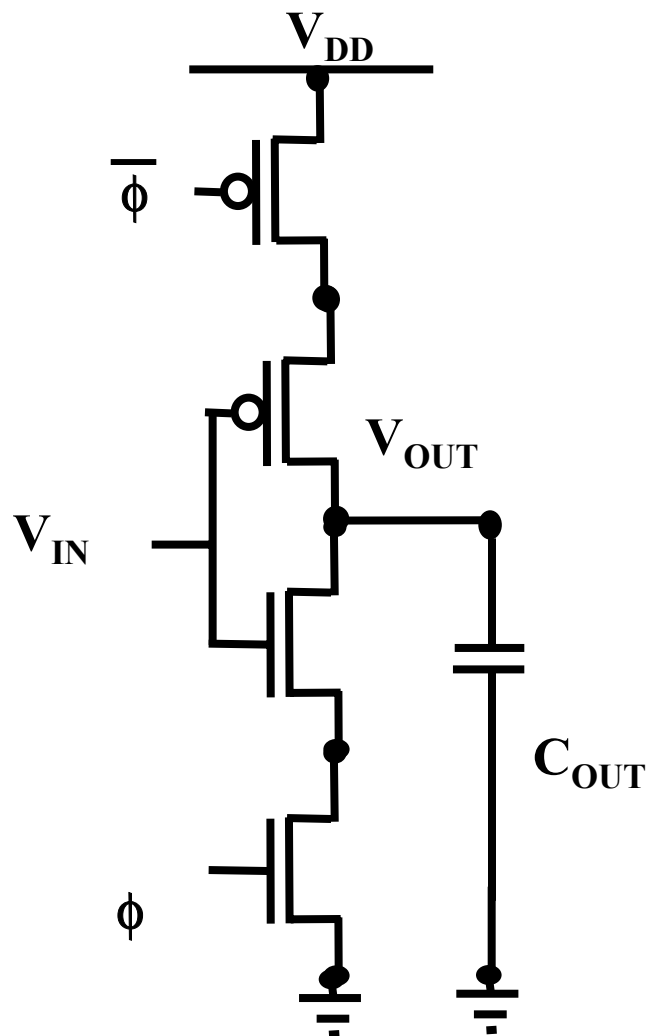


An inverter with clocked devices in series can form a latch.

When the clock ϕ is high its complement $\bar{\phi}$ is low and the inverter operates.

To synchronize the data the clock remains low until the data is correct at all locations on the chip. When the clock goes high the inverse of the data is passed.


Latch Work Best In Pairs

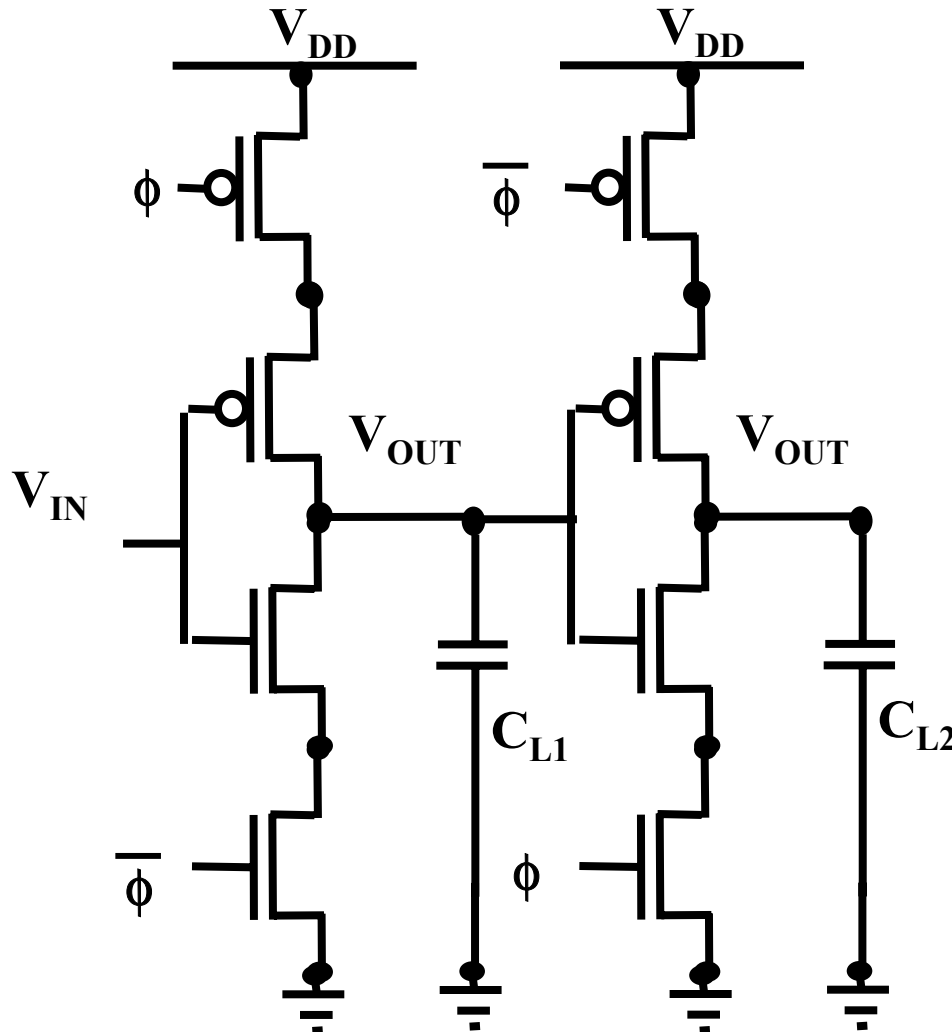

The first stage operates while the clock is low and inverts and amplifies the arriving signal and charges or discharges C_{L1} .

The second stage operates while the clock is high and inverts the signal on C_{L1} to charge or discharge C_{L2} and downstream logic gate inputs.

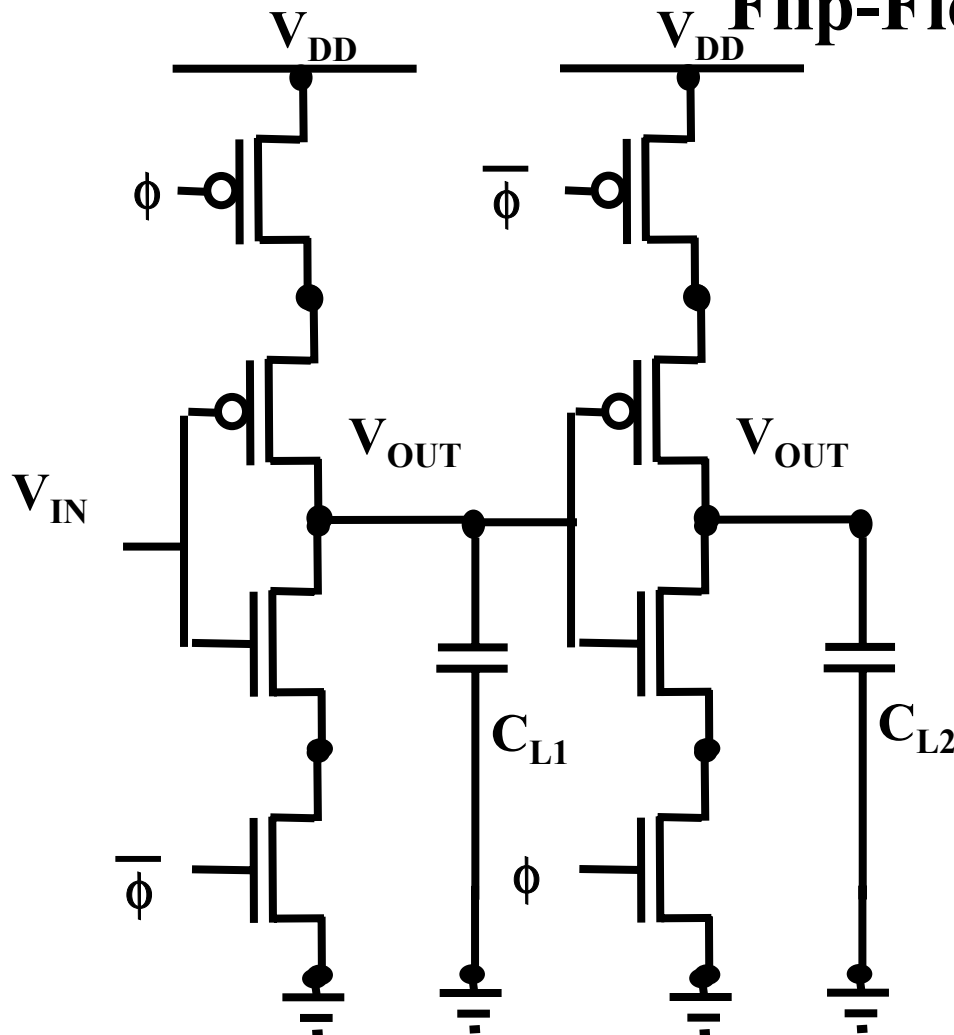
A Double Latch is an Edge-Triggered D Type Flip-Flop




During the low part of the clock cycle this circuit records the input value and when the clock goes high drives $V_{OUT 2}$ to the voltage level that arrived. (This is the classic function of a D flip-flop.)

Note that this circuit is not fooled by noise on the input and makes its decision on the rising edge of the clock (**edge-triggered**).


Feedback Can Provide Memory

 

Example of the Opposite State

 


Adding Memory Controls

 

Set-Reset Flip-Flop

Adding a Clock

 

Clocked S-R Flip-Flop

Switched Equivalent Resistance Values

The resistor values depend on the properties of silicon, geometrical layout, design style and technology node.

n-type silicon has a carrier mobility that is 2 to 3 times higher than p-type.

The resistance is inversely proportion to the gate width/length in the geometrical layout.

Design styles may restrict all NMOS and PMOS to be of a predetermined fixed size.

The current per unit width of the gate increases nearly inversely with the linewidth.

CMOS Device Parameters at 0.25 μm

Gate length is 0.25 μm = 250 nm

$$V_{DD} = 2.5V$$

A minimum sized device has $W = 0.5 \mu\text{m}$
and $L = 0.25 \mu\text{m}$ so $W/L=2$

$$k = k' \frac{(W/L)}{(W/L)_{\min}}$$

	$V_T(V)$	$V_{OUT-SAT}(V)$	$k' (\mu A/V^2)$
NMOS	0.43	0.63	115
PMOS	0.4	1	30

$$I_{OUT-SAT-D} = \left(115 \mu A/V^2\right) \left(\frac{2}{2}\right) (2.5V - 0.43V)(0.63V) = 150 \mu A$$