

## Lecture 21

# Bipolar Transistors (Briefly)


- A) Motivation and Diode Carriers
- B) Bipolar Transistor Structure and Carrier Flow
- C) Bipolar Transistor I vs. V
- D) Bipolar Transistor Circuits

**Reading: Schwarz and Oldham, pp. 499-509, 594-596**
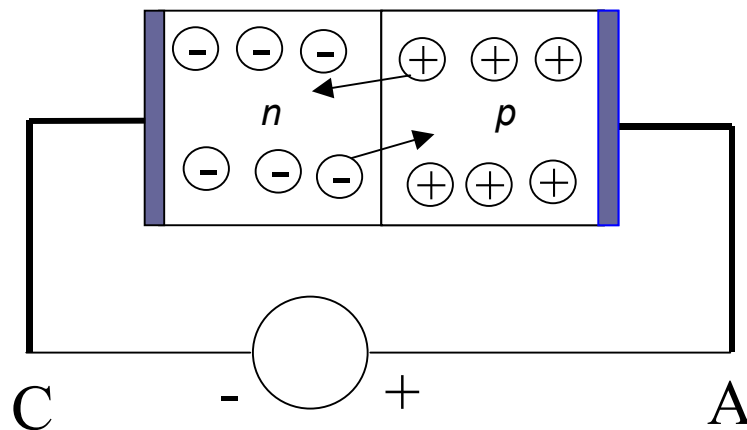
## pn Junction Carrier Flow

Forward bias 0.7 V (positive on the p-side):

$$N_D = 10^{20}/\text{cm}^3 \quad N_A = 10^{18}/\text{cm}^3$$



This is the direction of easy current flow. + charges flow to meet up with - charges. Essentially unlimited conduction.

Carriers types flowing are proportional to doping so see many more electrons than holes crossing the junction.


**100 electrons => Forward direction**

**1 hole <= Reverse direction**

After the carriers reach the other side of the junction they circle around a carrier of the opposite type and eventually recombine.
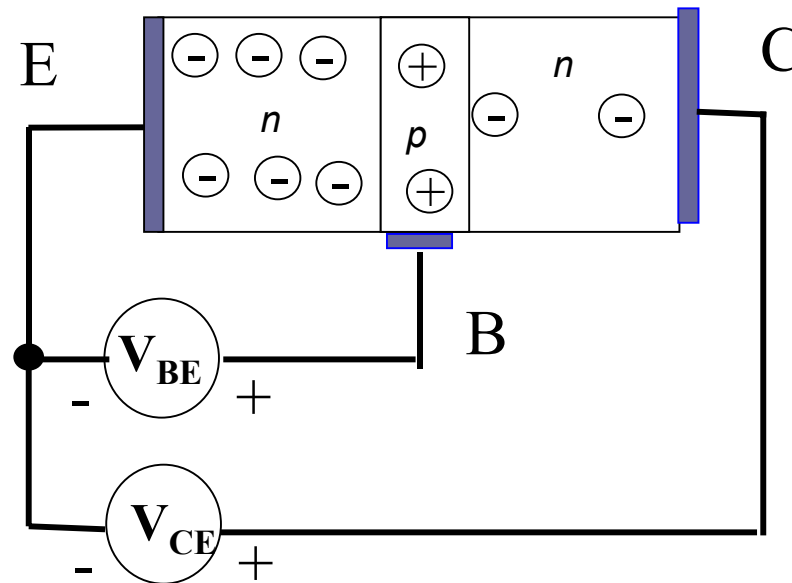
## nnp Bipolar Transistor Structure

$$N_D = 10^{20}/\text{cm}^3 \quad N_A = 10^{18}/\text{cm}^3 \quad N_D = 10^{16}/\text{cm}^3$$




Create a npn structure with decreasing doping levels.

Be sure that the base is thinner than the electron diffusion length.

Raise collector voltage with respect to emitter so it is electrically asymmetrical and electrons will prefer collector over emitter.
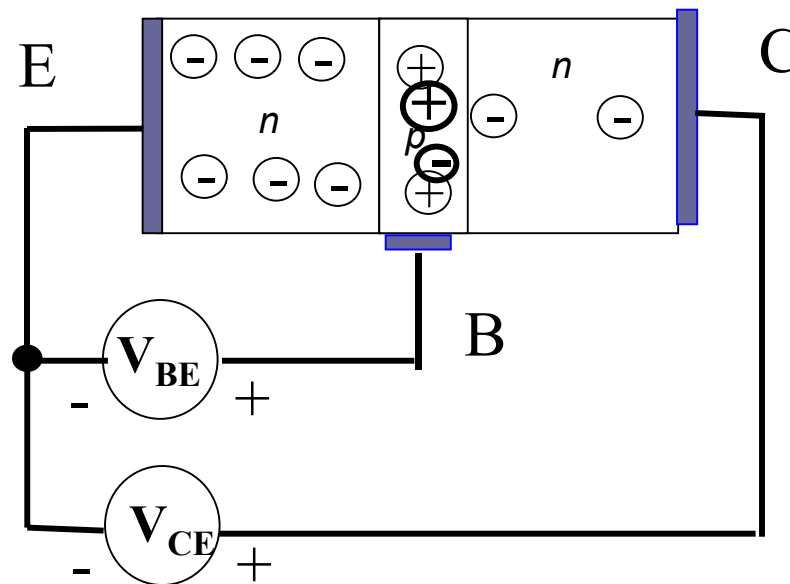
## nnp Bipolar Transistor Carrier Process



In a good npn transistor 149 electrons go into the collector for every one that recombines with a hole in the base. To accomplish this the base must be much narrower than the electron diffusion length.


Add an extra hole in base (by positive charge flowing into base lead).

This attracts an electron from the emitter (emitter current).  
The electron and hole circle about each other.

But if the electron gets too close to the collector the additional voltage on the collector sweeps it into the collector (current).
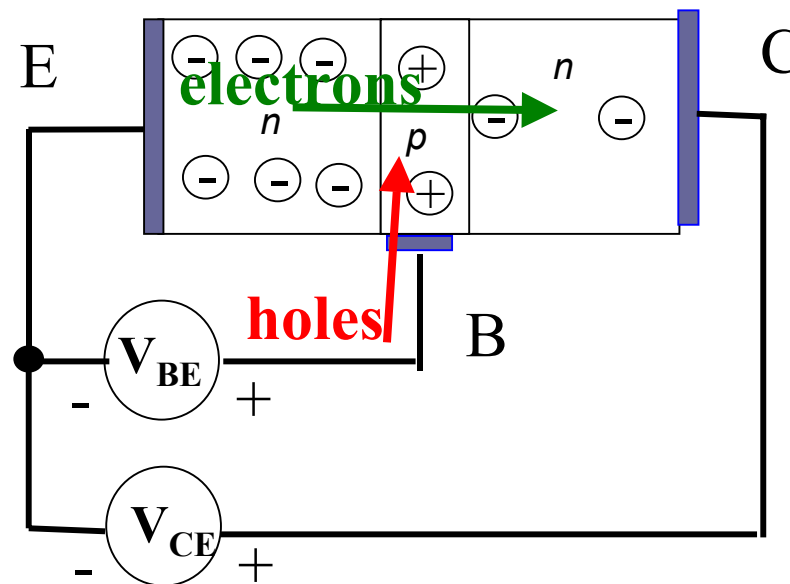
## npn Bipolar Transistor Carrier Flow

$$N_D = 10^{20}/\text{cm}^3 \quad N_A = 10^{18}/\text{cm}^3 \quad N_D = 10^{16}/\text{cm}^3$$




Gain mechanism: A hole in base attracts 150 electrons of which 149 go to collector and one recombines with the hole.

Extra loss mechanism: Like in a diode there is a small reverse flow (injection) of holes from the base into the emitter such as 10 out of every 100 holes.
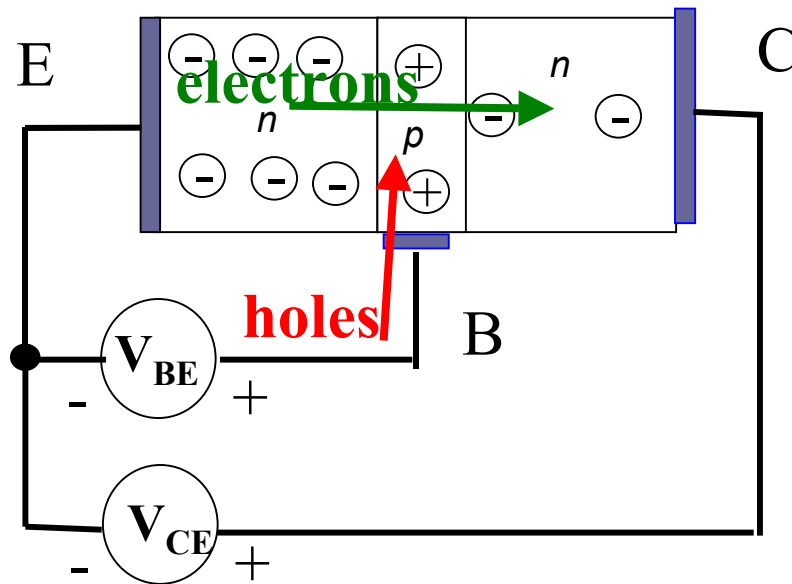
## npn Bipolar Transistor Gain

$$N_D = 10^{20}/\text{cm}^3 \quad N_A = 10^{18}/\text{cm}^3 \quad N_D = 10^{16}/\text{cm}^3$$



100 holes into base.

10 lost to emitter  
leaving 90 to attract  
electrons.


Each of the 90  
attracts 149 or  
13,410 electrons that  
reach collector.

$$\beta = (I_C/I_B) = (13,410)/(10+90) = 134$$

$$\alpha = (I_C/I_E) = (13,410)/(13,4010+10+90) = 0.9926$$


Note that since  $I_E = I_C + I_B$ ,  $\alpha$  and  $\beta$  are related by  $\beta = \alpha/(1-\alpha)$

## npn Bipolar Transistor Circuit

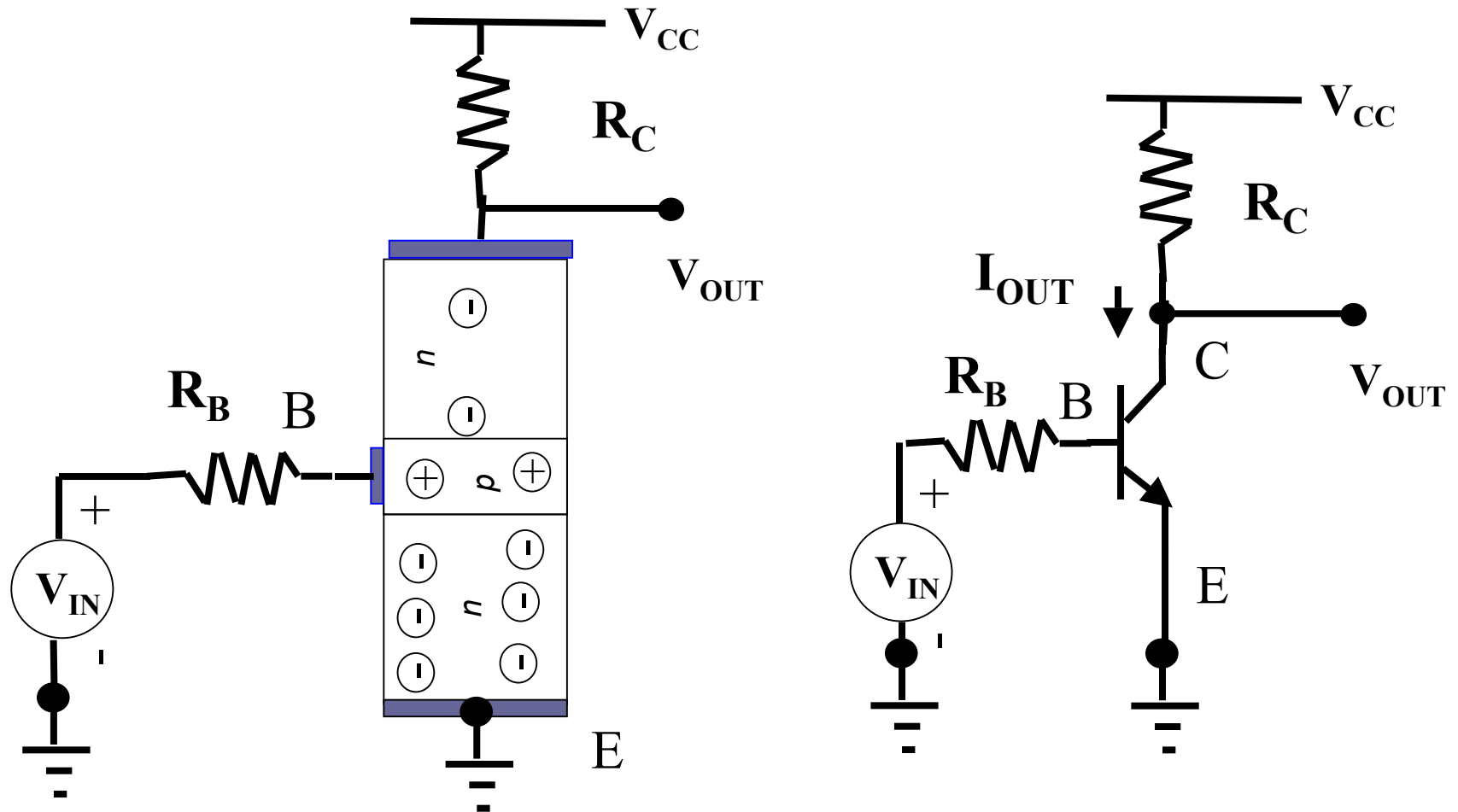

We need a model for the base and model for  $I_{OUT}$  versus  $V_{OUT}$  collector side of the bipolar transistor.

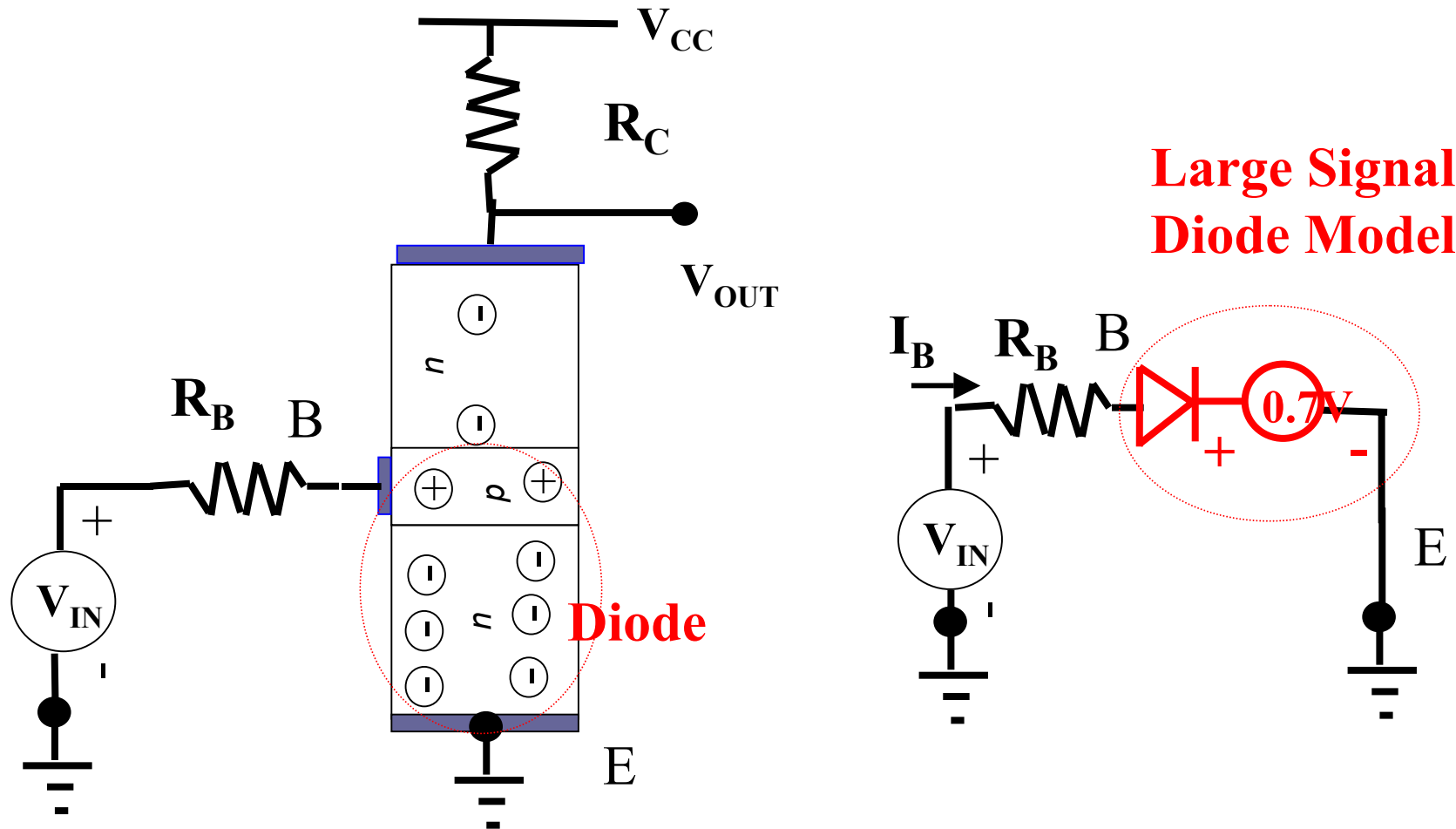
## npn Bipolar Transistor: Base Circuit Model




The base-emitter is modeled as a large signal diode.



# DIODE I-V CHARACTERISTICS AND MODELS

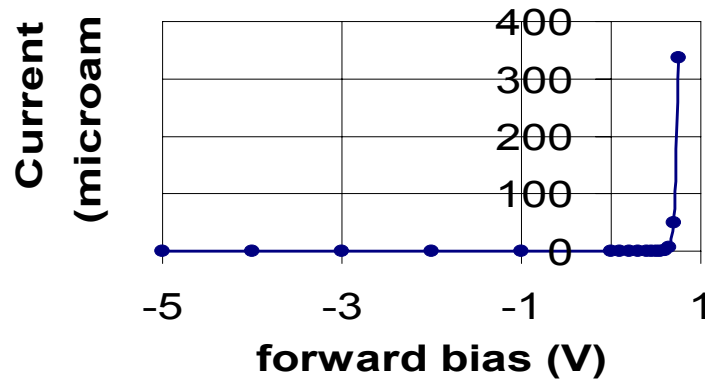


The Large-Signal Diode Model

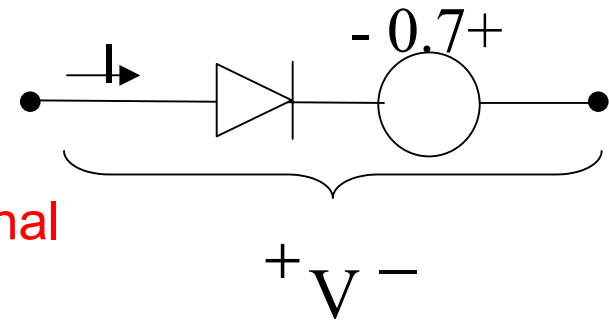

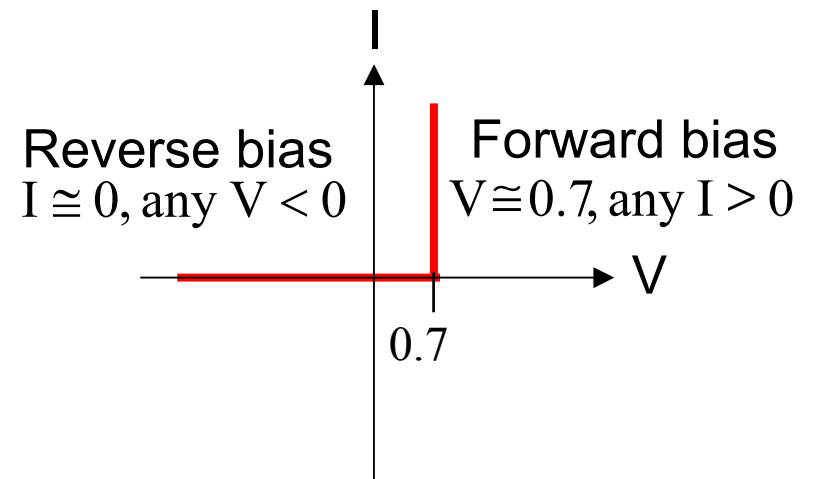
## Improved “Large-Signal Diode” Model:

If we choose not to ignore the small forward-bias voltage drop of a diode, it is a very good approximation to regard the voltage drop in forward bias as a constant, about 0.7V. the “Large signal model” results.



## npn Bipolar Transistor: Base Circuit Analysis

**Large Signal  
Diode Model**

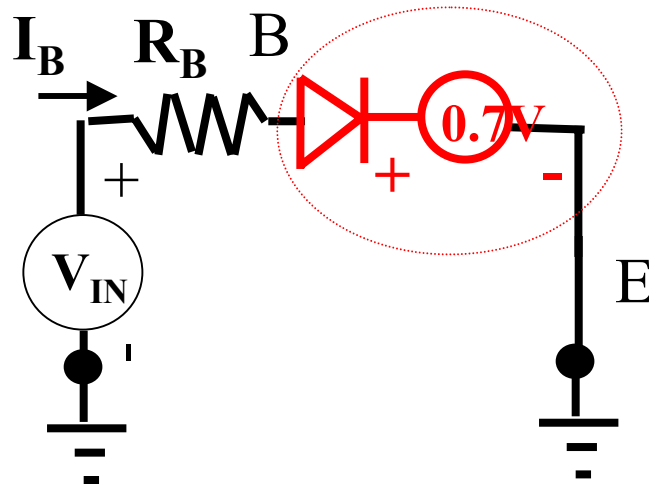

**Cutoff**

$$V_{BE} < 0.7V \Rightarrow I_B = 0$$

**On**

$$V_{BE} = 0.7V$$



$$I_B = (V_{IN} - 0.7V)/R_B$$

**Example:**  $V_{IN} = 2.5V$ ,  $R_B = 10k\Omega$

$$I_B = (2.5V - 0.7V)/10k\Omega = 180 \mu A$$


The base circuit analysis is the same as that for a diode.
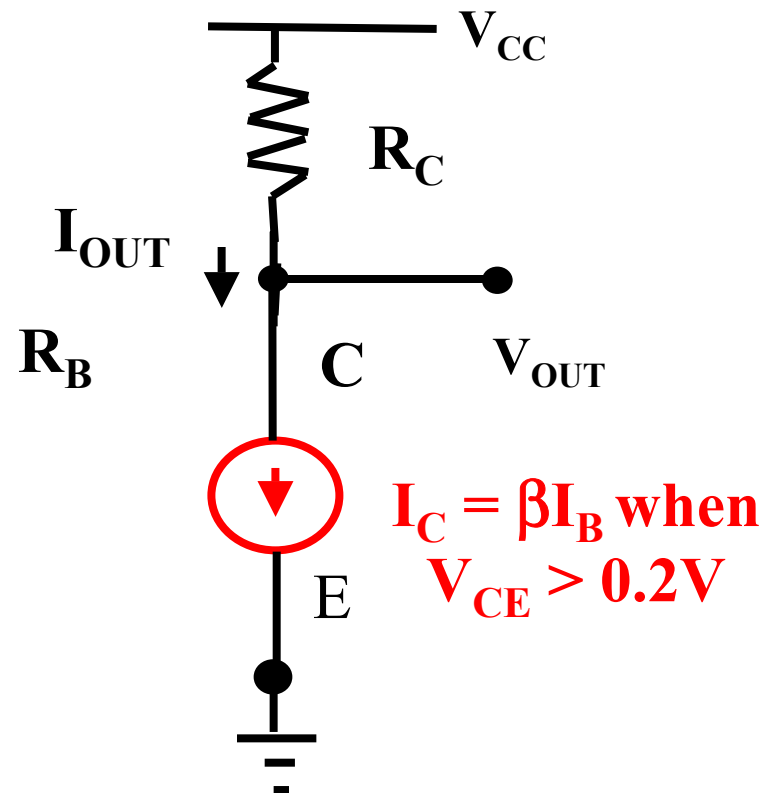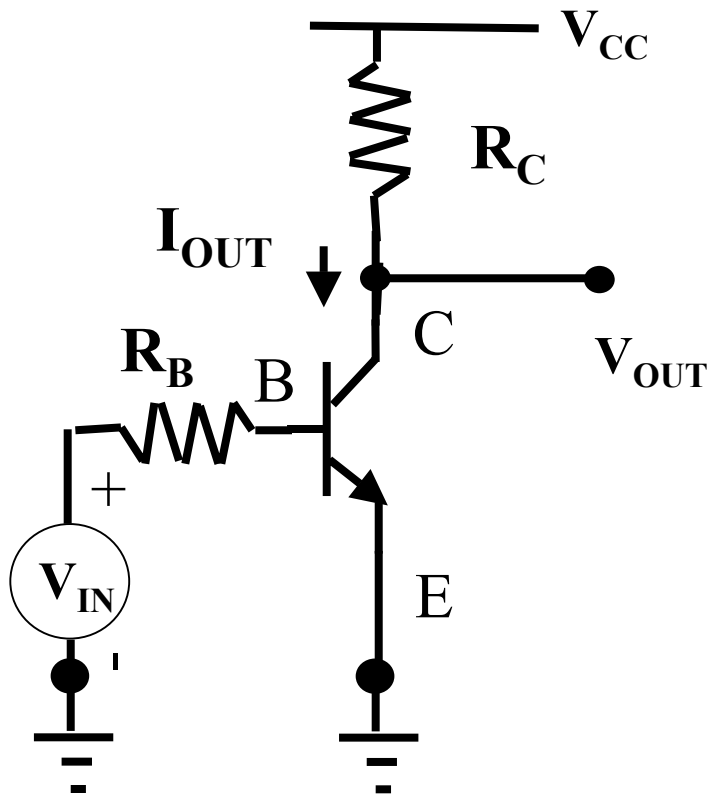
## npn Bipolar Transistor: Collector Circuit Model



The collector current is programmed by the base current to be  $\beta$  times the base current. However, the current stops growing larger whenever the collector base voltage drops to 0.2V.
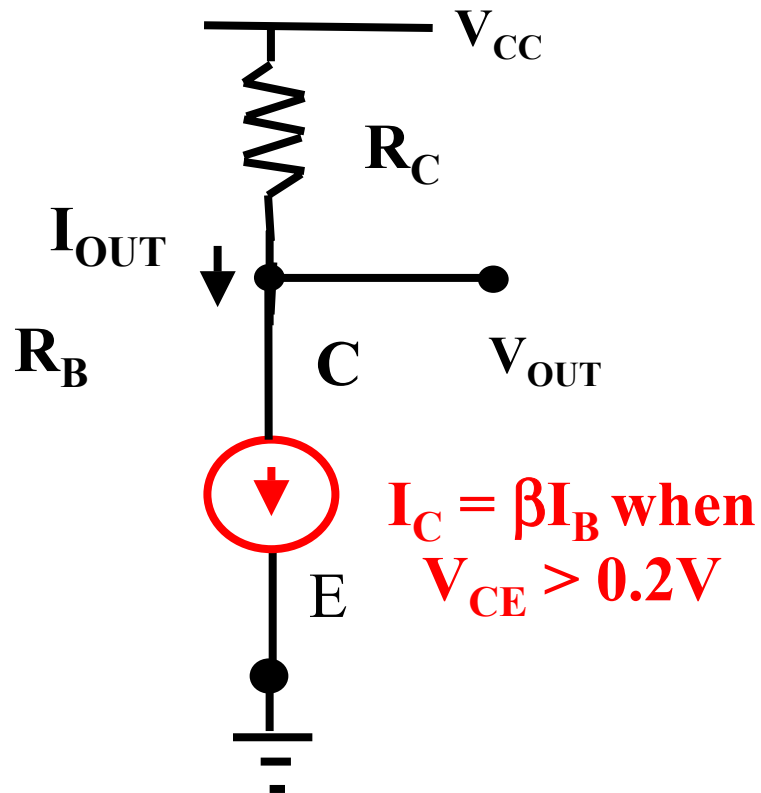
## npn Bipolar Transistor: Collector Circuit Analysis



**Cutoff:**  $V_{BE} < 0.7V$

$$I_B = I_C = 0$$

**Forward Active:**  $V_{BE} = 0.7V$   
and  $V_{CE} > V_{CE-SAT} = 0.2V$

$$I_B = (V_{IN} - 0.7V) / R_B$$

$$I_C = \beta I_B$$


**Saturated:**  $V_{BE} = 0.7V$   
and  $V_{CE} = V_{CE-SAT} = 0.2V$

$$I_B = (V_{IN} - 0.7V) / R_B$$

$$I_{C-SAT} = (V_{CC} - 0.2V) / R_C$$


The collector current is programmed by the base current to be  $\beta$  times the base current. However, the current stops growing larger whenever the collector base voltage drops to 0.2V.
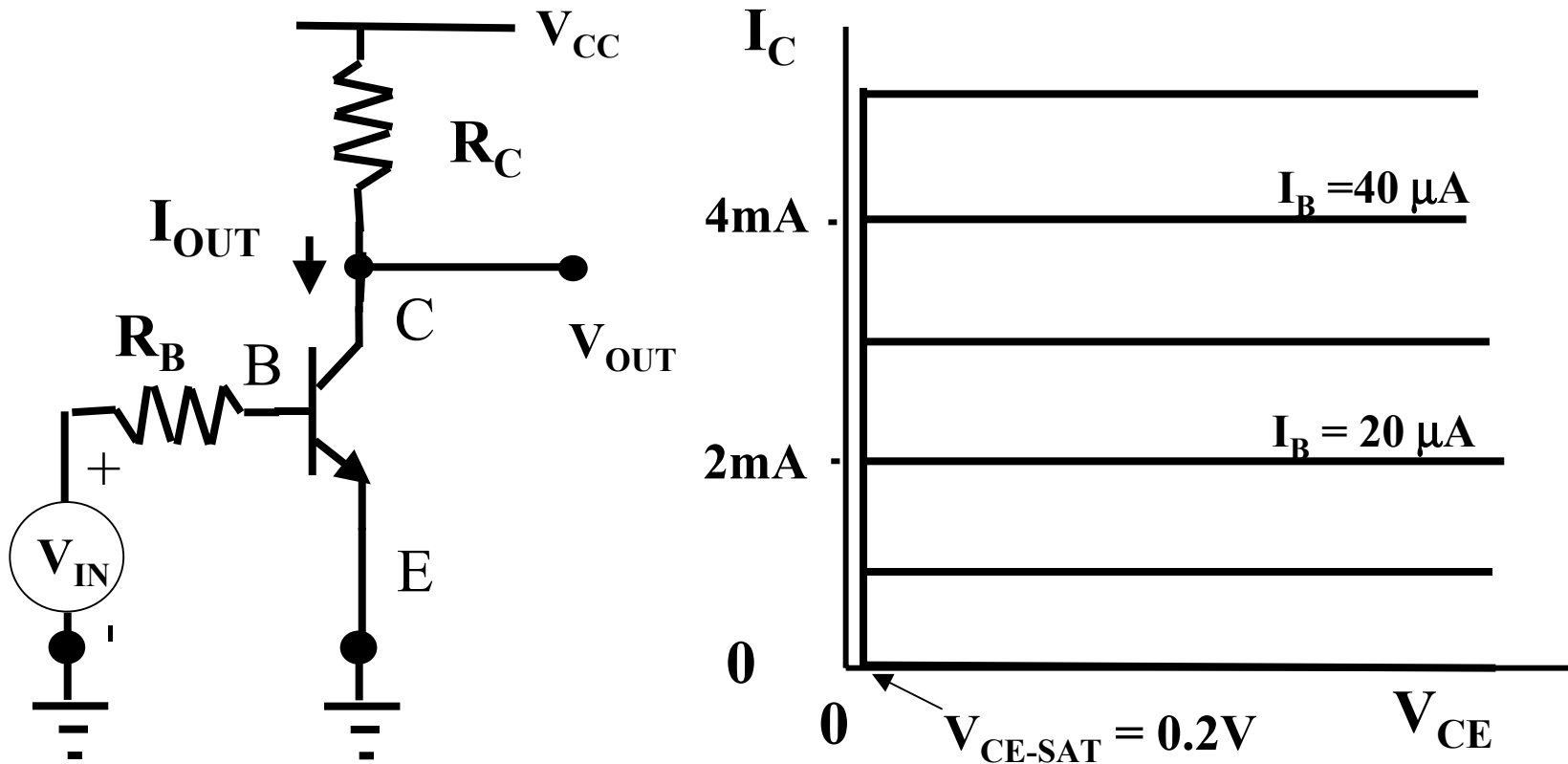
## npn Bipolar Transistor: $I_C$ vs. $V_{CE}$ Graph




The  $I_C$  versus  $V_{CE}$  graph for the first order model is a set of horizontal lines with heights  $\beta$  times  $I_B$ . Loadline techniques can easily be applied.
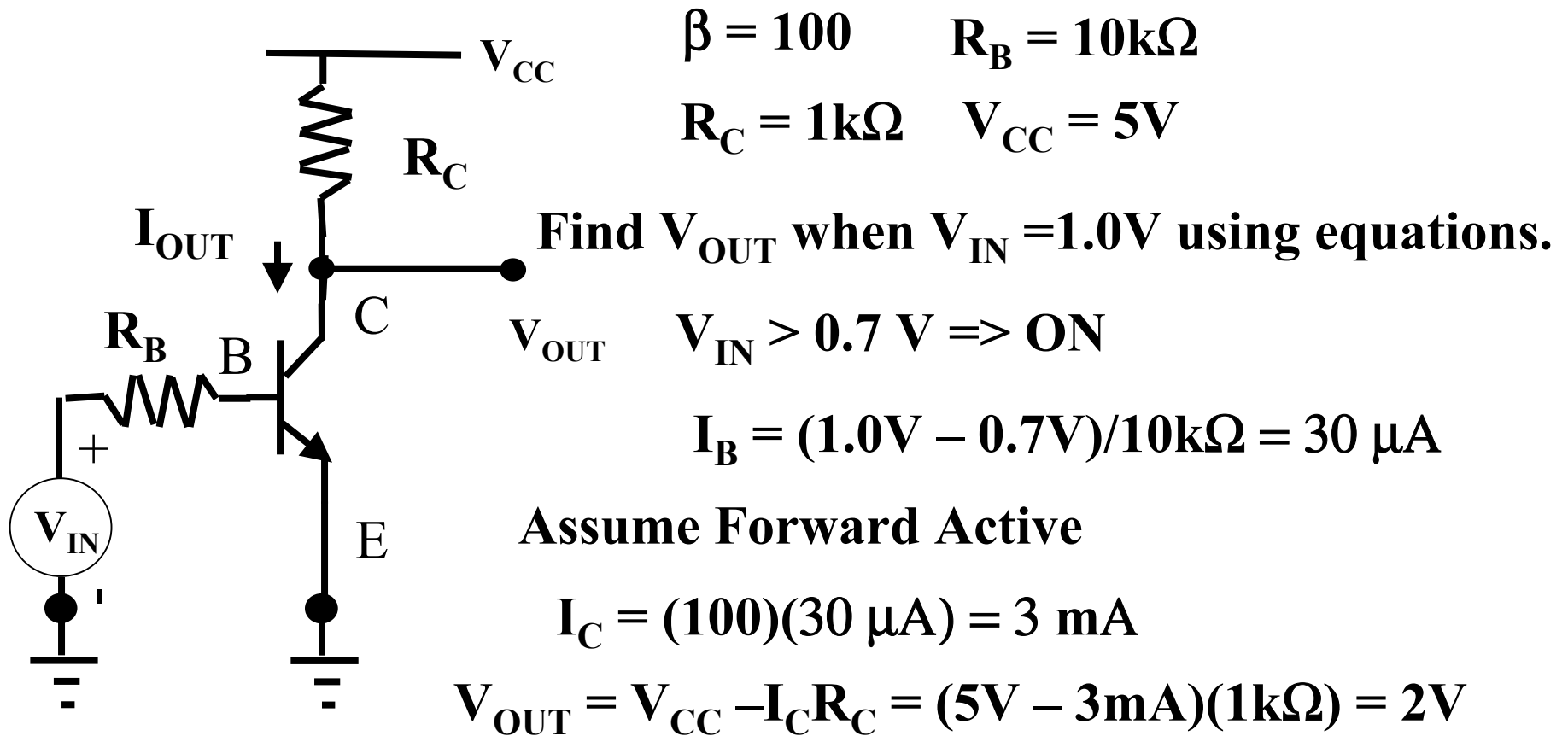
## npn Bipolar Transistor: Example Circuit



Check Assumption :  $V_{CE} = 2.0\text{V} - 0\text{V} = 2\text{V} > 0.2\text{V} \Rightarrow \text{Forward Active}$
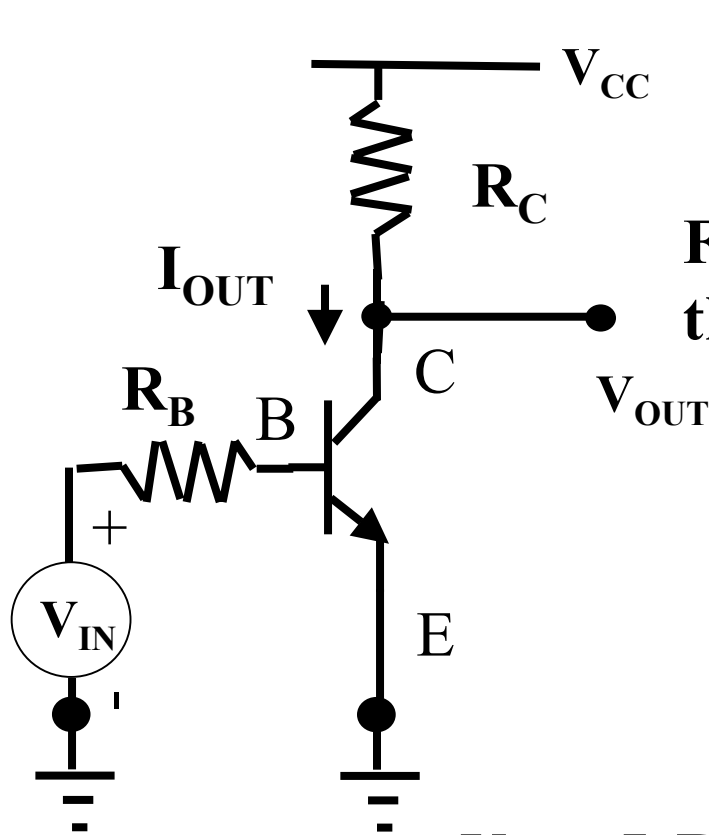
## npn Bipolar Transistor: Maximum Current



$$\beta = 100 \quad R_B = 10\text{k}\Omega$$

$$R_C = 1\text{k}\Omega \quad V_{CC} = 5\text{V}$$

**Find the maximum collector current and the input voltage at which it occurs.**


**Assume Edge of Saturation where still Forward Active**

$$I_C = (V_{CC} - V_{CE-SAT})/R_C \\ = (5\text{V} - 0.2\text{V})/1\text{k}\Omega = 4.8 \text{ mA}$$

$$I_B = I_C/\beta = 4.8\text{mA}/100 = 48 \mu\text{A}$$

$$V_{IN} = I_B R_B + 0.7\text{V} = (48 \mu\text{A})(1\text{k}\Omega) + 0.7\text{V} = 1.18\text{V}$$
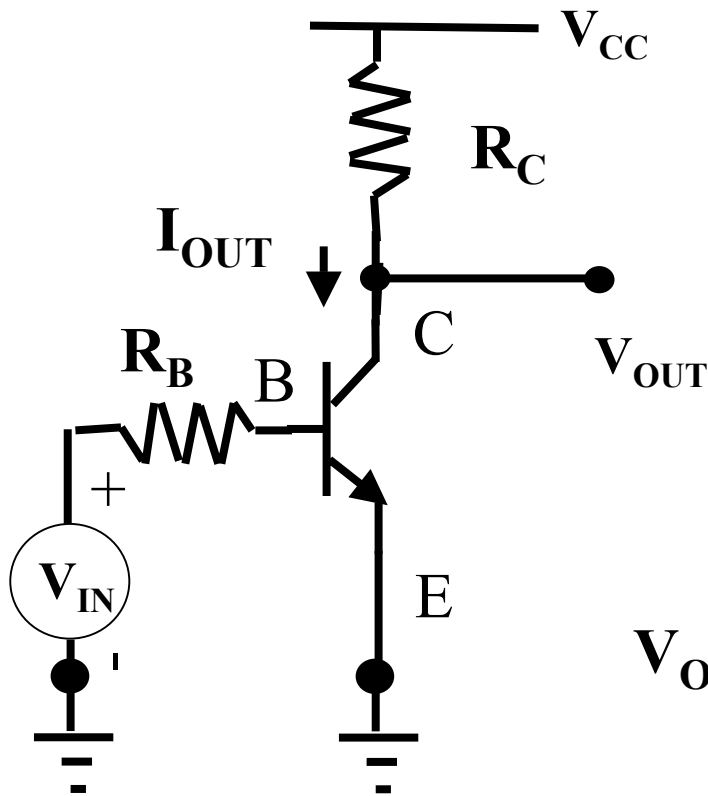
## npn Bipolar Transistor: $V_{OUT}$ vs. $V_{IN}$



$\beta = 100$       $R_B = 10k\Omega$

$R_C = 1k\Omega$       $V_{CC} = 5V$

1)  $V_{OUT}$  is  $V_{CC}$  till  $V_{IN}$  reaches 0.7V

2)  $V_{OUT}$  decreases linearly with  $V_{IN}$  until  $V_{OUT}$  reaches 0.2V at  $V_{IN} = 1.18V$

3)  $V_{OUT}$  remains at 0.2 V for all values of  $V_{IN}$  above 1.18V

