

## Lecture 23


# P-MOS Device and CMOS Inverters

- A) P-MOS Device Structure and Operation
- B) Relation of Current to  $t_{OX}$ ,  $\mu$   $V_{LIMIT}$
- C) CMOS Device Equations and Use
- D) CMOS Inverter  $V_{OUT}$  vs.  $V_{IN}$
- E) CMOS Short Circuit Current

**Reading: Schwarz and Oldham, pp. 518-526**

# CMOS = Complementary MOS

(PMOS is a second Flavor)

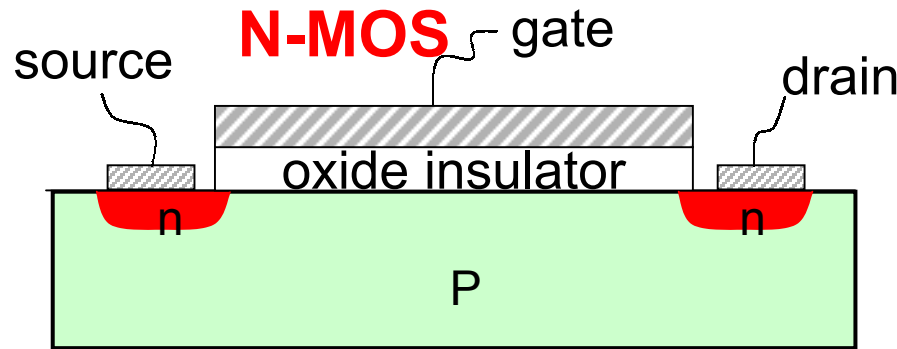


In this device the gate controls electron flow from source to drain.  
It is made in p-type silicon.

## The NEW FLAVOR! P-MOS

In this device the gate controls hole flow from source to drain.



It is made in n-type silicon.

 

# PMOS

In this device the gate controls hole flow from source to drain.

It is made in n-type silicon.

  

What if we apply a big negative voltage on the gate?





If  $|V_{GS}| > |V_t|$  (both negative)

then we induce a + charge on the surface (holes)

# NMOS and PMOS Compared Version Date 12/02/01

NMOS	
“Body”	– p-type
Source	– n-type
Drain	– n-type
$V_{GS}$	– positive
$V_T$	– positive
$V_{DS}$	– positive
$I_D$	– positive (into drain)

PMOS	
“Body”	– n-type
Source	– p-type
Drain	– p-type
$V_{GS}$	– negative
$V_T$	– negative
$V_{DS}$	– negative
$I_D$	– negative (into drain)

    

# CMOS


Version Date 12/02/01

**Challenge: build both NMOS and PMOS on a single silicon chip**

**NMOS needs a p-type substrate**

**PMOS needs an n-type substrate**

**Requires extra process steps**


 


## Why do we want PMOS?

We already have the ideal switch to connect any node to ground.


An NMOS transistor with gate held high has a very low resistance and essentially switches a node to ground (logic low).

  We also need a switch to switch nodes to whatever voltage is chosen as logic high (typically  $V_{DD}$ ).




- **A PMOS transistor is just the ticket. It is precisely as ideal a switch for connections to high as NMOS transistors are for connections to low.**
- **What's cool is that there is little more to learn about PMOS. These devices are essentially the same as NMOS except *all signs on V and I are reversed.***


# THE BASIC STATIC CMOS INVERTER

 

For  $V_{in} > 1.5V$  NMOS on , PMOS off

 

For  $V_{in} < 1V$  NMOS off , PMOS on

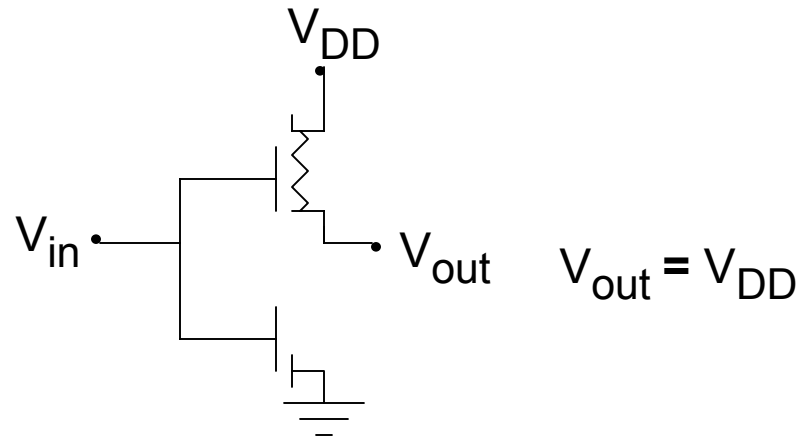

**Example for Discussion:**

**NMOS:  $V_{Tn} = 1V$**

**PMOS:  $V_{Tp} = -1V$**

**Let  $V_{DD} = 2.5V$**

# MOS Current Levels

**The current values depend on the properties of silicon, geometrical layout, design style and technology node.**

**n-type silicon has a carrier mobility that is 2 to 3 times higher than p-type.**

**The current proportion to the gate width/length in the geometrical layout.**

**Design styles may restrict all NMOS and PMOS to be of a predetermined fixed size.**

**The current per unit width of the gate increases nearly inversely with the linewidth.**



## Relation of Current to Physical Parameters

$$I_D = \mu_n C_{ox} \left( \frac{W}{L} \right)_n (V_{GS} - V_T) \cdot V_{OUT-SAT-n}$$

Mobility of carriers  $\nearrow$   
 Oxide thickness  $\nearrow$   
 Geometrical Layout  $\nearrow$   
 Excess Gate drive  $\nearrow$   
 Voltage of scattering velocity limit  $\nearrow$

$$\mu_n = 500 (cm^2 / Vs) \quad \mu_p = 150 (cm^2 / Vs)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(8.85 \times 10^{-14} F / cm)(3.9)}{6 \times 10^{-7} cm} = 5.75 \times 10^{-7} F / cm^2$$

$$V_{OUT-SAT-n} = E_{Crit} \cdot L = 10^4 (V / cm) \cdot 0.25 \times 10^{-4} cm = 0.25V$$

# CMOS Device Parameters at 0.25 $\mu\text{m}$

Gate length is 0.25  $\mu\text{m}$  = 250 nm

$$V_{DD} = 2.5V$$

	$V_T$ (V)	$V_{OUT-SAT}$ (V)	$k'$ ( $\mu\text{A}/\text{V}^2$ )
NMOS	0.43	0.63	100
PMOS	0.4	1	25

These parameters are from re-fitting I vs. V data in Chapter 3 of the EECS 141 Text Book by Rabaey with saturation current model we are using in EE42.

Here  $V_{IN} = V_{DD}$  is used to estimate the maximum  $I_{DS}$

$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

$$I_{OUT-SAT-D} = \left(100 \mu\text{A}/\text{V}^2\right) \left(\frac{0.375}{0.25}\right) (2.5V - 0.43V)(0.63V) = 196 \mu\text{A}$$

## Saturation Current 0.25 $\mu\text{m}$ NMOS Model

Current  $I_{\text{OUT}}$  only flows when  $V_{\text{IN}}$  is larger than the threshold value  $V_{\text{TD}}$  and the current is proportional to  $V_{\text{OUT}}$  up to  $V_{\text{OUT-SAT-n}}$  where it reaches the saturation current

$$I_{\text{OUT-SAT-n}} = k'_n \left( \frac{W}{L} \right)_n (V_{\text{IN}} - V_{\text{Tn}}) V_{\text{OUT-SAT-n}}$$

Note that we have added an extra parameter to distinguish between threshold ( $V_{\text{TD}}$ ) and saturation ( $V_{\text{OUT-SAT-D}}$ ).

Example:


$$k_n = 100 \mu\text{A}/\text{V}^2 \quad W = 0.375 \mu\text{m}$$

$$V_{\text{Tn}} = 0.43\text{V} \quad V_{\text{DD}} = 2.5\text{V}$$

$$V_{\text{OUT-SAT-n}} = 0.63\text{V}$$

$$I_n = 100 \frac{\mu\text{A}}{\text{V}^2} \left( \frac{0.375}{0.25} \right) (1.25\text{V} - 0.4\text{V}) 0.63\text{V}$$

$$= 77.5 \mu\text{A}$$

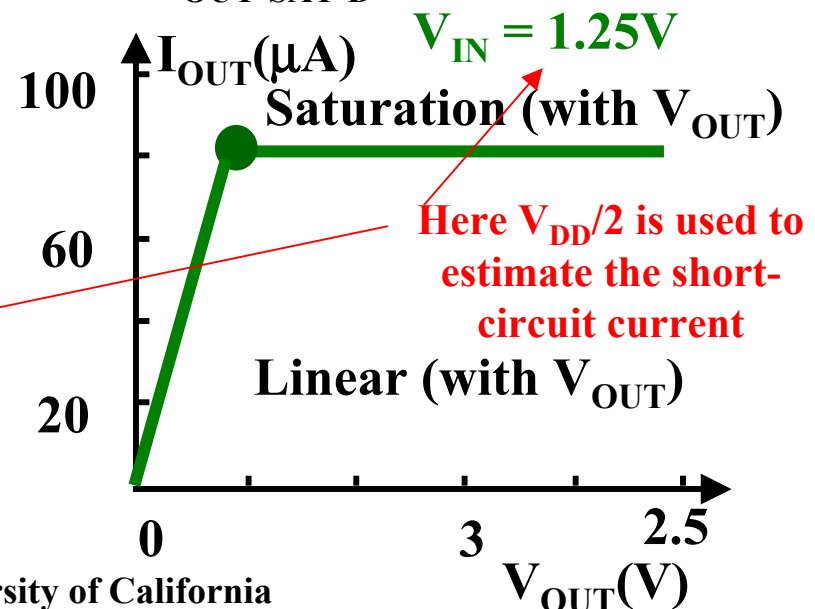

## Saturation Current 0.25 $\mu\text{m}$ PMOS Model

Current  $I_{\text{OUT}}$  only flows when  $V_{\text{IN}}$  is smaller than  $V_{\text{DD}}$  minus the threshold value  $V_{\text{TU}}$  and the current is proportional to  $(V_{\text{DD}} - V_{\text{OUT}})$  up to  $(V_{\text{DD}} - V_{\text{OUT-SAT-p}})$  where it reaches the saturation current

$$I_{\text{OUT-SAT-p}} = k'_p \left( \frac{W}{L} \right)_p \left( V_{\text{DD}} - V_{\text{IN}} - |V_{\text{Tp}}| \right) V_{\text{OUT-SAT-p}}$$

**Example:**

$$k'_p = 25 \mu\text{A}/\text{V}^2$$

$$W = 0.75 \mu\text{m}$$


$$V_{\text{Tp}} = 0.4\text{V}$$

$$V_{\text{DD}} = 2.5\text{V}$$


$$V_{\text{OUT-SAT-p}} = 1\text{V}$$

$$I_p = 25 \frac{\mu\text{A}}{\text{V}^2} \left( \frac{0.75}{0.25} \right) (2.5\text{V} - 1.25\text{V} - 0.4\text{V}) 1\text{V}$$

$$= 63.8 \mu\text{A}$$

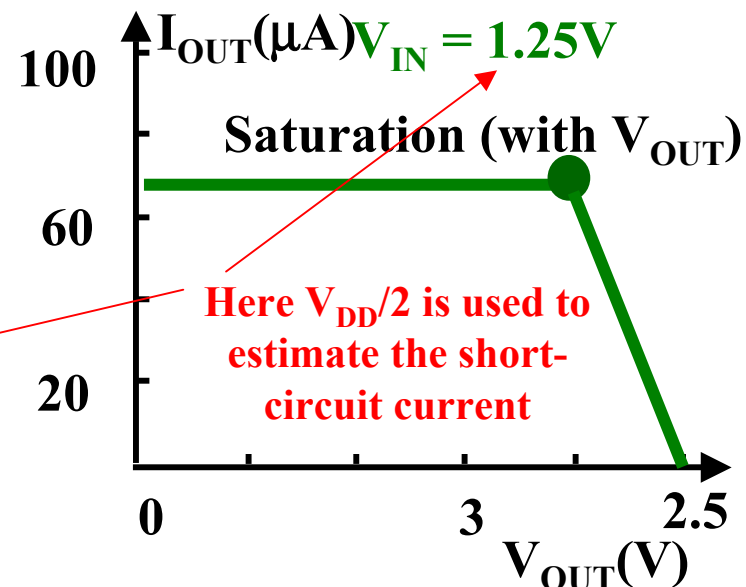
 
# Voltage Transfer Function for the 0.25 $\mu\text{m}$ CMOS Inverter



# Finding $V_M$ for $0.25 \mu\text{m}$ Inverter

At  $V_M$ ,

1)  $V_{\text{OUT}} = V_{\text{IN}} = V_M$

2) Both devices are in saturation

3)  $I_{\text{OUT-SAT-n}} = I_{\text{OUT-SAT-p}}$

Result will depend on  
(W/L) ratios.

$$I_{\text{OUT-SAT-n}} = k'_n \left( \frac{W}{L} \right)_n (V_{\text{IN}} - V_{Tn}) V_{\text{OUT-SAT-n}} =$$

$$I_{\text{OUT-SAT-p}} = k'_p \left( \frac{W}{L} \right)_p (V_{\text{DD}} - V_{\text{IN}} - V_{Tp}) V_{\text{OUT-SAT-p}}$$

Substitute  $V_M$  Solve for  $V_M$

For  $(W/L)_n = 1.5$  and  $(W/L)_p = 3.0$   $V_M$  is **1.17V**

## CMOS Short-Circuit Current

When  $V_{IN}$  is at an intermediate value both the NMOS and PMOS can conduct simultaneously.

If in addition  $V_{OUT}$  is at an intermediate value, both the NMOS and PMOS devices will have sizeable currents and only the difference between their currents will be flowing through the load.

Most of the current will simply flow from the power supply through both devices to ground as what is termed a 'short-circuit current.'

Example for the above inverter at the an instant  $V_{IN} = 1.25V$  and  $V_{OUT} = 1.25V$

$$I_p = 63.8 \mu A \text{ and } I_n = 77.5 \mu A$$


This means  $63.8 \mu A$  flows directly to ground and only  $13.7 \mu A$  flows out of the load and into the NMOS and on to ground.

**Lecture 23**

Version Date 12/02/01

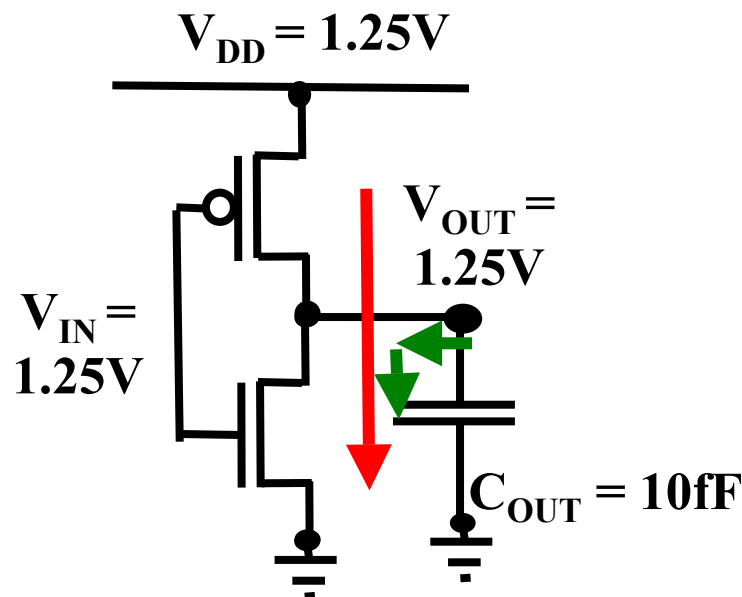**CMOS Inverter in Short-Circuit Condition**

Assume the CMOS inverter from above with  
 $V_{IN} = 1.25V$  and  $V_{OUT} = 1.25V$  driving a 10 fF capacitor



$I_{\text{Short-Circuit}} = 63.8 \mu A$   
 (We used  $V_{IN} = V_{DD}/2$ )

$I_{\text{Discharge\_Load}} = 13.7 \mu A$   
 (We Used  $V_{IN} = V_{DD}/2$ )

What happens to the output signal?

The capacitor slowly discharges to try to find an output voltage that balances the NMOS and PMOS currents for the given value of  $V_{IN}$ .

$$\frac{\partial V}{\partial t} = \frac{I}{C} = \frac{13.7 \mu A}{10 \text{ fF}} = 1.37 (V / ns)$$