

Lecture Review

Version Date 12/04/01

Review For Final

FINAL EXAM

12:30-3:30 Friday, December 14th, F0295 Haas

Closed Book, Device Equations Provided

Bring calculator, Paper Provided

Review Sessions:

Proposed 5-6:30 PM Mon Dec 10

Proposed 5-6:30 PM Wed Dec 12

Office hours:

Professor Neureuther: 11 M, Tu, W, Th, F but 10-11 on F Dec 14th

TA's: TBA on web

Congratulations Jason Gatt and Kevin Ha “Best in Show” in Tutbot/Calbot Contest



EE 42 Final Exam: Design Guidelines

- **Cover Material Since Midterm 2 at 2X compared to material on Midterms 1 and 2.**
 - About 100 of 200 points on material since Midterm 2 and about 100 points on material prior to Midterm 2
- **Change to an accomplishment basis instead of B- average standard normal distribution.**
 - about 60 points of B level material
 - about 60 points of A level material
 - as a consequence exam average will be 120/200
- **Results on 3 exams will be weighted by relative spread before merging to prevent large variation on final from wiping out Midterms.**

Key Material Since Midterm #2

- CMOS Static Type Analysis (big)
 - Current given voltage, V_{OUT} vs. V_{IN} , Short Circuit Current, D.C. power
- CMOS Transient Analysis (big)
 - Sources and amount of capacitance, propagation delay, a.c. power, clocked latches
- Diode and Bipolar Transistor (medium)
 - No physics but large signal analysis
- Physics (small)
 - Resistance from carrier motion, field effect carriers and resistance

About 100 pts with about

10-20 pts C, 20-30 pts B, and 40-50 pts A.


Key Material Before Midterm #2

- Equivalent Circuits and Load Lines
 - Simplify load circuits, find V_{OUT} vs. V_{IN}
 - Dependent Sources
 - Gain, input and output resistance
 - Ideal Op-Amps
 - Transients
 - Gates
 - Logic function and timing diagrams
- Total of about 100
Pts with about
50-60 pts C,
30-40 pts B, and
10-20 pts A.**

PULSE: Output is Rising exponential then Falling exponential

Lecture 7

 Example: Switch rises at $t = 0$, falls at $t = 0.1, 1$ or $10 \mu\text{sec}$ (Do $1 \mu\text{sec}$ case)



Now starting at $1 \mu\text{sec}$ we are discharging the capacitor so the form is a falling exponential with initial value 3.16 V:


Solution: for $RC = 1 \mu\text{sec}$:
during the first rise V obeys:

$$V = 5 \left[1 - e^{-\frac{t}{10^{-6}}} \right]$$

Thus at $t = 1 \mu\text{sec}$, rising voltage reaches


$$5 \left[1 - e^{-1} \right] = 3.16 \text{V}$$

What is equation?

 

EXAMPLE WITH BOTH SPECIAL CASES

Lecture 8

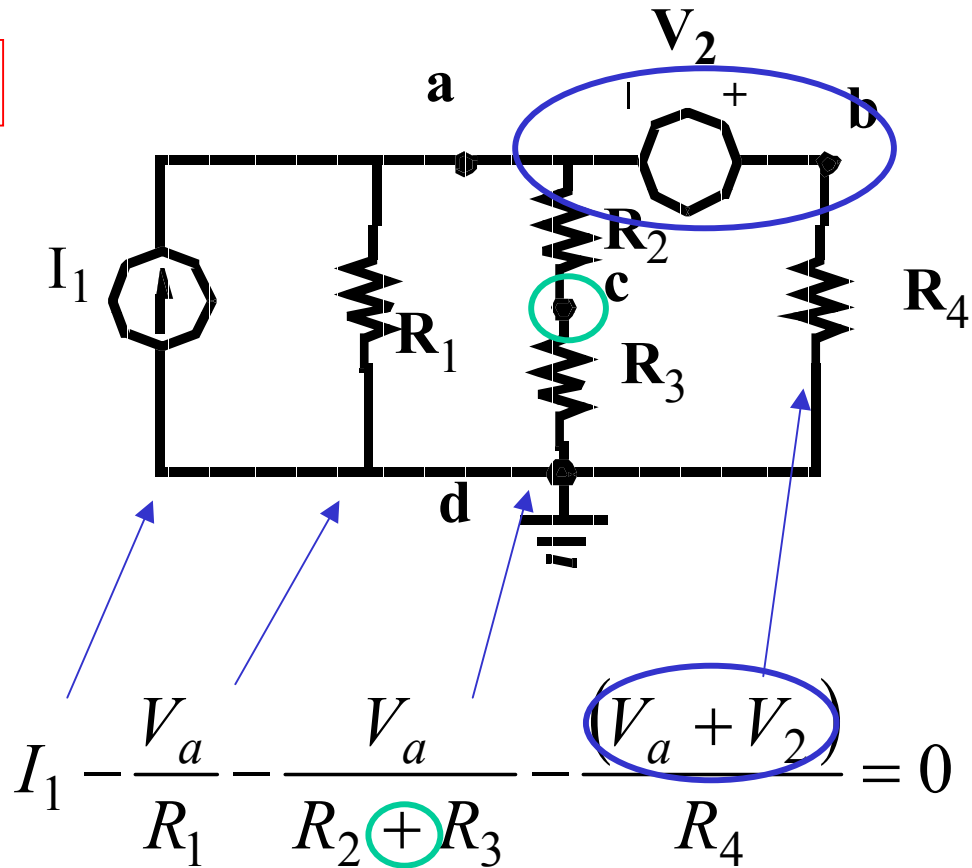


Lecture 10

Version Date 12/04/01

How to Combine Gate to Produce a Desired Logic Function? (More basic Logical Synthesis)

Example:

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

 

$$F = \bar{A} \bar{B} C + AB \bar{C}$$

Lecture 11


**Logical Synthesis
Guided by DeMorgan's Theorem**

DeMorgan's Theorem :

$$A + B + C = \overline{\overline{A} \overline{B} \overline{C}} \quad \text{or} \quad \overline{A} + \overline{B} + \overline{C} = \overline{[A B C]}$$

 Example of Using DeMorgan's Theorem:

$$F = A \bullet B + C \bullet D \bullet E = \overline{\overline{A \bullet B} \bullet \overline{C \bullet D \bullet E}}$$



Thus any sum of products expression can be immediately synthesized from NAND gates alone

Lecture 11

Logical Synthesis of XOR

| A | B | F |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


$$F = A \bullet \bar{B} + \bar{A} \bullet B$$

We Need a Timing Diagram!

Delay 1

Delay 2


Delay 3

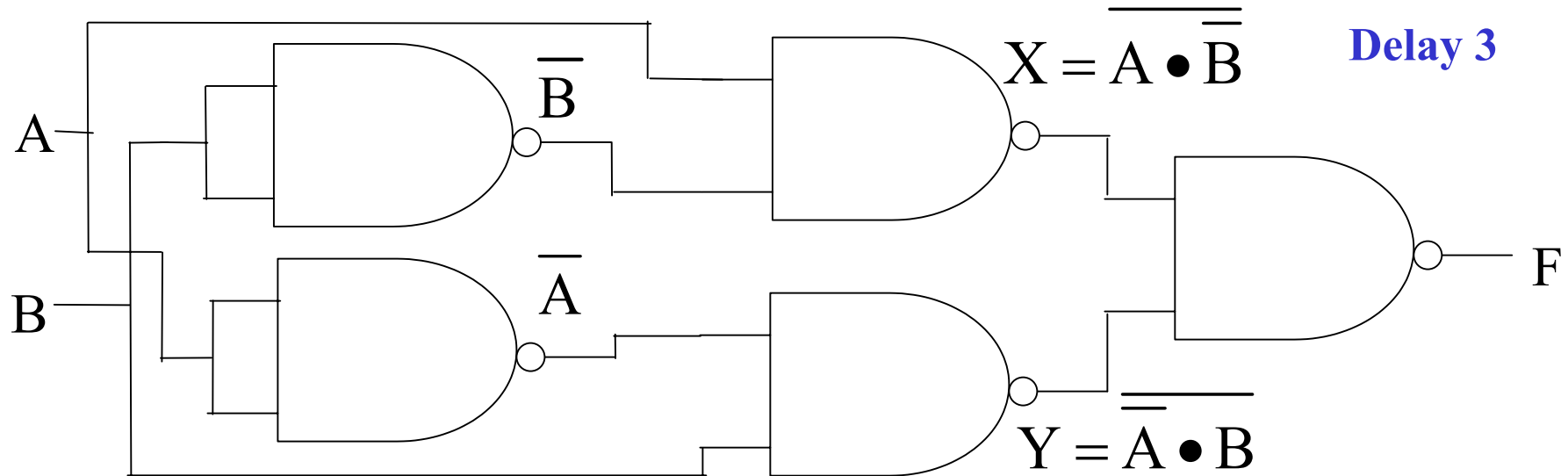

Lecture 11

Timing Diagram for Delays in Logic

Logic level

 


Lecture 11

TIMING DIAGRAMS

Version Date 12/04/01

Show transitions of variables vs time

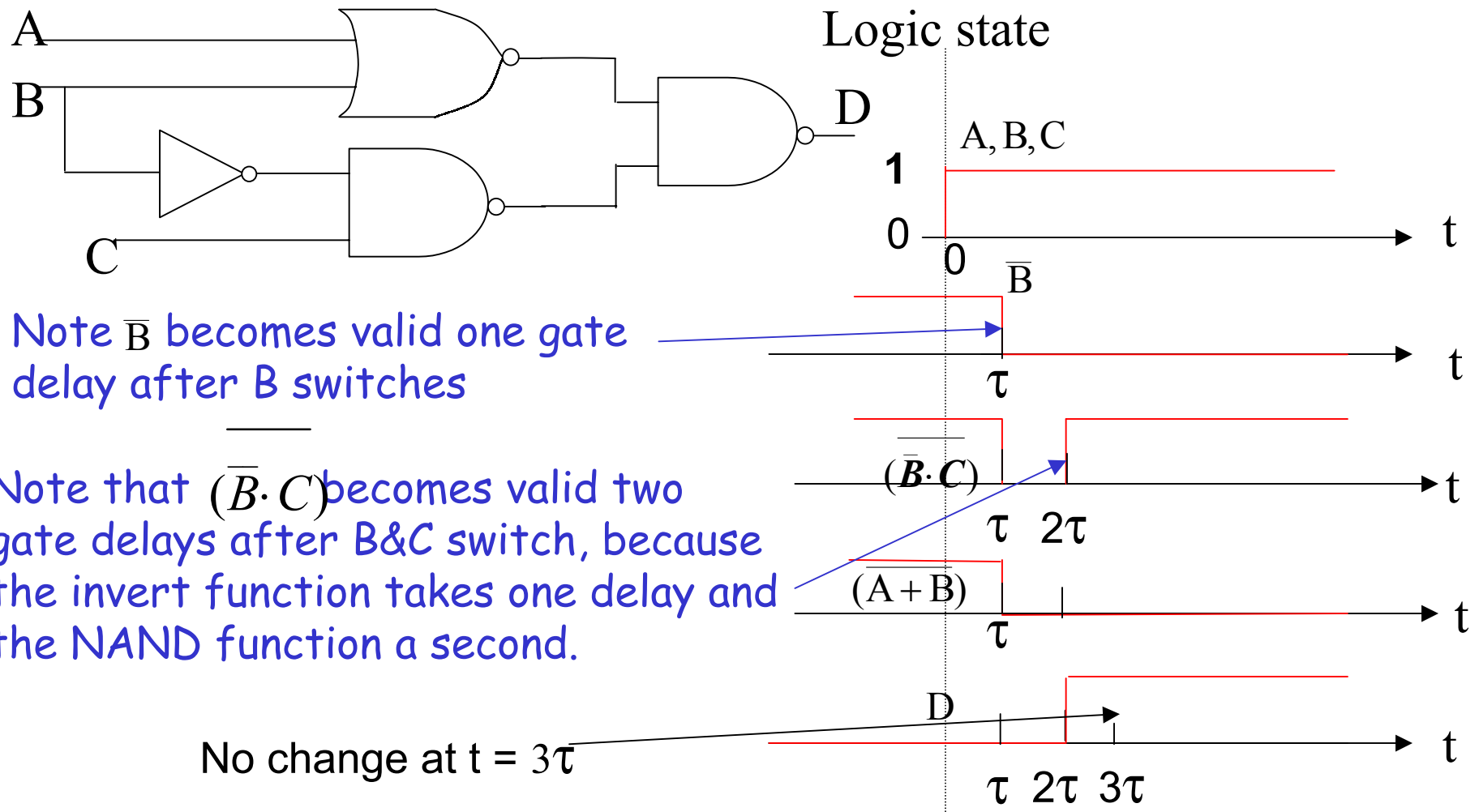

Note \bar{B} becomes valid one gate delay after B switches

Note that $(\bar{B} \cdot C)$ becomes valid two gate delays after B&C switch, because the invert function takes one delay and the NAND function a second.

No change at $t = 3\tau$

The 4 Basic Linear Dependent Sources

Lecture 13

Constant of proportionality

Parameter being sensed





Output

Voltage-controlled voltage source ... $V = A_v V_{cd}$

Current-controlled voltage source ... $V = R_m I_c$

Current-controlled current source ... $I = A_i I_c$


Voltage-controlled current source ... $I = G_m V_{cd}$

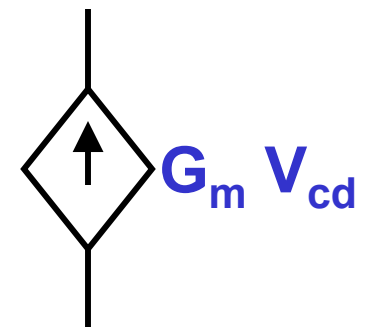   

Lecture 13

Version Date 12/04/01

 EXAMPLE CIRCUIT: INCREASED OUTPUT RESISTANCE



Analysis: apply i_{TEST} and evaluate v_{TEST}


Unknowns: i_{TEST} , v_{TEST} , v_{IN} , v_E

Need 3 equations to find the ratio of i_{TEST} / v_{TEST}

$v_{IN} = -v_E$ and is **not zero!**
KCL at v_E
KVL at v_{OUT}

Intuitive Explanation: $G_m V_{IN}$ burps current which has to also go through R_O . This raises v_{TEST} and the output impedance v_{TEST} / i_{TEST}

Finish this in the homework

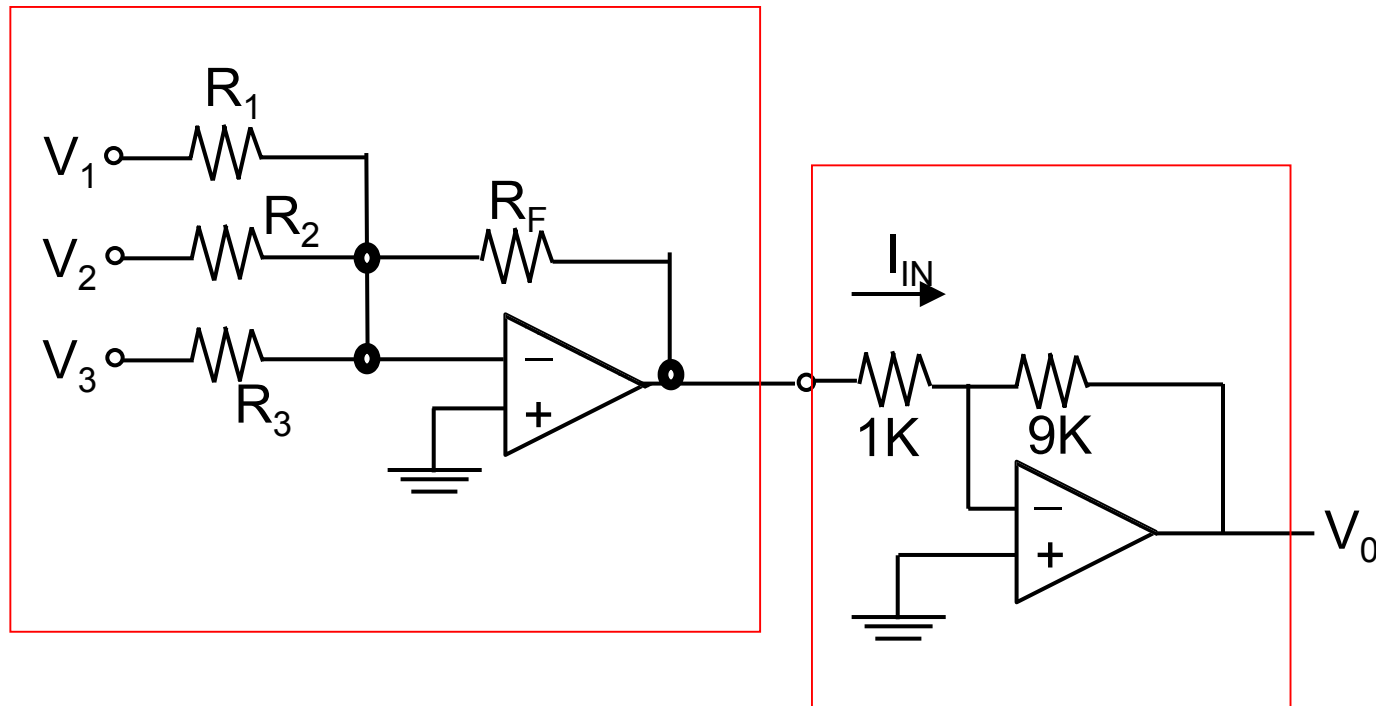Lecture 14**CASCADE OP-AMP CIRCUITS**

How do you get started on finding V_O ?

Hint: Identify Stages

Hint: I_{IN} does not affect V_{O1}


See the further examples of op-amp circuits in the reader

Logic Gates – How are they built in practice?


Lecture 15



 
Current flows when V_{IN} is high
 Can be modeled by a $10k\Omega$ resistor



Valves in Series => NAND

 

Valves in Parallel => NOR

 


What goes in this box?

How does it affect digital performance?


Composite Current Plot for the 42PD Circuit with 200kΩ Load to Ground

Lecture 15

 

Voltage Transfer Function for the 42PD Logic Circuit w/wo Load

Lecture 15

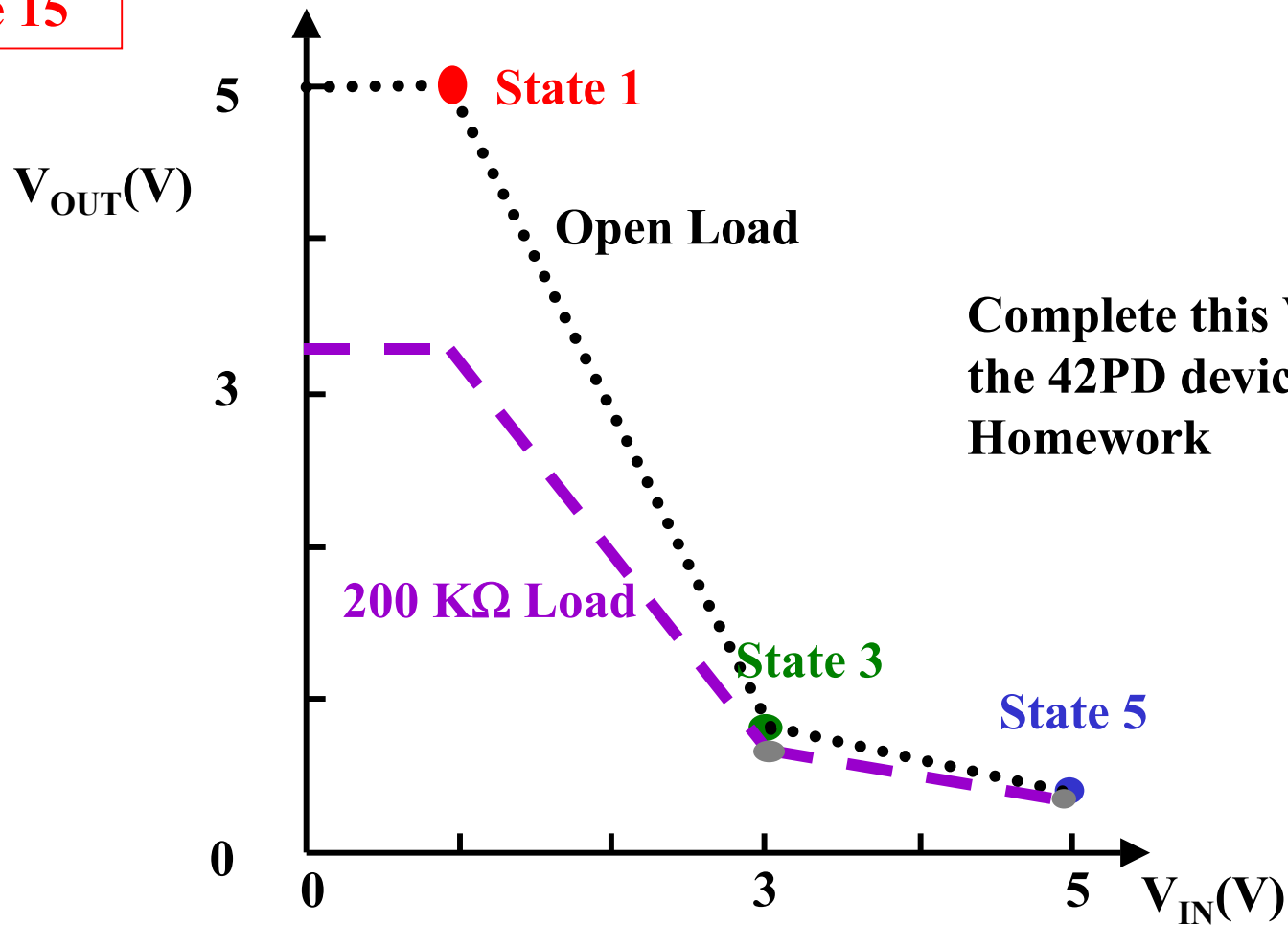


Pull-Down and Pull-Up Must Complement Rather Than Fight Each Other

Lecture 16


Reduce the Short-Circuit Current by making either one or the other device off.

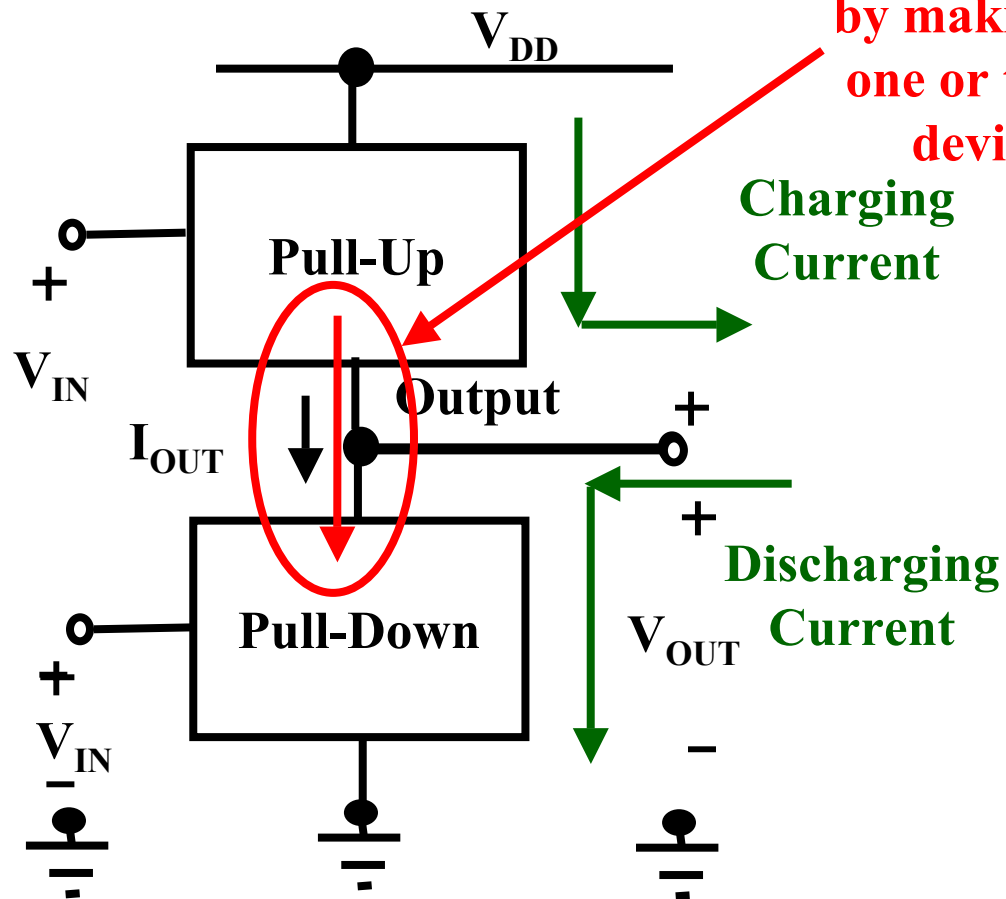Input for State Control Signal
Share Same Signal
Input for State Control Signal




Composite I_{OUT} vs. V_{OUT} for CMOS

Lecture 17

 

Voltage Transfer Function for the Complementary Logic Circuit

Lecture 17

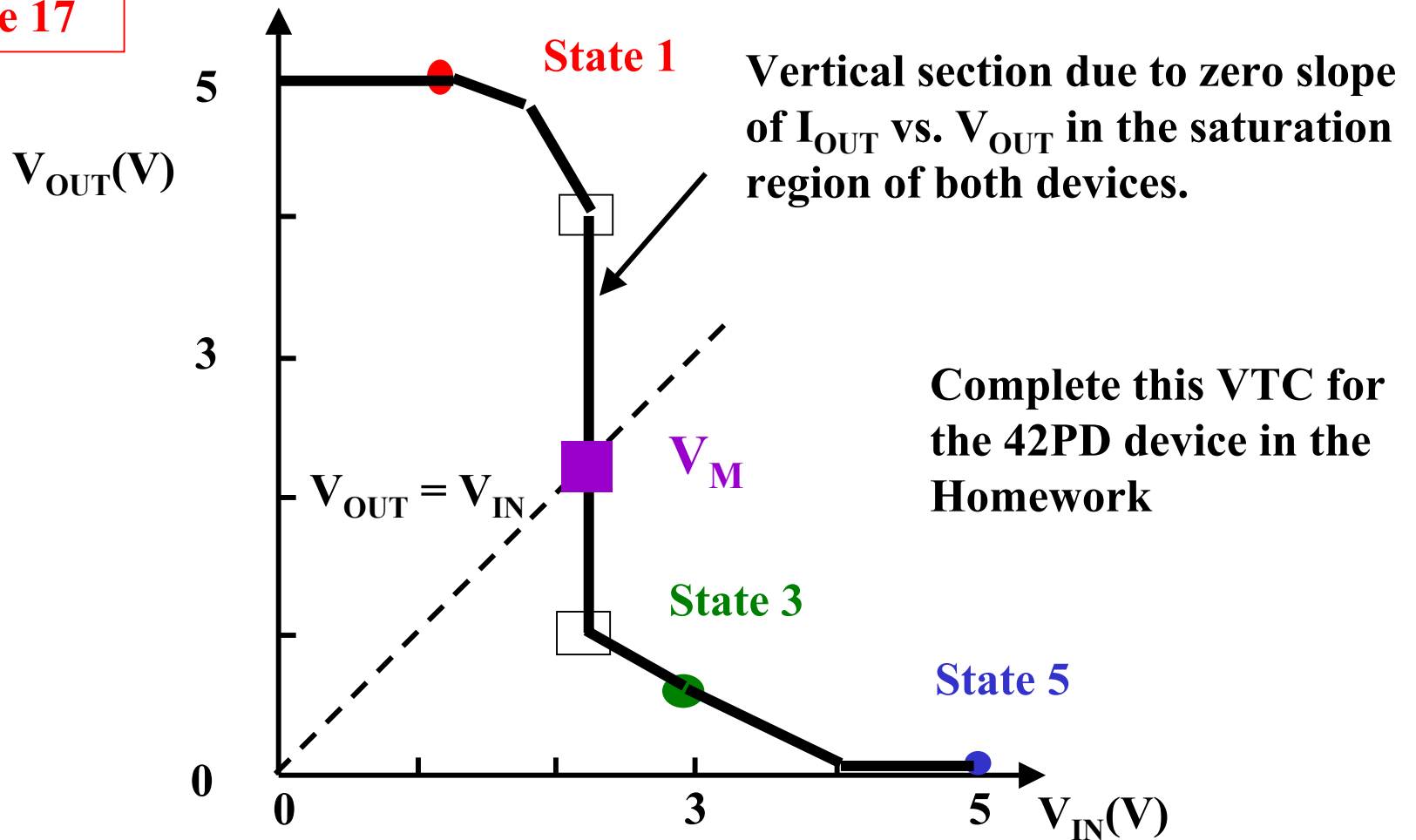

Lecture 17**Method for Finding V_M** **At V_M ,**

- 1) $V_{OUT} = V_{IN} = V_M$
- 2) **Both devices are in saturation**
- 3) $I_{OUT-PD} = I_{OUT-PU}$

$$I_{OUT-PD} = k_D (V_{IN} - V_{TD}) V_{TD} = I_{OUT-PU} = k_U (V_{DD} - V_{IN} - V_{TU}) V_{TU}$$

Substitute V_M

Solve for V_M **Example Result: When $k_D = k_P$ and $V_{TD} = V_{TU}$, $V_M = V_{DD}/2$**

Switched Equivalent Resistance Model

Lecture 17

The above model assumes the device is an ideal constant current source.


- 1) This is not true below $V_{OUT-SAT-D}$ and leads to inaccuracies.
- 2) Combining ideal current sources in networks with series and parallel connections is problematic.

Instead define an equivalent resistance for the device by setting $0.69R_D C$ equal to the Δt found above

$$\Delta t = \frac{C_{OUT} V_{DD}}{2I_{OUT-SAT-D}} = 0.69R_D C_{OUT}$$

This gives

 
$$R_D = \frac{V_{DD}}{2 \cdot (0.69) I_{OUT-SAT-D}} \approx \frac{3}{4} \frac{V_{DD}}{I_{OUT-SAT-D}} = \frac{3}{4} \frac{5V}{100\mu A} = 37.5k\Omega$$



Each device can now be replaced by this equivalent resistor.

Logic Gate Propagation Delay (Cont.)

Lecture 17

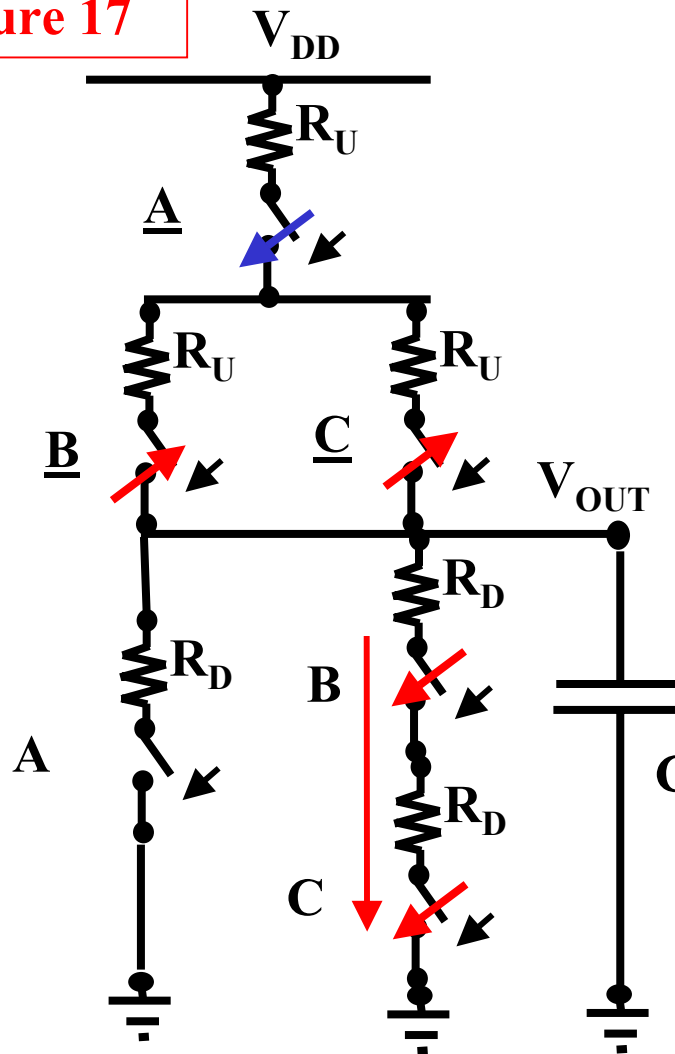

At $t=0$, B and C switch to high = V_{DD} and A remains low.


C_{OUT} discharges through the pull-down resistance of gates B and C in series.

$$\Delta t = 0.69(R_{DB} + R_{DC})C_{OUT} = 0.69(20k\Omega)(50fF) = 690 \text{ ps}$$

The propagation delay is **two times longer** than that for the inverter!

Lecture 18 Logic Gate Cascade

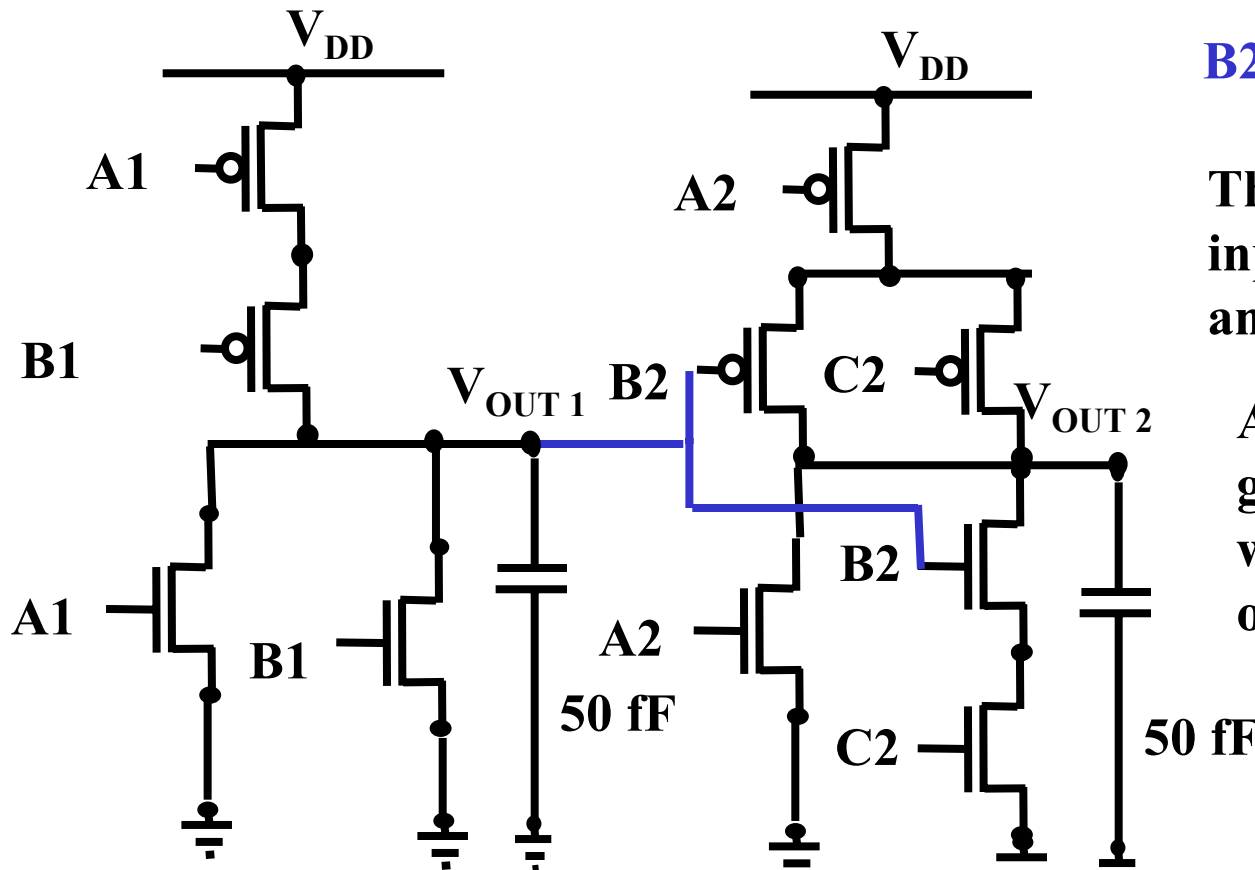To avoid large resistance due to many gates in series, logic functions with 4 or more inputs are usually made from cascading two or more 2-4 input blocks.



$$B2 = V_{OUT1}$$

The four independent input are A1, B1, A2 and C2.


A2 high discharges gate 2 without even waiting for the output of gate 1.

C2 high and A2 low makes gate 2 wait for Gate 1 output

Lecture 18

Version Date 12/04/01

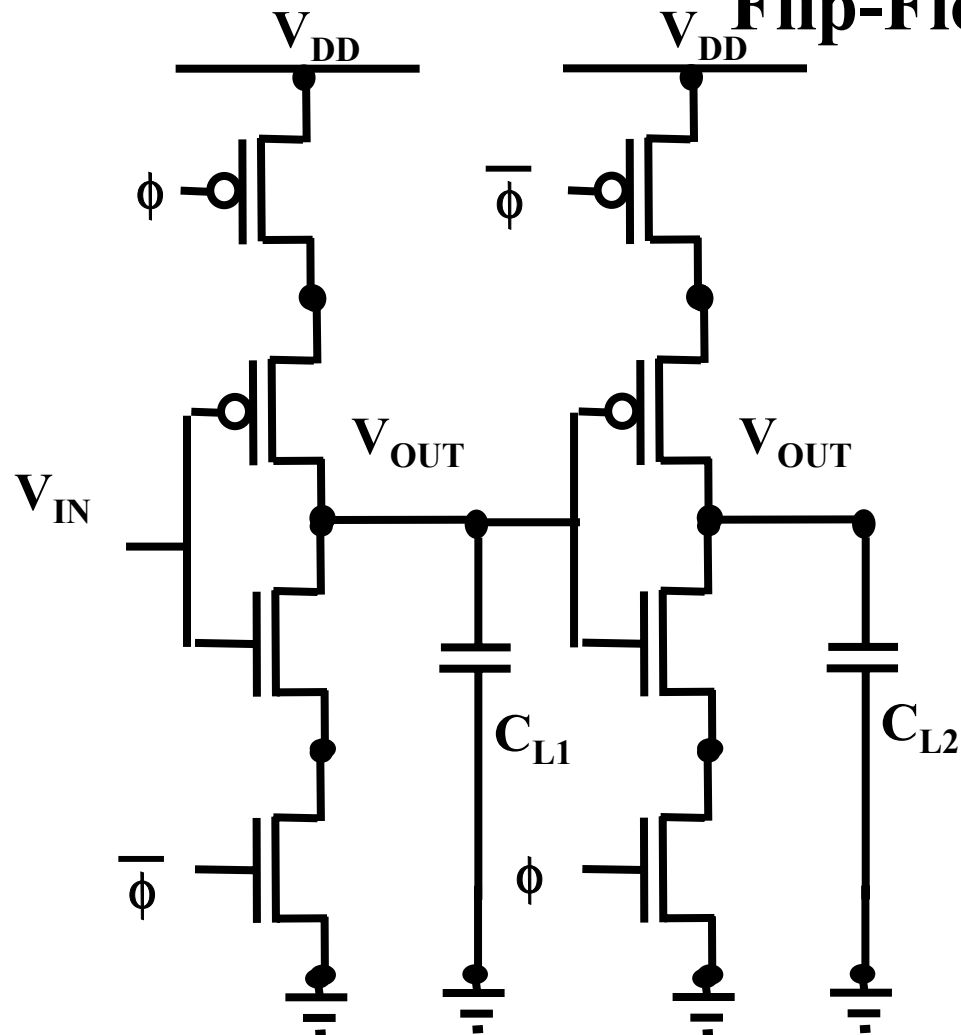A Double Latch is an Edge-Triggered D Type Flip-Flop




During the low part of the clock cycle this circuit records the input value and when the clock goes high drives V_{OUT2} to the voltage level that arrived. (This is the classic function of a D flip-flop.)

Note that this circuit is not fooled by noise on the input and makes its decision on the rising edge of the clock (**edge-triggered**).


Feedback Can Provide Memory

Lecture 19

 


Lecture 20 DIODE I-V CHARACTERISTICS AND MODELS

 The equation $I = I_0 \exp\left(\frac{qV}{kT} - 1\right)$ is graphed below for $I_0 = 10^{-15} \text{ A}$




 The characteristic is described as a “rectifier” – that is, a device that permits current to pass in only one direction. (The hydraulic analog is a “check valve”.) Hence the symbol:



Simple “Perfect Rectifier” Model


If we can ignore the small forward-bias voltage drop of a diode, a simple effective model is the “perfect rectifier,” whose I-V characteristic is given below:

 

Lecture 20


COOL THINGS A DIODE CAN DO

(Use perfect rectifier model)

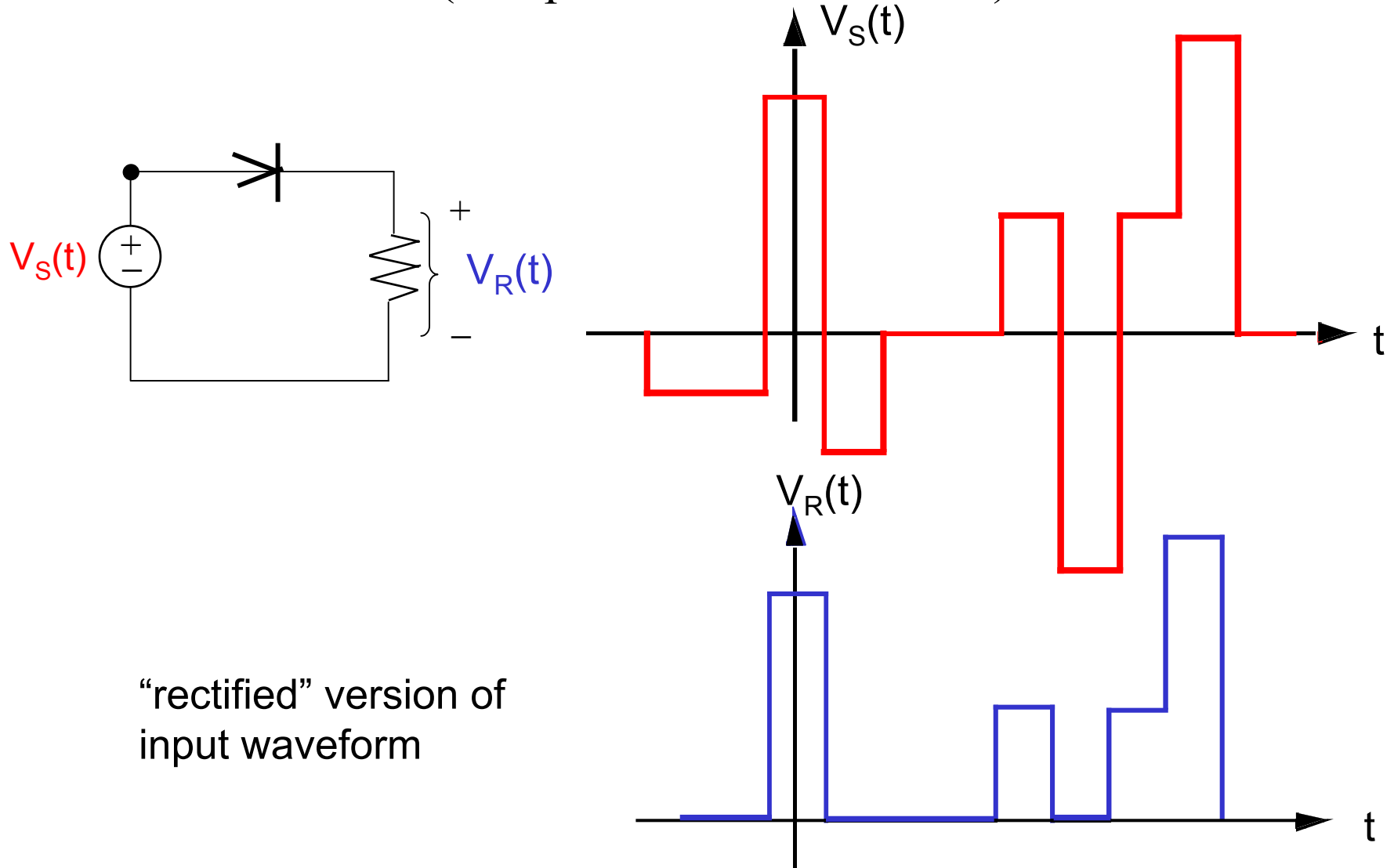

“rectified” version of input waveform

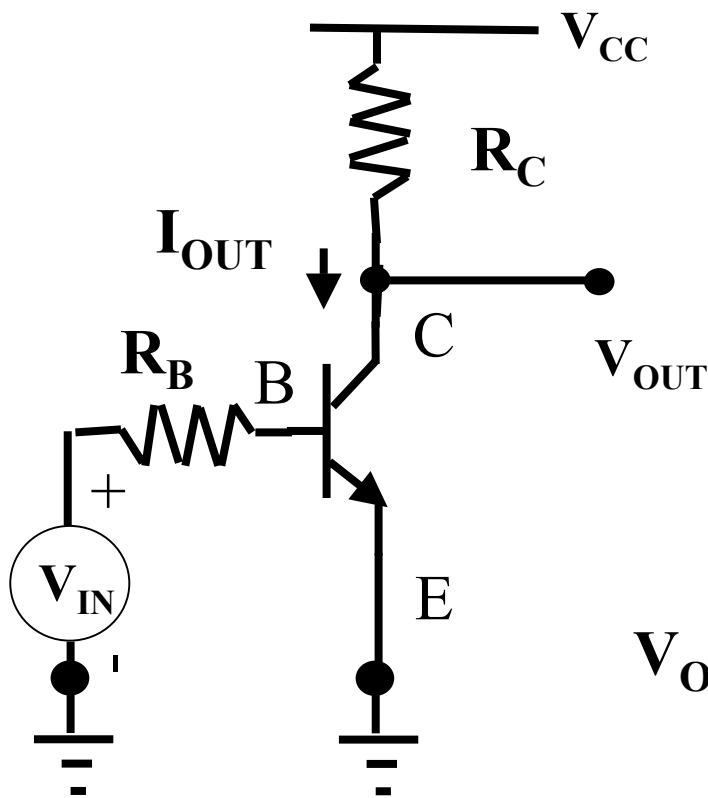Lecture 21 npn Bipolar Transistor: V_{OUT} vs. V_{IN}




$\beta = 100$ $R_B = 10k\Omega$
 $R_C = 1k\Omega$ $V_{CC} = 5V$

1) V_{OUT} is V_{CC} till V_{IN} reaches 0.7V

2) V_{OUT} decreases linearly with V_{IN} until V_{OUT} reaches 0.2V at $V_{IN} = 1.18V$

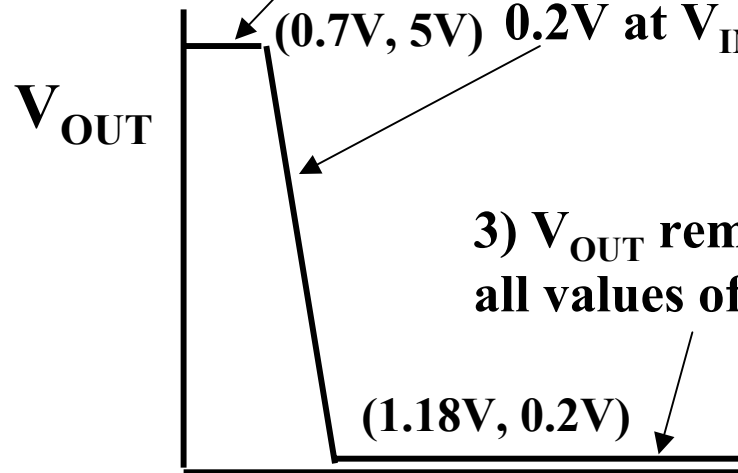
3) V_{OUT} remains at 0.2 V for all values of V_{IN} above 1.18V



2/04/01

Physics of Current Flow, Resistance, Resistivity

Lecture 22

 

$$E = V/L.$$

$$I = V/R$$

$$R = \rho L/A = (1/q \mu N) L/W t = (L/W) / \mu(q N t)$$

Carrier mobility

Carriers per unit volume

But $q N t$ has the dimensions of charge per unit area and represents the charge per unit area in a film of thickness t when the film has N carriers/cm³ and is t units thick. Thus we call $q N t$ the “ Q ” and

$$R = (L/W) / \mu Q = L/W R_{\square}$$

Where R_{\square} is the resistance of a “square” of the film. Clearly if L is four times W , then $R = 4 R_{\square}$.

Relation of Current to Physical Parameters

Lecture 23

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right)_n (V_{GS} - V_T) \cdot V_{OUT-SAT-n}$$

Mobility of carriers \nearrow
 Oxide thickness \nearrow
 Geometrical Layout \nearrow
 Excess Gate drive \nearrow
 Voltage of scattering velocity limit \nearrow

$$\mu_n = 500 \left(cm^2 / Vs \right) \quad \mu_p = 150 \left(cm^2 / Vs \right)$$

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = \frac{(8.85 \times 10^{-14} F / cm)(3.9)}{6 \times 10^{-7} cm} = 5.75 \times 10^{-7} F / cm^2$$

$$V_{OUT-SAT-n} = E_{Crit} \cdot L = 10^4 (V / cm) \cdot 0.25 \times 10^{-4} cm = 0.25V$$

CMOS Device Parameters at 0.25 μm

Lecture 23

Gate length is 0.25 μm = 250 nm

$$V_{DD} = 2.5V$$

| | V_T (V) | $V_{OUT-SAT}$ (V) | k' ($\mu\text{A}/\text{V}^2$) |
|------|-----------|-------------------|-----------------------------------|
| NMOS | 0.43 | 0.63 | 100 |
| PMOS | 0.4 | 1 | 25 |

These parameters are from re-fitting I vs. V data in Chapter 3 of the EECS 141 Text Book by Rabaey with saturation current model we are using in EE42.


Here $V_{IN} = V_{DD}$ is used to estimate the maximum I_{DS}

$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

$$I_{OUT-SAT-D} = \left(100 \mu\text{A}/\text{V}^2\right) \left(\frac{0.375}{0.25}\right) (2.5V - 0.43V)(0.63V) = 196 \mu\text{A}$$

Lecture 23

Voltage Transfer Function for the 0.25 μm CMOS Inverter

 

Lecture 23

Finding V_M for $0.25 \mu\text{m}$ Inverter

At V_M ,

1) $V_{\text{OUT}} = V_{\text{IN}} = V_M$

2) Both devices are in saturation

3) $I_{\text{OUT-SAT-n}} = I_{\text{OUT-SAT-p}}$

Result will depend on
(W/L) ratios.

$$I_{\text{OUT-SAT-n}} = k'_n \left(\frac{W}{L} \right)_n (V_{\text{IN}} - V_{Tn}) V_{\text{OUT-SAT-n}} =$$

$$I_{\text{OUT-SAT-p}} = k'_p \left(\frac{W}{L} \right)_p (V_{\text{DD}} - V_{\text{IN}} - V_{Tp}) V_{\text{OUT-SAT-p}}$$

Substitute V_M Solve for V_M


For $(W/L)_n = 1.5$ and $(W/L)_p = 3.0$ V_M is **1.17V**

Lecture 23

Version Date 12/04/01

CMOS Inverter in Short-Circuit Condition

 Assume the CMOS inverter from above with
 $V_{IN} = 1.25V$ and $V_{OUT} = 1.25V$ driving a 10 fF capacitor



$I_{\text{Short-Circuit}} = 63.8 \mu A$
 (We used $V_{IN} = V_{DD}/2$)

$I_{\text{Discharge_Load}} = 13.7 \mu A$
 (We Used $V_{IN} = V_{DD}/2$)

What happens to the output signal?

The capacitor slowly discharges to try to find an output voltage that balances the NMOS and PMOS currents for the given value of V_{IN} .


$$\frac{\partial V}{\partial t} = \frac{I}{C} = \frac{13.7 \mu A}{10 \text{ fF}} = 1.37 (V / ns)$$

Study this page carefully as three starting point mistakes were corrected.

Version Date 12/04/01

Lecture 24

Example CMOS Circuit

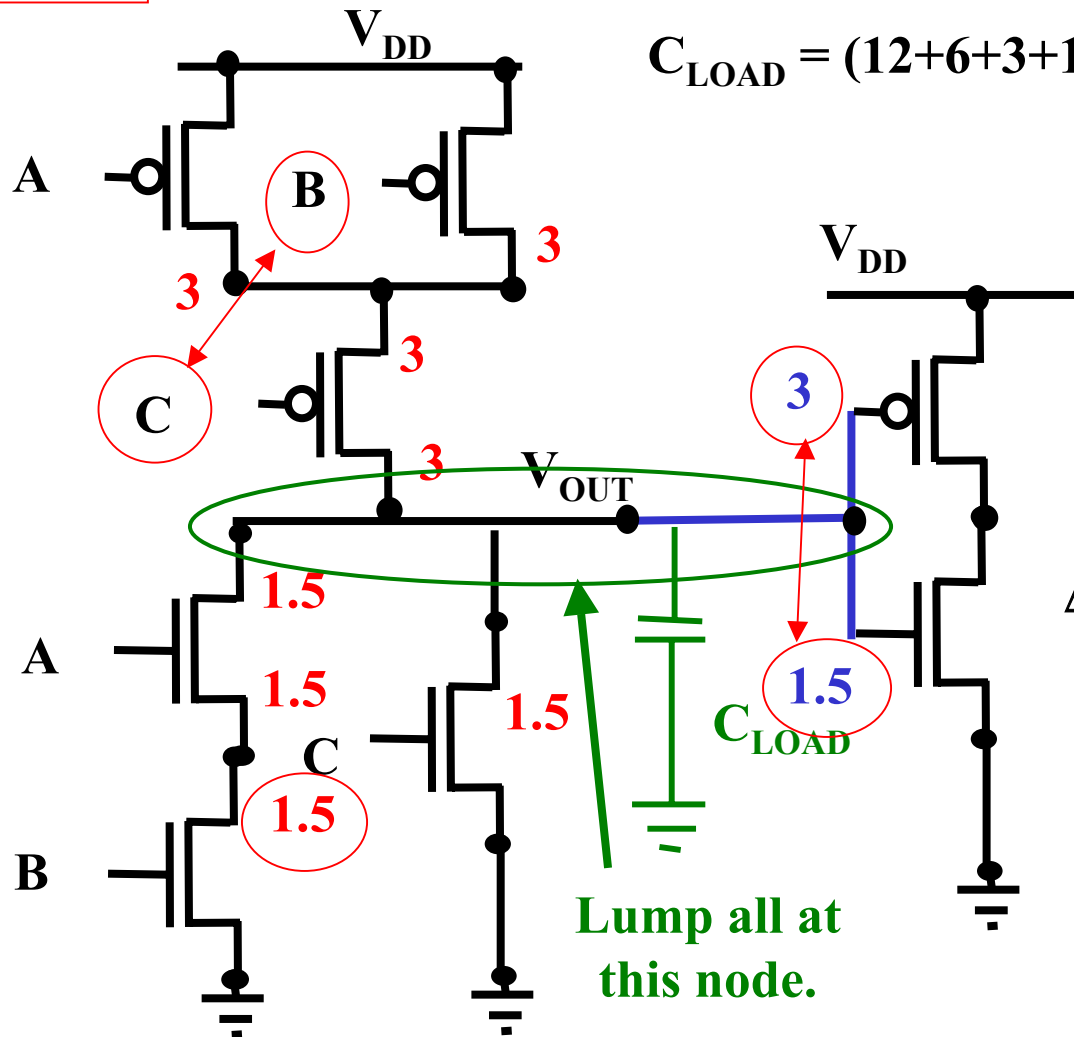

$$C_{LOAD} = (12+6+3+1.5)(0.4fF) = 9 fF$$

Worst case is $a=1, c=0,$
and b changes $1 \Rightarrow 0$

$$R = 2R_{DP} = 24k\Omega$$

$$\Delta t = 0.69(24k\Omega)(9 fF) = 149 ps$$

For comparison the inverter had a pull-up delay of 30 ps


Lecture 24

Fanout

Fanout is always ≥ 1 (there is always a load)

Gate capacitances sum and are charged by the driver resistance

 One load device was included in the initial estimate of C_{LOAD} .



$$C'_{LOAD} = C_{LOAD} + (FO - 1)((W/L)_p + (W/L)_n)(C_{G/MS})$$

$$C'_{LOAD} = C_{LOAD} + (FO - 1)(1.5 + 3.0)(0.4 \text{ fF})$$

Assumes minimum length devices.

Lecture 24

Coping with Power Consumption

D.C. POWER

a.c. POWER

Tube: 300V x 20 mA = 6W

Bipolar Transistor: 5V x 20 mA = 200 mW

NMOS Transistor: 5V x 200 μA = 1 mW

CMOS Transistors: 5V x 100 nA = 0.5 μW

← True of every gate!

Assumes 1/2 of the gates change state

$$P_{\text{SHORT-CIRCUIT}} = (1/2) I_{\text{SHORT-CIRCUIT}} V_{\text{DD}} \tau_{30-70} f_{\text{CLOCK}}$$

$$= (1/2) (60 \mu\text{A}) 2.5\text{V} (0.1\text{ns}) (10^9) = 7.5 \mu\text{W}$$

Only the L => H takes energy from V_{DD}


$$P_{\text{DYNAMIC}} = (1/2)(1/2) C V_{\text{DD}}^2 f_{\text{CLOCK}}$$

$$= (1/2) (1/2)(10 \text{ fF}) (2.5)^2 10^9 = 15.6 \mu\text{W}$$

True for only active gates.

Combinatorial Logic and Clocked Latches: Signal Flow

HW 13
Lecture 25

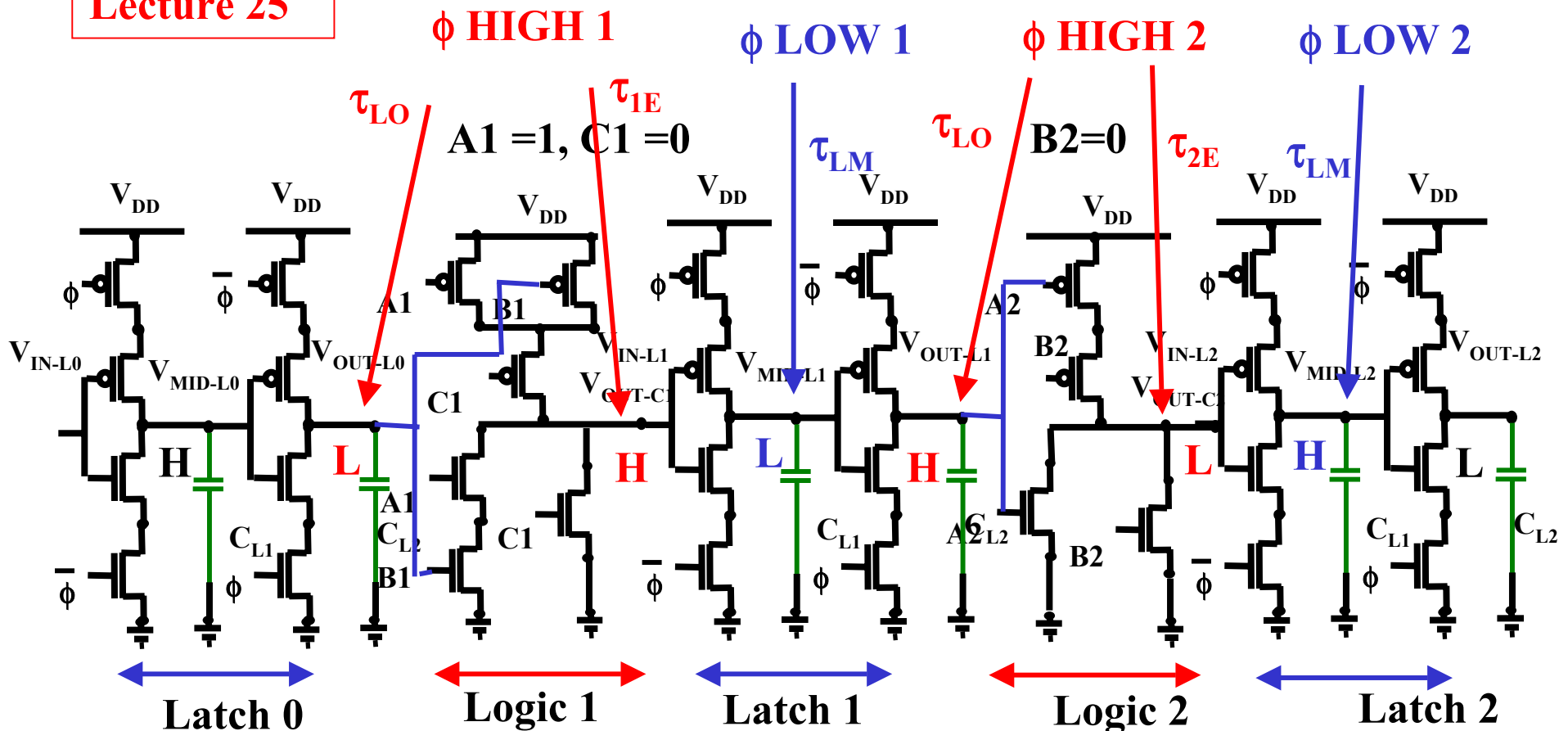

$$\tau_{\phi\text{-HIGH}} > \tau_{LO} + \text{Max}(\tau_{1E} \text{ or } \tau_{2E}) \quad \tau_{\phi\text{-LOW}} > \tau_{LM} \quad f_{\text{CLOCK}} = 1/(\tau_{\phi\text{-HIGH}} + \tau_{\phi\text{-LOW}})$$