

## EECS 42 Introduction Digital Electronics

Andrew R. Neureuther

### Lecture #8 Node Equations

- Systematic Node Equations
- Example: Voltage and Current Dividers
- Example 5 Element Circuit

Schwarz and Oldham 53-58, 2.5, & 2.6

**Quiz 9/25 20 min:**

**Basic Circuit Analysis and Basic Transient**

**Midterm 10/2: Lectures # 1-9: 4 Topics – See slide 2**

**Length/Credit Review TBA**

**<http://inst.EECS.Berkeley.EDU/~ee42/>**

## First Midterm Exam: Topics

- **Basic Circuit Analysis (KVL, KCL)**
- Equivalent Circuits and Graphical Solutions for Nonlinear Loads
- **Transients in Single Capacitor Circuits**
- Node Analysis Technique and Checking Solutions

**Exam is in class 9:40-10:45 AM, Closed book, Closed notes, Bring a calculator, Paper provided**

## Class Input on Midterm/Review

- Midterm Options
  - Option 1: 65 min and 23% of grade in course (Final is 49%)
  - Option 2: 80 min and 28% of grade in course (Final is 39%)
- Review Options
  - Date Tu 9/30 or Wed 10/1
  - Time 5-6:30 PM or Other

## FORMAL CIRCUIT ANALYSIS

Systematic approaches to writing down KCL and KVL: Section 2.3 of Text - In particular use of KCL gives NODAL ANALYSIS


Mathematical foundation is rigorous: EE 104 Circuit Theory

Nodal Analysis: Node voltages are the unknowns } Use one or the other for circuit analysis  
Mesh Analysis: Branch currents are the unknowns }


We will do only nodal analysis – (because voltages make more convenient variables than currents) Thus omit Text Section 2.4 ; it is redundant.

## THE IV CHARACTERISTICS OF AN ELEMENT ALLOW EITHER NODAL OR MESH (LOOP) ANALYSIS

### REVIEW FOR A RESISTOR: OHM'S Law

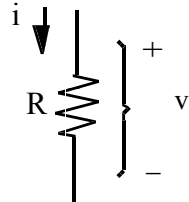

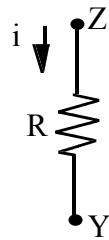If we use associated current and voltage (i.e.,  $i$  is defined as into + terminal), then  $v = iR$  (Ohm's law)



Another version of the same statement, and the one most important to us:

$$i = (V_Z - V_Y)/R \text{ (Ohm's law)}$$

NOTE ORDER OF NODES:  $V_Z - V_Y!$

## FORMAL CIRCUIT ANALYSIS USING KCL: NODAL ANALYSIS

(Memorize these steps and apply them rigorously!)

- 1 Choose a Reference Node  $\underline{\underline{\quad}}$
- 2 Define unknown node voltages (those not fixed by voltage sources)
- 3 Write KCL at each unknown node, expressing current in terms of the node voltages (using the constitutive relationships of branch elements\*)
- 4 Solve the set of equations (N equations for N unknown node voltages)

\* With inductors or floating voltages we will use a modified Step 3: The Supernode Method – see Lecture #8

### NODAL ANALYSIS USING KCL -Example: The Voltage Divider -

1 Choose reference node


2 Define unknown node voltages

3 Write KCL at unknown nodes

$$\frac{V_{SS} - V_2}{R_1} = \frac{V_2 - 0}{R_2}$$

4 Solve:
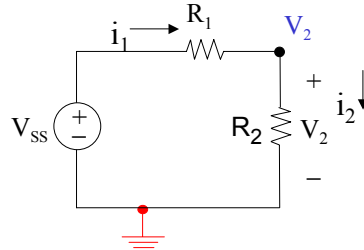
$$V_2 = V_{SS} \cdot \frac{R_2}{R_1 + R_2}$$




This is of course the voltage divider formula and is by itself very useful.

### RESISTORS IN PARALLEL

1 Select Reference Node

2 Define unknown node voltages

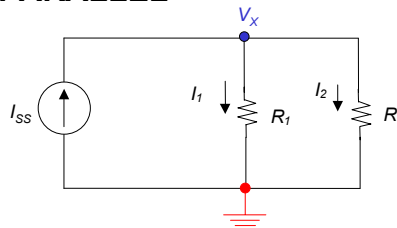

Note:  $I_{SS} = I_1 + I_2$ , i.e.,

$$I_{SS} = \frac{V_X}{R_1} + \frac{V_X}{R_2} \Rightarrow V_X = I_{SS} \cdot \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} = I_{SS} \cdot \frac{R_1 R_2}{R_1 + R_2}$$

RESULT 1 EQUIVALENT RESISTANCE:  $R_{||} \equiv R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$


RESULT 2 CURRENT DIVIDER:

$$I_1 = \frac{V_X}{R_1} = I_{SS} \times \frac{R_2}{R_1 + R_2}$$

$$I_2 = \frac{V_X}{R_2} = I_{SS} \times \frac{R_1}{R_1 + R_2}$$
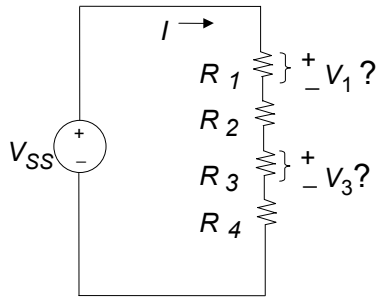
### GENERALIZED VOLTAGE DIVIDER (solved without Nodal Analysis)

Circuit with several resistors *in series*




- We know  

$$I = V_{SS} / (R_1 + R_2 + R_3 + R_4)$$
- Thus,  

$$V_1 = \frac{R_1}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$
- and  


$$V_3 = \frac{R_3}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$
- etc.. etc..**
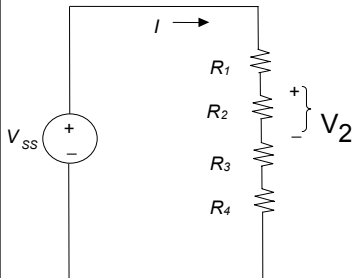
### WHEN IS VOLTAGE DIVIDER FORMULA CORRECT?



$$V_2 = \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

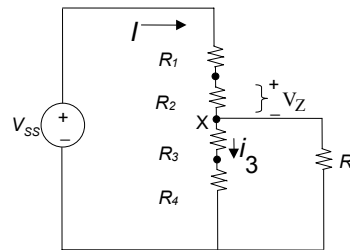Correct if nothing else connected to nodes




$$V_Z \neq \frac{R_2}{R_1 + R_2 + R_3 + R_4} \cdot V_{SS}$$

because  $R_5$  removes condition of resistors in series – i.e.  $i_3 \neq I$

What is  $V_Z$ ?
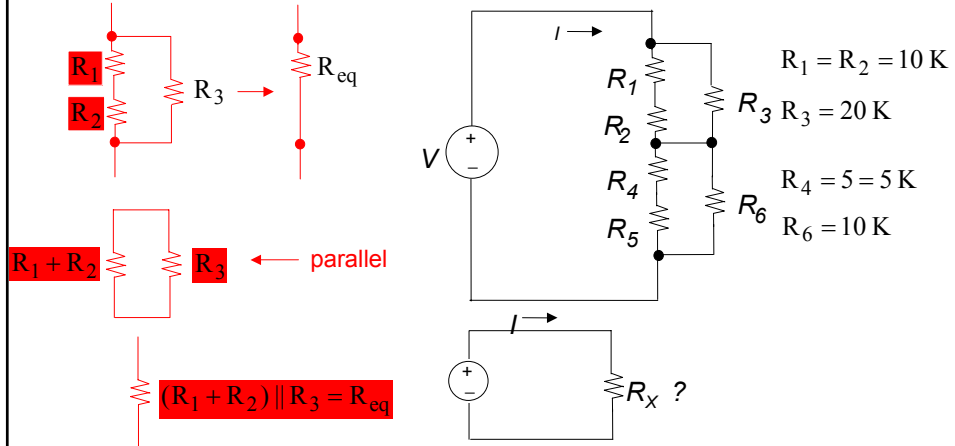
### IDENTIFYING SERIES AND PARALLEL COMBINATIONS


Use series/parallel equivalents to simplify a circuit before starting KVL/KCL



Please note the order of math operators here!
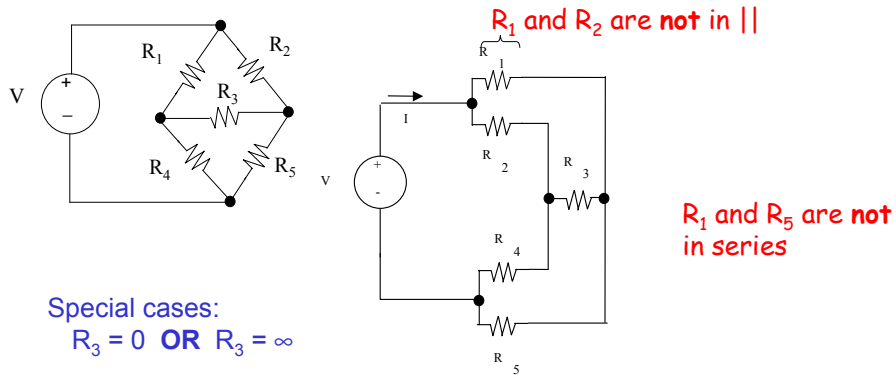
### IDENTIFYING SERIES AND PARALLEL COMBINATIONS (cont.)

Some circuits *must* be analyzed (not amenable to simple inspection)



Example:  $R_3 = 0 \Rightarrow R_1 \parallel R_2; R_4 \parallel R_5$  in series;


$R_{eq} = R_1 \parallel R_2 + R_4 \parallel R_5$

OR IF  $R_3 = \infty \Rightarrow (R_1 + R_5) \parallel (R_2 + R_4)$

### ANOTHER EXAMPLE OF NODAL ANALYSIS

Choose a reference node and define the node voltages (except reference node and the one set by the voltage source);

node voltage known

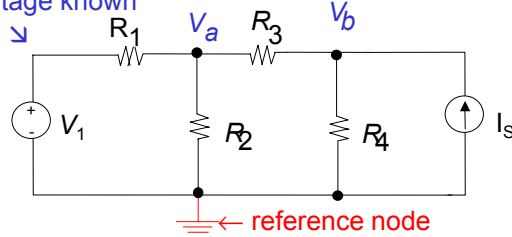

Apply KCL:

$$\frac{V_a - V_1}{R_1} + \frac{V_a - V_b}{R_3} + \frac{V_a}{R_2} = 0$$

$$\frac{V_b - V_a}{R_3} + \frac{V_b}{R_4} - I_S = 0$$


Note the systematic use of the present node minus each of the other nodes divided by the element resistance that connects them.

You can solve for  $V_a, V_b$ .

What if we used different ref node?
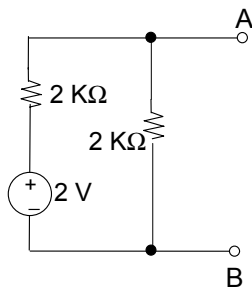
### EXAMPLE 1: Thevenin/Norton

Find the Thévenin and Norton equivalents of:




Find  $V_{AB} = V_{OC}$  from voltage divider. :

If open circuit,  $V_{AB} = V_{OC} = 2 \times 2/4 = 1V$

If A-B is shorted,  $I_{SC} = - 2V/2K = -1 \text{ mA (into A)}$


$$R_{TH} = \frac{1}{10^{-3}} = 1K$$

equivalent to

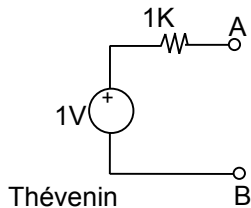

Thévenin

and equivalent to

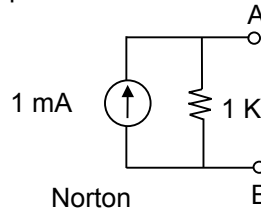


Norton

**EXAMPLE 1 Thevenin/Norton Continued**

Version Date 09/14/03

In what sense is this circuit

equivalent to these?

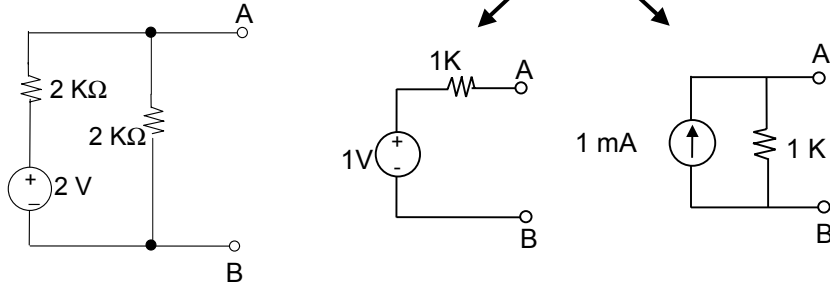

They have identical I-V characteristics and therefore have


The same open circuit voltage

The same short circuit current

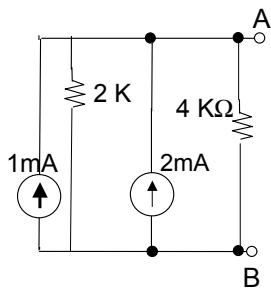**EXAMPLE 2 Thevenin/Norton**

Version Date 09/14/03

Find the Thévenin and Norton equivalents of:



Find Norton equivalent of circuit leg on the left:


(1mA and 2K)  $\Rightarrow$  Two Norton circuits in parallel

Thus combine current sources  $(2+1=3) = I_N$   
and combine resistors in parallel:  $8/6 K = R_N$

So,  $V_{TH} = R_N I_N = 4V$

$R_{TH} = R_N = 4/3 K$

equivalent to

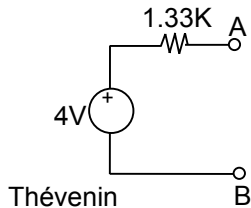

and equivalent to

