

EECS 42 Introduction to Digital Electronics

Andrew R. Neureuther

Lecture #9 Prof. King: Node Equations - Advanced

- Supernode for voltage supplies
- Checking Solutions

Schwarz and Oldham 53-58, 2.5 and 2.6

Quiz 9/25 20 min:

Basic Circuit Analysis and Basic Transient

Midterm 10/2: Lectures # 1-9: For Topics – See slide 2

Length/Credit Review TBA

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2003, Regents of University of California

First Midterm Exam: Topics

- **Basic Circuit Analysis (KVL, KCL)**
- Equivalent Circuits and Graphical Solutions for Nonlinear Loads
- **Transients in Single Capacitor Circuits**
- Node Analysis Technique and Checking Solutions

**Exam is in class 9:40-10:45 AM, Closed book,
Closed notes, Bring a calculator, Paper provided**

Copyright 2003, Regents of University of California

ReCap

Version Date 09/14/03

FORMAL CIRCUIT ANALYSIS USING KCL: NODAL ANALYSIS

(Memorize these steps and apply them rigorously!)

- 1 Choose a Reference Node \perp
- 2 Define unknown node voltages (those not fixed by voltage sources)
- 3 Write KCL at each unknown node, expressing current in terms of the node voltages (using the constitutive relationships of branch elements*)
- 4 Solve the set of equations (N equations for N unknown node voltages)


* With inductors or floating voltages we will use a modified Step 3: The Supernode Method – see slide 10

Copyright 2003, Regents of University of California

Version Date 09/14/03

NODAL ANALYSIS WITH “FLOATING” VOLTAGE SOURCES

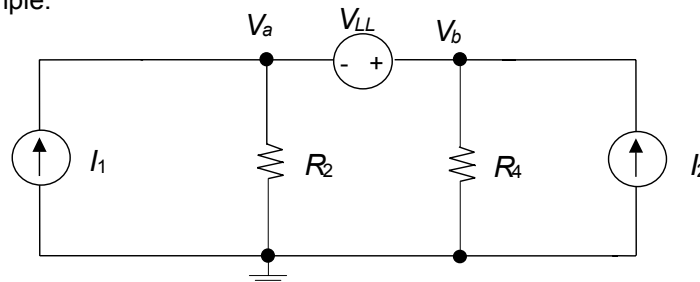A “floating” voltage source is a voltage source for which neither side is connected to the reference node. V_{LL} in the circuit below is an example.



What is the problem? → We cannot write KCL at node a or b because there is no way to express the current through the voltage source in terms of v_a or v_b .


Solution: Define a “supernode” – that chunk of the circuit containing nodes a and b. Express KCL at this supernode.

Copyright 2003, Regents of University of California

FLOATING VOLTAGE SOURCES (cont.)

Version Date 09/14/03

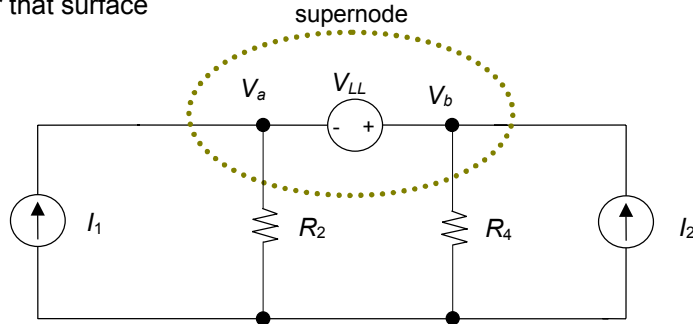Use a Gaussian surface to enclose the floating voltage source; write KCL for that surface



We have two unknowns: V_a and V_b .


We obtain one equation from KCL at supernode: $I_1 - \frac{V_a}{R_2} - \frac{V_b}{R_4} + I_2 = 0$

We obtain a second "auxiliary" equation from the property of the voltage source: $V_{LL} = V_b - V_a$ (often called the "constraint")

⇒ 2 Equations & 2 Unknowns

ANOTHER EXAMPLE

Version Date 09/14/03

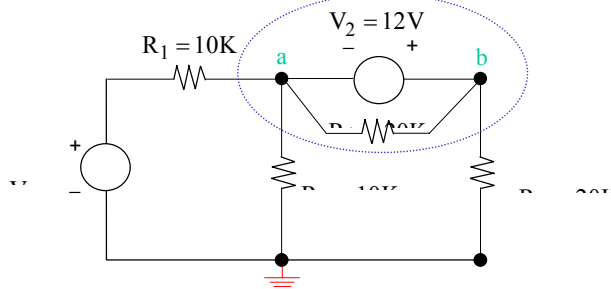

1 Choose reference node (can it be chosen to avoid floating voltage source?)

2 Label unknowns V_a and V_b

3 Equation at supernode: $V_1 - V_a = \frac{V_b}{R_4} + \frac{V_a}{R_2} \rightarrow V_a \left(\frac{1}{R_1} + \frac{1}{R_2} \right) + \frac{V_b}{R_4} = \frac{V_1}{R_1}$

4 Auxiliary equation: $V_a - V_b = -V_2 \rightarrow V_a - V_b = -V_2$


Solve: $V_a \left(\frac{R_4}{R_1} + \frac{R_4}{R_2} + 1 \right) = \frac{V_1 R_4}{R_1} - V_2$

$V_b = V_a + V_2$

SOLUTION: $V_a = 0$

NODAL ANALYSIS COMPLETE EXAMPLE

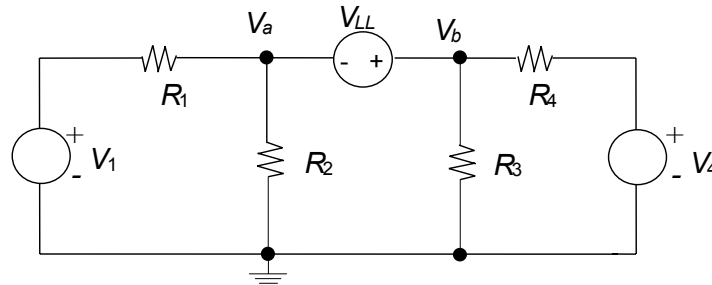Find V_a , V_b if $R_1 = R_2 = R_3 = R_4 = 1\text{M}\Omega$, and $V_1 = V_4 = 1.5\text{V}$ with $V_{LL} = 1\text{V}$



Solution: At supernode enclosing nodes a and b :


$$(V_1 - V_a)/R_1 - V_a/R_2 = V_b/R_3 + (V_b - V_4)/R_4 \quad \text{and}$$

$$V_b = V_a + V_{LL} \quad \text{Thus:} \quad V_a = 0.25 \quad \text{Be sure to check answer with KCL!}$$

$$V_b = 1.25$$

ANSWER CHECKING TECHNIQUE: USE KCL

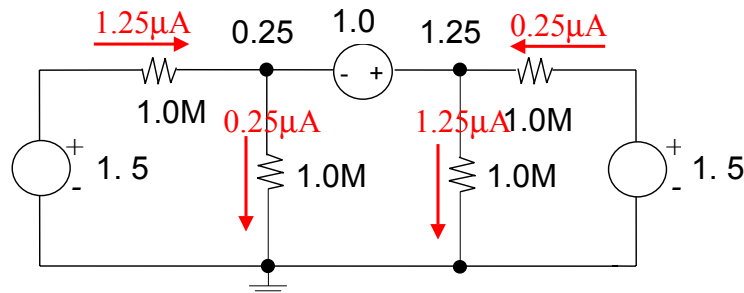Is $V_a = 1.25$ and $V_b = 0.25$ if $R_1 = R_2 = R_3 = R_4 = 1\text{M}\Omega$, and $V_1 = V_4 = 1.5\text{V}$ with $V_{LL} = 1\text{V}$????




KCL at the Supernode:

Clearly the current into the supernode is zero and we have verified that the solution is correct. :

Review for Quiz 9/25

Version Date 09/14/03

GRAPHICAL EQUIVALENT CIRCUIT

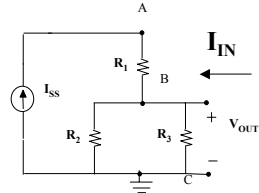


$$\begin{aligned} I_{SS} &= 1 \text{ mA} \\ R_1 &= 1 \text{ k}\Omega \\ R_2 &= 6 \text{ k}\Omega \\ R_3 &= 3 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} \text{Short Circuit: } V_{OUT} &= 0 \\ I_{IN} &= -I_{SS} = -1 \text{ mA} \end{aligned}$$

$$\text{Open Circuit: } I_{IN} = 0$$

$$\text{Note } R_2 \parallel R_3 = 2 \text{ k}\Omega$$
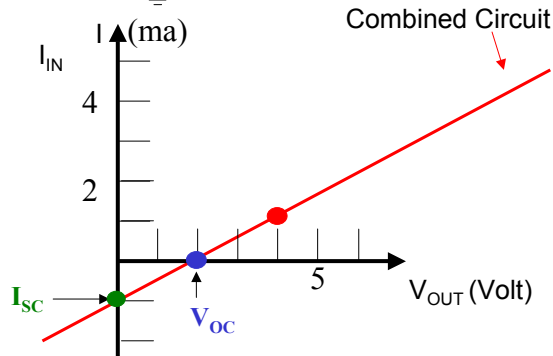
$$\begin{aligned} V_{OUT} &= I_{SS} \times R_2 \parallel R_3 \\ &= 1 \text{ mA} \times 2 \text{ k}\Omega = 2 \text{ V} \end{aligned}$$



Third Point

$$I_{IN} = 1 \text{ mA}$$

$$\text{KCL} \Rightarrow I_{2 \parallel 3} = I_{SS} + I_{IN}$$

$$\begin{aligned} V_{OUT} &= I_{2 \parallel 3} \times R_2 \parallel R_3 \\ &= 2 \text{ mA} \times 2 \text{ k}\Omega = 4 \text{ V} \end{aligned}$$


Key: It will always be the case that for linear circuit elements the I vs. V is a straight line.

Copyright 2003, Regents of University of California

Review for Quiz 9/25

Version Date 09/14/03

$R_{TH} = R_N$ SHORTCUT METHODS

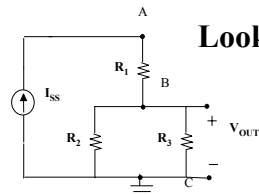

Look at algebraic relation for the example circuit.

$$V_{OC} = I_{SS} \times R_2 \parallel R_3$$

$$I_{SC} = -I_{SS}$$

$$R_{TH} = R_N = V_{OC} / (-I_{SC})$$

$$R_{TH} = R_N = (I_{SS} \times R_2 \parallel R_3) / (-(-I_{SS})) = R_2 \parallel R_3$$

In General turn all of the independent sources to zero and find the remaining equivalent resistance seen looking into the terminals.

Currents sources are turned to zero current (with any voltage)

=> OPEN CIRCUIT. Voltage sources are turned to zero

voltage (with any current)=> SHORT CIRCUIT.


Copyright 2003, Regents of University of California

Review for Quiz 9/25

Version Date 09/14/03

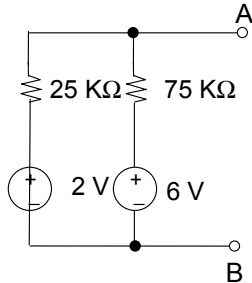EXAMPLE 3 Thevenin/Norton

Find the Thévenin and Norton equivalents of:



Find $V_{AB} = V_{OC}$ from voltage divider. Left to right:

(4 V rise across 25K + 75K) \Rightarrow


3 V across 75K, 1 V across 25k.

So, $V_{AB} = -3 + 6 = 3V = V_{OC}$


$$I_{SC} = -6V/75K + 2V/25K = -0.16 \text{ mA}$$

$$R_{TH} = \frac{3}{.16 \times 10^{-3}} = 18.8K$$

equivalent to

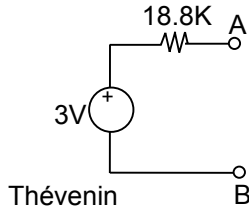

and equivalent to

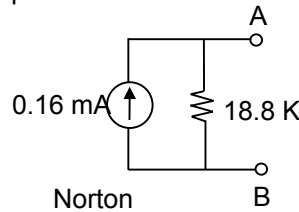


Copyright 2003, Regents of University of California

Review for Quiz 9/25

RC RESPONSE

Version Date 09/14/03

Generalization

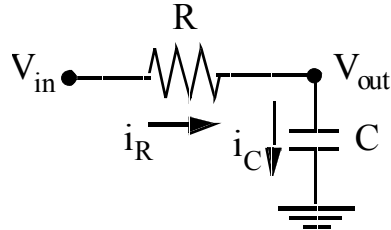

V_{in} switches at $t = 0$; then for any time interval $t > 0$, in which V_{in} is a constant, V_{out} is **always** of the form:

$$V_{out} = A + Be^{-t/RC}$$

We determine A and B from the initial voltage on C, and the value of V_{in} . Assume V_{in} "switches" at $t=0$ from V_{co} to V_1 :

First, at $t = 0$ $V_C \equiv V_{Co}$ initial voltage

\Rightarrow Thus, $A + B = V_{Co}$

as $t \rightarrow \infty$, $V_C \rightarrow V_1$

\Rightarrow Thus, $A = V_1 \Rightarrow B = V_{Co} - V_1$

RC is $R_{TH}C$ where R_{TH} is the Thevenin Resistance seen C with independent sources set to zero.

Copyright 2003, Regents of University of California

Review for Quiz 9/25

Version Date 09/14/03

Re-Cap: Charging and discharging in RC Circuits



Last Time:

We learned that simple the simple RC circuit with a step input has a universal exponential solution of the form:

$$V_{out} = A + Be^{-t/RC}$$

Example 0: R = 1K, C = 1pF, V_{in} steps from zero to 10V at t=0:

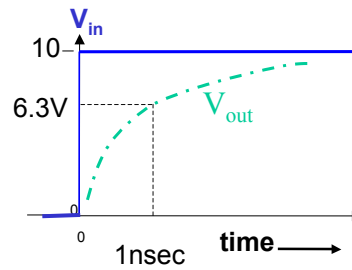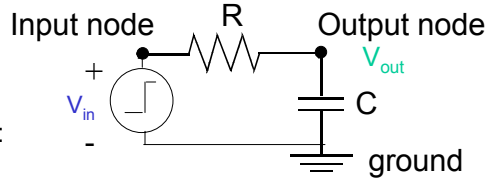- 1) Initial value of V_{out} is 0
- 2) Final value of V_{out} is 10V
- 3) Time constant is $RC = 10^{-9}$ sec
- 4) V_{out} reaches 0.63×10 in 10^{-9} sec



Copyright 2003, Regents of University of California

Review for Quiz 9/25



Version Date 09/14/03

Charging and discharging in RC Circuits

Find $V_c(t)$ for the following circuit: (input switches from 2V to -1V at t = 0)

We have : Initial value of V_c is 2V, final value is -1V and $\tau = 20$ nsec

5) Sketch $V_c(t)$:

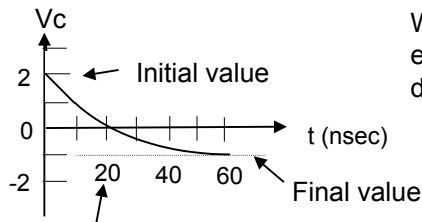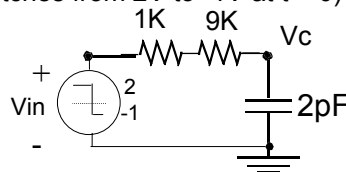

37% of transient remaining at one time constant

What is the equation for an exponential beginning at 2V, decaying to -1V, with $\tau = 20$ nsec?

$$V_c(t) = -1 + 3e^{-t/20\text{nsec}}$$

$$V_{FINAL} =$$

$$V_{INITIAL} =$$

$$B = V_{INITIAL} - V_{FINAL} =$$

Copyright 2003, Regents of University of California