

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

EECS 42 Introduction to Digital Electronics

Andrew R. Neureuther

Lecture #9 Prof. King: Node Equations - Advanced

- Supernode for voltage supplies
- Checking Solutions

Schwarz and Oldham 53-58, 2.5 and 2.6

Quiz 9/25 20 min:

Basic Circuit Analysis and Basic Transient

Midterm 10/2: Lectures # 1-9: For Topics – See slide 2

Length/Credit Review TBA

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

NODAL ANALYSIS WITH "FLOATING" VOLTAGE SOURCES

A "floating" voltage source is a voltage source for which neither side is connected to the reference node. V_{LL} in the circuit below is an example.

What is the problem? → We cannot write KCL at node a or b because there is no way to express the current through the voltage source in terms of $V_a - V_b$.

Solution: Define a "supernode" – that chunk of the circuit containing nodes a and b. Express KCL at this supernode.

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

First Midterm Exam: Topics

- Basic Circuit Analysis (KVL, KCL)
- Equivalent Circuits and Graphical Solutions for Nonlinear Loads
- Transients in Single Capacitor Circuits
- Node Analysis Technique and Checking Solutions

Exam is in class 9:40-10:45 AM, Closed book, Closed notes, Bring a calculator, Paper provided

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

FLOATING VOLTAGE SOURCES (cont.)

Use a Gaussian surface to enclose the floating voltage source; write KCL for that surface

We have two unknowns: V_a and V_b .

We obtain one equation from KCL at supernode: $I_1 - \frac{V_a}{R_2} - \frac{V_b}{R_4} + I_2 = 0$

We obtain a second "auxiliary" equation from the property of the voltage source: $V_b - V_a = V_{LL}$ (often called the "constraint")

⇒ 2 Equations & 2 Unknowns

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

ReCap

FORMAL CIRCUIT ANALYSIS USING KCL: NODAL ANALYSIS

(Memorize these steps and apply them rigorously!)

- 1 Choose a Reference Node ---
- 2 Define unknown node voltages (those not fixed by voltage sources)
- 3 Write KCL at each unknown node, expressing current in terms of the node voltages (using the constitutive relationships of branch elements*)
- 4 Solve the set of equations (N equations for N unknown node voltages)

* With inductors or floating voltages we will use a modified Step 3: The Supernode Method – see slide 10

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

ANOTHER EXAMPLE

- 1 Choose reference node (can it be chosen to avoid floating voltage source?)
- 2 Label unknowns V_a and V_b
- 3 Equation at supernode: $I_1 - \frac{V_a}{R_1} - \frac{V_b}{R_2} - \frac{V_b}{R_4} + I_2 = 0$
- 4 Auxiliary equation: $V_b - V_a = V_{LL}$

Solve: $V_a \left(\frac{R_4}{R_1} + \frac{R_4}{R_2} + 1 \right) = \frac{V_1 R_4}{R_1} - V_2$

SOLUTION: $V_a = 0$
 $V_b = V_a + V_2$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

NODAL ANALYSIS COMPLETE EXAMPLE

Find V_a, V_b if $R_1 = R_2 = R_3 = R_4 = 1\text{M}\Omega$, and $V_1 = V_4 = 1.5\text{V}$ with $V_{LL} = 1\text{V}$

Solution: At supernode enclosing nodes a and b :
 $(V_1 - V_a)/R_1 - V_a/R_2 = V_b/R_3 + (V_b - V_4)/R_4$ and
 $V_b = V_a + V_{LL}$ Thus: $V_a = 0.25$ Be sure to check answer with KCL!
 $V_b = 1.25$

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

Review for Quiz 9/25

$R_{TH} = R_N$ SHORTCUT METHODS

Look at algebraic relation for the example circuit.

$V_{OC} = I_{SS} \times R_2 \parallel R_3$
 $I_{SC} = -I_{SS}$
 $R_{TH} = R_N = V_{OC} / (-I_{SC})$
 $R_{TH} = R_N = (I_{SS} \times R_2 \parallel R_3) / (-(-I_{SS})) = R_2 \parallel R_3$

In General turn all of the independent sources to zero and find the remaining equivalent resistance seen looking into the terminals.
 Currents sources are turned to zero current (with any voltage) => OPEN CIRCUIT. Voltage sources are turned to zero voltage (with any current) => SHORT CIRCUIT.

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

ANSWER CHECKING TECHNIQUE: USE KCL

Is $V_a = 1.25$ and $V_b = 0.25$ if $R_1 = R_2 = R_3 = R_4 = 1\text{M}\Omega$, and $V_1 = V_4 = 1.5\text{V}$ with $V_{LL} = 1\text{V}$????

KCL at the Supernode:
 Clearly the current into the supernode is zero and we have verified that the solution is correct. :

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

Review for Quiz 9/25

EXAMPLE 3 Thevenin/Norton

Find the Thévenin and Norton equivalents of:

Find $V_{AB} = V_{OC}$ from voltage divider. Left to right:
 $(4\text{ V rise across } 25\text{K} + 75\text{K}) \Rightarrow$
 $3\text{ V across } 75\text{K}, 1\text{ V across } 25\text{K}.$
 So, $V_{AB} = -3 + 6 = 3\text{V} = V_{OC}$
 $I_{SC} = -6\text{V}/75\text{K} + 2\text{V}/25\text{K} = -0.16\text{ mA} \Rightarrow R_{TH} = 3 / -0.16 = 18.8\text{K}$

equivalent to and equivalent to

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

Review for Quiz 9/25

GRAPHICAL EQUIVALENT CIRCUIT

$I_{SS} = 1\text{ mA}$
 $R_1 = 1\text{ k}\Omega$
 $R_2 = 6\text{ k}\Omega$
 $R_3 = 3\text{ k}\Omega$

Short Circuit: $V_{OUT} = 0$
 $I_{IN} = -I_{SS} = -1\text{ mA}$

Open Circuit: $I_{IN} = 0$
 Note $R_2 \parallel R_3 = 2\text{ k}\Omega$
 $V_{OUT} = I_{SS} \times R_2 \parallel R_3 = 1\text{ mA} \times 2\text{ k}\Omega = 2\text{V}$

Third Point
 $I_{IN} = 1\text{ mA}$
 KCL $\Rightarrow I_{2||3} = I_{SS} + I_{IN}$
 $V_{OUT} = I_{2||3} \times R_2 \parallel R_3 = 2\text{ mA} \times 2\text{ k}\Omega = 4\text{V}$

Key: It will always be the case that for linear circuit elements the I vs. V is a straight line.

Copyright 2003, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 9: 09/23/03 A.R. Neureuther
Version Date 09/14/03

Review for Quiz 9/25

RC RESPONSE

Generalization

Vin switches at $t = 0$; then for any time interval $t > 0$, in which Vin is a constant, Vout is **always** of the form: $V_{out} = A + B e^{-t/RC}$

We determine A and B from the initial voltage on C, and the value of Vin. Assume Vin "switches" at $t=0$ from V_{co} to V_1 :

Thus, $V_{out}(0) = V_{co} = A + B$

Thus, $V_{out}(\infty) = V_1 = A$

Key: RC is $R_{TH}C$ where R_{TH} is the Thévenin Resistance seen C with independent sources set to zero.

Copyright 2003, Regents of University of California

Review for Quiz 9/25

Version Date 09/14/03

Re-Cap: Charging and discharging in RC Circuits



Last Time:

We learned that simple the simple RC circuit with a step input has a universal exponential solution of the form:

$$V_{out} = A + Be^{-t/RC}$$

Example 0: $R = 1K$, $C = 1pF$, V_{in} steps from zero to 10V at $t=0$:

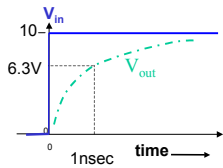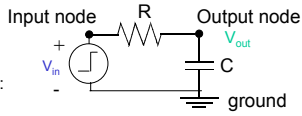- 1) Initial value of V_{out} is 0
- 2) Final value of V_{out} is 10V
- 3) Time constant is $RC = 10^{-9}$ sec
- 4) V_{out} reaches 0.63×10 in 10^{-9} sec



Copyright 2003, Regents of University of California

Review for Quiz 9/25



Version Date 09/14/03

Charging and discharging in RC Circuits

Find $V_c(t)$ for the following circuit: (input switches from 2V to -1V at $t = 0$)

We have : Initial value of V_c is 2V, final value is -1V and $\tau = 20nsec$

5) Sketch $V_c(t)$:

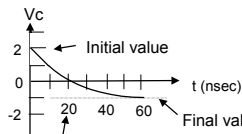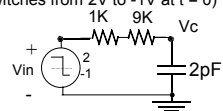

What is the equation for an exponential beginning at 2V, decaying to -1V, with $\tau = 20nsec$?

$$V_c(t) = -1 + 3e^{-t/20nsec}$$

37% of transient remaining at one time constant

$$V_{FINAL} =$$

$$V_{INITIAL} =$$

$$B = V_{INITIAL} - V_{FINAL} =$$

Copyright 2003, Regents of University of California