

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

EECS 42 Introduction Digital Electronics

Andrew R. Neureuther

Lecture # 13 Dependent Sources

A) Dependent Source Concept
B) Four Basic Dependent Source Types
C) Use in Amplifier Models
D) Feedback and Ideal Op-Amp Model
E) Examples of Op-Amp Circuits

<http://inst.EECS.Berkeley.EDU/~ee42/>

Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

Dependent Voltage and Current Sources

A linear dependent source is a voltage or current source that depends linearly on some other circuit current or voltage.

Example: you watch a certain voltmeter V_1 and manually adjust a voltage source V_s to be 2.5 times this value.

Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

Dependent Voltage Source Example

The voltage V_s source depends linearly on V_1 (because you set it to 2.5 times V_1 , no matter what V_1 is).

If you and the voltmeter are placed inside a box, the box functions as a voltage-dependent voltage source.

Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

Dependent Voltage and Current Sources

- A linear dependent source is a voltage or current source that depends linearly on some other circuit current or voltage.
- We can have voltage or current sources depending on voltages or currents elsewhere in the circuit.

Here the voltage V is proportional to the voltage across the element c-d.

A diamond-shaped symbol is used for dependent sources, just as a reminder that it's a dependent source.

Circuit analysis is performed just as with independent sources.

Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

The 4 Basic Linear Dependent Sources

Constant of proportionality Parameter being sensed
 Output

Voltage-controlled voltage source ... $V = A_v V_{cd}$
Current-controlled voltage source ... $V = R_m I_c$
Current-controlled current source ... $I = A_i I_c$
Voltage-controlled current source ... $I = G_m V_{cd}$

Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

WHY DEPENDENT SOURCES? EXAMPLE: MODEL FOR AN AMPLIFIER

AMPLIFIER SYMBOL

Differential Amplifier

V_0 depends only on input $(V_+ - V_-)$.

EXAMPLE: $A = 20$ Then if input $(V_+ - V_-) = 10\text{mV}$; $V_0 = 200\text{mV}$.


An actual amplifier has dozens (to hundreds) of devices (transistors) in it. But the dependent source allows us to model it with a very simple element.

Copyright 2002, Regents of University of California


EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

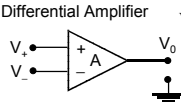Example :Dependent Source In an Amplifier

AMPLIFIER SYMBOL
Differential Amplifier $V_0 = A(V_+ - V_-)$



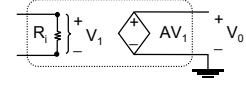AMPLIFIER MODEL
Circuit Model *in linear region*



V_0 depends only on input $(V_+ - V_-)$


See the utility of this: this Model when used correctly mimics the behavior of an amplifier but omits the complication of the many many transistors and other components.

Copyright 2002, Regents of University of California


EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

OP-AMP AND USE OF FEEDBACK

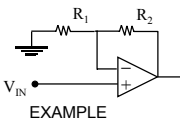A very high-gain differential amplifier can function in an extremely linear fashion as an operational amplifier by using negative feedback.



EXAMPLE

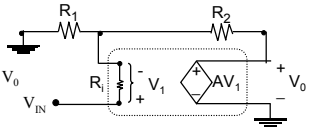

Circuit Model

Negative feedback \Rightarrow **Stabilizes** the output

We can show that that for $A \rightarrow \infty$ and $R_1 \rightarrow \infty$,

$$V_0 \cong V_{IN} \cdot \frac{R_1 + R_2}{R_1}$$

Stable, finite, and independent of the properties of the OP AMP!


Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

IDEAL OP-AMPS ANALYSIS TECHNIQUE

Assumption 1: The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

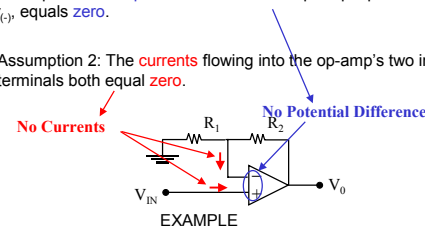Assumption 2: The **currents** flowing into the op-amp's two input terminals both equal **zero**.



No Currents (red arrows)
No Potential Difference (blue arrows)

EXAMPLE

Copyright 2002, Regents of University of California


EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

IDEAL OP-AMPS ANALYSIS EXAMPLE #1

Assumption 1: The **potential** between the op-amp input terminals, $v_{(+)} - v_{(-)}$, equals **zero**.

Assumption 2: The **currents** flowing into the op-amp's two input terminals both equal **zero**.

KCL with currents in only two branches

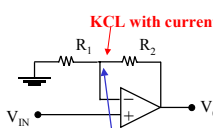

EXAMPLE

$$\frac{v_{in}}{R_1} + \frac{v_{in} - v_{out}}{R_2} = 0$$

$$v_{out} = \frac{R_1 + R_2}{R_1} v_{in}$$


Non-inverting Amplifier

V_{IN} appears here

Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

IDEAL OP-AMPS ANALYSIS EXAMPLE #2

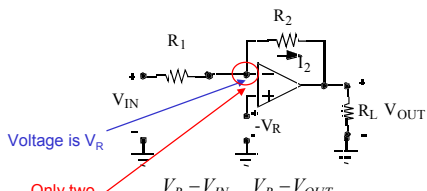

Voltage is V_R

Only two currents for KCL

$$\frac{V_R - V_{IN}}{R_1} + \frac{V_R - V_{OUT}}{R_2} = 0$$

$$V_{OUT} = V_R - \frac{R_2}{R_1}(V_{in} - V_R)$$

Inverting Amplifier with reference voltage



Copyright 2002, Regents of University of California

EECS 42 Intro. Digital Electronics Fall 2003 Lecture 13: 10/07/03 A.R. Neureuther
Version Date 10/05/03

THE RAILS

The output voltage of an amplifier is of course limited by whatever voltages are supplied (the "power supplies"). Sometimes we show them explicitly on the amplifier diagram, but often they are left off.

Differential Amplifier

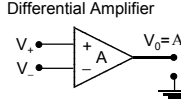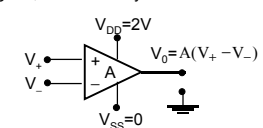$V_0 = A(V_+ - V_-)$

If the supplies are 2V and 0V, the output cannot swing beyond these values. (You should try this experiment in the lab.) So in this case we have upper rail = 2V, lower rail = 0V.

The rails cannot be larger than the supply voltages. **For simplicity we will use the supply voltages as the rails.**

Copyright 2002, Regents of University of California