

EECS 42 Introduction to Digital Electronics

Andrew R. Neureuther

Lecture # 14 Circuit analysis with dependent sources (4.1-4.3)

- A) Node Equations
- B) Equivalent Sources
- C) Amplifier Parameters:

Gain, R_{IN} , R_{OUT}

- D) Non-Ideal Op-Amp Model

<http://inst.EECS.Berkeley.EDU/~ee42/>

The 4 Basic Linear Dependent Sources

Constant of proportionality Parameter being sensed


Output

Voltage-controlled voltage source ... $V = A_v V_{cd}$


Current-controlled voltage source ... $V = R_m I_c$

Current-controlled current source ... $I = A_i I_c$

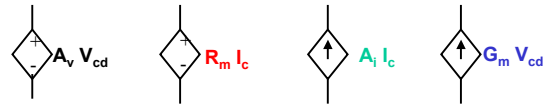Voltage-controlled current source ... $I = G_m V_{cd}$



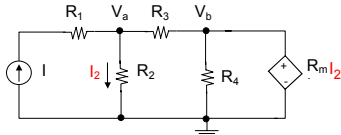EXAMPLE OF NODAL ANALYSIS WITH DEPENDENT SOURCES



Standard technique, except an additional equation is needed if the dependent variable is an unknown current as here. Note V_b is redundant.

$$I = V_a / R_2 + (V_a - R_m I_2) / R_3 \quad \text{and} \quad I_2 = V_a / R_2$$

$$\text{Solving:} \quad I = V_a (1/R_2 + 1/R_3 - R_m / R_2 R_3)$$

$$\text{So } V_a = I R_2 R_3 / (R_2 + R_3 - R_m)$$

THEVENIN EQUIVALENT WITH DEPENDENT SOURCES

Method 1: Use V_{oc} and I_{sc} as usual to find V_T and R_T (and I_N as well)


Method 2: To find R_T by the "ohmmeter method" turn off only the *independent* sources; let the dependent sources just do their thing.

See examples in text (such as Example 4.3).

This method also works when computing **incremental signals** such as a change in the source V_S (given by ΔV_S or v_s) produces a change in V_{IN} or V_{OUT} , (given by ΔV_{IN} or ΔV_{OUT} also written v_{IN} and v_{OUT}), and their ratio called the small-signal gain ($\Delta V_{OUT} / \Delta V_S$) or (v_{OUT} / v_s)

NODAL ANALYSIS WITH DEPENDENT SOURCES

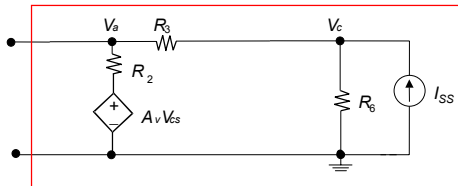Example : Find Thévenin equivalent of stuff in red box.




With method 2 we first find open circuit voltage (V_T) and then we "measure" input resistance with source I_{SS} turned off.


$$\text{You verify the solution: } V_{TH} = \frac{I_{SS} R_6 (R_2 + A R_3)}{R_2 + R_3 + R_6 (1-A)} \quad R_{TH} = \frac{R_2 (R_6 + R_3)}{R_2 + R_3 + R_6 (1-A)}$$

EXAMPLE CIRCUIT WITH MULTIPLE SOURCES

Original circuit

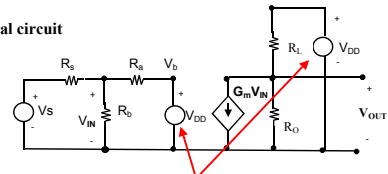


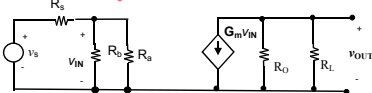Circuit with **independent sources** turned to zero



Note R_L has been rotated down.

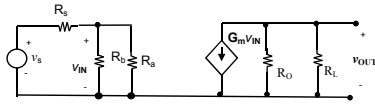EXAMPLE CIRCUIT: GAIN $= (\Delta V_{OUT} / \Delta V_S) = (V_{OUT} / V_S)$




$$R_{IN} = \frac{R_a R_b}{R_a + R_b} \quad v_{IN} = \frac{R_{IN}}{R_S + R_{IN}} v_S$$

$$v_{OUT} = -G_m v_{IN} \frac{R_O R_L}{R_O + R_L} = -G_m \frac{R_{IN}}{R_S + R_{IN}} \frac{R_O R_L}{R_O + R_L} v_S$$

Input voltage divider and output current divider reduce the gain

EXAMPLE CIRCUIT: INPUT/OUTPUT RESISTANCE

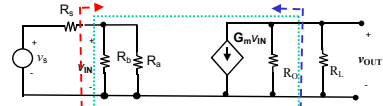

$$R_{IN} = \frac{R_a R_b}{R_a + R_b}$$


Output does not feed back to input

$$R_{OUT} = R_O$$

Assume $v_S = 0 \Rightarrow v_{IN} = 0 \Rightarrow$ no current in dependent source

Can circuit design improve R_{IN} and R_{OUT} or do we need better devices?

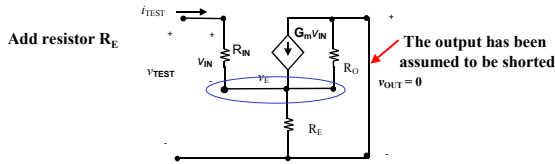EXAMPLE CIRCUIT: INCREASED INPUT RESISTANCE



The output has been assumed to be shorted

Analysis: apply i_{TEST} and evaluate v_{TEST}

$$v_{IN} = R_{IN} i_{TEST} \quad v_{TEST} = R_{IN} i_{TEST} + v_E$$


Finish this in the homework

$$\text{KCL} \quad \frac{v_E}{R_E} + \frac{v_E}{R_O} - i_{TEST} - G_m R_{IN} i_{TEST} = 0$$

Intuitive Explanation: R_E puts R_{IN} on a node whose voltage increases in response to current in R_{IN} .

$$\text{Check for special case for } R_E \text{ infinite} \quad \frac{v_{TEST}}{i_{TEST}} = R_{IN} + (1 + G_m R_{IN}) R_E$$

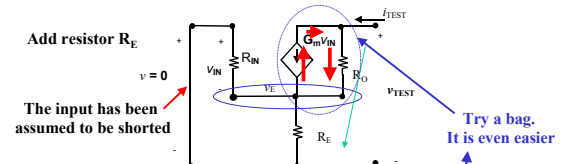EXAMPLE CIRCUIT: INCREASED OUTPUT RESISTANCE



Add resistor R_E

The input has been assumed to be shorted

Try a bag. It is even easier

Analysis: apply i_{TEST} and evaluate v_{TEST}

Unknowns: i_{TEST} , v_{TEST} , v_{IN} , v_E

Need 3 equations to find the ratio of i_{TEST} / v_{TEST}

$v_{IN} = -v_E$ and is not zero!
KCL at v_E
KVL at v_{OUT}

Intuitive Explanation: $G_m v_{IN}$ burps current which has to also go through R_O . This raises v_{TEST} and the output impedance v_{TEST} / i_{TEST}


Finish this in the homework

NON-IDEAL OP-AMPS

JUST ANOTHER CASE OF ANALYSIS WITH DEPENDENT SOURCES

Example:

Circuit (assume $R_{IN} \approx \infty$)

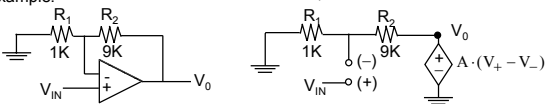

Analysis: Outline your circuit analysis strategy here.

Hint: 1) Find V_- in terms of V_0 , 2) plug into expression for V_0 and then 3) solve for V_0 which appears on both sides of the equation.

$$\text{Answer:} \quad V_0 = V_{IN} \frac{A(R_1 + R_2)}{(A+1)R_1 + R_2} \approx V_{IN} \frac{R_1 + R_2}{R_1} = 10V_{IN} \quad \text{if } A \rightarrow \infty$$