

EECS 42 Introduction to Digital Electronics

Andrew R. Neureuther

These viewgraphs will be handed out in class 10/21/03

Lecture # 16 Logic with a State Dependent Device

S&O pp. 593-595, 604-606 (read for graphs and not physics or equations), plus Handout of these viewgraphs.

A) State Dependent Device I_{OUT} vs. V_{OUT}

B) Load Line Analysis for Logic Levels


C) Voltage Transfer Characteristics

VTC = plot of V_{OUT} vs. V_{IN}


D) 42S_NMOS Pull-Down Device and Logic

<http://inst.EECS.Berkeley.EDU/~ee42/>


Logic Gates – How are they built in practice?

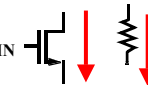A Valve is a Transistor V_{IN} 

 
Current flows when V_{IN} is high
Can be modeled by a $10k\Omega$ resistor



Valves in Series => NAND

 

Valves in Parallel => NOR

 

What goes in this box?

How does it affect digital performance?

Digital Logic from State-Dependent Three-Terminal Devices


Three-terminal devices such as MOS transistors have **output characteristics** (such as I_{OUT} vs. V_{OUT} curves) on the output side that can be programmed by changing signals on the **input side** (such as the **input voltage**).

The input voltage V_{IN} can thus be viewed as changing or programming the 'State' of the **output** of the device.

Three-terminal devices whose input voltage V_{IN} or 'State' can be programmed can be used to make digital logic devices for computers whose **outputs** respond to **input signals**.


Copyright 2003, Regents of University of California

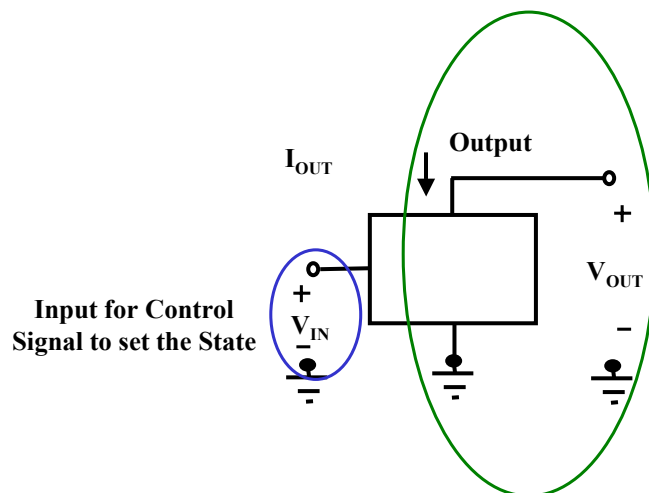State-Dependent Three-Terminal Device Element




Copyright 2003, Regents of University of California

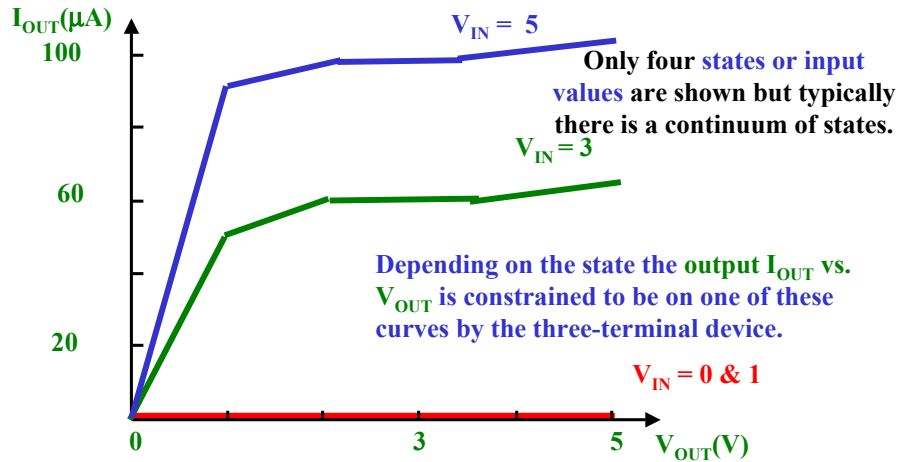State-Dependent Device I_{OUT} vs. V_{OUT}




Copyright 2003, Regents of University of California

Terminology for a Logic Circuit

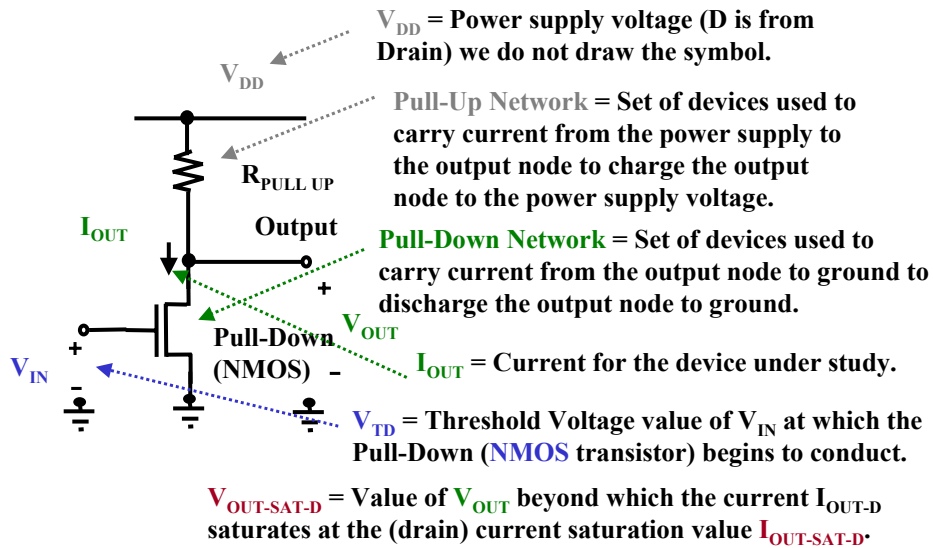

Copyright 2003, Regents of University of California


Thevenin Model For Pull-Up Device

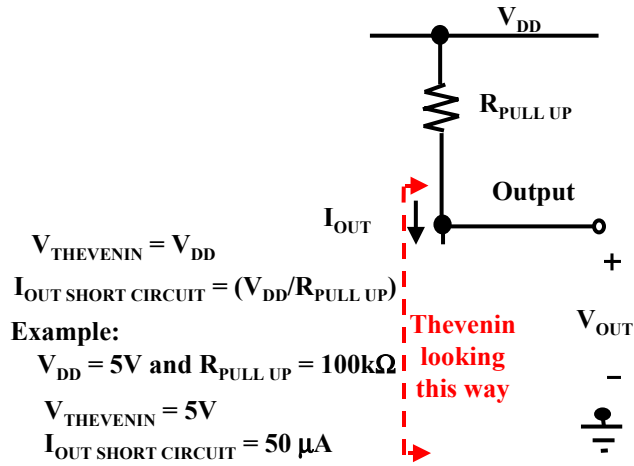

Copyright 2003, Regents of University of California

Thevenin Model For Pull-Up Device

 
I_{OUT} vs. V_{OUT}
For the Pull-Up Resistor and V_{DD}




Copyright 2003, Regents of University of California

Composite Current Plot for the Logic Circuit

 Three-Terminal Device Plus Load Line for the Pull-Up Device




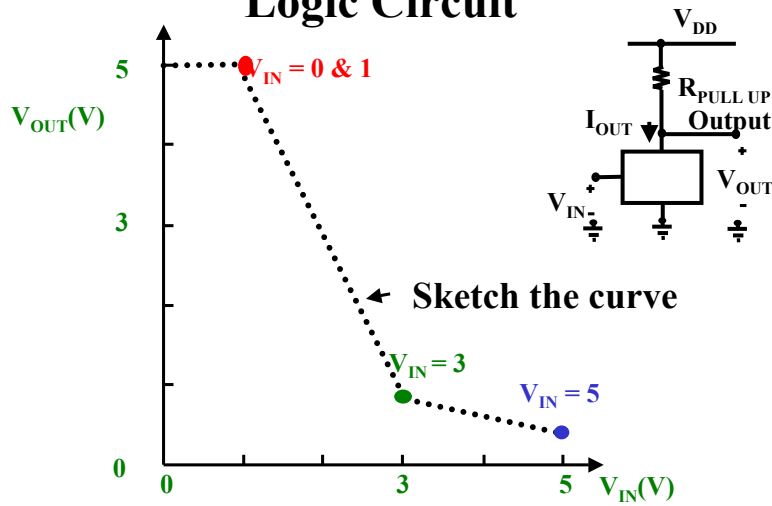Voltage Transfer Function for the Logic Circuit



Voltage Transfer Function: V_{OUT} vs. V_{IN}

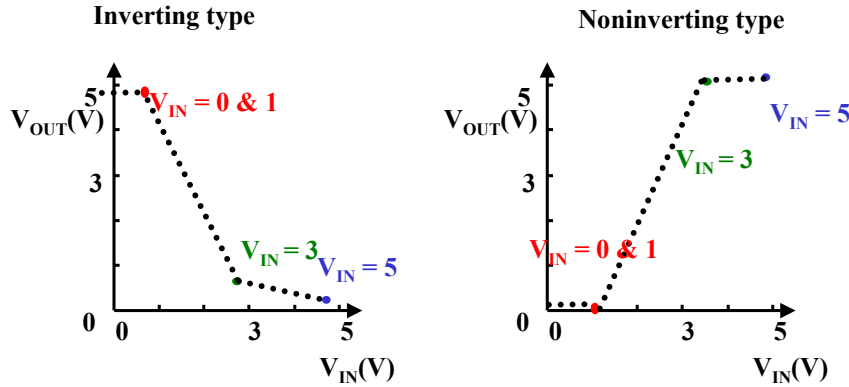The V_{OUT} vs. V_{IN} characteristic is another view of the logic gate that is used to determine the inverting and noninverting nature of a gate.



Copyright 2003, Regents of University of California

Saturation Current 42S_NMOS Model

Current I_{OUT} only flows when V_{IN} is larger than the threshold value V_{TD} and the current is proportional to V_{OUT} up to $V_{OUT-SAT-D}$ where it reaches the **saturation current**


$$I_{OUT-SAT-D} = k_D (V_{IN} - V_{TD}) V_{OUT-SAT-D}$$

Note that we have added an extra parameter to distinguish between threshold (V_{TD}) and saturation ($V_{OUT-SAT-D}$).

 Example:

$k_D = 25 \mu A/V^2$ Use these values in the homework.
 $V_{TD} = 1V$
 $V_{OUT-SAT-D} = 1V$

$$I_{OUT-SAT-PD} = 25 \frac{\mu A}{V^2} (3V - 1V) 1V = 50 \mu A$$



Copyright 2003, Regents of University of California

Drawing I_{OUT} as function of V_{IN} and V_{OUT} for the 42S_NMOS Pull-Down Device


The equations are expressly designed for EE42 to make it very simple to draw I_{OUT} vs. V_{OUT}

1) For $V_{IN} < V_{TD}$, the current is zero.

2) For $V_{IN} > V_{TD}$, first evaluate the current I_{OUT} at $V_{OUT} = V_{OUT-SAT-D}$ and plot the single point (I_{OUT}, V_{OUT})


3) Draw a line from this point to the origin to create the linear region.

 4) Draw a horizontal line from this point to create the saturation region




Copyright 2003, Regents of University of California

 States of 42S_NMOS are Voltage Levels of V_{IN}




Copyright 2003, Regents of University of California

 Composite Current Plot for the 42S_NMOS Logic Circuit



Copyright 2003, Regents of University of California

 Composite Current Plot for the 42S_NMOS Circuit with 200kΩ Load to Ground



Copyright 2003, Regents of University of California

Voltage Transfer Function for the 42S_NMOS Logic Circuit w/wo Load

